PRACTICAL
ELECTRONICS
APRIL 1973

50c
Toorak Village Newsagency

SIMPLE ALL AROUND
SECURITY ALARM

Australia	50c
New Zealand	45c
South Africa	45c
Rhodesia	45c
Nigeria	K. 40
Sweden	Kr. 3.50
Malaysia	$1.80

Also Inside: NOVEL BATTERY ELIMINATOR
P.E. Sound Synthesiser—VOLTAGE CONTROLLED OSCILLATOR and INVERTER

is this the price you pay?

Probably, if you're still using an ordinary soldering iron. Ordinary soldering irons can cause damage to transistors and integrated circuits – damage which wastes time and costs money. Now, with the unique ANTEX X25 and CCN low leakage soldering irons no harm can come to the most delicate equipment, even when soldered 'Live'.

(You could be making quite a saving).

All prices mentioned exclusive of VAT

MODEL X25

220-240 Volts or 100-120 Volts. The leakage current of the NEW X25 is only a few microamps and cannot harm the most delicate equipment even when soldered "live". Tested at 1500v. A.C. This 25 watt iron with it's truly remarkable heat-capacity will easily "out-solder" any conventionally-made 40 and 60 watt soldering irons, due to its unique construction.advantages. Fitted long-life iron-coated bit 1/8". 2 other bits available 3/32" and 3/16". Totally enclosed element ceramic and steel shaft. Bits do not "freeze" and can easily be removed

PRICE: £1.75 (rec. retail)

Suitable for production work and as a general purpose iron.

MODEL CCN

220 volts or 240 volts. The 15 watt miniature model CCN also has negligible leakage. Test voltage 4000v. A.C. Totally enclosed element in ceramic shaft. Fitted long-life iron-coated bit 3/32". 4 other bits available 1/8", 3/16", 1/4" and 3/64".

PRICE: £1.80 (rec. retail)

OR Fitted with triple-coated, iron nickel and Chromium bit 1/8".

PRICE: £1.95 (rec. retail)

MODEL G

18 watt miniature iron, fitted with long life iron-coated bit 3/32". Voltages 240,220 or 110. **PRICE: £1.83** (rec. retail).

MODEL CN

Miniature 15 watt soldering iron fitted 3/32" iron-coated bit. Many other bits available from 3/64" to 3/16". Voltages 240, 220, 110, 50 or 24.

PRICE: £1.70 (rec. retail)

MODEL CN2

Miniature 15 watt soldering iron fitted with nickel plated bit 3/32". Voltages 240 or 220.

PRICE: £1.70 (rec. retail)

as selected for the DESIGN CENTRE

MODEL MES.KIT

Battery-operated 12v. 25 watt iron fitted with 15' lead and 2 heavy clips for connection to car battery. Packed in strong plastic wallet with booklet "How to Solder"

PRICE: £1.95 (rec. retail)

MODEL SK.1 KIT

Contains 15 watt miniature iron fitted with 3/16" bit, 2 spare bits 5/32" and 3/32", heat sink, solder, stand and "How to Solder" booklet.

PRICE: £2.75 (rec. retail)

MODEL SK.2 KIT

Contains 15 watt miniature iron fitted with 3/16" bit, 2 spare bits 5/32" and 3/32" heat sink, solder, stand and "How to Solder" booklet.

PRICE: £2.40 (rec. retail)

ANTEX

From radio or electrical dealers, car accessory shops or in case of difficulty direct from:–

ANTEX LTD. FREEPOST (no stamp required) **PLYMOUTH PL1 1BR** Tel: 0752 67377.

☐ Please send the ANTEX colour catalogue.

☐ Please send the following:

.....

.....

.....

.....

I enclose cheque/P.O./Cash (Giro No. 2581000)

.....

NAME .....

ADDRESS .....

.....

.....

PE4

PRACTICAL
ELECTRONICS
VOLUME 9 No. 4 APRIL 1973

CONSTRUCTIONAL PROJECTS

P.E. SOUND SYNTHESISER—3 *by G. D. Shaw*
Voltage controlled oscillators and inverter 306

NOVEL BATTERY ELIMINATOR *by J. S. Goddard*
A stabilised 9V supply from the mains 313

HI FI TAPE LINK *by P. S. Ewer*
Constructional details 326

ALL-AROUND SECURITY ALARM *by J. Andrews*
Domestic burglar alarm with fail-safe features 338

P.E. DIGI-CAL—10 *by R. W. Coles*
M counter board 342

GENERAL FEATURES

ELECTRONIC TIMEPIECES—2 *by J. B. Dance*
Quartz crystal control and time displays 318

DESIGNING WITH I.C.s—7 *by A. Foord*
Counters and displays 350

NEWS AND COMMENT

EDITORIAL—Fashions In Building 305

BOOK REVIEWS
Selected new books we have received 317

SPACEWATCH *by Frank W. Hyde*
Space budget—Lunokhod 2—Skylab 325

ELECTRONORAMA
Focus on Post Office telephone paging system 334

STRICTLY INSTRUMENTAL *by K. Lenton-Smith*
Comments on contemporary sounds 337

INDUSTRY NOTEBOOK *by Nexus*
What's happening inside industry? 349

VALUE ADDED TAX

Prices quoted in this issue were correct at time of going to press. From 1st April 1973 there will be no purchase tax, but a large number of goods will carry Value Added Tax.

Our May issue will be published on Friday, April 13, 1973

© IPC Magazines Limited 1973. Copyright in all drawings, photographs and articles published in PRACTICAL ELECTRONICS is fully protected, and reproduction or imitations in whole or part are expressly forbidden. All reasonable precautions are taken by PRACTICAL ELECTRONICS to ensure that the advice and data given to readers are reliable. We cannot, however, guarantee it, and we cannot accept legal responsibility for it. Prices quoted are those current as we go to press. Subscription Rates including postage for one year, to any part of the world, £2·65.

Connoisseur

SAU2 Pick-up Arm

Recognised as one of today's most advanced pickup arms it features.

- Auto-bias Compensator
- Hydraulic Lowering Device
- Precision Balance
- New Adjustable Head Shell

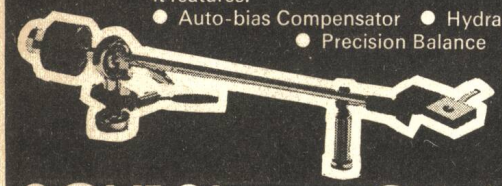

SCU1 Stereo Cartridge

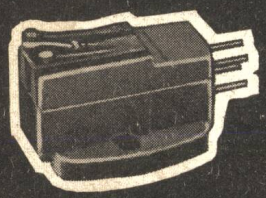

A quality cartridge designed specifically for the person who appreciates his equipment.

Precision Stylus Balance

An inexpensive and useful gift for the hi-fi enthusiast. It's simplicity itself to work out and adjust the weight of the stylus so as to give correct working conditions and perfect results. Covers a range from 0-6 grams with ½ gram calibrations.

A.R. SUGDEN & CO. (ENGINEERS) LTD.

Atlas Mill Road, Brighouse, Yorkshire
HD6 1ER. Telephone 2142

VISIT OUR STAND AT SONEX

I-N-T-E-R-L-O-C-K-I-N-G PLASTIC STORAGE DRAWERS

NEAT! HANDY! TIDY!

DISCOUNT PRICES

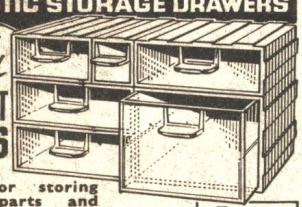

5 SIZES ALL INTERLOCK

Ideal for storing small parts and components. Rigid plastic units. Countless vertical and horizontal combinations of sizes for wall, bench or table top. Transparent plastic drawers have label slots/handles. **Trade Prices: Single Units** (2½in × 2½in × 5in deep) **£1·35** for 12; **Double Units: £2·25** for 12; **Treble Units £2·35** for 8; **Double Trebles** (2 drawers) **£3·65** for 8. **Extra large, £3·30** for 8. Carr. 35p. Orders over £10, post free. **Quantity Discounts:** 5% in £1 for orders over £5, 7½% over £10, 10% over £20. Quotations for larger quantities.

4-WAY IN-LINE 13 AMP POWER PANEL

PATENT CABLE LOCK

NEON INDICATOR LAMP

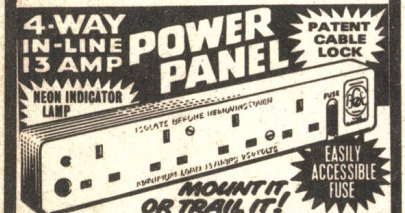

EASILY ACCESSIBLE FUSE

MOUNT IT, OR TRAIL IT!

Modern, slimline power panel. Countless uses in home, office and factory. Perfectly safe and unbreakable. **Can be mounted on wall or trailed anywhere in room.** Neat, rubber base, smart P.V.C. outer cover. **Black, £1·95, White, £2·40,** p. & p. 30p. State cable length required at **10p** yard with **Free** 13 amp plug.

IVORYET LIMITED

(Dept. PE4) 124 Cricklewood Broadway, London, N.W.2
Tel. 01-450 4844

OSMABET LTD.

We make transformers amongst other things

AUTO-TRANSFORMERS
500W, **£8·85**; 750W, **£12**; 1,000W, **£15**; 1,500W, **£21**; 2,000W, **£27**; 3,000W, **£37·50**; 4,000W, **£52·50.**

LOW VOLTAGE TRANSFORMERS
Prim. 200/240V a.c. 6·3V 1·5A, **£1·05**; 3A, **£1·30**; 6A CT **£2·05**; 12V 1·5A, **£1·35**; 3A CT, **£2·15**; 6A CT, **£2·80**; 18V 1·5A CT, **£2·15**; 24V 1·5A CT, **£2·15**; 3A CT, **£2·80**; 5A, **£4·30**; 8A, **£6·75**; 12A, **£9·40**; 40V 3A CT, **£3·75**; 50V 6A CT, **£10.**

MIDGET RECTIFIER TRANSFORMERS
For FW rect., 200/240V a.c. 9–0–9V 0·3A, 12–0–12V 0·25A or 20–0–20V 0·15A, **£1·45** each; 9–0–9V 1A, **£1·15**; 12–0–12V 1A or 20–0–20V 0·75A, **£1·35** each.

O/P TRANSFORMERS FOR POWER AMPLIFIERS
P.P. sec. tapped 3–7·5–15 ohms, A–A 6·6 Kn 30W (KT66, etc.), **£4·65**; A–A 3Kn 50W, **£7·50**; 100W (EL34,KT88, etc.), **£12·50.** Multi O/P 10W, **£2·25.**

MAINS TRANSFORMERS POWER AMPLIFIERS
Prim. 200/240V a.c., TX6 sec, 425–0–425V 500 Ma, 6·3V CT 6A, 6·3V CT 6A, 0–5–6·3V 3A, **£14·25**; TX1 425–0–425V 250Ma, 6·3V CT 4A, 6·3V CT 4A, 0–5–6·3V 3A, **£9.** 250V 100Ma, 6·3V 2A, **£2·70.**

G.E.C. MANUAL OF POWER AMPLIFIERS
Covering valve amplifiers of 30 to 400W, with price list of transformers and chokes specified, **30p.** Bernards Amplifier Manual, 5 to 1,000W, **75p.**

LOUDSPEAKERS FOR POWER AMPLIFIERS
FANE 15W w/tweeter, **£4·99**; 50W, **£10·90**; 60W, **£12·90**; 100W, **£22·50**; BAKER 25W, **£6·40**; 35W, **£7·20**; Hi-Fi Major Module, 20W W/Tweeter and Xover 30–17kHz, **£9·20**; EMI 13in × 8in, **£2·25**; 8in × 5in 8n, **£1·85**; Goodmans Tweeter 3Ω, **£2.**

LOUDSPEAKERS
2½in 16n, 2½in 25n, 3in 30n, **75p**; 3½in 3 or 15n, 4in 8 or 15n, 5in 3, 8, 15 or 25n, 5in × 3in 3, 8, 15 or 25n, **£1·05** each; 6½in 3n, 6in × 4in 8 or 25n, 7in × 4in 3 or 15n, 8 × 2½in 3n, **£1·25**; 8in × 5in 3, 8, 15 or 25n **£1·50**; 10in 15Ω, **£2·50**; 10 × 6in 3Ω, **£2·25.**

SPEAKER AUTO MATCHING TRANSFORMERS
12W, 3 to 8 or 15n, up or down, **£1·05.**

BULK TAPE ERASERS
Instant erasure, tape spools, cassettes, demagnetises tape heads a.c. 200/240V, **£2·50** plus 25p P. & P.

RELAYS Sub mini, 6/9V, 250Ω.
15, 20 or 30V d.c., 2 C.O's **50p** each.

12V DC FLUORESCENT LIGHTING
Silicon transistor invertor for 20W tube, **£5·75.**

PAPER CONDENSERS
Tubular W/E 2·2 mfd, 250V Xovers, etc., **15p, £5** 100. Block 4 mfd, 800V, **75p,** 1,500V, **£1·25.**

Carriage extra on all orders, etc.

S.A.E. ENQUIRIES-LISTS. MAIL ORDER ONLY
46 Kenilworth Road, Edgware, Middx. HA8 8YG
Tel. 01-958 9314

4-STATION INTERCOM

£7·25

Solve your communication problems with this **4-Station Transistor Intercom** system (**1 master** and **3 Subs**), in de-luxe plastic cabinets for desk or wall mounting. Call/talk/listen from **Master** to **Subs** and **Subs** to **Master.** Ideally suitable for Business, Surgery, Schools, Hospital, Office and Home. Operates on one 9V battery. On/off switch. Volume control. Complete with 3 connecting wires each 66ft. and other accessories. P. & P. 40p.

MAINS INTERCOM (new model)

No batteries—no wires. Just plug in the mains for instant two-way, loud and clear communication. On/off switch and volume control with lock system. Price **£14·40.** P. & P. 55p extra.

INTERCOM/BABY ALARM

£3·35

Same as 4-Station Intercom for two-way instant communication. Ideal as Baby Alarm and Door Phone. Complete with 66ft. connecting wire. Battery **14p.** P. & P. 25p.

Transistor TELEPHONE AMPLIFIER

£2·99

Why not boost business efficiency with this incredible De-Luxe **Telephone Amplifier.** Take down long telephone messages or converse without holding the handset. A useful office aid. On/off switch. Volume control. Battery **14p** extra. P. & P. 22p. Full price refunded if not satisfied in 7 days.

WEST LONDON DIRECT SUPPLIES (PE/4)
169 KENSINGTON HIGH STREET, LONDON, W.8

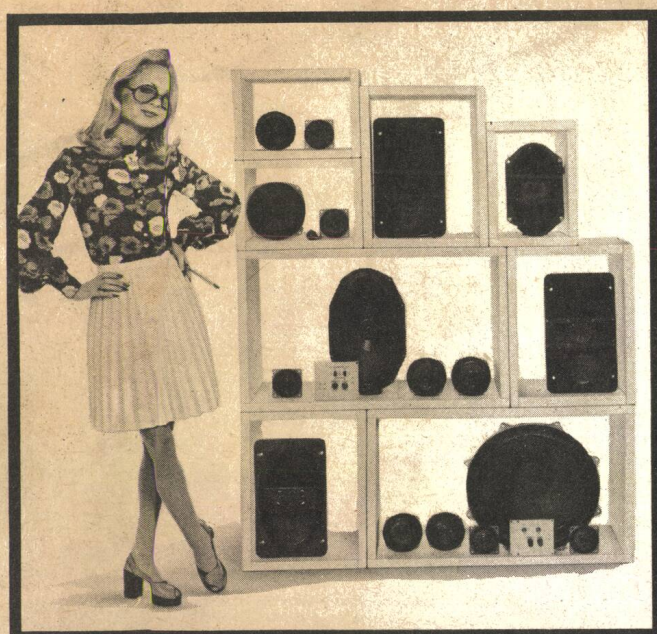

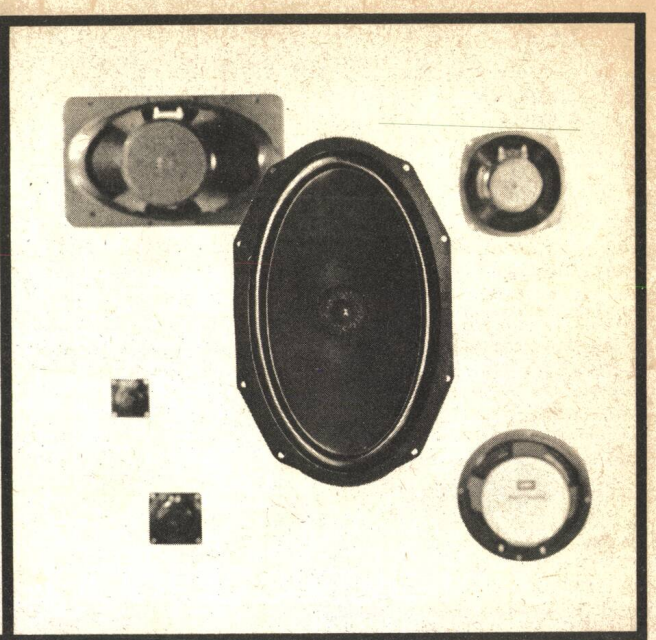

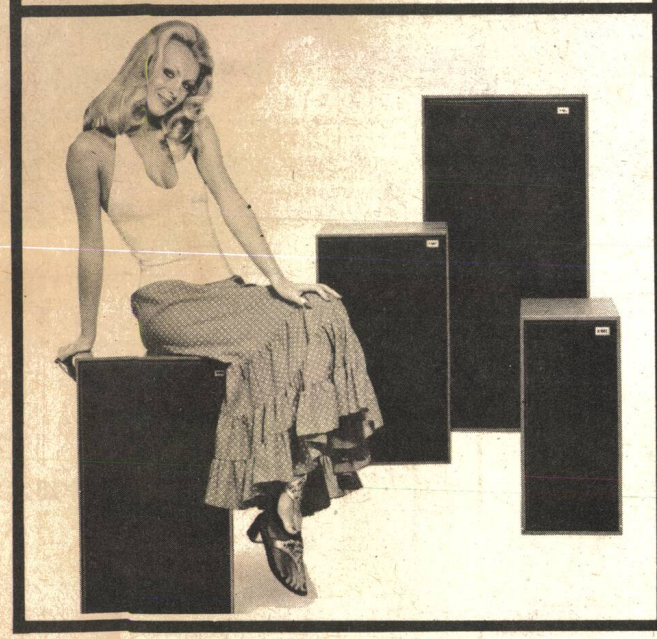

A Speaker System to meet every need

EMI provides the speaker system to suit your needs and your budget, all with one thing in common, superb quality of sound over the full audio range. Choose from new elegant speaker enclosures for the connoisseur; home assembly enclosure kits and matched speaker kits and a range of basic chassis loudspeakers as used in the highest quality sound reproduction equipment.
Send for full details and name of your nearest stockist.

To: EMI Sound & Vision Equipment Limited. EMI Pathe Division, 252 Blyth Road, Hayes, Middlesex. 01-573 3888
Please send me details of EMI loudspeaker's and name of nearest stockist.

Name_____

Address_____

PE/4

EMI **Perfection in Sound**

A member of the EMI Group of Companies. International leaders in Electronics, Records and Entertainment.

JAMES SCOTT

SALE OF SURPLUS ELECTRONIC EQUIPMENT

The following items are available for immediate delivery at very competitive prices—

SCANNING ALARM INDICATOR

Can be used for Automatic Monitoring of All Types of Test Points (Up to 25)
Incorporates: Auto and Manual Facilities
Illuminated Digital Input Identification
Double Pole Gold Plated Contacts on Uni-selectors
Units Supplied Untested Less Indicating Meter. Price £25·00
Carriage and Insurance (U.K. only) £1·50

DOSIMETER CHARGING UNIT TYPE 200

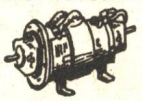

PORTABLE INSTRUMENTS USED TO CHARGE QUARTZ FIBRE TYPE POCKET DOSIMETER TO ZERO. SUITABLE FOR USE WITH ALL STANDARD TYPES OF QUARTZ FIBRE DOSIMETERS HAVING A MAXIMUM OUTSIDE CHARGING END DIAMETER OF 0·605IN. TELEPHONE TYPE A.C. AND GENERATOR, THE OUTPUT OF WHICH IS RECTIFIED AND CHARGES UP A RESERVOIR CAPACITOR TO A MAXIMUM POTENTIAL OF ABOUT 300 VOLTS D.C. SUPPLIED LESS GENERATOR HANDLES. PRICE £1·50. P. & P. 20p.

SEALED RELAYS (NATO APPROVED)

GEC 4 pole c/o 24V 670 ohm. GEC 2 pole on/off 24V 670 ohm. GEC 2 pole c/o 65V 5,000 ohm. STC 2 pole c/o 12V 170 ohm.
Price each: 75p. P. & P. 10p.

PC102 Supply voltage 220-250V a.c. Output voltages: 21 Volts d.c. at 330MA 21 Volts a.c. at 540MA

NEWMARKET TRANSISTORS

NKT351	73p	NKT12329	27p	2N2222	18p	NKT218	23p
NKT352	25p	NKT12429	27p	NKT12	30p	NKT221	30p
NKT406	60p	NKT13329	27p	NKT72	25p	NKT222	18p
NKT420	£1·80	NKT13429	27p	NKT73	22p	NKT223	25p
NKT450	30p	NKT16229	27p	NKT121	21p	NKT224	22p
NKT603	22p	NKT20329	29p	NKT124	28p	NKT227	25p
NKT613F	28p	NKT80111	65p	NKT125	38p	NKT237	29p
NKT674	30p	NKT80113	98p	NKT126	35p	NKT238	16p
NKT677	18p	NKT80125	80p	NKT127	23p	NKT249	29p
NKT713	27p	BC107	8p	NKT128	18p	NKT261	19p
NKT734	24p	BC108	8p	NKT129	22p	NKT270	18p
NKT736	30p	BCY70	13p	NKT135	24p	NKT271	16p
NKT773	23p	BFY51	17p	NKT137	30p	NKT272	15p
NKT0216	20p	BSY95A	10p	NKT142	48p	NKT273	18p
NKT3055	23p	2N697	13p	NKT143	48p	NKT274	16p
NKT8917	27p	2N706	8p	NKT212	23p	NKT275	21p
NKT10339	23p	2N914	15p	NKT213	23p	NKT278	18p
NKT10419	17p	2N918	28p	NKT214	21p	NKT301	70p
NKT10439	25p	2N930	22p	NKT215	19p	NKT302	85p
NKT10519	20p	2N1990	22p	NKT217	48p	NKT303	70p
						NKT304	76p

S.T.C. RELAYS—BRAND NEW

TYPE	CONTACT FORM	NOMINAL COIL VOLTAGE	COIL RESISTANCE (OHMS)	PRICE EACH
250 ARO	4 CHANGEOVER	6V d.c.	52	£0·68
250 ABO	4 CHANGEOVER	48V d.c.	2,500	£0·68

TYPE	CONTACT FORM	COIL VOLTAGE	SWITCHING CURRENT	PRICE EACH
SL7222212	3 Pole on/off	12V a.c.	10A at 440V a.c.	£1·00
SL7622715	2 Pole C/O	220V a.c.	10A at 440V a.c.	£0·87

TYPE	CONTACT FORM	COIL VOLTAGE	COIL RESISTANCE	PRICE EACH
SP13372	Single Pole C/O	6V d.c.	140 ohm	£0·40
SP13366	Single Pole C/O	12V d.c.	350 ohm	£0·40
11301D	Single Pole C/O	18V d.c.	875 ohm	£0·40

UNISELECTOR SWITCHES

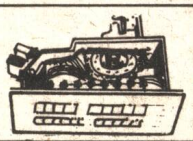

6 bank 25 way. 75 coil 50V d.c. operation. Mounted on Modular Type Chassis with front panel containing 20 illuminated Push Button Switches. Completely wired for operation.
Price £15
P. & P. £0·55

AUTOMATIC CYCLER UNIT

This unit generates stepping pulses (50V d.c.) at intervals of 6 pulses per min. to 120 pulses per min.—continuously variable. Can be used for Automatic Stepping of one or more uniselector switches shown above. Price £12·50
P. & P. £0·45

NEWMARKET PACKAGED AUDIO AMPLIFIER

PC1 150mW Audio Amplifier. Price £1·00 each. P. & P. £0·10
PC10 Magnetic replay head amplifier supply voltage 9V d.c. Input impedance 150. Price £0·90 each. P. & P. £0·10

WE HAVE A LARGE RANGE OF CAPACITORS AND RESISTORS. PLEASE SEND A STAMPED AND ADDRESSED FOOLSCAP ENVELOPE FOR YOUR CATALOGUE

POST & PACKING OVER £2—FREE. OVER £1 AND UNDER £2—15p. UNDER £1—10p UNLESS SPECIFICALLY MENTIONED. P. & P. U.K. ONLY

JAMES SCOTT (ELECTRONIC ENGINEERING) LIMITED
CARNTYNE INDUSTRIAL ESTATE, GLASGOW G32 6AB
TEL: 041-778 4206

NOT JUST A RADIO BUT A COMPLETE COMMUNICATIONS RECEIVER

BATTERY/MAINS PORTABLE RECEIVER

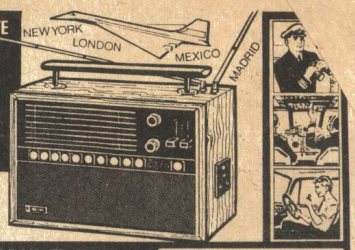

What radio priced at under £120 gives you such a varied choice of transmissions?

CASH PRICE £49·50 + 50p P. & P. or £14·50 dep. + 50p P. & P. and 6 months at £7 (£56·50).

Picks up ALL THE USUAL BBC Programmes. ★All the new local radio stations ★Continental ★World-wide transmissions ★Pop Pirates ★Radio Hams ★Aircraft ★Shipping ★Police ★Taxis ★RAC ★AA ★Fire Brigade ★TV Sound ★Ambulances and 1,000s more.

THE BEST PORTABLE RADIO EVER MADE! We think so. As well as the standard long and medium wavebands it has three short wave bands (including the Marine and Trawler Band) **AND NO LESS THAN THREE VHF BANDS.** Listen to your favourite BBC programme and then—at the flick of a switch—tune into the control tower and hear a "crippled airliner" being talked down to safety. Or listen to the trawlers and ocean-going liners—Eavesdrop on the taxi-cabs, fire brigades, ambulances, AA, RAC and 100s of other RT mobiles! Extensive shortwave coverage can give you Australia, Pakistan, North America, Far East, etc., etc. World famous manufacturer. **FULL 3-YEAR WRITTEN GUARANTEE.** Beautifully finished in Teak Wood and Stainless Steel. Portable 12in × 9in × 4in, using standard batteries—or can be plugged directly into mains. **14 transistors, 6 diodes, 1 thermistor, internal ferrite rod aerial PLUS two external telescopic antennae**—with sockets for additional aerials, or car aerials. Automatic **Drift-Free Reception.** Sliding tone control. Hi-Fidelity earphone for private listening, local DX switch. **FREQUENCIES:** Long W 150–350kHz. Medium W 540–1605kHz, Marine 1·6–4 MHz. Short W 1 3·7–9MHz, Short W 2 9–22MHz. F.M. (VHF) 88–108MHz. Aircraft (VHF) 108–136MHz. Public Service (VHF) 148–174MHz.

NOTE.—The Ministry of Posts & Telecommunications state a Licence (not generally available to the public) is required for the reception of transmissions by Fire Brigade, Aircraft, Shipping, etc.

PROFESSIONAL 2 CHANNEL WALKIE-TALKIE SYSTEM UP TO 8 MILES RANGE

ENQUIRIES FROM SMALL PROFESSIONAL & AMATEUR ASSOCIATIONS, CLUBS ETC. WELCOME

COMPLETE SYSTEM

£51·75
Plus 25p P & P

JUST ARRIVED—a NEW system from Switzerland—the home of precision built electronics equipment. **GENUINE 2-WAY WALKIE-TALKIE SYSTEMS. Ideal for all crowd control,** doctors, fishermen and general marine use. The telescopic antenna pulls in the voice at the other end with crystal clear clarity—**even 8 miles away!** Frequency 29·9MHz (interchangeable according to your licence stipulation). Battery-operated—no wires. A tremendous time and money saver. 2 Units complete with **FREE** carrying cases. Credit terms available, details on request. NOTE: Licence required to operate.

Send 5p stamp for Discount Brochure of Unusual Frequency Radios
SCIENTIFIC & TECHNICAL (PE4), TOWERFIELD TRADING ESTATE, SOUTHEND, ESSEX

---

become a RADIO-AMATEUR!

learn how to become a radio-amateur in contact with the whole world. We give skilled preparation for the G.P.O. licence

RAPY

free! Brochure, without obligation to:

BRITISH NATIONAL RADIO & ELECTRONICS SCHOOL
P.O. BOX 156, JERSEY

NAME : _____

ADDRESS : _____ EB43

_____ BLOCK CAPS please

There are 195 other good reasons for buying AMTRON electronic kits

Apart from the five items shown above, there are another 195 kits to choose from in the vast AMTRON range of electronic kits.

A few examples of equipment you can construct from AMTRON kits are: Power supplies, preamplifiers, amplifiers, accessories for musical instruments, amateur and radio control transmitters and receivers, battery chargers, electronic car accessories, psychedelic lighting equipment, measuring instruments, tuners, receivers, I.C. digital equipment.

The unique quality of AMTRON kits is their simplicity of construction which appeals to dabbler and expert alike.

Only 1st class fully guaranteed components are used — solder is included with every kit.

Prices range from £1.10 to £80 and each kit is sold in a protective blister pack containing complete instructions.

Write for catalogue.

Should you experience any difficulty in obtaining AMTRON kits please contact us direct.

TRADE & EDUCATIONAL ENQUIRIES WELCOME

AMTRON® UK

AMTRON U.K. 4 & 7 CASTLE STREET, HASTINGS, SUSSEX. TEL: HASTINGS 2875

UNISOUND FOR THE NEW SOUND

AT £26·12 INC. VAT

It's the RT-VC system that screws together to save you pounds! Unisound comprises two superb speakers and an amplifier/record deck plinth—all beautifully finished in simulated teak. The stereo amplifier (4 watts per channel into 8 ohms) is based on the famous Mullard Unilex system brought up-to-date by RTVC using intergrated circuits. Turntable is the proven Garrard 2025TC complete with stereo cartridge and tinted acrylic cover. Speakers are big EMI Twin-cone units all ready for mounting in their elegant cabinets, which simply need screwing and glueing together. Easy step-by-step instructions. **£26·12 complete plus £1·40 packing + £1·40 post.** Diamond Stylus £1·25 extra. Stereo headphones with adaptor £4 extra. Send for leaflet.

AN RTVC EXCLUSIVE DESIGN

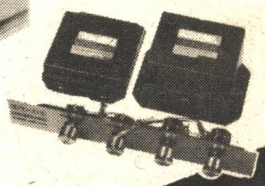

UNISOUND MODULES ONLY £6·95 + 50p. p. & p.
For the man who wants to design his own stereo—here's your chance to start, with Unisound—pre-amp, power amplifier and control panel. No soldering—just simply screw together. 4 watts per channel into 8 ohms. Inputs: 120mV (for ceramic cartridge). The heart of Unisound is high efficiency I.C. monolithic power chips **very low distortion at all power levels. over the audio spectrum.**

RTVC No price in

If you can sold
on printed circuit boa
you can build this push-butt
car radio kit. It's simple—ju
follow the step-by-step instructio

THE TOURIST PB CAR RADIO KIT
AN INCREDIBLE BUY
ONLY FROM RTVC

£7·70 inc. vat

The Tourist PB is suitable for 12 volt working on both negative and positive earth vehicles. It covers the full medium and long wave bands. It is permeability tuned and sturdily constructed. Output is a full 2·5 watts into an 8ohms speaker. But the Tourist PB will operate into any loudspeaker from 8 to 15 ohms.
Apart from the output stage, which is an intergrated circuit, the only other electronic components that need soldering are some capacitors, resistors, etc. The kit includes a pre-built RF tuner unit, and fully modulised IF stages which are pre-aligned before despatch. As well as electronic components this kit also contains 2 diamond-spun aluminium knobs, elegant matching front panel, dial, washers, screws and wire.
The Tourist PB can be mounted in any standard size dash panel and it has an illuminated tuning scale. Chassis size is: 7" wide, 2" high and 4⅝" deep.

* Circuit diagram and comprehensive instructions 50p free with parts.

* Fully retractable lockable car aerial £1· post paid.

PRICE ONLY £7·70 p. and p. 55p
Speaker with baffle and fixing strips £1· 25 p. & p., post free if bought with the
Send for leaflet.

RELIANT MkIV

A GOOD QUALITY AMPLIFIER—12 Wat £10·50 (inc. VAT). 20 Watts £13·50 (inc. VA

*5 Electrically Mixed inputs. *3 Individual Mixing controls. *Separate bass and treb controls common to all 5 inputs. *Mixer employing F.E.T. (Field Effect Transistors *Solid State Circuitry. *Attractive Styling INPUTS 1. Crystal Mic or Guitar 9mV. Moving coil Mic. or Guitar 8mV Inputs. 3, 4 & 5 are suitable for a wide range of medium output equipment (Gram. Tuner, Monitor, Organ, etc.) All 250mV sensitivity. Power output: 12/20 watts into 8 ohms. Size approx. 12½ x 6 x 3½ ins.

12W version £10·50 plus 60p p & p

20W version £13·50

SOUND 50

50 WATT AMPLIFIER. Output Power: 45 watts R.M.S. (Sine Wave) Frequency Response 3dB points 30Hz and 18KHz. Total Distortion: less than 2% at rated output. Signal to noise ratio: better than 60dB. Bass Control Range: 13dB at 60Hz. Treble Control Range: 12dB at 10KHz. Inputs: 4 inputs at 5mV into 470K. Each pair of inputs conrotlled by separate volume control. 2 inputs at 200mV into 470K. Size: 19½ x 10½ x 8ins. Amplifier £31·85 plus £1·50 p. and p. **£38·51 (inc. VAT)**

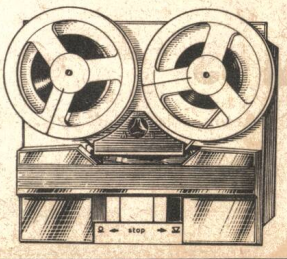

PE TAPE LINK CONSTRUCTORS
Suitable 3 speed deck, less leads. C up to 7ins. spools. Un but store soiled hence no war- ranty. plu £1 p

* Denotes VAT has been absorbed in the price without increase on VISCOUNT audio systems.

crease* with VAT!

PRICES: SYSTEM 1

Viscount III R 101 amplifier	£24·20 + £1 p & p
2 Duo Type II speakers	£15·40 + £2·20 p & p
Garrard SP25 Mk.III with MAG. cartridge plinth & cover	£25·00 + £1·75 p & p
total	£64·60

Available complete for only **£52*** + £3·50 p & p

PRICES: SYSTEM 2

Vicount R 101 amplifier	£24·20 + £1 p & p
2 Duo Type III speakers	£35·20 + £3·30 p & p
Garrard SP25 Mk. III with MAG. cartridge plinth & cover	£25·00 + £1·75 p & p
total	£84·40

Available complete for **£69*** + £4 p & p

VISCOUNT III AUDIO STILL ONLY £52* COMPLETE

14 + 14w. r.m.s. 40Hz to 40kHz ± 3dB. Total distortion at 10w. at 1kHz – 0·1%. This is real value for money! We have designed 2 systems and the heart of them both is the Viscount III amplifier. A unit of great eye appeal with teak finished cabinet. FET's (Field effect, transistors) are incorporated on the input stages, just like top priced units. FET's give you more of the signal you want and almost none of the hiss you don't. Both units have output sockets for headphones and tape recorder.

For both systems we have chosen the famous Garrard SP25 Mk. III deck, with fitted magnetic cartridge, which comes complete with simulated teak plinth and tinted acrylic cover.

The exclusive Duo loudspeaker systems are incomparable for quality within their price range. Large speakers in extremely substantial cabinets. There's a choice of the Duo II's for the smaller room or the big Duo III's for real bass response.

PEAKERS: Duo Type II Size approx. 17in. × 10¾in. × 6¾in. Drive unit 13in. x 8in. with parasitic eeter. Max. power 10 watts ohms. Simulated Teak cabinet. £15·40 a pair (inc. VAT), £3·30 p. and p. uo Type III Size approx. 23½in. × 11½in. × 9½in. Drive unit 13½in. 8½in. with H.F. speaker. Max. power watts ohms. Freq. range 20Hz to 20KHz. Teak veneer cabinet.

PECIFICATION R101: 14 watts per channel into 3 to 4 ohms (suitable 3–15 ohms.) Total distortion @ W 1kHz @ 0·1%. P.U.1 (for ceramic cartridges) 150mV into 3 Meg. P.U.2 (for magnetic cartridges) V @ 1kHz into 47K equalised within idB R.I.A.A. *Radio* 150mV into 220K. (Sensitivities given at full wer). Tape out facilities: headphone socket, power out 250mW per channel. Signal-to-noise ratio: controls at max.)—P.U.I. and radio — 65dB, P.U.2 — 58dB. Cross talk better than — 35dB on all uts. Size approx. 13¾in. × 9in. × 3¾in. Send S.A.E. for fully illustrated brochure. 12 month's tten guarantee.

NLY FROM US

MES OF OPENING: Acton—Mon.–Sat. 9.30–5.
osed all day Wed.
gware Rd.—Mon.–Sat. 9.30–5. Closed all day Thurs

VISIT OUR SHOWROOMS

R T V C

Radio and TV Components (Acton) Ltd.
21c High Street, Acton, London W3 6NG
323 Edgware Road, London W2
Mail orders to Acton. Terms C.W.O.
Goods not despatched outside U.K.
All enquiries S.A.E.

BI-PRE-PAK

SUPPLIERS OF SEMI-CONDUCTORS TO THE WORLD

COMPLETE TELEPHONES

EX. G.P.O. NORMAL HOUSEHOLD TYPE

ONLY 95p

POST & PACKING 35p EACH

TELEPHONE DIALS

Standard Post Office type Guaranteed in working order.

ONLY 25p

POST & PACKING 15p

TESTED AND GUARANTEED PAKS

B79	4	IN4007 Sil. Rec. diodes. 1,000 PIV 1 amp. plastic	50p
B81	10	Reed Switches, mixed types large and small	50p
B99	200	Mixed Capacitors. Approx. quantity, counted by weight	50p
H4	250	Mixed Resistors. Approx. quantity counted by weight	50p
H7	40	Wirewound Resistors. Mixed types and values	50p
H9	2	OCP71 Light Sensitive Photo Transistor	50p
H28	20	OC200/1/2/3 PNP Silicon uncoded TO-5 can	50p
H30	20	1 Watt Zener Diodes, Mixed Voltages 6·8–43V	50p
H35	100	Mixed Diodes, Germ. Gold bonded, etc. Marked and Unmarked	50p
H38	30	Short lead Transistors, NPN Silicon Planar types	50p
H39	10	Integrated circuits 6 gates BMC 962, 4 flip flops BMC 945	50p
H40	20	BFY 50/2, 2N696, 2N1613, NPN Silicon uncoded TO-5	50p
H41	2	BD131/BD132 Complementary Plastic Transistors	50p

UNMARKED UNTESTED PAKS

B1	50	Germanium Transistors PNP, AF and RF	50p
B66	150	Germanium Diodes Min. glass type	50p
B83	200	Trans. manufacturers' rejects all types NPN, PNP, Sil. and Germ.	50p
B84	100	Silicon Diodes DO-7 glass equiv. to OA200, OA202	50p
B86	100	Sil. Diodes sub. min. IN914 and IN916 types	50p
B88	50	Sil. Trans. NPN, PNP equiv. to OC200/1 2N706A, BSY95A, etc.	50p
H6	40	250mW. Zener Diodes DO-7 Min. Glass Type	50p
H15	30	Top Hat Silicon Rectifiers, 750mA. Mixed volts	50p
H16	15	Experimenters' Pak of Integrated Circuits. Data supplied	50p
H17	20	3 amp. Silicon Stud Rectifiers, mixed volts	50p
H20	20	BY126/7 Type Silicon Rectifiers 1 amp. plastic. Mixed volts	50p
H34	15	Power Transistors, PNP, Germ. NPN Silicon TO–3 Can	50p

MAKE A REV COUNTER FOR YOUR CAR

The 'TACHO BLOCK'. This encapsulated block will turn any 0-1mA meter into a linear and accurate rev. counter for any car with normal coil ignition system.

£1 each

OVER TRANSISTORS IN STOCK 1,000,000

We hold a very large range of fully marked, tested and guaranteed transistors, power transistors, diodes and rectifiers at very competitive prices. Please send for free catalogue.

600,000 Silicon planar plastic transistors. Unmarked, untested, factory clearance. A random sampling showed these to be of remarkably high quality.

Audio PNP, similar to ZTX500, 2N3702/3, BCY70, etc.

Audio NPN, similar to ZTX300, 2N3708/9 BC107/8/9, BC168/9, etc.

R.F. NPN and switching NPN Types also.

Please state type of transistor required when ordering.

ALL AT 500 for £3, 1,000 for £5, 10,000 for £40

OUR VERY POPULAR 3p TRANSISTORS

TYPE "A" PNP Silicon Alloy, TO-5 can.
TYPE "B" PNP Silicon, plastic encapsulation.
TYPE "E" PNP Germanium AF or RF.
TYPE "F" NPN Silicon plastic encapsulation.
TYPE "G" NPN Silicon, similar ZTX300 range.
TYPE "H" PNP Silicon, similar ZTX500 range.

8 RELAYS FOR VARIOUS TYPES P & P 25p £1

VALUE ADDED TO YOU } On orders of £4 or over. See below:

Please read very carefully:
We will give a discount to customers who send in an order for £4 or over. This discount will be equal to the V.A.T. rate current at this time. If your order does amount to £4 or over, all you need to send is the total cost of goods and postage as stated in this advertisement. No addition for V.A.T. is needed.
V.A.T. for orders under £4:
If the total cost of goods plus postage and packing is less than £4, kindly add 10% (10p in the £) to your remittance. Incorrect amounts will delay your order

A CROSS HATCH GENERATOR FOR £3·50 ! ! !

YES, a complete kit of parts including Printed Circuit Board. A four position switch gives X-hatch, Dots, Vertical or Horizontal lines. Integrated Circuit design for easy construction and reliability. This is a project in the September edition of Practical Television.

This complete kit of parts costs £3·50, post paid.

A MUST for Colour T.V. Alignment.

Our famous PI Pak is still leading in value for money.

Full of Short Lead Semiconductors & Electronic Components, approx. 170. We guarantee at least 30 really high quality factory marked Transistors PNP & NPN, and a host of Diodes & Rectifiers mounted on Printed Circuit Panels. Identification Chart supplied to give some information on the Transistors.

Please ask for Pak P.I. Only 50p.
10p P & P on this Pak.

FREE CATALOGUE FOR TRANSISTORS, RECTIFIERS, DIODES, INTEGRATED CIRCUITS, FULL PRE-PAK LISTS

100,000 Plastic Power Transistors

in stock, more on way!

NOW IN TWO RANGES

These are 40W and 90W Silicon Plastic Power Transistors of the very latest design, available in NPN or PNP at the most shatteringly low prices of all time. We have been selling these successfully in quantity to all parts of the world and we are proud to offer them under our Tested and Guaranteed terms.

Range 1

	VCE Min. 15	HFE Min. 15	
	1–12	13–25	26–50
40 watt	20p	18p	16p
90 watt	24p	22p	20p

Range 2

	VCE Min. 40	HFE Min. 40	
	1–12	13–25	26–50
40 watt	30p	28p	26p
90 watt	35p	33p	30p

Complementary pairs matched for gain at 3 amps. 10p extra per pair. Please state NPN or PNP on order.

INTEGRATED CIRCUITS. We stock a large range of I.C.s at very competitive prices (from 10p each). These are all listed in our FREE Catalogue, see coupon below.

METRICATION CHARTS now available. This fantastically detailed conversion calculator carries thousands of classified references between metric and British (and U.S.A.) measurements of length, area, volume, liquid measure, weights, etc. Pocket Size, 15p, Wall Chart, 18p.

LOW COST DUAL IN LINE I.C. SOCKETS

14 pin type at 15p each } Now new low
16 pin type at 16p each } profile type.

BOOKS

We have a large selection of Reference and Technical Books in stock.
These are just two of our popular lines:
B.P.I. Transistor Equivalents and Substitutes: 40p
This includes many thousands of British, U.S.A., European and C.V. equivalents.
The Iliffe Radio Valve & Transistor Data Book 9th Edition: 75p
Characteristics of 3,000 valves and tubes. 4,500 Transistors, Diodes, Rectifiers and Integrated Circuits. Post and Packing 21p
Send for lists of these English publications.

N.B.—Books are void of V.A.T.

Please send me the FREE Bi-Pre-Pak Catalogue.

NAME.....

ADDRESS .....

.....

MINIMUM ORDER 50p. CASH WITH ORDER PLEASE. Add 10p post and packing per order. OVERSEAS ADD EXTRA FOR POSTAGE.

BI-PRE-PAK LTD DEPT. A, 222-224 WEST ROAD, WESTCLIFF-ON-SEA, ESSEX
TELEPHONE: SOUTHEND (0702) 46344

Do it yourself comes to calculators.

The Advance Executive 8 is in kitform.

So, instead of paying £80.00, you need only pay £39.20 plus 75p postage and packing.

Moreover it should only take you three hours to build. (Dick Railton of Electronics Weekly holds the record at 2 hours 10 minutes – so far.)

Spend the time – and, we regret, the money and you'll have a calculator with: four functions; multiplication and division by a constant; chain calculations; automatic squaring; 8 digits.

It's superb value at twice the price.

Let alone half.

Please rush me
your Executive 8 in kitform.
I enclose my cheque for £39.20 and 75p
postage and packing.

Name _____

Address _____

_____

Post to Calculator Division,
Advance Electronics Limited,
Raynham Road, Bishop's Stortford, Herts.
Telephone: 0279 55155
Telex: 81510

Registered No.: 263834

IT'S FREE

FULLY ILLUSTRATED

ELECTRONIC COMPONENTS CATALOGUE

If you have not yet seen our latest catalogue, drop us a line right away and we will be delighted to forward a copy to you. In it you will find many useful components at very competitive prices, plus details of how you can receive **ONE POUNDS WORTH** of goods **ABSOLUTELY FREE.**

MAPLIN ELECTRONIC SUPPLIES P.O. BOX 3, RAYLEIGH, ESSEX SS6 8LR

You may telephone any time of the day or night. Out of office hours your message may be left on our answering machine.

LOOK!

HERE ARE JUST A FEW OF THE THOUSANDS OF LOW-PRICED ITEMS IN THE CATALOGUE.

EVERYTHING GUARANTEED BRAND NEW MARKED BY MANUFACTURER

BC107 BC108 BC109 only **10p** each

115 Watt Power Transistor 2N3055 ..... **49p**
mounting kit supplied free

This very popular FET 2N 3819 ..... **24p**

Versatile Unijunction TIS 43 (SS43) **28p**

Until further notice
PRICE REDUCED
8 PIN DIL OP AMP
741C 36p

SPECIAL IC. for organ builders, 7 stage frequency divider in one 14 pin DIL package **£2.63** or special price for pack of 12, **£25.**

Why not ask us to slip a data sheet in with your catalogue.

Postage and packing FREE in UK. But we have to ask you to send a 10p handling charge with order under 50p.

SOUND BARGAINS

GIANT POWER MULTI-WAVEBAND COMMUNICATIONS RECEIVER

WITH 3 in 1 AC/DC POWER SUPPLY SYSTEM
MAINS/BATTERY plus BUILT-IN BATTERY BOOSTER

OUR PRICE £10·50
+40p P. & P.

No less than **3 VHF BANDS.** Picks up **Aircraft Transmissions, Pop Pirates, Taxis, Ambulances, Local Radio, Continental and all BBC, VHF Stations plus fascinating Public Service Transmissions we are not allowed to mention! Even TV sound in certain areas. PLUS A SPECIAL WEATHERBAND.** Frequency ranges: MW540-1600kHz, FM88-108MHz, Airband 108-145 MHz, VHF 145-175 MHz, 23 semiconductors—12 transistors, 11 diodes and thermistors. Automatic frequency control. 31in telescopic aerial. Runs off mains a.c. 230/250V or off 4 U11 batteries, or use re-chargeable nickel alkali cell. Finished in strong leather grained case with carrying handle. Approx. size 10¾in × 6¾in × 3¾in. Written guarantee. Special **magnetic ear-piece for personal listening, dry batteries free. HURRY!** Limited quantity only from Sonic Sound.

OUR PRICE £28·95
+50p P. & P.

Tune into the world with this amazing communications receiver. A truly exceptional unit in performance and looks—leatherette with Stainless steel trim. Looks good anywhere. Use either as a portable with standard batteries or plug it directly into 220-240V domestic mains supply. 14 transistors; 9 diodes; 1 thermistor. Internal ferrite rod antenna plus telescopic aerial. Separate tone, volume and tuning controls with push-button selectors for the **8 WAVEBANDS.** Complete with Hi-Fi earphone for personal listening. Frequency ranges: **Long wave** 150-350 kHz. **Medium** 353-1605 kHz. **Marine** 1·6-4·5 MHz. **Short Wave** 12-24 MHz. **FM/VHF** 88-108 MHz. **Aircraft** 108-135 MHz. **PUBLIC SERVICE BANDS** 135-174 MHz. Fully guaranteed. *N.B. The Ministry of Post & Telecommunications has pointed out that a licence (not generally available to the public) is required for reception of transmissions by Fire Brigade, Aircraft, Shipping, etc.*

SONIC SOUND AUDIO LTD. (Dept. PE11), 372 EDGWARE ROAD
LONDON, W.2. Tel. 01-723 0094
Callers welcome Mon. to Sat. 9 a.m.-6 p.m.

NOW! A FAST *EASY* WAY TO LEARN BASIC RADIO & ELECTRONICS

Build as you learn with the exciting new TECHNATRON Outfit! No mathematics. No soldering—you learn the *practical* way.

Learn basic Radio and Electronics at home—the fast, modern way. Give yourself essential technical "know-how"—like reading circuits, assembling standard components, experimenting, building—quickly and without effort, and enjoy every moment. B.I.E.T.'s simplified study method and the remarkable TECHNATRON Self-Build Outfit take the mystery out of the subject, making learning easy and interesting.

Even if you don't know the first thing about Radio now, you'll build your own Radio set within a month or so!

. . . and what's more, you will understand exactly what you are doing. The TECHNATRON Outfit contains everything you need, from tools to transistors—even a versatile Multimeter which we teach you to use. All you need give is a little of your spare time and the surprisingly low fee, payable monthly if you wish. And the equipment remains yours, so you can use it again and again.

You LEARN—but it's as fascinating as a hobby.

Among many other interesting experiments, the Radio set you build—and it's a good one—is really a bonus. This is first and last a teaching course, but the training is as fascinating as any hobby and it could be the springboard for a career in Radio and Electronics.

A 14-year-old could understand and benefit from this course—but it teaches the real thing. The easy to understand, practical projects—from a burglar-alarm to a sophisticated Radio set—help you master basic Radio and Electronics—even if you are a "non-technical" type. And, if you want to make it a career, B.I.E.T. has a fine range of courses up to City and Guilds standards.

Specialist Booklet

If you wish to make a career in Electronics, send for your FREE copy of "NEW OPPORTUNITIES". This brand new booklet—just out—tells you all about TECHNATRON and B.I.E.T.'s full range of courses.

FREE

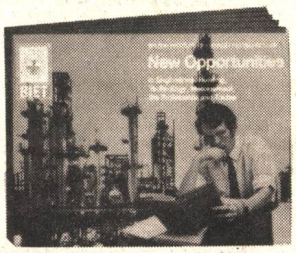

BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY

Dept. BPE14, ALDERMASTON COURT, READING RG7 4PF

Accredited by the Council for the Accreditation of Correspondence Colleges.

POST THIS COUPON FOR FREE BOOK

CL | BPE14

NAME (BLOCK CAPITALS) ..... AGE .....

ADDRESS .....

.....

.....

SUBJECT OF INTEREST .....

FERRANTI ZN414 MICROCIRCUIT RADIO

AS SEEN ON TV!

Only £1.32

WITH FREE DATA

WE ARE SPECIALISTS IN FERRANTI SEMICONDUCTORS

BFS59	15p	ZTX310	9p	ZTX504	43p	ZS170	10p
BFS60	20p	ZTX311	10p	ZTX510	17p	ZS171	13p
BFS61	20p	ZTX312	10p	ZTX530	21p	ZS172	16p
BFS96	15p	ZTX313	11p	ZTX531	22p	ZS174	17p
BFS97	23p	ZTX314	13p	ZTX550	17p	ZS176	23p
BFS98	20p	ZTX320	31p	ZTX551	17p	ZS178	38p
ZTX107	9p	ZTX330	15p	2N3055	72p	ZS270	11p
ZTX108	8p	ZTX331	16p			ZS271	16p
ZTX109	11p	ZTX382	13p	DIODES		ZS272	18p
ZTX212	14p	ZTX383	15p	ZS120	8p	ZS274	19p
ZTX213	14p	ZTX384	18p	ZS121	10p	ZS276	26p
ZTX214	15p	ZTX450	17p	ZS122	13p	ZS278	37p
ZTX300	12p	ZTX451	17p	ZS123	16p		
ZTX301	13p	ZTX500	12p	ZS124	18p	ZENERS	
ZTX302	17p	ZTX501	13p	ZS140	25p	KS030A to	
ZTX303	14p	ZTX502	17p	ZS141	43p	KS180A—	
ZTX304	21p	ZTX503	14p	ZS142	33p	all types	19p

ALL DEVICES TOP GRADE, BRAND NEW, AND FULLY GUARANTEED WE CAN SUPPLY ANY FERRANTI DEVICE. Send S.A.E. for quotation.
R.C.A. CA3090Q £4·73; CA3075 £1·49.
MOTOROLA. MJE2955 £1·17; MJE3055 72p; 2N4444 £2·48.
P.E. TRIFFID. ZT1711 24p; 2N1132 25p.
POSTAGE AND PACKING 10p. Free over £2. Send S.A.E. for our full price list and data sheet.

ALL PRICES INCLUDE V.A.T. 10% DISCOUNT IF YOU ORDER BEFORE MARCH 28th

DAVIAN ELECTRONICS

PO BOX 38, OLDHAM, LANCS. OL2 6XJ

Lasky's Audio-Tronics Catalogue 1973

The great 1973 edition of Lasky's famous Audio-Tronics catalogue is available – FREE on request. The 48 newspaper size pages – many in full colour – are packed with 1,000s of items from the largest stocks in Great Britain of everything for the Radio and Hi-Fi enthusiast, Electronics hobbyist, Serviceman and Communications Ham. Over half the pages are devoted exclusively to every aspect of Hi-Fi (including Lasky's budget Stereo Systems and Package Deals), Tape recording and Audio Accessories. See the great new Lasky's Credit Plan Scheme – enabling you to buy your ideal choice of equipment on easy terms.

FREE Send this coupon with 15p for post and inclusion on our regular mailing list.

NAME .....

ADDRESS .....

.....

PE2

.....

LASKY'S RADIO LIMITED, 3-15 CAVELL STREET, LONDON E.1.

SAXON ENTERTAINMENTS

STANDARD and CUSTOM-BUILT AUDIO and ELECTRONIC EQUIPMENT
NEW and SECONDHAND MUSICAL INSTRUMENTS. MAIN DISTRIBUTORS
FOR A.K.G. HIGH QUALITY MICROPHONES

SA25-SA35-SA100

LOW-PRICED AUDIO MODULES FOR
DOMESTIC and COMMERCIAL USE

THESE THREE MODULES HAVE ENJOYED UNPARALLELED SUCCESS DURING THE FIRST FEW MONTHS OF THEIR BEING MADE AVAILABLE TO THE GENERAL PUBLIC. WE ARE PLEASED TO ANNOUNCE THAT WE CAN NOW OFFER FAST DISPATCH ON MOST OF OUR ADVERTISED ITEMS, INCLUDING THESE THREE MODULES.

SA25 £2·95 carr. free
25 WATTS R.M.S. 7 transistors, 7 diodes

SA35 £4·45 carr. free
35 WATTS R.M.S. 7 transistors, 7 diodes

SA100 £10·90 carr. free
100 WATTS R.M.S. 11 transistors, 6 diodes

ALL THREE MODULES HAVE OPEN AND SHORT CIRCUIT PROTECTION, AND THE SA100 IS PROOF AGAINST OVER-DISSIPATION AND FAULTY INDUCTIVE LOADS.

ONLY ADVANCED DESIGN TECHNIQUES MAKE THESE EXTRAORDINARILY LOW PRICES POSSIBLE.

BRIEF SPEC. FOR ALL THREE MODULES

Freq. response	20–40,000Hz ± 1dB
Distortion	0·2% at 1kHz
Loads	4 to 16 ohms
Quiescent current	15mA
Noise	Better than −75dB
Supply voltage	25–45V, SA25/35 40–70V, SA100
Size	4½in × 4in × 1in (SA100) 4in × 3in × 1in (SA25, SA35)

Circuits, connecting instructions and application data are supplied free with all modules.

POWER SUPPLIES FOR THE SA25/35 and SA100 AUDIO MODULES

PU45	Unstabilised supply for 2 SA25/35's, **£4·90.**
PU70	Unstabilised supply for one or two SA100's, **£7·75,** carr. 40p
MT45	Transformer for above, heavy duty, **£2·85,** carr. 20p
PS45	Stabilised module for 2 SA25's or two SA35's, **£3·50,** carr. free
MT70	Transformer for PS70, **£4·90,** carr. 40p
PS70	Stabilised supply module for one or two SA100's, **£4·90,** carr. free

ALL MODULES ARE BUILT ON GLASS FIBRE P.C. BOARD

OTHER SAXON PRODUCTS . . .

120 WATT HEAVY DUTY MODULE

£13·90+20p carr. or with supply **£18·95**+40p carr.

Featuring a rugged class A driver stage, this module will run from all our mixers etc., and most other makes of mixer. It delivers 120W into an eight ohm load and employs 4 TO3 can (115W) output transistors.

SPECIFICATION

Power output	120W into 8 ohms
Freq. response	20–20,000Hz ± 2dB
Input sensitivity	200mV into 10K
Construction	Fibreglass board
Size	8in × 4in × 4in (5in with supply)

Low distortion parallel push–pull output stage.

NEW: 160 Watt version & supply **£27·90**

SINGLE CHANNEL SOUND/LIGHT CONVERTER

This compact and reliable unit operates from amplifiers with outputs from 5–100W. Does not impose a heavy load on the amplifier, or, if connected in the wrong polarity, cause any damage, as with some units.

Operation is simplicity itself and the unit is fully fused. The unit is supplied to function from bass notes but may easily be converted to respond only to treble or mid-range notes by the addition of components costing less than 5p.

£8·90 carr. free

THREE CHANNEL SOUND TO LIGHT UNIT

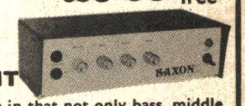

Handling the total of 3,000W (3kW) this unit is unique for its price in that not only bass middle and treble but also master controls are provided. Two amplifier sockets eliminate the need for split leads, etc. Supplied in tough white steel case with a blue hooded cover. Fully guaranteed.

£19·75 carr. 30p

MONO VERSION **£6·50,** carr. 20p
(As illustrated below. S.A.E. details. 9V operation)
OUTPUTS UP TO 1V RMS

£15·80 carr. 30p
SAXON STEREO CONTROL UNIT

Two decks, and full headphone monitoring. The unit is mains operated and measures 17½in × 3in × 4in deep and is finished with a smart white on black facia. The controls are: Left/Right deck fader, volume, bass, treble, headphone selector and volume, microphone volume, bass, treble, mains on/off. **THIS IS A MUST FOR THE HOME BUILT HIGH QUALITY DISCOTHEQUE AND IS COMPARABLE TO UNITS AT OVER TWICE THE PRICE.**

COMPLETE AMPLIFIERS

THE CS 100. £34·90 carr. free

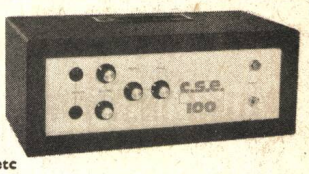

This versatile unit is now available in a black vynide case and so represents even better value than ever, delivering speech and music powers of up to 100W R.M.S. and continuous signal outputs of 70W.
Two individually controlled inputs with wide range bass and treble controls. Ideal for small groups, D.J's, etc

The SAXON 100. £48·50, carr. free.
With an R.M.S. output of 120W speech and music, 100W continuous power, four individually controlled F.E.T. input stages and wide range bass and treble controls, this amplifier has established itself as a unit offering quality and reliability at low cost.

LOUDSPEAKERS **British made bargains ! ! !**

12in 25W 8/15 ohms **£5·95,** carr. 30p. 15in 50W 8/15 ohm, **£14·50,** carr. 50p.
12in 40W 15,000 gauss magnet system 8/15 ohm, **£11·50,** carr. 40p.

A.K.G. MICROPHONES suitable for disco, group or general P.A. use
D11DHL r.r.p. £11, our price **£9·45** post free.
D190C High Z r.r.p. £21·50, our price **£17·45** post free.
D1000C 24 ct. gold plate r.r.p. £37, our price **£32** post free.

SEND S.A.E. FOR OUR A.K.G. PRICE LIST. DISCOUNTS ON ALL MICS.

CALLERS AND MAIL ORDER:
351 Whitehorse Road
Thornton Heath, Surrey
Tel. 01-689 3685

CALLERS ONLY:
OUR NEW DISTRIBUTORS.
CIRCLE SOUND
328-330 The Banks
Rochester.
Medway 404199

BUSINESS HOURS:
9.30 a.m. to 5.30 p.m.

TERMS OF BUSINESS: **C.W.O. or C.O.D. (35p extra).** All cash in regd. envelopes please! Telephone orders to our CROYDON BRANCH. TRADE AND EXPORT ENQUIRIES INVITED

PCB'S FROM PHONOSICS

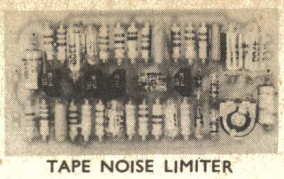

TAPE NOISE LIMITER

All PCB's Fibreglass, Drilled, Roller Tinned Circuit Diagram and Assembly. Notes Free with each PCB. Rotary Pots supplied as standard except where stated. PCB's designed by Phonosonics except where stated otherwise.

DESIGNS PUBLISHED IN P.E.

AURORA (Apr./Aug. 71) Multichannel Sound Controlled Light
S/c's (excl. SCRs), Rs, Cs, Cores, Pots., 8 ch., **£17·75**; 4 ch., **£10·15**. Power Supply (supplies 8 chans.), unstab., **£2·85**; stab., **£3·65**. PCB (4½in × 11in) for P/A and 4 chans. incl. pots, **£2·35**. PCB (4½in × 5in) for PSU, Sync. Gen, 8 cores, 8 SCRs, **£1·35**.

A.F. SIGNAL GENERATOR (Nov. 72)
S/c's, Rs, Cs, Pots, Sw's, **£2·25**. PCB (2½in × 4in) also holds Sw's, **90p**.

AUDIO MIXER (Jan. 72)
Rs, Cs, Pots (i.c. excl.), PCB (1½in × 2in), **£1·55**.

BIOLOGICAL AMPLIFIER (Jan./Feb. 73)—Pre-amp Set
S/c's, Rs, Cs, Pots (i.c.'s excl.) **£2·05**. PCB (1½in × 3½in), **85p**.

CALLERCORD (Jul./Aug. 72) Automatic Answering Machine
S/c's, Rs, Cs, Pots, Switches, Relays, Transformer, **£12·15**. PCB (4in × 7½in) also holds relays, connectors, **£1·50**. Recorder, **£6·95**. Pips Gen with PCB, **£1·50**.

DOOR BELL YODELLER (Apr. 71)—S/c's, Rs, Cs, Pots, Transformer, Loudspeaker, PCB (3in × 3½in), **£7·70**.

ELECTRONIC PIANO (Sept. 72/Jan. 73) PRICES DOWN!
PA/Trem—Rs, Cs, Pots (excl. 2K), **£1·70**. PCB as publ., **£1·50**. Power Supply—Rs, Cs, **£1·10**. PCB as publ., **90p**. Pitch 1–12—Rs, Cs, **£1·90** each set. Pitch 13—Rs, Cs, **£1·30**. Pitch PCB as publ., **£1·80** each. Combined sets for PA/Trem, PSU, all 13 Pitch—Rs, Cs, Pots (excl. 2K), **£23·70**; PCBs, **£23·20**.

GEMINI STEREO AMP (Nov. 70/Mar. 71) Stereo Sets and PCBs
Pre-Amp—S/c's, Cs, Pots, Maka-Sw's—with ¼W 2% M.O. Rs, **£13·45**—with ¼W 5% C.F. Rs, **£11·20**.—with ¼W 5% C.F. Rs, **£10·75**. PCB (3½in × 10½in) for kits with M.O. or ¼W C.F. Rs. Holds pots and Maka-Sw's, **£2·10**. Main Amp—Rs, Cs, Pots, **£5·40**. PCB (3½in × 5in), **£1·40**. PSU—Rs, Cs, Pot, **£3·70**. PCB (2in × 4in), **75p**.

GEMINI STEREO TUNER (Apr./Jun. 72)
Rs, Cs, Pot, **£3·80**. PCB as published, **£1·80**.

LOGICAL RADIO CONTROL (Dec. 71/Jan. 72)—Sets incl. Rs, Cs, S/c's and Pots (where requ.) but excl. I.C's. Coder 1 and Clock Pulse Gen., **£2·95**. Coder 2A, **£2·80**. Coder 2B, **£3**. Decoder, **55p**. PCBs as pub., **75p each**.

MODEL SERVO CONTROL (Feb./Mar. 72)—Sets incl. Rs, Cs, S/c's and Pots (where requ.) but excl. I.C's. Servo Amps: "A", **£1·40**; "B", **£2·55**; "C", **£1·30**. Fail-Safe, **65p**. PCBs as published: "A" and "B", **60p each**; "C" and Fail-Safe, **50p each**.

MICROPHONE MIXER (Apr. 69)—S/c's, Rs, Cs, Pots, **£2·90**. PCB (3¾in × 4¼in)—also holds pots, **£1·20**.

PHOTOPRINT PROCESS CONTROL (Jan./Feb. 72)
Finds exposure, controls timing, stabilises mains voltage. S/c's, SCR, LDR, Rs, Cs, Pots, Relay, Keyswitch, T/former, **£7·60**. PCB (3½in × 5½in) also holds pots, relay, keyswitch, **£1·20**.

SOUND SYNTHESISER—Details on request.

TAPE NOISE LIMITER (Feb. 72)—Mono Circuit
S/c's, Rs, Cs, Pot, PCB (1½in × 3in), **£2·20**. Regulated Power Supply (will feed 2 units) and PCB (1½in × 2½in), **£3·20**.

ULTRASONIC TRANSMITTER-RECEIVER (May 72)
Rs, Cs, Pot, S/c's, Transducers, Relay, **£9·90**. Dual PCB (2in × 5½in), **75p**.

VERSATILE LIGHT EFFECTS UNIT (Jun. 72)—Single Channel Sound Controlled Light—also has built-in variable strobe. S/c's (excl. SCR), Rs, Cs, Pots, T/formers, Keyswitch, **£8·85**. PCB (3½in × 7½in) also holds Pots, Sw, T/former (T/T7), **£1·50**.

SOME OTHER DESIGNS AVAILABLE

REVERBERATION UNIT (Practical Wireless Nov.–Dec. 72)
S/c's, Rs, Cs, Slider Pots, T/former, **£6·80** (with rotary pots **£5·70**). PCB (2in × 11½in) also holds sliders (compatible with publ. panel) **£1·20**.

8 WATT AMPLIFIER (Practical Wireless Nov. 72)
Main Amplifier—S/c's, Rs, Cs, Pot (Mono Set), **£3·90**. PCB (2½in × 3in) (Mono), **60p**. Pre-amp—S/c's, Rs, Cs, Pots, Maka-Sw., Mono, **£2·50**; Stereo, **£5·20**. PCB (3½in × 7½in) (Stereo)—also holds all pots and Maka-Sw., **£1·50**.

AURORA AUXILIARY CONTROL UNIT (2 variable freq. strobe gens. and 4 variable amplitude freq. gens.), Rs, Cs, Pots, S/c's, **£3·25**. PCB (3¾in × 5½in), also holds all pots, **£1·35**.

THYRISTORS (400V P.I.V.)
1A **50p**. 3A **55p**. 7A **70p**. 16A **95p**.

SLIDER POTS (PCB Mounting)
Mono, **40p**; Dual, **60p**; Knobs, **13p**.

S.A.E. for Free List of these and other designs.

Orders: U.K. 10p *P. & P. Overseas P. & P. at cost.*
V.A.T.—All prices V.A.T. Exclusive

PHONOSONICS, Dept. P.E.4, 25 Kentish Road, Belvedere, Kent DA17 5BW. **Mail Order only**

Vary the strength of your lighting with a DIMMASWITCH

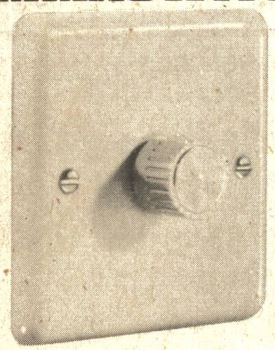

The DIMMASWITCH is an attractive and efficient dimmer unit which fits in place of the normal light switch and is connected up in exactly the same way. The white mounting plate of the DIMMASWITCH matches modern electric fittings. Two models are available, with the bright chrome knob controlling up to 300w or 600w of all lights except fluorescents at mains voltages from 200-250v, 50Hz. The DIMMASWITCH has built-in radio interference suppression:

600 Watt—**£3·20***. Kit Form **£2·70***
300 Watt—**£2·70***. Kit Form **£2·20***

All plus 10p post and packing

***From 1st April please add the appropriate percentage of V.A.T. increase**

Please send C.W.O. to:

DEXTER & COMPANY
1 ULVER HOUSE, 19 KING STREET
CHESTER CH1 2AH Tel. 0244-25883

VEROBOARD

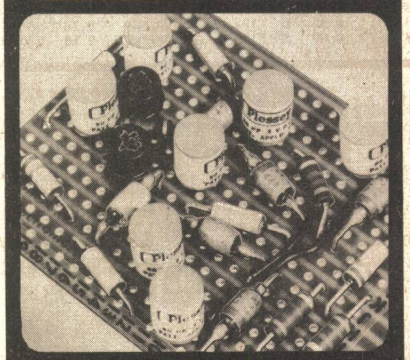

VEROBOARDS GIVE A PROFESSIONAL FINISH TO YOUR WORK

0.1" and 0.15" pitch, plain and copper clad universal circuit boards.

AVAILABLE FROM YOUR LOCAL RETAILER.

TRADE DISTRIBUTOR N. Rose (Electrical) Ltd., London, W.C.1.

vero

VERO ELECTRONICS LTD.
Industrial Estate, Chandler's Ford, SO5 3ZR Tel: Chandler's Ford 2952

EX COMPUTER PRINTED CIRCUIT PANELS
2 × 4in packed with semiconductors and top quality resistors, capacitors, diodes, etc. Our price 10 boards **50p** (8p). With a guaranteed min. of 35 transistors—data included.

SPECIAL BARGAIN PACK
25 boards for £1 (25p).

ELECTROLYTICS
10,000μ 75V, 33,000μ 40V, 4½ × 2½in dia., 25,000μ 25V, 20,000μ 30V, 8,000μ 55V, 4½ × 3in dia. **50p** (12p). 15,000μ 15V, 4½ × 2in dia. **20p** (10p). 2,000μ 25V wire ended, 3 × 1in dia. **15p** (5p) or 12 for **£1·50** (15p).

250 MIXED CAPACITORS **60p** (8p)
250 MIXED RESISTORS **60p** (8p)
3A STUD RECTIFIERS, 100 p.i.v. 4 for **50p** (5p)
ASSORTED RELAYS 8 for **£1** (25p)
SUB-MIN. CO-AX. PLUGS & SKTS. 4 pairs **50p** (5p)
MINIATURE GLASS NEONS 12 for **50p** (5p)
REED RELAYS, MIXED 10 for **50p** (5p)
MICRO SWITCHES, MIXED 8 for **50p** (8p)
PAPST EXTRACTOR/BLOWER FANS 100cfm 4½ × 4½ × 2in **£3·50** (28p)
QUARTZ HALOGEN BULBS 12V 55W **50p** (5p)

Postage and package for each item shown in brackets.

KEYTRONICS
(Mail Order only)
44 EARLS COURT ROAD
LONDON W8
01-478 8499

THIS IS THE FIRST PAGE OF THE GREAT BI-PAK SECTION

BRAND NEW FULLY GUARANTEED DEVICES

AC107	0·20	AD162	0·33	BC148	0·10	BD137	0·45	BF188	0·40	OC19	0·35	2G371	0·16	2N2219	0·20	2N3054	0·46	2N4059	0·10
AC113	0·20	AD161 &		BC149	0·12	BD138	0·50	BF194	0·12	OC20	0·63	2G371B	0·12	2N2220	0·22	2N3055	0·50	2N4060	0·12
AC115	0·23	AD162 (MP)		BC150	0·18	BD139	0·55	BF195	0·12	OC22	0·38	2G373	0·17	2N2221	0·20	2N3391	0·14	2N4061	0·12
AC117K	0·20		0·55	BC151	0·20	BD140	0·60	BF196	0·14	OC23	0·42	2G374	0·17	2N2222	0·20	2N3391A	0·16	2N4062	0·12
AC122	0·12	ADT140	0·50	BC152	0·17	BD155	0·80	BF197	0·14	OC24	0·56	2G377	0·30	2N2368	0·17	2N3392	0·14	2N4284	0·17
AC125	0·17	AF114	0·24	BC153	0·28	BD175	0·60	BF200	0·45	OC25	0·38	2G378	0·16	2N2369	0·14	2N3393	0·14	2N4285	0·17
AC126	0·17	AF115	0·24	BC154	0·30	BD176	0·60	BF222	0·95	OC26	0·25	2G381	0·16	2N2369A	0·14	2N3394	0·14	2N4286	0·17
AC127	0·17	AF116	0·24	BC157	0·18	BD177	0·65	BF257	0·45	OC28	0·50	2G382	0·16	2N2411	0·24	2N3395	0·17	2N4287	0·17
AC128	0·17	AF117	0·24	BC158	0·12	BD178	0·65	BF258	0·60	OC29	0·50	2G401	0·30	2N2412	0·24	2N3402	0·21	2N4288	0·17
AC132	0·14	AF118	0·35	BC159	0·12	BD179	0·70	BF259	0·85	OC35	0·42	2G414	0·30	2N2646	0·47	2N3403	0·21	2N4289	0·17
AC134	0·14	AF124	0·30	BC160	0·45	BD180	0·70	BF262	0·55	OC36	0·50	2G417	0·25	2N2711	0·21	2N3404	0·28	2N4290	0·17
AC137	0·14	AF125	0·25	BC161	0·50	BD185	0·65	BF263	0·55	OC41	0·20	2N388	0·35	2N2712	0·21	2N3405	0·42	2N4291	0·17
AC141	0·14	AF126	0·28	BC167	0·12	BD186	0·65	BF270	0·35	OC42	0·24	2N388A	0·55	2N2714	0·21	2N3414	0·15	2N4292	0·17
AC141K	0·17	AF127	0·28	BC168	0·12	BD187	0·70	BF271	0·30	OC44	0·15	2N404	0·20	2N2904	0·17	2N3415	0·15	2N4293	0·17
AC142	0·14	AF139	0·30	BC169	0·12	BD188	0·70	BF272	0·80	OC45	0·12	2N404A	0·28	2N2904A	0·21	2N3416	0·28	2N5172	0·12
AC142K	0·17	AF178	0·50	BC170	0·12	BD189	0·75	BF273	0·35	OC70	0·10	2N524	0·42	2N2905	0·21	2N3417	0·28	2N5457	0·32
AC151	0·15	AF179	0·50	BC171	0·14	BD190	0·75	BF274	0·35	OC71	0·10	2N527	0·49	2N2905A	0·21	2N3525	0·75	2N5458	0·32
AC154	0·20	AF180	0·50	BC172	0·14	BD195	0·85	BFW10	0·60	OC72	0·14	2N598	0·42	2N2906	0·15	2N3646	0·09	2N5459	0·40
AC155	0·20	AF181	0·45	BC173	0·14	BD196	0·85	BFX29	0·27	OC74	0·14	2N599	0·45	2N2906A	0·18	2N3702	0·10	28301	0·50
AC156	0·20	AF186	0·45	BC174	0·14	BD197	0·90	BFX84	0·22	OC75	0·15	2N696	0·12	2N2907	0·20	2N3703	0·10	28302A	0·42
AC157	0·24	AF239	0·37	BC175	0·22	BD198	0·90	BFX85	0·30	OC76	0·15	2N697	0·13	2N2907A	0·22	2N3704	0·11	28302	0·42
AC165	0·20	AL102	0·65	BC177	0·19	BD199	0·95	BFX86	0·22	OC77	0·25	2N698	0·24	2N292a	0·14	2N3705	0·10	28303	0·55
AC166	0·20	AL103	0·65	BC178	0·19	BD200	0·95	BFX87	0·24	OC81	0·15	2N699	0·35	2N2924	0·14	2N3706	0·09	28304	0·70
AC167	0·20	ASY26	0·25	BC179	0·19	BD205	0·80	BFX88	0·22	OC81D	0·15	2N706	0·08	2N2925	0·14	2N3707	0·11	28305	0·84
AC168	0·24	ASY27	0·30	BC180	0·24	BD206	0·80	BFY50	0·20	OC82	0·15	2N706A	0·09	2N2926 (G)		2N3708	0·07	28306	0·84
AC169	0·14	ASY28	0·25	BC181	0·24	BD207	0·95	BFY51	0·20	OC82D	0·15	2N708	0·12		0·12	2N3709	0·09	28307	0·84
AC176	0·20	ASY29	0·25	BC182	0·10	BD208	0·95	BFY52	0·20	OC83	0·20	2N711	0·30	2N2926 (Y)		2N3710	0·09	28321	0·56
AC177	0·24	ASY50	0·25	BC182L	0·10	BDY20	1·00	BFY53	0·17	OC84	0·20	2N717	0·35		0·11	2N3711	0·09	28322	0·42
AC178	0·28	ASY51	0·25	BC183	0·10	BF115	0·24	BPX25	0·85	OC139	0·20	2N718	0·24	2N2926 (O)		2N3819	0·28	28322A	0·42
AC179	0·28	ASY52	0·25	BC183L	0·10	BF117	0·45	BSX19	0·15	OC140	0·20	2N718A	0·50		0·10	2N3820	0·50	28323	0·56
AC180	0·17	ASY54	0·25	BC184	0·12	BF118	0·70	BSX20	0·15	OC169	0·25	2N726	0·28	2N2926 (R)		2N3821	0·35	28324	0·70
AC180K	0·20	ASY55	0·25	BC184L	0·12	BF119	0·70	BSY25	0·15	OC170	0·25	2N727	0·28		0·10	2N3823	0·28	28325	0·70
AC181	0·17	ASY56	0·25	BC186	0·28	BF121	0·45	BSY26	0·15	OC171	0·25	2N743	0·20	2N2926 (B)		2N3903	0·28	28326	0·70
AC181K	0·20	ASY57	0·25	BC187	0·28	BF123	0·50	BSY27	0·15	OC200	0·25	2N744	0·20		0·10	2N3904	0·30	28327	0·70
AC187	0·22	ASY58	0·25	BC207	0·11	BF125	0·45	BSY28	0·15	OC201	0·28	2N914	0·14	2N3010	0·70	2N3905	0·28	28701	0·42
AC187K	0·20	ASZ21	0·40	BC208	0·11	BF127	0·50	BSY29	0·15	OC202	0·28	2N918	0·30	2N3011	0·14	2N3906	0·27	40361	0·40
AC188	0·22	BC107	0·09	BC209	0·12	BF152	0·55	BSY38	0·18	OC203	0·25	2N929	0·21	2N3053	0·17	2N4058	0·12	40362	0·45
AC188K	0·20	BC108	0·09	BC212L	0·11	BF153	0·45	BSY39	0·18	OC204	0·25	2N930	0·21						
ACY17	0·25	BC109	0·10	BC213L	0·11	BF154	0·45	BSY40	0·28	OC205	0·35	2N1131	0·20						
ACY18	0·20	BC113	0·10	BC214L	0·14	BF155	0·70	BSY41	0·28	OC309	0·40	2N1132	0·22						
ACY19	0·20	BC114	0·15	BC225	0·25	BF156	0·48	BSY95	0·12	P346A	0·20	2N1302	0·14						
ACY20	0·20	BC115	0·15	BC226	0·35	BF157	0·55	BSY95A	0·12	P397	0·42	2N1303	0·14						
ACY21	0·20	BC116	0·15	BCY30	0·24	BF158	0·55	Bu105	2·00	OCP71	0·43	2N1304	0·17						
ACY22	0·16	BC117	0·15	BCY31	0·26	BF159	0·60	C111E	0·50	ORP12	0·43	2N1305	0·17						
ACY27	0·18	BC118	0·10	BCY32	0·30	BF160	0·40	C400	0·30	ORP60	0·40	2N1306	0·21						
ACY28	0·19	BC119	0·30	BCY33	0·22	BF162	0·40	C407	0·25	ORP61	0·40	2N1307	0·21						
ACY29	0·35	BC120	0·80	BCY34	0·25	BF163	0·40	C424	0·20	ST140	0·12	2N1308	0·23						
ACY30	0·28	BC125	0·12	BCY70	0·14	BF164	0·40	C425	0·50	ST141	0·17	2N1309	0·23						
ACY31	0·28	BC126	0·18	BCY71	0·18	BF165	0·40	C426	0·35	TIS43	0·30	2N1613	0·20						
ACY34	0·21	BC132	0·12	BCY72	0·14	BF167	0·22	C428	0·20	UT46	0·27	2N1711	0·20						
ACY35	0·21	BC134	0·18	BCZ10	0·20	BF173	0·22	C441	0·30	2G301	0·09	2N1889	0·32						
ACY36	0·28	BC135	0·12	BCZ11	0·25	BF176	0·35	C442	0·30	2G302	0·19	2N1890	0·45						
ACY40	0·17	BC136	0·15	BCZ12	0·25	BF177	0·35	C444	0·35	2G303	0·19	2N1893	0·37						
ACY41	0·18	BC137	0·15	BD121	0·60	BF178	0·30	C450	0·22	2G304	0·24	2N2147	0·72						
ACY44	0·35	BC139	0·40	BD123	0·65	BF179	0·30	MAT100	0·19	2G306	0·40	2N2148	0·57						
AD130	0·38	BC140	0·30	BD124	0·60	BF180	0·30	MAT101	0·20	2G308	0·35	2N2160	0·60						
AD140	0·48	BC141	0·30	BD131	0·50	BF181	0·30	MAT120	0·19	2G309	0·35	2N2192	0·35						
AD142	0·48	BC142	0·30	BD132	0·60	BF182	0·40	MAT121	0·20	2G339	0·20	2N2193	0·35						
AD143	0·38	BC143	0·30	BD133	0·65	BF183	0·40	MPF102	0·42	2G339A	0·16	2N2194	0·35						
AD149	0·50	BC145	0·45	BD135	0·40	BF184	0·25	MPF104	0·37	2G344	0·18	2N2217	0·22						
AD161	0·33	BC147	0·10	BD136	0·40	BF185	0·30	MPF105	0·37	2G345	0·16	2N2218	0·20						

DIODES AND RECTIFIERS

AA119	0·08	BY133	0·21	OA10	0·35
AA120	0·08	BY164	0·50	OA47	0·07
AA129	0·08	BYX38/30		OA70	0·07
AAY30	0·09		0·42	OA79	0·07
AAZ13	0·10	BYZ10	0·35	OA81	0·07
BA100	0·10	BYZ11	0·30	OA85	0·09
BA116	0·21	BYZ12	0·30	OA90	0·06
BA126	0·22	BYZ13	0·25	OA91	0·06
BA148	0·14	BYZ16	0·40	OA95	0·07
BA154	0·12	BYZ17	0·35	OA200	0·06
BA155	0·14	BYZ18	0·35	OA202	0·07
BA156	0·13	BYZ19	0·28	SD10	0·05
BY100	0·15	CG62		SD19	0·05
BY101	0·12	(Eg) OA91		IN34	0·07
BY105	0·17		0·05	IN34A	0·07
BY114	0·12	CG651		1N914	0·06
BY126	0·14	(Eq) OA70-		1N916	0·06
BY127	0·15	OA79	0·06	IN414B	0·06
BY128	0·15	OA5	0·35	IS021	0·10
BY130	0·16	OA58L	0·21	IS951	0·06

Cut these 3 pages out and keep for reference

NEW COMPONENT PAK BARGAINS

Pack No.	Qty.	Description	Price
C 1	250	Resistors mixed values approx. count by weight	0·50
C 2	200	Capacitors mixed values approx. count by weight	0·50
C 3	50	Precision Resistors ·1%, ·01% mixed values	0·50
C 4	75	¼th W Resistors mixed preferred values	0·50
C 5	5	Pieces assorted Ferrite Rods	0·50
C 6	2	Tuning Gangs, MW/LW VHF	0·50
C 7	1	Pack Wire 50 metres assorted colours	0·50
C 8	10	Reed Switches	0·50
C 9	3	Micro Switches	0·50
C10	15	Assorted Pots & Pre-Sets	0·50
C11	5	Jack Sockets 3 × 3·5m 2 × Standard Switch Types	0·50
C12	40	Paper Condensers preferred types mixed values	0·50
C13	20	Electrolytics Trans. types	0·50
C14	1	Pack assorted Hardware—Nuts/Bolts, Grommets etc.	0·50
C15	4	Mains Toggle Switches, 2 Amp D/P	0·50
C16	20	Assorted Tag Strips & Panels	0·50
C17	10	Assorted Control Knobs	0·50
C18	4	Rotary Wave Change Switches	0·50
C19	3	Relays 6—24V Operating	0·50
C20	4	Sheets Copper Laminate approx. 10" × 7"	0·50

Please add 10p post and packing on all component packs, plus a further 10p on pack Nos. C1, C2, C19, C20.

PLUS-MUCH MORE - **SEND NOW FOR THE BI-PAK *"Component Catalogue"***

5p to cover postage, etc.

Please note that as from April 1st 10% must be added to all the above prices.

JUMBO COMPONENT PAKS

MIXED ELECTRONIC COMPONENTS
Exceptionally good value

Resistors, capacitors, pots, electrolytics and coils plus many other useful items. Approximately 3lbs in weight. Price incl. P. & P. **£1·50 only.**

BRAND NEW POST OFFICE TYPE TELEPHONE DIALS

ONLY 75p each

THE NEW S.G.S. EA 1000 AUDIO AMP MODULE ***Guarantee***

3 Watts R.M.S. ONLY £2·63 each

Modual Tested and Guaranteed.
Qty. 1—9 **£2·63**; 10—25 **£2·28** Price each. Larger quantities quoted on request. Full hook-up diagrams and complete technical data supplied free with each modual or available separately at 10p each.

SYSTEM 12 STEREO

Each Kit contains two Amplifier Modules, 3 watts RMS, two loudspeakers, 15 ohms, the pre-amplifier, transformer, power supply module, front panel and other accessories, as well as an illustrated stage-by-stage instruction booklet designed for the beginner.
Further details available on request.

ONLY £16·95 FREE P. & P.

NOW-TURN OVER FOR MORE FANTASTIC OFFERS

The largest selection

NEW LOW PRICE TESTED S.C.R.'s

PIV	1A TO5	3A TO66	5A TO66	5A TO64	7A TO48	10A TO48	16A TO48	30A TO48
50	0·23	0·25	0·35	0·35	0·47	0·50	0·53	1·15
100	0·25	0·33	0·47	0·47	0·50	0·58	0·63	1·40
200	0·35	0·37	0·49	0·49	0 57	0·61	0·75	1·60
400	0·43	0·47	0·56	0·56	0·67	0·75	0·93	1·75
600	0·53	0·57	0·68	0·68	0·77	0·97	1·25	—
800	0·63	0·70	0·80	0·80	0·90	1·20	1·50	4·00

SIL. RECTS. TESTED

PIV	300mA	750mA	1A	1·5A	3A	10A	30A
50	0·04	0·05	0·05	0·07	0·14	0·21	0·60
100	0·04	0·06	0·05	0·13	0·16	0·23	0·75
200	0·05	0·09	0·06	0·14	0·20	0·24	1·00
400	0·06	0·13	0·07	0·20	0·27	0·37	1·25
600	0·07	0·16	0·10	0·25	0·34	0·45	1·86
800	0·10	0·17	0·11	0·25	0·37	0·55	2·00
1000	0·11	0·25	0·14	0·30	0·46	0·63	2·50
1200	—	0·33	—	0·38	0·57	0·75	—

TRIACS

VBOM	2A TO-1	6A TO-66	10A TO-88
	£p	£p	£p
100	30	50	76
200	50	60	90
400	70	75	1·10

DIACS

FOR USE WITH TRIACS
BR100 (D32) **37p** each

FREE

One 50p Pak of your own choice free with orders valued £4 or over.

BRAND NEW TEXAS GERM. TRANSISTORS

Coded and Guaranteed

Pak No.		EQVT
T1	8	2G3713 OC71
T2	8	D1374 OC75
T3	8	D1216 OC81D
T4	8	2G381T OC81
T5	8	2G382T OC82
T6	8	2G344B OC44
T7	8	2G345B OC45
T8	8	2G378 OC78
T9	8	2G399A 2N1302
T10	8	2G417 AF117

All 50p each pak

2N2060 NPN SIL. DUAL TRANS. CODE D1699 TEXAS. **Our price 25p each.**

120 VCB MIXIE DRIVER TRANSISTOR. Sim. BSX21 & C407, 2N1893 FULLY TESTED AND CODED ND 120. 1-24 **17p** each. TO.5 N.P.N. 25 up **15p** each.

Sil. trans. suitable for P.E. Organ. Metal TO-18 Eqvt. ZTX300 **5p** each. Any Qty.

FULL RANGE OF ZENER DIODES VOLTAGE RANGE

2-33V. 400mV (DO-7 Case) **13p** ea. 1½W (Top-Hat) **18p** ea. 10W (SO-10 Stud) **25p** ea. All fully tested 5% tol. and marked. State voltage required.

10 amp POTTED BRIDGE RECTIFIER on heat sink. 100PIV. 90p each

NEW LINE

Plastic Encapsulated 2 Amp. BRIDGE RECTS.

50 v RMS **32p** each
100 v RMS **37p** ,,
400 v RMS **46p** ,,
Size 15 mm × 6 mm.

UNIJUNCTION

UT46. Eqvt. 2N2646, Eqvt. TIS43. BEN3000 **27p** each, 25–99 **25p** 100 UP **20p.**

CADMIUM CELLS

ORP12 **43p**
ORP60, ORP61 **40p** each

GENERAL PURPOSE NPN SILICON SWITCHING TRANS. TO-18

SIM. TO 2N706/8. BSY-27/28/95A. All usable devices no open or short circuits. ALSO AVAILABLE in PNP Sim. to 2N2906, BCY70. When ordering please state preference NPN or PNP.

		£p
20	For	0·50
50	For	1·00
100	For	1·75
500	For	7·50
1000	For	13·00

SIL. G.P. DIODES £p

300mW	30	0·50
40PIV(Min.)	100	1·50
Sub-Min.	500	5·00
Full Tested	1,000	9·00

Ideal for Organ Builders.

POWER TRANS BONANZA!

GENERAL PURPOSE GERM. PNP

Coded GP100. BRAND NEW TO-3 CASE. POSS. REPLACE.:—OC25–28–29–30–35–36. NKT 401–403–404–405–406–430–451–452–453. TI3027–3028, 2N250A, 2N456A–457A–458A, 2N511 A & B. 2G220–222, ETC. VCBO 80V VCEO 50V IC 10A PT. 30 WATTS Hfe 30–170.

PRICE	1–24	25–99	100 up
	43p each	**40p** each	**36p** each

SILICON High Voltage 250V NPN TO-3 case. G.P. Switching & Amplifier Applications. Brand new Coded R 2400 VCBO 250/VCEO 100/IC 6A/30 Watts. HFE type 20/fT 5MHZ.

OUR PRICE EACH :		
1–24	25–99	100 up
50p	**45p**	**40p**

2N3055

115 WATT SIL POWER NPN 50p EACH

AD161/162 *PNP*

M/P COMP GERM TRANS. OUR LOWEST PRICE OF **55p** *PER PAIR*

SILICON 50 WATTS MATCHED NPN/PNP
BIP 19 NPN TO-3 Plastic. BIP 20 PNP. Brand new. VCBO 100/VCEO 50/IC 10A. HFE type 100/ft 3mHZ.
OUR PRICE PER PAIR:
1–24 prs. **60p** 25–99 prs. **55p** 100 prs. **50p**

KING OF THE PAKS — Unequalled Value and Quality

SUPER PAKS — NEW BI-PAK UNTESTED SEMICONDUCTORS

Satisfaction GUARANTEED in Every Pak, or money back.

Pak No.		Description	Price
U 1	120	Glass Sub-Min. General Purpose Germanium Diodes	0·50
U 2	60	Mixed Germanium Transistors AF/RF	0·50
U 3	75	Germanium Gold Bonded Sub-Min. like OA5, OA47	0·50
U 4	40	Germanium Transistors like OC81, AC128	0·50
U 5	60	200mA Sub-Min. Silicon Diodes	0·50
U 6	30	Sil. Planar Trans. NPN like BSY95A. 2N706	0·50
U 7	16	Sil. Rectifiers TOP-HAT 750mA VLTG. RANGE up to 1000	0·50
U 8	50	Sil. Planar Diodes DO-7 Glass 250mA like OA200/202	0·50
U 9	20	Mixed Voltages, 1 Watt Zener Diodes	0·50
U10	20	BAY50 charge storage Diodes DO-7 Glass	0·50
U11	25	PNP Sil. Planar Trans. TO-5 like 2N1132, 2N2904	0·50
U12	12	Silicon Rectifiers Epoxy 500mA up to 800 PIV	0·50
U13	30	PNP-NPN Sil. Transistors OC200 & 28 104	0·50
U14	150	Mixed Silicon and Germanium Diodes	0·50
U15	25	NPN Sil. Planar Trans. TO-5 like BFY51, 2N697	0·50
U16	10	3 Amp Silicon Rectifiers Stud Type up to 1000PIV	0·50
U17	30	Germanium PNP AF Transistors TO-5 like ACY 17-22	0·50
U18	8	6 Amp Silicon Rectifiers BYZ13 Type up to 600 PIV	0·50
U19	25	Silicon NPN Transistors like BC108	0·50
U20	12	1·5 Amp Silicon Rectifiers Top Hat up to 1000 PIV	0·50
U21	30	AF. Germanium Alloy Transistors 2G300 Series & OC71	0·50
U23	30	MADT's like MHz Series PNP Transistors	0·50
U24	20	Germanium 1 Amp Rectifiers GJM Series up to 300 PIV	0·50
U25	25	300 MHz NPN Silicon Transistors 2N708, BSY27	0·50
U26	30	Fast Switching Silicon Diodes like IN914 Micro-Min.	0·50
U27	12	NPN Germanium AF Transistors TO-1 like AC127	0·50
U29	10	1 Amp SCR's TO-5 can, up to 600 PIV CRS1/25-600	1·00
U30	15	Plastic Silicon Planar Trans. NPN 2N2926	0·50
U31	20	Silicon Planar Plastic NPN Trans. Low Noise Amp 2N3707	0·50
U32	25	Zener Diodes 400mW DO-7 case 3–18 volts mixed	0·50
U33	15	Plastic Case 1 Amp Silicon Rectifiers IN4000 Series	0·50
U34	30	Silicon PNP Alloy Trans. TO-5 BCY26 2S302/4	0·50
U35	25	Silicon Planar Transistors PNP TO-18 2N2906	0·50
U36	25	Silicon Planar NPN Transistors TO-5 BFY50/51/52	0·50
U37	30	Silicon Alloy Transistors SO-2 PNP OC200, 2S322	0·50
U38	20	Fast Switching Silicon Trans. NPN 400 MHz 2N3011	0·50
U39	30	RF. Germ. PNP Transistors 2N1303/5 TO-5	0·50
U40	10	Dual Transistors 6 lead TO-5 2N2060	0·50
U41	25	RF Germanium Transistors TO-5, OC45, NKT72	0·50
U42	10	VHF Germanium PNP Transistors TO-1 NKT667, AF117	0·50
U43	25	Sil. Trans. Plastic TO-18 A.F. BC113/114	0·50
U44	20	Sil. Trans. Plastic TO-5 BC115/NPN	0·50
U45	7	3A SCR. TO66 up to 600PIV	1·00

Code No's. mentioned above are given as a guide to the type of device in the pak. The devices themselves are normally unmarked.

SILICON PHOTO TRANSISTOR.

TO-18 Lens end NPN Sim. to BP × 25 and P21. BRAND NEW. Full data available. Fully guaranteed.
Qty. 1·24 25·99 100 up
Price each **45p** **40p** **35p**

F.E.T.'S

2N3819	35p	2N5458	50p
2N3820	50p	2N5459	40p
2N3821	35p	BFW10	40p
2N3823	30p	MPF105	40p

NEW EDITION 1971

TRANSISTOR EQUIVALENTS BOOK. A complete cross reference and equivalents book for European, American and Japanese Transistors. Exclusive to BI-PAK **90p** each.

A LARGE RANGE OF TECHNICAL AND DATA BOOKS ARE NOW AVAILABLE EX. STOCK. SEND FOR FREE LIST.

QUALITY TESTED SEMICONDUCTORS

Pak No.			Price £p
Q1	20	Red spot transistors PNP	0·50
Q2	16	White spot R.F. transistors PNP	0·50
Q3	4	OC 77 type transistors	0·50
Q4	6	Matched transistors OC44/45/81/81D	0·50
Q5	4	OC 75 transistors	0·50
Q6	5	OC 72 transistors	0·50
Q7	4	AC 128 transistors PNP high gain	0·50
Q8	4	AC 126 transistors PNP	0·50
Q9	7	OC 81 type transistors	0·50
Q10	7	OC 71 type transistors	0·50
Q11	2	AC 127/128 Complementary pairs PNP/NPN	0·50
Q12	3	AF 116 type transistors	0·50
Q13	3	AF 117 type transistors	0·50
Q14	3	OC 171 H.F. type transistors	0·50
Q15	7	2N2926 Sil. Epoxy transistors mixed colours	0·50
Q16	2	GET880 low noise Germanium transistors	0·50
Q17	5	NPN 2 × ST.141 & 3 × ST.140	0·50
Q18	4	MADT'S 2 × MAT 100 & 2 × MAT 120	0·50
Q19	3	MADT'S 2 × MAT 101 & 1 × MAT 121	0·50
Q20	4	OC 44 Germanium transistors A.F.	0·50
Q21	4	AC 127 NPN Germanium transistors	0·50
Q22	20	NKT transistors A.F. R.F. coded	0·50
Q23	10	OA 202 Silicon diodes sub-min.	0·50
Q24	8	OA 81 diodes	0·50
Q25	15	IN914 Silicon diodes 75 PIV 75mA	0·50
Q26	8	OA95 Germanium diodes sub-min IN69	0·50
Q27	2	10A PIV Silicon rectifiers IS425R	0·50
Q28	2	Silicon power rectifiers BYZ 13	0·50
Q29	4	Silicon transistors 2 × 2N696, 1 × 2N697, 1 × 2N698	0·50
Q30	7	Silicon switch transistors 2N706 NPN	0·50
Q31	6	Silicon switch transistors 2N708 NPN	0·50
Q32	3	PNP Silicon transistors 2 × 2N1131, 1 × 2N1132	0·50
Q33	3	Silicon NPN transistors 2N1711	0·50
Q34	7	Silicon NPN transistors 2N2369, 500MHz (code P397)	0·50
Q35	3	Silicon PNP TO-5. 2 × 2N2904 & 1 × 2N2905	0·50
Q36	7	2N3646 TO-18 plastic 300 MHz NPN	0·50
Q37	3	2N3053 NPN Silicon transistors	0·50
Q38	7	NPN transistors 4 × 2N3703, 3 × 2N3702	0·50

ELECTRONIC SLIDE-RULE

The MK Slide Rule, designed to simplify Electronic calculations features the following scales:—Conversion of Frequency and Wavelength. Calculation of L, C and fo of Tuned Circuits. Reactance and Self Inductance. Area of Circles. Volume of Cylinders. Resistance of Conductors. Weight of Conductors. Decibel Calculations. Angle Functions. Natural Logs and 'e' Functions. Multiplication and Division. Squaring, Cubing and Square Roots. Conversion of kW and Hp. A must for every electronic engineer and enthusiast. Size: 2 cm × 4cm. Complete with case and instructions. Price each: **£3·35**

INTEGRATED CIRCUIT PAKS

Manufacturers "Fall Outs" which include Functional and Part-Functional Units. These are classed as 'out-of-spec' from the maker's very rigid specifications, but are ideal for learning about I.C's and experimental work.

Pak No.	Contents	Price
UIC00	= 12 × 7400	0·50
UIC01	= 12 × 7401	0·50
UIC02	= 12 × 7402	0·50
UIC03	= 12 × 7403	0·50
UIC04	= 12 × 7404	0·50
UIC05	= 12 × 7405	0·50
UIC06	= 8 × 7406	0·50
UIC07	= 8 × 7407	0·50
UIC10	= 12 × 7410	0·50
UIC13	= 8 × 7413	0·50
UIC20	= 12 × 7420	0·50
UIC30	= 12 × 7430	0·50
UIC40	= 12 × 7440	0·50
UIC41	= 5 × 7441	0·50
UIC42	= 5 × 7442	0·50
UIC43	= 5 × 7443	0·50
UIC44	= 5 × 7444	0·50
UIC45	= 5 × 7445	0·50
UIC46	= 5 × 7446	0·50
UIC47	= 5 × 7447	0·50
UIC48	= 5 × 7448	0·50
UIC50	= 12 × 7450	0·50
UIC51	= 12 × 7451	0·50
UIC53	= 12 × 7453	0·50
UIC54	= 12 × 7454	0·50
UIC60	= 12 × 7460	0·50
UIC70	= 8 × 7470	0·50
UIC72	= 8 × 7472	0·50
UIC73	= 8 × 7473	0·50
UIC74	= 8 × 7474	0·50
UIC75	= 8 × 7475	0·50
UIC76	= 8 × 7476	0·50
UIC80	= 5 × 7480	0·50
UIC81	= 5 × 7481	0·50
UIC82	= 5 × 7482	0·50
UIC83	= 5 × 7483	0·50
UIC86	= 5 × 7486	0·50
UIC90	= 5 × 7490	0·50
UIC91	= 5 × 7491	0·50
UIC92	= 5 × 7492	0·50
UIC93	= 5 × 7493	0·50
UIC94	= 5 × 7494	0·50
UIC95	= 5 × 7495	0·50
UIC96	= 5 × 7496	0·50
UIC100	= 5 × 74100	0·50
UIC121	= 5 × 74121	0·50
UIC141	= 5 × 74141	0·50
UIC151	= 5 × 74151	0·50
UIC154	= 5 × 74154	0·50
UIC193	= 5 × 74193	0·50
UIC199	= 5 × 74199	0·50
UICXI	= 25 Assorted 74's	1·50

Packs cannot be split, but 25 assorted pieces (our mix) is available as PAK UIC X1.

BI-PAKS NEW COMPONENT SHOP NOW OPEN WITH A WIDE RANGE OF ELECTRONIC COMPONENTS AND ACCESSORIES AT COMPETITIVE PRICES—
18 BALDOCK STREET (A10), WARE, HERTS.
(STD 0920) 61593. MON.–SAT. 9.15a.m. to 6p.m., FRI. till 8p.m

Please note that as from April 1st 10% must be added to all prices.

-the lowest prices!

74 Series T.T.L. I.C's

BI-PAK STILL LOWEST IN PRICE. FULL SPECIFICATION GUARANTEED. ALL FAMOUS MANUFACTURERS

	1	25	100+		1	25	100+
SN7400	0·15	0·14	0·12	SN7489	£5·50	£5·25	£5·00
SN7401	0·15	0·14	0·12	SN7490	0·67	0·64	0·58
SN7402	0·15	0·14	0·12	SN7491	£1·00	0·95	0·90
SN7403	0·15	0·14	0·12	SN7492	0·67	0·64	0·58
SN7404	0·15	0·14	0·12	SN7493	0·67	0·64	0·58
SN7405	0·15	0·14	0·12	SN7494	0·77	0·74	0·68
SN7406	0·35	0·31	0·28	SN7495	0·77	0·74	0·68
SN7407	0·35	0·31	0·28	SN7496	0·87	0·84	0·78
SN7408	0·18	0·17	0·16	SN74100	£1·65	£1·60	£1·55
SN7409	0·18	0·17	0·16	SN74104	0·97	0·94	0·88
SN7410	0·15	0·14	0·12	SN74105	0·97	0·94	0·88
SN7411	0·25	0·24	0·23	SN74107	0·40	0·38	0·36
SN7412	0·35	0·31	0·28	SN74110	0·55	0·53	0·50
SN7413	0·29	0·26	0·24	SN74111	£1·25	£1·15	£1·10
SN7416	0·43	0·40	0·38	SN74118	£1·00	0·95	0·90
SN7417	0·43	0·40	0·38	SN74119	£1·35	£1·25	£1·10
SN7420	0·15	0·14	0·12	SN74121	0·40	0·37	0·34
SN7422	0·50	0·48	0·45	SN74122	£1·40	£1·30	£1·10
SN7423	0·50	0·48	0·45	SN74123	£2·80	£2·70	£2·60
SN7425	0·50	0·48	0·45	SN74141	0·67	0·64	0·53
SN7427	0·45	0·42	0·40	SN74145	£1·50	£1·40	£1·30
SN7428	0·70	0·65	0·60	SN74150	£3·00	£2·70	£2·50
SN7430	0·15	0·14	0·12	SN74151	£1·00	0·95	0·90
SN7432	0·45	0·42	0·40	SN74153	£1·20	£1·10	0·95
SN7433	0·80	0·75	0·70	SN74154	£1·80	£1·70	£1·60
SN7437	0·64	0·62	0·60	SN74155	£1·40	£1·30	£1·20
SN7438	0·84	0·62	0·60	SN74156	£1·40	£1·30	£1·20
SN7440	0·15	0·14	0·12	SN74157	£1·90	£1·80	£1·70
SN7441	0·67	0·64	0·58	SN74160	£1·80	£1·70	£1·60
SN7442	0·67	0·64	0·58	SN74161	£1·80	£1·70	£1·60
SN7443	£1·30	£1·25	£1·20	SN74162	£4·00	£3·75	£3·50
SN7444	£1·30	£1·25	£1·20	SN74163	£4·00	£3·75	£3·50
SN7445	£1·80	£1·77	£1·75	SN74164	£2·20	£2·15	£2·10
SN7446	0·97	0·94	0·88	SN74165	£2·25	£2·20	£2·15
SN7447	£1·00	0·97	0·95	SN74166	£3·50	£3·25	£3·00
SN7448	£1·00	0·97	0·95	SN74174	£2·30	£2·20	£2·10
SN7450	0·15	0·14	0·12	SN74175	£1·60	£1·50	£1·40
SN7451	0·15	0·14	0·12	SN74176	£2·50	£2·40	£2·30
SN7453	0·15	0·14	0·12	SN74177	£2·50	£2·40	£2·30
SN7454	0·15	0·14	0·12	SN74180	£2·00	£1·60	£1·40
SN7460	0·15	0·14	0·12	SN74181	£5·50	£5·00	£4·75
SN7470	0·29	0·26	0·24	SN74182	£2·00	£1·80	£1·60
SN7472	0·29	0·26	0·24	SN74184	£3·50	£3·25	£3·00
SN7473	0·37	0·35	0·32	SN74190	£1·95	£1·90	£1·85
SN7474	0·37	0·35	0·32	SN74191	£1·90	£1·85	£1·80
SN7475	0·45	0·43	0·42	SN74192	£1·95	£1·90	£1·85
SN7476	0·40	0·39	0·38	SN74193	£2·00	£1·80	£1·75
SN7480	0·67	0·64	0·58	SN74194	£2·70	£2·60	£2·50
SN7481	£1·20	£1·15	£1·10	SN74195	£2·00	£1·90	£1·80
SN7482	0·87	0·86	0·85	SN74196	£1·80	£1·70	£1·60
SN7483	£1·10	£1·05	0·95	SN74197	£1·80	£1·70	£1·60
SN7484	£1·00	0·95	0·90	SN74198	£5·50	£5·00	£4·50
SN7485	£3·60	£3·50	£3·40	SN74199	£5·50	£5·00	£4·50
SN7486	0·32	0·31	0·30				

LINEAR I.C.'s—FULL SPEC.

Type No.	1–24	Price 25–99	100 up
BP201C—SL201C	68p	58p	45p
BP701C—SL701C	68p	50p	45p
BP702C—SL702C	68p	50p	45p
BP702—72702	53p	45p	40p
BP709—72709	36p	34p	30p
LBP709P—μA709C	36p	34p	30p
BP710—72710	44p	42p	40p
BP711—μA711	45p	43p	40p
BP741—72741	75p	60p	50p
μA703C—μA703C	28p	26p	24p
TAA263—	70p	60p	55p
TAA293—	90p	75p	70p
TAA350	170p	158p	150p

S.G.S. EA1000 2·63

ROCK BOTTOM PRICES
LOGIC DTL 930 Series I.C's

Type No.	1–24	Price 25–99	100 up
BP930	12p	11p	10p
BP932	13p	12p	11p
BP933	13p	12p	11p
BP935	13p	12p	11p
BP936	13p	12p	11p
BP944	13p	12p	11p
BP945	25p	24p	22p
RP946	12p	11p	10p
BP948	25p	24p	22p
BP951	65p	60p	55p
BP962	12p	11p	10p
BP9093	40p	38p	35p
BP9094	40p	38p	35p
BP9097	40p	38p	35p
BP9099	40p	38p	35p

Devices may be mixed to qualify for quantity price. Larger quantity prices on application. (DTL 930 Series only).

NUMERICAL INDICATOR TUBES

MODEL	CD66	GR116	3015F Minitron
Anode voltage (Vdc)	170min	175min	5
Cathode Current (mA)	2·3	14	8
Numerical Height (mm)	16	13	9
Tube Height (mm)	47	32	22
Tube Diameter (mm)	19	13	12 wide
I.C. Driver Rec.	BP41 or 141	BP41 or 141	BP47
PRICE EACH	£1·70	£1·55	£1·90

All indicators 0·9 + Decimal point. All side viewing. Full data for all types available on request.

RTL MICROLOGIC CIRCUITS

Epoxy TO-5 case	1–24	Price each 25–99	100 up
uL900 Buffer	35p	33p	27p
uL914 Dual 2i/p gate	35p	33p	27p
uL923 J-K flip-flop	50p	47p	45p

Date and Circuits Booklet for IC's Price 7p.

DUAL IN LINE SOCKETS.
14 & 16 Lead Sockets for use with

DUAL-IN-LINE I.C's. TWO Ranges PROFESSIONAL & NEW LOW COST.

PROF. TYPE No.	1–24	25–99	100up.
TSO 14 pin type	30p	27p	25p
TSO 16 „ „	35p	32p	30p

LOW COST No.			
BPS 14	15p	13p	11p
BPS 16	16p	14p	12p

BI-PAK DO IT AGAIN!

50W pk 25w (RMS)

0·1% DISTORTION!
HI-FI AUDIO AMPLIFIER

THE AL50

★ Frequency Response 15Hz to 100,000—1dB.

★ Load—3, 4, 8 or 16 ohms.

★ Distortion—better than ·1% at 1KHz.

★ Signal to noise ratio 80dB.

ONLY £3.25p each

★ Supply voltage 10–35 Volts.

★ Overall size 63mm × 105mm × 13mm.

Tailor made to the most stringent specifications using top quality components and incorporating the latest solid state circuitry and AL50 was conceived to fill the need for all your A.F. amplification needs.
FULLY BUILT — TESTED — GUARANTEED.

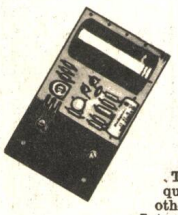

STABILISED POWER MODULE SPM80

AP80 is especially designed to power 2 of the AL50 Amplifiers, up to 15 watt (r.m.s.) per channel simultaneously. This module embodies the latest components and circuit techniques incorporating complete short circuit protection. With the addition of the Mains Transformer MT80, the unit will provide outputs of up to 1·5 amps at 35 volts. Size: 63mm × 105mm × 30mm. These units enable you to build Audio Systems of the highest quality at a hitherto unobtainable price. Also ideal for many other applications including:—Disco Systems, Public Address, Intercom Units, etc. Handbook available, 10p **PRICE £2·95**

TRANSFORMER BMT80 £1·95 p. & p. 25p.

STEREO PRE-AMPLIFIER TYPE PA100

Built to a specification and NOT a price, and yet still the greatest value on the market, the PA100 stereo pre-amplifier has been conceived from the latest circuit tecnniques. Designed for use with the AL50 power amplifier system, this quality made unit incorporates no less than eight silicon planar transistors, two of these are specially selected low noise NPN devices for use in the input stages.
Three switched stereo inputs, and rumble and scratch filters are features of the PA100, which also has a STEREO/MONO switch, volume, balance and continuously variable bass and treble controls.

SPECIFICATION

Frequency Response	20Hz — 20KHz ± 1dB
Harmonic Distortion	better than 0·1%
Inputs : 1. Tape Head	1·25 mV into 50K Ω
2. Radio, Tuner	35 mV into 50K Ω
3. Magnetic P.U.	1·5 mV into 50K Ω

All input voltages are for an output of 250mV. Tape and P.U. inputs equalised to RIAA curve within ± 1dB. from 20Hz to 20KHz.

Bass Control	± 15dB at 20Hz
Treble Control	± 15dB at 20KHz
Filters : Rumble (High Pass)	100Hz
Scratch (Low Pass)	8KHz
Signal/Noise Ratio	better than — 65dB
Input overload	+ 26dB
Supply	+ 35 volts at 20mA
Dimensions	292mm × 82mm × 35mm

ONLY £11·95

SPECIAL COMPLETE KIT COMPRISING 2 AL50's, 1 SPM80, 1 BMT80 & 1 PA100 ONLY £23·00 FREE p. & p.

All prices quoted in new pence *Giro No. 388-7006*
Please send all orders direct to warehouse and despatch department

BI-PAK

P.O. BOX 6, WARE · HERTS

Postage and packing add 10p. Overseas add extra for airmail. Minimum order 50p. Cash with order please.

Guaranteed Satisfaction or Money Back

DISCOUNTS UP TO 60%

Global's GOLDEN Guarantee

WE GUARANTEE THAT WITHIN 7 DAYS OF PURCHASE IF ANY ITEM OF GOODS IS FOUND TO BE GENUINELY DEFECTIVE WE WILL REPLACE THE SAID GOODS WITHOUT QUESTION. AFTER 7 DAYS GOODS ARE COVERED BY MANUFACTURERS 12 MONTHS GUARANTEE.

GARRARD SP25 Mk. III

Special Purchase. Limited number available
Garrard SP25 Mk. III
Goldring G800 **£17.45**
Teak plinth and tinted cover
All leads supplied.
Please add £1.25 P. & P. & Ins.

TURNTABLES

Please add 75p P. & P. & Ins.

Connoisseur BD1 Chassis	£12.75
Garrard SP25 Mk. III	£9.90
Garrard AP76	£17.20
Garrard SL65B	£13.95
Garrard 401	£28.75
Garrard Zero 100 (Auto)	£36.90
Garrard Zero 100 (Single)	£35.90
BSR MP60	£9.40
Goldring GL72	£20.90
Goldring GL72 P	£27.45
Goldring GL75	£26.85
Goldring GL75 P	£34.95
Goldring 101 P.C.	£20.00
Wharfedale Linton + cart.	£25.90
Thorens TD125AB Mk. II	£27.95
Thorens TD150 Mk. II	£91.45
Thorens TD160 AB & C	£53.95

TUNERS

Please add 85p P. & P. & Ins.

Amstrad Multiplex 3000	£27.25
Armstrong 523	£39.50
Armstrong 524	£31.45
Rogers R/brook FET4 (Chassis)	£35.75
Rogers R/brook FET4 (Cased)	£38.95
Rogers R/bourne FET4 (Chassis)	£45.00
Rogers R/bourne FET4 (Cased)	£49.50
Sinclair PR060 (Module)	£16.95
Sinclair 2000/3000 Tuner	£29.90
Leak Delta FM (Cased)	£53.60
Leak Delta AM/FM (Cased)	£63.75
Alpha Highgate FT150	£37.95
Metrosound FMS 20	£38.65
Philips RH 690	£33.00

TUNER/AMPLIFIERS

Please add £1 P. & P. & Ins.

Alpha Highgate 150	£49.75
Armstrong 525 (Teak cased)	£69.45
Armstrong 526 AM/FM (Teak cased)	£77.25
Leak Delta 75	£119.00
Teleton 2100	£32.50
Goodmans One Ten	£98.90
Goodmans Mod 90	£85.50
Rotel 150	£49.50
Rotel 400	£75.50
Rogers Ravensbrook (Teak cased)	£77.00
Rogers R/brook (Chassis)	£72.00
Alpha FR 3000. New product	£72.00

AMPLIFIERS

Please add 85p P. & P. & Ins.

Amstrad 8000 Mk. II	£14.95
Amstrad IC2000	£27.50
Amstrad Integra 4000	£22.50
Armstrong 521 (Teak cased)	£43.90
Alpha Highgate 212	£24.85
Alpha Highgate FA300	£32.25
Alpha Highgate FA400	£35.65
Leak Delta 30	£44.85
Leak Delta 70	£54.90
Metrosound ST20E	£24.20
Metrosound ST60	£45.95
Pioneer SA600 & 610	£57.25
Pioneer SA5000A	£71.95
Pioneer SA1000	£96.95
Rogers R/brook (Chassis)	£37.95
Rogers R/brook (Cased)	£41.50
Rogers R/bourne (Chassis)	£49.95
Rogers R/bourne (Cased)	£52.75
Sinclair PR060 2 × Z 30 PZ5	£14.70
Sinclair PR060 2 × Z30 PZ6	£16.70
Sinclair PR060 2 × Z50 PZ8 Trans	£22.95
Sinclair AFU (Filter Unit)	£4.20
Sinclair 605	£17.95
Sinclair 2000 Mk. II	£21.50
Sinclair 3000 Mk. II	£28.00
Wharfedale Linton	£39.70
Teleton SAQ 307	£22.95
Rotel RA310	£34.95
Rotel RA610	£52.95

SPEAKERS

Please add £1.50 per pair P. & P. & Ins.

	Price per pair
Amstrad 138	£13.90
Wharfedale Denton 2	£28.40
Wharfedale Linton 2	£35.40
Wharfedale Melton 2	£45.90
Wharfedale Dovedale 3	£59.80
Celestion Ditton 120	£38.40
Celestion Ditton 15	£51.00
Celestion Ditton 25	£84.50
Celestion County (new prod)	£34.50
Goodmans Double Maxim	£47.40
Goodmans Mezzo 3	£45.95
Goodmans Magister	£82.95

Special bulk purchase

£2·90*

Plus 65p P. & P. & Ins.
Finished in teak veneer with tinted dust cover. (Fully assembled). For Garrard SP25; 2025TC; 3000; AT60; 2000; 2500; 3500; 5100; 1025; SL65B. Also for BSR McDonald MP60 and others. For AP76; AP75; SL72B; SL75; SL95B*. £3·90 + 65p. P. & P. & Ins. Also finished in walnut to match Japanese equipment—at no extra.

CARTRIDGES

Please add 10p P. & P. & Ins.

Goldring G850	£3.35
Goldring G800	£4.70
Goldring G800E	£7.50
Goldring G800 Super E	£14.15
Shure M3D	£3.70
Shure M44E	£4.75
Shure M55E	£5.55
Ortofon SL15	£15.85
Sonotone 9TAHC	£1.35

All prices correct at time of press E. & O.E. and are subject to alterations.

GLOBAL AUDIO DISCOUNT WAREHOUSES

Dept. (PE4), 174 Pentonville Road, London, N.1. Tel. 01-278 1769
Or: 4 High View Parade, Redbridge Lane East, Woodford Avenue Ilford, Essex. Tel. 01-550 1086

Open Monday to Saturday 9.30 a.m. to 6 p.m. **LATE NIGHT FRIDAY 7 p.m.**

MAIL ORDERS: Order with confidence. Send Postal Order, Cheque, Money Order, Bank Draft, Giro or Cash by Registered Mail. **CALLERS:** Please note that cheques can only be accepted together with cheque cards (not Barclay Card).

ELECTROKIT

Now available from one company are complete kits for many of the articles published in the Electronics, Radio and TV Journals. Examples of our range are:

SCORPIO IGNITION SYSTEMS (P.E. Nov. 1971), **£9·50.** This kit includes all the parts for the assembly of this popular and reliable system. The hardware and instruction data are included.

ELECTRONIC PIANO (P.E. Sept. 1972). We can supply the various sections for this article in kit form. Power supply, price **£6·60.** Preamp and Tremolo **£3·20.** Main Amplifier (less speakers) **£3·30.** 13 Pitch boards **£39·50** (less inductors).

DRILL SPEED CONTROLLER (E.E. Aug. 1972). Kit consists of resistors, rectifiers, thyristor and tag board as specified in the article, price **£1·05.** Kit with M.K. box, plate and switch, price **£2·05.**

LIGHT DIMMER. Kit contains all parts including circuit and construction data, 480 watts, fully suppressed, price **£2·10.**

We shall also be offering kits for most articles published in the P.E. and other popular electronics magazines and will be pleased to quote prices.

All kits sent Post FREE.

Send for details of all other kits available (please enclose S.A.E.).

ELECTROKIT
12 Lauderdale Road, London, W.9
Telephone 01-286 0011
Mon.-Fri. 9.30-5.30 Thurs. 9.30-6.30

Are you alright for Jacks?

Ask for Rendar Jack plugs and sockets at your local stockist. They come in a wide variety of configurations, and in cases of difficulty can be ordered DIRECT from the Rendar factory.

Standard, mini and sub-miniature sizes . . . plugs in both screened and unscreened versions . . . socket bodies in high melting point thermoplastic . . . several unique features (some protected by UK and US Patents) . . . Post Office and NATO specifications.

If you want to study all the facts and figures, all the ingenious construction details, send for the Rendar Electronic Components Catalogue of technical data sheets covering their entire range of products.

The cost of the catalogue is 25p, including P & P, and it's money very well spent!

COMPONENTS FOR LAND, SEA & AIR

RENDAR®

Rendar Instruments Ltd., Victoria Road
Burgess Hill, Sussex. Tel. Burgess Hill 2642-4
Cables: Rendar, Burgess Hill

I.L.P. (Electronics) Ltd

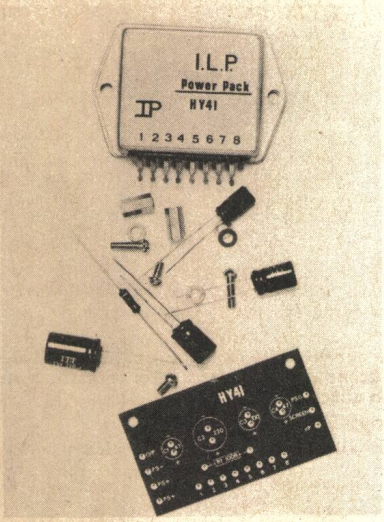

THE HY41

The HY41 supersedes the popular HY40 introduced by ILP last year. This highly improved module achieves true High Fidelity with a dramatic reduction in distortion (typically 0.05% at 1KHz into 8 ohms!) and is electronically and mechanically compatible with the HY40.

With this important improvement the HY41 retains all of the quality characteristics found in the earlier version and P.C. board, Resistor, Capacitors, Hardware Mountings and comprehensive manual are included in the basic kit. No further components are required to construct a complete power amplifier of extremely high performance sufficiently versatile to provide power not merely for Hi-Fi but also for public address systems and industry.

The free manual gives a full circuit diagram of the HY41 and its various applications including a complete stereo amplifier.

Like its predecessor the HY41 is based on conventional and proven circuit techniques developed over recent years.

OUTPUT POWER: British Rating 40 WATTS PEAK, 20 watts R.M.S. continuous.
LOAD IMPEDANCE: 4–16 ohms.
INPUT IMPEDANCE: 30K ohms at 1KHz.
VOLTAGE GAIN: 30db at 1KHz

TOTAL HARMONIC DISTORTION: less than 0.15% (typical 0.05%) at 1KHz.
FREQUENCY RESPONSE: 5Hz–50KHz ± 1db.
SUPPLY VOLTAGE: + 22.5volts D.C.
SUPPLY CURRENT: 0.8 amps maximum.

PRICE: inc. comprehensive manual, P.C. board, five extra components and P. & P.:–
MONO: £4.90 **STEREO: £9.80**

UNIQUE HYBRID PRE-AMPLIFIER

The HY5 has rapidly established a position in the WORLD as the sole hybrid pre-amplifier to contain all feedback and equalization networks within an integrated pre-amplifier circuit.

Supplied with the HY5 are two stabilizing capacitors and by the addition of volume, treble and bass potentiometers it is ready for use.

Internally the HY5 provides equalization for almost every conceivable input, the desired function is achieved by use of a multi-way switch or by direct interconnection,

Two distinctive features of the HY5 are its inbuilt stabilization circuit, allowing it to be run off any unregulated power supply from **16–25** Volts and a balance circuit which, when linked by a balance control to a second HY5, forms a complete stereo pre-amplifier.

Specifically and critically designed to meet exacting Hi-Fi standards, the HY5 combines extremely low noise with a high overload capability. When used in conjunction with the HY41 and PSU45 forms a completely intergrated system.

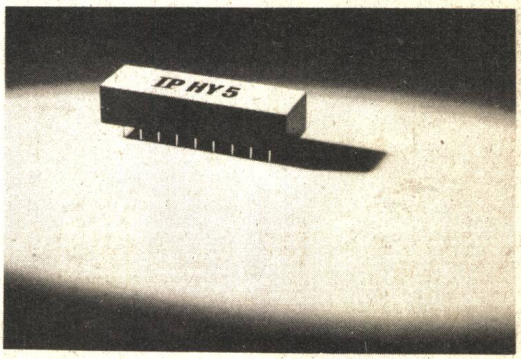

INPUTS
Magnetic Pick-up (within ±1db RIAA curve) 2mV. 47K Ω
Tape Replay (external components to suit head). 4mV. 47KΩ
Microphone (flat) 10mV. 47KΩ
Ceramic Pick-up (equalized and compensatable). 20–2000mV. variable.
Tuner (flat) 250mV. 100K Ω
Auxiliary 1 250mV. 47K Ω
Auxiliary 2 2–20mV. 100K Ω

OUTPUTS
Main Pre-amp output 500mV.
Direct tape output 120mV.

ACTIVE TONE CONTROLS (Baxendall)
Treble + 12db.
Bass + 12db.
INTERNAL STABILIZATION
Enables the HY5 to share an unregulated supply with the Power Amplifier.
SUPPLY VOLTAGE
16–25 volts

SUPPLY CURRENT
6mA approx.
OVERLOAD CAPABILITY
better than 26db on most sensitive input infinite on tuner and auxl.
OUTPUT NOISE VOLTAGE: 0.5mV.

PRICE: **MONO: £3.60** **STEREO: £7.20**

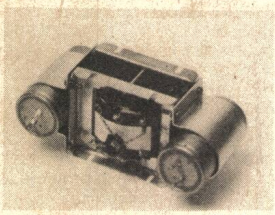

POWER SUPPLY PSU45

The versatile P.S.U.45 is designed to supply your HY41's +HY5's in stereo or mono format.

Specification

Input: 200–240 Volts.
Output: ± 22.5 Volts at 2 amps.
Overall Dimensions: L. 7"; D. 3.8"; H. 3.1"

PRICE: **£4.50 inc. P. & P.**

CROSSLAND HOUSE · NACKINGTON · CANTERBURY · KENT

CANTERBURY 63218

RST VALVE MAIL ORDER CO.

16a WELLFIELD ROAD, LONDON SW16 2BS

SPECIAL EXPRESS MAIL ORDER SERVICE

Express postage 1p per transistor, over ten post free
INTEGRATED CIRCUITS 5p + 1p each added

	£p		£p		£p		£p		£p
1N21	0·17	AFZ12	1·00	BYZ10	0·35	OAZ211	0·32	Z8170	0·10
1N23	0·20	ASY26	0·25	BYZ11	0·32	OAZ222	0·45	Z8271	0·18
1N85	0·88	ASY27	0·32	BYZ12	0·30	OAZ223	0·45	ZT21	0·25
1N253	0·50	ASY28	0·25	BYZ13	0·25	OAZ224	0·45	ZT43	0·25
1N256	0·50	ASY29	0·30	BYZ15	1·00	OAZ241	0·22	ZTX107	0·15
1N645	0·25	ASY36	0·25	BYZ16	0·62	OAZ242	0·23	ZTX108	0·12
1N725A	0·20	ASY50	0·17	BYZ88C3V3		OAZ244	0·22	ZTX300	0·12
1N914	0·07	ASY51	0·40		0·15	OAZ246	0·23	ZTX304	0·25
1N4007	0·20	ASY53	0·20	C111	0·65	OAZ290	0·38	ZTX500	0·16
18113	0·15	ASY55	0·20	CR81/05	0·25	OC16	0·50	ZTX503	0·17
18130	0·13	ASY62	0·25	CR81/40	0·45	OC16T	0·38	ZTX531	0·25
18131	0·13	ASY86	0·38	CS4B	2·50	OC19	0·37		
18202	0·23	ASZ21	0·42	CS10B	3·13	OC20	0·85		
2G371	0·22	ASZ23	0·75	DD000	0·15	OC22	0·50		
2G381	0·25	AUY10	0·98	DD003	0·15	OC23	0·60	INTEGRATED CIRCUITS	
2G414	0·30	AU101	1·50	DD006	0·18	OC24	0·60		
2G417	0·22	BC107	0·10	DD007	0·40	OC25	0·37	7400	0·20
2N404	0·20	BC108	0·10	DD008	0·38	OC26	0·25	7401	0·20
2N697	0·15	BC109	0·10	GD3	0·33	OC28	0·60	7402	0·20
2N698	0·40	BC113	0·15	GD4	0·05	OC29	0·60	7403	0·20
2N706	0·10	BC115	0·20	GD5	0·33	OC30	0·40	7404	0·20
2N706A	0·12	BC116	0·25	GD8	0·25	OC35	0·50	7405	0·20
2N708	0·15	BC116A	0·30	GD12	0·05	OC36	0·60	7406	0·30
2N709	0·63	BC118	0·25	GET102	0·30	OC41	0·25	7407	0·30
2N1091	0·33	BC121	0·20	GET103	0·22	OC42	0·30	7408	0·20
2N1131	0·25	BC122	0·20	GET113	0·20	OC43	0·40	7409	0·45
2N1132	0·25	BC125	0·68	GET114	0·15	OC44	0·17	7410	0·20
2N1302	0·18	BC126	0·65	GET115	0·45	OC44M	0·17	7411	0·23
2N1303	0·18	BC140	0·55	GET116	0·50	OC45	0·12	7412	0·42
2N1304	0·22	BC147	0·15	GET120	0·25	OC45M	0·18	7413	0·30
2N1305	0·22	BC148	0·13	GET872	0·30	OC46	0·27	7416	0·30
2N1306	0·25	BC149	0·15	GET875	0·25	OC57	0·60	7417	0·30
2N1307	0·25	BC157	0·15	GET880	0·37	OC58	0·60	7420	0·20
2N1308	0·25	BC158	0·12	GET881	0·25	OC59	0·65	7422	0·48
2N2147	0·75	BC160	0·63	GET882	0·25	OC66	0·50	7423	0·48
2N2148	0·60	BC169	0·13	GET885	0·25	OC70	0·12	7425	0·48
2N2160	0·60	BCY31	0·35	GEX44	0·08	OC71	0·12	7427	0·42
2N2218	0·20	BCY32	0·55	GEX45/1	0·10	OC72	0·20	7428	0·50
2N2219	0·20	BCY33	0·25	GEX941	0·15	OC73	0·30	7430	0·20
2N2369A	0·15	BCY34	0·30	GJ3M	0·25	OC74	0·30	7432	0·42
2N2444	1·99	BCY38	0·40	GJ4M	0·38	OC75	0·25	7433	0·70
2N2613	0·28	BCY39	1·00	GJ5M	0·25	OC76	0·25	7437	0·65
2N2646	0·45	BCY40	0·50	GJ7M	0·37	OC77	0·40	7438	0·65
2N2904	0·20	BCY42	0·25	HG1005	0·50	OC78	0·20	7440	0·20
2N2904A	0·25	BCY70	0·15	HS100A	0·20	OC79	0·22	7441AN	0·75
2N2906	0·20	BCY71	0·20	MAT100	0·25	OC81	0·20	7442	0·75
2N2907	0·23	BCZ10	0·35	MAT101	0·30	OC81D	0·20	7450	0·20
2N2924	0·23	BCZ11	0·50	MAT120	0·25	OC81M	0·20	7451	0·20
2N2925	0·15	BD121	0·65	MAT121	0·30	OC81DM	0·18	7453	0·20
2N2926	0·10	BD123	0·80	MJE520	0·87	OC81Z	0·40	7454	0·20
2N3054	0·50	BD124	0·75	MJE2955	1·37	OC82	0·25	7460	0·20
2N3055	0·75	BDY11	1·62	MJE3055	0·87	OC82D	0·20	7470	0·30
2N3702	0·10	BF115	0·25	NKT128	0·35	OC83	0·25	7472	0·30
2N3705	0·10	BF117	0·50	NKT129	0·30	OC84	0·25	7473	0·40
2N3706	0·23	BF167	0·25	NKT211	0·25	OC114	0·38	7474	0·40
2N3707	0·12	BF173	0·25	NKT213	0·25	OC122	0·60	7475	0·55
2N3709	0·10	BF181	0·35	NKT214	0·15	OC123	0·65	7476	0·45
2N3710	0·10	BF184	0·20	NKT216	0·37	OC139	0·25	7480	0·80
2N3711	0·10	BF185	0·20	NKT217	0·35	OC140	0·35	7482	0·87
2N3819	0·85	BF194	0·17	NKT218	1·13	OC141	0·60	7483	1·00
2N5027	0·53	BF195	0·15	NKT219	0·33	OC169	0·20	7484	0·90
2N5088	0·33	BF196	0·15	NKT222	0·20	OC170	0·25	7486	0·45
28301	0·50	BF197	0·15	NKT224	0·22	OC171	0·30	7490	0·75
28304	0·75	BF861	0·28	NKT251	0·24	OC200	0·40	7491AN	1·00
28501	0·37	BF898	0·28	NKT271	0·25	OC201	0·70	7492	0·75
28703	0·62	BFX12	0·20	NKT272	0·25	OC202	0·80	7493	0·75
AA129	0·20	BFX13	0·25	NKT273	0·15	OC203	0·40	7494	0·80
AAZ12	0·30	BFX29	0·25	NKT274	0·20	OC204	0·40	7495	0·80
AAZ13	0·12	BFX30	0·25	NKT275	0·25	OC205	0·75	7496	1·00
AC107	0·37	BFX35	0·98	NKT277	0·20	OC206	0·90	7497	6·25
AC126	0·20	BFX63	0·50	NKT278	0·25	OC207	0·90	74100	2·50
AC127	0·25	BFX84	0·25	NKT301	0·40	OC460	0·20	74107	0·50
AC128	0·20	BFX85	0·30	NKT304	0·75	OC470	0·30	74110	0·80
AC187	0·25	BFX86	0·25	NKT403	0·75	OCP71	0·97	74111	1·45
AC188	0·25	BFX87	0·25	NKT404	0·55	ORP12	0·50	74118	1·00
ACY17	0·30	BFX88	0·20	NKT678	0·30	ORP60	0·40	74119	1·90
ACY18	0·25	BFY10	1·00	NKT713	0·25	ORP61	0·42	74121	0·60
ACY19	0·25	BFY11	1·25	NKT773	0·25	S19T	0·30	74122	1·35
ACY20	0·20	BFY17	0·25	NKT777	0·38	SAC40	0·25	74123	2·70
ACY21	0·20	BFY18	0·25	O78B	0·38	SFT308	0·38	74141	1·00
ACY22	0·10	BFY19	0·25	OA5	0·20	ST722	0·38	74145	1·50
ACY27	0·25	BFY24	0·45	OA6	0·12	ST7231	0·63	74150	3·35
ACY28	0·17	BFY44	1·00	OA47	0·10	SX68	0·20	74151	1·10
ACY39	0·50	BFY50	0·22	OA70	0·10	SX631	0·30	74154	2·00
ACY40	0·15	BFY51	0·20	OA71	0·10	SX635	0·40	74155	1·55
ACY41	0·15	BFY52	0·22	OA73	0·10	SX640	0·50	74156	1·55
ACY44	0·25	BFY53	0·17	OA74	0·10	SX641	0·55	74157	1·80
AD140	0·50	BFY64	0·42	OA79	0·10	SX642	0·60	74170	4·10
AD149	0·50	BFY90	0·65	OA81	0·08	SX644	0·75	74174	2·00
AD161	0·37	BSX27	0·50	OA85	0·12	SX645	0·75	74175	1·35
AD162	0·37	BSX60	0·93	OA86	0·15	V15/30P	0·50	74176	1·60
AF106	0·30	BSX76	0·15	OA90	0·08	V30/201P	0·75	74190	1·95
AF114	0·25	BSY26	0·18	OA91	0·07	V60/201	0·50	74191	1·95
AF115	0·25	BSY27	0·17	OA95	0·07	V60/201P	0·75	74192	2·00
AF116	0·25	BSY51	0·50	OA200	0·07	XA101	0·10	74193	2·00
AF117	0·25	BSY95A	0·12	OA202	0·10	XA102	0·18	74194	2·50
AF118	0·62	BSY95	0·12	OA210	0·25	XA151	0·15	74195	1·85
AF119	0·20	BT102/500R		OA211	0·30	XA152	0·15	74196	1·50
AF124	0·25		0·75	OAZ200	0·55	XA161	0·25	74197	1·50
AF125	0·20	BTY42	0·92	OAZ201	0·50	XA162	0·25	74198	4·60
AF126	0·17	BTY79/100R		OAZ202	0·42	XB101	0·43	74199	4·60
AF127	0·17		0·75	OAZ203	0·42	XB102	0·10		
AF139	0·30	BTY79/400R		OAZ204	0·30	XB103	0·25	Plug in sockets —low profile	
AF178	0·55		1·25	OAZ205	0·42	XB113	0·12	14 pin DIL	0·15
AF179	0·65	BY100	0·15	OAZ206	0·42	XB121	0·43	16 pin DIL	0·17
AF180	0·52	BY126	0·15	OAZ207	0·47	ZR24	0·63		
AF181	0·42	BY127	0·17	OAZ208	0·32				
AF186	0·40	BY182	0·85	OAZ209	0·32				
AFY19	1·18	BY213	0·25	OAZ210	0·32				
AFZ11	0·60								

Open daily to callers: Mon.-Fri. 9 a.m.-5 p.m.
Valves, Tubes and Transistors · Closed Sat. 1 p.m.-3 p.m.
Terms C.W.O. only | Tel. 01-677 2424-7

P.E. SOUND SYNTHESISER

Get away to a flying start with this exciting Space Age project. Precision cut metal parts to form modular units as described in the March issue are available NOW.

A. Power supply subframe with tab drillings only **£1·35** (P. & P. 25p).

B. Circuit board support plates fully drilled, **94p.**

Panels drilled with locating holes only: C. 20mm, **18p**; D. 38mm, **21p**; E. 60·5mm, **28p**; F. 64mm, **31p**; G. Module locking rods complete, **£1·20.** SAVE MONEY by obtaining a complete kit of hardware which comprises 1 off each A, C, D, F, 5 off E, and 7 off B, G **£17·42,** Post Free. REGULATED POWER SUPPLY fully assembled and GUARANTEED by "SCOPE" Designs & Mfg. Ltd. Voltage rails adjustable from 8–17V. Nom. 15–0–15V at 500mA per rail. Stab. ratio 250 : 1; Ripple and Noise 500μV at full load. Load regulation < 1% zero to full load, line regulation < ½% for 10% change in mains voltage. Size 4in × 2½in × 7in fits easily into power supply subframe. Terrific value at **£19·50** Post Free. (Include 15p for insurance if required.)

High Quality components for oscillator and inverter module at highly competitive prices. SAE for free lists.

EATON AUDIO

P.O. Box No. 3
ST. NEOTS
HUNTINGDON
PE19 3JB

TERMS: MAIL ORDER ONLY. C.W.O. Cheques or crossed P.O. payable to Eaton Audio. Minimum order £2.
Where P. & P. charges are not shown please add 10p in the £1 to orders under £5. Orders over £5 will be sent free of P. & P.
All prices subject to V.A.T. increases from 1st April.

Stereo radio from your existing tuner.

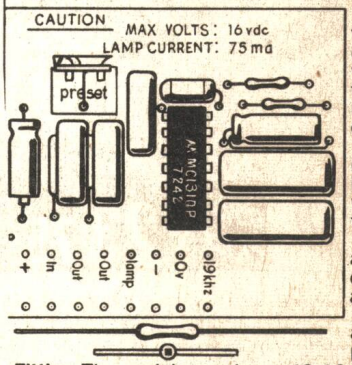

A complete set of parts from Jermyn to build a stereo decoder module that will convert your existing mono tuner for stereo reception whilst maintaining a high standard of reproduction.

The distortion is very low (typically 0.3% at 560 mV RMS composite input signal) with 40dB channel separation.

The stereo switching is automatic and there is a light emitting diode which acts as a stereo beacon.

The kit requires no coil and there are no alignment problems.

Fitting. The module requires a 10-16 volt power supply which can normally be tapped off the existing tuner. The signal input is taken off before the de-emphasis circuit which in practice means disconnecting one, or at the most, two capacitors. Any radio engineer will be able to spot these capacitors, but if you're really stuck send the circuit with a SAE to us and one of our engineers will indicate the output point. (This is the full extent of our involvement, no hardware please).

Of course, if you have a modern mono tuner with a multiplex output our module simply plugs in.

The outputs go via a screened twin cable to the tuner inputs of your stereo amplifier.

And the cost? £4.90 for the Kit with 100% tested integrated circuit.

Also available assembled and aligned, checked and ready for use at £6.90 (includes 12 month guarantee). Beat that!

To Jermyn Industries 76 Vestry Estate Sevenoaks Kent	Please rush me ☐ Kit(s), ☐ made up Stereo decoders. I enclose cheque/postal order for £
Block Capitals Please	Name Address

THOUSANDS of MILES REDUCED to INCHES?

1973 RUSSIAN RADIO TECHNOLOGY SHRINKS THE WORLD! *COMPUTERISED?

THIS FANTASTIC **EARTH SHRINKER**

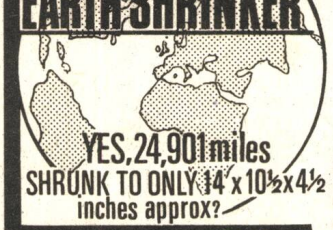

YES, 24,901 miles SHRUNK TO ONLY 14" x 10½" x 4½" inches approx?

BRAND NEW FABULOUS **ASTRAD 17** PORTABLE RADIO & COMMUNICATIONS RECEIVER

WORLD WIDE RECEPTION — THOUSANDS OF TRANSMISSIONS & STATIONS POUR IN FROM THE FOUR CORNERS OF THE EARTH!

28 TRANSISTORS AND DIODES!

WAVEBANDS: STANDARD LONG and MEDIUM

Plus 5 SHORT WAVEBANDS

Plus ULTRA SHORT WAVES

(V.H.F. AM. FM. MW. LW. USW.)

*COMPARE ITS PERFORMANCE with £80 RADIOS!

BATTERY MODEL **£20·75** BOX POST ETC. 50p

MAINS/BATTERY ELIMINATOR £1·48 extra

FIRST TIME EVER!

*NOW AVAILABLE WITH fabulous "COMPUTERISED" WORLD TUNING GUIDE!

NO MORE GUESSWORK— INSTANT DATA at your fingertips — enables you to TUNE IN A FLASH to transmissions the world over!

THIS OFFER ONLY FROM US!

YES, "YOU'VE GOT THE WHOLE WIDE WORLD IN YOUR HANDS"! ALMOST UNBELIEVABLE! Think of the year 1984 and what might be produced then—now get the fantastic ASTRAD 17 and SEE for yourself that the incredible Russians have done it all NOW! It's the radio perfectionist's dream come true! THIS ONE SUPERSEDES ALL EARLIER MODELS! It will probably make your present radio seem like a "crystal set"! Complete with optional battery eliminator for both battery and mains use! We're almost giving them away at only £20·75—**a mere fraction of even today's Russian miracle price!** We challenge you to compare performance and value with £80 radios! ★**Send quickly, after receiving goods test 7 days, refund if not delighted. Or call. Elegant black & chrome finish facia, set in fabulous Cabinet built case—constructed of fine Russian hardwood in beautiful Teak Veneer finish—prevents vibration, ensures purer & sweeter tone than ever!** Volume controlled from a whisper to a roar that would fill a hall! **Much wider band spread, for absolute "pin-point" station selection! Plus "MAGIC EYE" tuning level indicator for ultra perfect tuning sensitivity!** Yes, the Russians have surpassed themselves, proving again their fantastic ability in the field of electronics and brilliantly reflecting their advanced micro-circuitry techniques in the field of spaceship and satellite communications. **Yes, EVERY WAVEBAND** instantly at your fingertips **including Standard Long, Medium, Short and Ultra Short Waves to cover the four corners of the earth during 24 hours a day including all normal transmissions. VHF, FM/USW, AM: LW, MW, SW, gets, locally, local & new stations not yet operational, and messages from all over the world! Expensive TURRET TUNER** side control waveband selection unit (as used on expensive T.V.'s!). Every waveband clicks into position giving incredible ease of station tuning! Genuine push-pull output! ON/OFF volume and separate Treble and Bass tone controls for utter perfection of reproduction and tone! **Press-button dial illumination! Take it anywhere**—runs economically on standard batteries (obtainable everywhere) or direct through battery eliminator from 220/240V AC mains supply. Internal ferrite rod aerial plus built-in "rotatable" telescopic aerial extending to 39in approx. **It's also a fabulous CAR RADIO. Can also be used through extension amplifier, tape recorder or public address system. SIZE** 14in × 10½in × 4½in overall approx. Magnificently designed, made to give **years of perfect service.** (U.K. service facilities & spares available for years & years to come, if ever necessary!). With WRITTEN GUARANTEE manual with simple operating instructions & circuit diagram. **ONLY £20·75** (with mains/battery eliminator £1·48 extra). **BOX, POST, ETC. 50p. *BUT WAIT, for only 55p extra** you get the sensational **"COMPUTERISED" WORLD TUNING GUIDE** (it enables you to time, pinpoint & get transmissions the whole world over—even a child can do it in a flash—**it even lets you know when to tune into the U.K. when abroad,** NO GUESSING! NO MESSING!) **PLUS Standard 'longlife' batteries PLUS ultra sensitive earphone for personal listening.** (Sorry—We cannot change these new radios for any earlier model purchased.) HURRY!
SHOPERTUNITIES SAVE YOU £££'s & £££'s.

BUY ONE FROM US!

SAVE £20·25 NOW!

Fabulous BRAND NEW **SOLID STATE**

This equipment's got EVERYTHING!

BATTERY/MAINS AC *Combined* **V.H.F AM/FM RADIO and CASSETTE TAPE RECORDER & PLAYER**

WITH REMOTE CONTROL MICROPHONE

RECOMMENDED RETAIL PRICE £44

OUR PRICE **£23·75** CARR ETC. 35p

Shopertunities "thunder" ahead with an offer that's FANTASTIC (even by our standards!). We've snapped up 500 magnificent machines. **Latest sensation in the world of sound!** First-class makers! Fabulous **VHF, AM/FM Radio AND Cassette Tape Recorder & Player combined & it also runs off standard batteries or mains.** (Simply plug in the 220/240V AC line cord.) **Record and play back anything, anywhere! RECOMMENDED RETAIL PRICE GENUINELY £44! WE OFFER AT ALMOST HALF PRICE!** Wonderful features: ★ **Press-button Keyboard Control Panel or latest MASTER SWITCH CONTROL!** ★ **"MAGIC EYE" Visual Battery check/recording level indicator or built-in automatic Leveller!** ★ **Separate ON/OFF and HI-LO volume controls!** ★ **Heavy duty built-in speaker!** ★ **Earphone** (for personal listening or "monitoring") **and extension speaker sockets!** ★ **Remote control microphone!** ★ **Built-in swivel telescopic extension aerial (24in approx.)! Magnificently made case with carry handle. (DESIGNS VARY SLIGHTLY.)** Takes standard 30, 60, 90 or 120-minute Cassette Tapes, obtainable everywhere. **AND the amazing built-in full circuit VHF, AM/FM Radio** gives you superb clarity of tone, incredible station **selection.** Unique rotating Station Selector Dial—gets, locally, city and regional stations in every part of the country, plus B.B.C. National, VHF. Picks up dozens of foreign stations. **Fabulous in your car!** You could pay £ £ £'s more for a Car Radio or Car Cassette player ALONE! **£23·75, CARR. ETC. 35p. Complete with simple instructions, remote control microphone with on/off switch and microphone stand. WITH WRITTEN GUARANTEE.** Send quickly, after receiving goods, test 7 days, refund if not delighted. Or call. **BONUS OFFER: Batteries and Cassette Tape 25p extra if required.**

FIRST TIME EVER! *SAVE £14·48!

BRAND NEW **AC/DC BATTERY/MAINS**

Cassette TAPE RECORDER & PLAYER

With remote control microphone.

FIRST CLASS MAKERS

WE COULD CHARGE UP TO £26·97!

OUR PRICE **£12·49** POST ETC. 31p

THE ONE STEP FORWARD EVERYONE HAS WAITED FOR! **NOW** a superb de-luxe portable **BATTERY/MAINS** tape recorder and player—and incredible **Shopertunities** bring it to you for ONLY £12·49! Due to our cut price we cannot name first-class makers—but rest assured **you're getting one of the BEST!** Expensive **"PIANO KEYBOARD" CONTROL PANEL (or latest MASTER SWITCH control) AND AUTOMATIC LEVEL CONTROL.** No fiddling with awkward tape and reels, **just "slap-in" a cassette and off you go!** (Takes 30, 60, or 90 minute standard cassette tapes obtainable everywhere). **Amazing** performance ensures perfect tapings and superb reproduction! Remote control microphone. Rapid Rewind! Fast forward! Beautiful tone from a whisper to a roar! Completely self contained—**record anywhere,** indoors or out! **Runs on standard batteries AND 220/240V AC mains.** Separate jacks for remote control microphone, etc. Size 9½in × 5in × 2½in approx. Design can vary slightly. With carry handle. WRITTEN GUARANTEE and full instructions. (Recommended selling price £26·97.) **OUR PRICE ONLY £12·49 post, etc., 31p.** ★ Send quickly, after receiving goods test 7 days refund if not delighted, or call. **BONUS OFFER (strictly rationed one per customer)—Cassette tape, set of standard batteries AND microphone stand all for 50p extra, if required.**

Order by post to Uxbridge Road address or call at either store.

Bargains galore at both stores.—**(COMMERCIAL TRAVELLERS PLEASE NOTE:** Merchandising office at Holborn Store.)

SHOPERTUNITIES LTD.

Dept. PE/27, 164 UXBRIDGE RD. (facing Shepherds Bush Green), **LONDON W12 8AQ. (Thurs. 1, Fri. 7). Also at 37/39 HIGH HOLBORN** (opposite Chancery Lane), **LONDON, W.C.1. (Thurs. 7 p.m.) BOTH OPEN MON. TO SAT. 9 A.M. TILL 6 P.M.**

SEW PANEL METERS

USED EXTENSIVELY BY GOVERNMENT DEPARTMENTS, INDUSTRY, EDUCATIONAL AUTHORITIES, ETC.
● LOW COST RANGES IN STOCK ● QUICK DELIVERY ● OVER 200 OTHER RANGES TO ORDER

CLEAR PLASTIC PANEL METERS

TYPE SW.100 100mm × 80mm Fronts

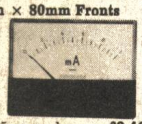

30μA	£3·80	5 amp. d.c.	£3·40
50–0–50μA	£3·80	300V a.c.	£3·40
100μA	£3·80	VU Meter	£4·15
100–0–100μA	£3·70		
500μA	£3·50		
1mA	£3·40		
20V d.c.	£3·40		
50V d.c.	£3·40		
300V d.c.	£3·40		
1 amp. d.c.	£3·40		

Type SD.830 82·5mm × 110mm Fronts

50μA	£2·75	10mA	£2·50
50–0–50μA	£2·70	50mA	£2·50
100μA	£2·70	100mA	£2·50
100–0–100μA	£2·70	500mA	£2·50
200μA	£2·70	1 amp.	£2·50
500μA	£2·55	5 amp.	£2·50
1mA	£2·50	10 amp.	£2·50
5mA	£2·50	5V d.c.	£2·50
		10V d.c.	£2·50
		20V d.c.	£2·50
		50V d.c.	£2·50
		300V d.c.	£2·50
		15V a.c.	£2·75
		300V a.c.	£2·75
		VU Meter	£3·00

Type SD.640 63·5mm × 85mm Fronts

50μA	£2·60	500mA	£2·35
50–0–50μA	£2·55	1 amp.	£2·35
100μA	£2·55	5 amp.	£2·35
100–0–100μA	£2·55	10 amp.	£2·35
200μA	£2·55	5Vd.c.	£2·35
500μA	£2·35	20V d.c.	£2·35
1mA	£2·35	50V d.c.	£2·35
5mA	£2·35	300V d.c.	£2·35
10mA	£2·35	15V a.c.	£2·40
50mA	£2·35	300V a.c.	£2·40
100mA	£2·35	VU Meter	£2·70

Type SD.460 46mm × 59·5mm Fronts

50μA	£2·40	1 amp.	£2·15
50–0–50μA	£2·35	5 amp.	£2·15
100μA	£2·35	10 amp.	£2·15
100–0–100μA	£2·35	5V d.c.	£2·15
200μA	£2·35	10V d.c.	£2·15
500μA	£2·20	20V d.c.	£2·15
1mA	£2·15	50V d.c.	£2·15
5mA	£2·15	300V d.c.	£2·15
10mA	£2·15	15V a.c.	£2·30
50mA	£2·15	300V a.c.	£2·30
100mA	£2·15	VU Meter	£2·55
500mA	£2·15		

***MOVING IRON— ALL OTHERS MOVING COIL**

Please add postage

Type MR.85P. 4½in. × 4½in. Fronts

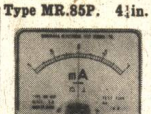

50μA	£3·95	50mA	£3·10
50–0–50μA	£3·40	100mA	£3·10
100μA	£3·40	500mA	£3·10
100–0–100μA	£3·30	1 amp.	£3·10
200μA	£3·30	5 amp.	£3·10
500μA	£3·20	15 amp.	£3·10
500–0–500μA	£3·10	30 amp.	£3·20
1mA	£3·10	20V d.c.	£3·10
1–0–1mA	£3·10	50V d.c.	£3·10
5mA	£3·10	150V d.c.	£3·10
10mA	£3·10	300V d.c.	£3·10
		15V a.c.	£3·10
		300V a.c.	£3·10
		8 Meter 1mA.	£3·15
		VU Meter	£3·95
		1 amp. a.c.	*£3·10
		5 amp. a.c.	*£3·10
		10 amp. a.c.	*£3·10
		20 amp. a.c.	*£3·10
		30 amp. a.c.	*£3·10

Type MR.52P. 2½in. square Fronts.

50μA	£3·40	10V d.c.	£2·20
50–0–50μA	£2·85	20V d.c.	£2·20
100μA	£2·85	50V d.c.	£2·20
100–0–100μA	£2·75	300V d.c.	£2·20
500μA	£2·55	15V a.c.	£2·30
1mA	£2·20	300V a.c.	£2·30
5mA	£2·20	8 Meter 1mA.	£2·30
10mA	£2·20	VU Meter	£3·50
50mA	£2·20	1 amp. a.c.	*£2·20
100mA	£2·20	5 amp. a.c.	*£2·20
500mA	£2·20	10 amp. a.c.	*£2·20
1 amp.	£2·20	20 amp. a.c.	*£2·20
5 amp.	£2·20	30 amp. a.c.	*£2·20

Type MR.65P. 3½in. × 3½in. Fronts

50μA	£3·70	10V d.c.	£2·40
50–0–50μA	£3·00	20V d.c.	£2·40
100μA	£3·00	50V d.c.	£2·40
100–0–100μA	£2·90	150V d.c.	£2·40
200μA	£2·90	300V d.c.	£2·40
500μA	£2·65	15V a.c.	£2·55
500–0–500μA	£2·40	50V a.c.	£2·55
1mA	£2·40	150V a.c.	£2·55
5mA	£2·40	300V a.c.	£2·55
10mA	£2·40	500V a.c.	£2·55
50mA	£2·40	8 Meter 1mA.	£2·60
100mA	£2·40	VU Meter	£3·70
500mA	£2·40	50mA a.c.	*£2·40
1 amp	£2·40	100mA a.c.	*£2·40
5 amp	£2·40	200mA a.c.	*£2·40
10 amp.	£2·40	500mA a.c.	*£2·40
15 amp.	£2·40	1 amp. a.c.	*£2·40
20 amp.	£2·40	5 amp. a.c.	*£2·40
30 amp.	£2·55	10 amp. a.c.	*£2·40
50 amp.	£2·75	20 amp. a.c.	*£2·40
5V d.c.	£2·40	30 amp. a.c.	*£2·40

Send for illustrated brochure on SEW Panel Meters—discounts for quantities.

Type MR.38P. 1 21/32in. square Fronts.

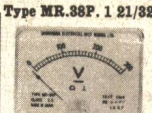

50μA	£2·30	200mA	£1·75
50–0–50μA	£2·10	300mA	£1·75
100μA	£2·10	500mA	£1·75
100–0–100μA	£1·95	750mA	£1·75
200μA	£1·95	1 amp.	£1·75
500μA	£1·80	2 amp.	£1·75
500–0–500μA	£1·75	5 amp.	£1·75
1mA	£1·75	10 amp.	£1·75
1–0–1mA	£1·75	3V d.c.	£1·75
2mA	£1·75	10V d.c.	£1·75
5mA	£1·75	15V d.c.	£1·75
10mA	£1·75	20V d.c.	£1·75
20mA	£1·75	50V d.c.	£1·75
50mA	£1·75	100V d.c.	£1·75
100mA	£1·75	150V d.c.	£1·75
150mA	£1·75	300V d.c.	£1·75
		500V d.c.	£1·75
		750V d.c.	£1·75
		15V a.c.	£1·85
		50V a.c.	£1·85
		150V a.c.	£1·85
		300V a.c.	£1·85
		500V a.c.	£1·85
		8 Meter 1mA.	£1·85
		VU Meter	£2·30

Type MR.45P. 2in. square Fronts.

50μA	£2·50	5 amp.	£1·85
50–0–50μA	£2·30	10V d.c.	£1·85
100μA	£2·30	20V d.c.	£1·85
100–0–100μA	£2·05	50V d.c.	£1·85
200μA	£2·05	300V d.c.	£1·85
500μA	£1·95	15V a.c.	£2·00
500–0–500μA	£1·85	300V a.c.	£2·00
1mA	£1·85	8 Meter 1mA	£2·05
5mA	£1·85	VU Meter	£2·50
10mA	£1·85	1 amp. a.c.	*£1·85
50mA	£1·85	5 amp. a.c.	*£1·85
100mA	£1·85	10 amp. a.c.	*£1·85
500mA	£1·85	20 amp. a.c.	*£1·85
1 amp.	£1·85	30 amp. a.c.	*£1·85

"SEW" EDGEWISE METERS

Type PE.70. 3 17/32in. × 1 15/32in. × 2¼in. deep.			
50μA	£3·40	500μA	£3·05
50–0–50μA	£3·30	1mA	£2·70
100μA	£3·30	300V a.c.	£2·70
100–0–100μA	£3·20	VU Meter	£3·75
200μA	£3·20		

"SEW" BAKELITE PANEL METERS

Type MR.65. 3½in. square Fronts.

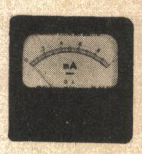

25μA	£3·85	1 amp.	£2·15
50μA	£3·00	5 amp.	£2·15
50–0–50μA	£2·60	15 amp.	£2·15
100μA	£2·60	30 amp.	£2·15
100–0–100μA	£2·50	50 amp.	£2·15
500μA	£2·45	5V d.c.	£2·15
500–0–500μA	£2·15	10V d.c.	£2·15
1mA	£2·15	20V d.c.	£2·15
1–0–1mA	£2·15	50V d.c.	£2·15
5mA	£2·15	150V d.c.	£2·15
10mA	£2·15	300V d.c.	£2·15
50mA	£2·15	50mV d.c.	£2·40
100mA	£2·15	100mV d.c.	£2·40
500mA	£2·15	30V a.c.*	£2·20
		50V a.c.*	£2·20
		150V a.c.*	£2·20
		300V a.c.*	£2·20
		500mA a.c.*	£2·15
		1 amp. a.c.*	£2·15
		5 amp. a.c.*	£2·15
		10 amp. a.c.*	£2·15
		20 amp. a.c.*	£2·15
		30 amp. a.c.*	£2·15
		50 amp. a.c.*	£2·15
		VU Meter	£3·40

Type S-80 80mm square Fronts

50μA	£3·50	300V a.c.	£2·85
50–0–50μA	£3·40	VU Meter	£3·70
100μA	£3·40		
100–0–100μA	£3·30		
500μA	£3·05		
1mA	£2·85		
20V d.c.	£2·85		
50V d.c.	£2·85		
300V d.c.	£2·85		
1 amp. d.c.	£2·85		
5 amp. d.c.	£2·85		

"SEW" EDUCATIONAL METERS

Type ED.107. Size overall 100mm × 90mm × 108mm.

A new range of high quality moving coil instruments ideal for school experiments and other bench applications. 3in. mirror scale. The meter movement is easily accessible to demonstrate internal working. Available in the following ranges:

50μA	£5·50	10V d.c.	£4·85
100μA	£5·10	20V d.c.	£4·85
1mA	£4·85	50V d.c.	£4·85
50–0–50μA	£5·10	300V d.c.	£4·85
1–0–1mA	£4·85	Dual range	
1A d.c.	£4·85	500mA/5A d.c.	£5·10
5A d.c.	£4·85	5V/50V d.c.	£5·10

POWER RHEOSTATS

High quality ceramic construction. Windings embedded in vitreous enamel. Heavy duty brush wiper. Continuous rating. Wide range ex-stock. Single hole fixing, ¾in. dia. shafts. Bulk quantities available.
25 WATT. 10/25/50/100/250/500/1000/2500 or 5000 ohms, **90p.** Post 10p.
50 WATT. 10/25/50/100/250/500/1000/2500 or 5000 ohms, **£1·15.** Post 10p.
100 WATT. 1/5/10/25/50/100/250/500/1000 or 2500 ohms. **£1·65.** Post 15p.

"YAMABISHI" VARIABLE VOLTAGE TRANSFORMERS

Excellent quality. Low price. Immediate delivery

S-260 General Purpose Bench Mounting

1 amp.	£7·00
2·5 amp.	£8·05
5 amp.	£11·75
8 amp.	£15·90
10 amp.	£22·50
12 amp.	£23·60
20 amp.	£49·00
25 amp.	£58·00
40 amp.	£82·50

S-260 Panel Mounting

1 amp	£7·00
2·5 amp	£8·05

Please add postage

ALL MODELS
INPUT 230V 50/60 CYCLES
OUTPUT VARIABLE 0–260 VOLTS.

Special discounts for quantity

AUTO TRANSFORMERS

0/115/230V. Step up or step down. Fully shrouded.

80W	£2·10	P. & P. 18p
150W	£2·70	P. & P. 18p
300W	£3·60	P. & P. 23p
500W	£5·25	P. & P. 33p
1000W	£7·50	P. & P. 38p
1500W	£10·20	P. & P. 43p
2250W	£17·25	P. & P. 50p
5000W	£35·00	P. & P. £1

230 VOLT A.C. 50 CYCLES RELAYS

Brand new. 3 sets of changeover contacts at 5 amp. rating. **50p** each. Post 10p (100 lots **£40**) Quantities available.

AVOMETER MOVEMENTS

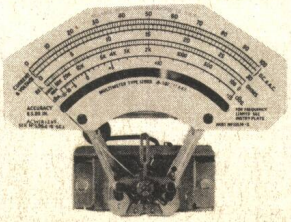

Spare movements for Model 8 or 9. (Fitted with Model 9 scale) or basis for any multimeter. Brand New and Boxed.
£3·50 Post 25p.

240° Wide Angle 1mA Meters

MW1-6 60mm square **£3·97**
MW1-8 80mm square **£4·97**
Post extra

RP214 REGULATED POWER SUPPLY

Solid state. Variable output 0–24V d.c. up to 1 amp. Dual scale meter to monitor voltage and current. Input 220/240V a.c. Size 185 × 85 × 105mm. **£8·97** Post 25p.

PS.200 REGULATED P.S.U.

Solid state. Variable output 5–20V d.c. up to 2 amp. Independent meters to monitor voltage and current. Output 220/240V. a.c. Size 7½in. × 5½in. × 3½in. **£14·97.** Post 25p.

PS.1000B REGULATED POWER SUPPLY

Solid state. Output 6, 9 or 12V d.c. up to 3 amps. Meter to monitor current. Input 220/240V a.c. Size 4in. × 3½in. × 6½in. **£11·97.** Post 25p.

230V/240V SMITHS SYNCHRONOUS GEARED MOTORS

Built in gearbox. All brand new and boxed. 30 RPH CW; 2 RPH CW; 20 RPH CW; 2 RPH ACW; 30 RRH CW. **50p** each, Post 12p.

LB4 TRANSISTOR TESTER

Tests PNP or NPN transistors. Audio indication. Operates on two 1·5V batteries. Complete with all instructions, etc. **£4·50.** Post 20p.

LB3 TRANSISTOR TESTER

Tests ICO and B. *Pnp/npn.* Operates from 9V battery. Complete with all instructions, etc. **£3·95.** Post 20p.

MCA.220 AUTOMATIC VOLTAGE STABILISER

Input 88–125V a.c. or 176–250V a.c. Output 120V a.c. or 240V a.c. 200VA rating. **£11·97.** Post 50p.

SEND S.A.E. FOR LIST OF SEMICONDUCTORS AND VALVES

G. W. SMITH & CO. (RADIO) LTD.
Also see next three pages

MULTIMETERS *for EVERY purpose!*

T560 POCKET MULTIMETER
High-precision at low-cost. Ranges: D.c. 15V, 150V, 1,000V (10,000 O.P.V.). A.c. 15V, 150V, 100V (1,000 O.P.V.).
D.c. Current 150mA. Resistance 100k ohms.
£1·85. Post 15p.

MODEL 1092 Testmeter.
5,000 O.P.V.
0/3/15/150/300/1,200V d.c.
0/6/30/300/600V a.c.
0/300μA/300MA
0/10K/1 meg Ω
Decibels —10 to +16 dB
£2·75 each. Post 15p.

HIOKI MODEL 720X
20,000 O.P.V.
Overload protection
5/25/100/500/1,000V d.c.
10/50/250/1,000V a.c.
50μA/250mA. 20K/2 meg. ohm. —5 to +62dB.
£4·97. Post 15p.

HIOKI MODEL 730X
30,000 O.P.V. Overload protection. 6/30/60/300/600/1,200V d.c. 12/60/120/600/1,200V a.c. 60μA/30mA/300 mA. 2K/200K/2 megohm. —10 to +63 dB.
£6·50. Post 15p.

MODEL TE-12
20,000 O.P.V. 0/0·6/6/30/120/600/1,200/3,000/6,000V d.c. 0/6/30/120/600/1,200V a.c. 0/60μA/6/60/600mA. 0/6K/600K/6Meg./60 Meg. Ω 50pF. 0·2mFd. **£5·97.** Post 17p.

MODEL TE-200 20,000 O.P.V. Mirror scale, overload protection. 0/5/25/125/1,000V d.c. 0/10/50/250/1,000V a.c. 0/50μA/250mA. 0/60K/6 meg Ω. —20 to +62dB. **£3·95.** Post 15p.

MODEL 500 30,000 O.P.V. with overload protection mirror scale 0/0·5/2·5/10/25/100/250/500/1,000V d.c. 0/2·5/10/25/100/250/500/1,000V a.c. 0/50μA/5/50/500mA. 12 amp. d.c. 0/60/K/6 Meg./60 MegΩ.
£8·87. Post paid.

HIOKI MODEL 750X
50,000 O.P.V.
43 ranges 0·0·3 to 1,200V d.c.
0·3 to 1,200V a.c.
0·30μA/300mA.
0·3K/30 meg ohms. —10 to +17dB.
£8·97. Post 20p.

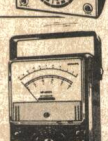

HT100B4 MULTI-METER
Features a.c. current ranges. 100,000 O.P.V. Mirror Scale. Overload protection.
0/0·5/2·5/10/50/250/500/1,000V d.c.
0/2·5/10/50/250/500/1,000V a.c.
0/10/250μA/2·5/25/250MA/10 amp. d.c.
10 amp. a.c. 0/20K/200K/2MEG/20 MEG. —20 +62dB. **£12·50.** Post 25p.

370 WTR MULTIMETER
Features a.c. current ranges. 20,000 O.P.V.
0/0·5/2·5/10/50/250/500/1,000V d.c.
0/2·5/10/50/250/500/1,000V a.c.
0/50μA/1/10/100mA/1/10 amp. d.c.
0/100mA/1/10 amp. a.c.
0/5K/50K/500K/5MEG/50MEG. —20 +62dB. **£15.** Post 25p.

RUSSIAN 22 RANGE MULTIMETER
Model U437 10,000 O.P.V.
A first class versatile instrument manufactured in U.S.S.R. to the highest standards. Ranges: 2·5/10/50/250/500/1,000V d.c. 2·5/10/50/250/500/1,000V a.c. D.c. current 100vA/1/10/100mA/1A. Resistance 300 ohms/3/30/300K/3mΩ. Complete with batteries, test leads, instructions and sturdy steel carrying case.
OUR PRICE **£5·97.** Post 25p.

ROUND SCALE TYPE PENCIL TESTER MODEL TS.68
Completely portable, simple to use pocket sized tester. Ranges 0/3/30/300V a.c. and d.c. at 2,000 O.P.V. Resistance 0·20K ohms.
ONLY £1·97, Post 13p.

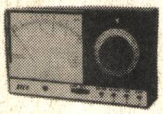

LT 601 MULTI-METER
New style 20,000 O.P.V. pocket multimeter. 5/25/50/250/500/2,500V d.c. 10/50/100/500/1,000V a.c. 50μA/250A. 6K/6 meg ohms. —20 to +22 dB.
£3·75. Post 20p.

MODEL TH-12
20,000 O.P.V. Overload protection. Slide switch selector. 0/0·25/2·5/10/50/250/1,000V d.c. 0/10/50/250/1,000V a.c. 0/50μA/25/250mA d.c. 0/3K/30K/300K/3 meg. —20 to +50dB.
£4·97. Post 15p.

MODEL TE-300. 30,000 O.P.V. Mirror scale, overload protection 0/0·6/3/15/60/300/1,200V d.c. 0/6/30/120/600/1,200V a.c. 0/30μA/6mA/60mA/300mA/600mA. 0/8K/80K/800K/8 meg. ohm —20 to —63dB. **£5·97.** Post 15p.

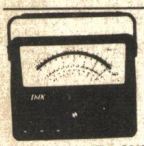

MODEL PL436
20kΩ/V d.c. 8kΩ/V a.c. Mirror scale. 0·6/3/12/30/120/600V d.c. 3/30/120/600V a.c. 50/600μA/60/600mA. 10/100K/1 Meg/10 MegΩ.
—20 to +46dB. **£6·97,** Post 12p.

TMK MODEL TW-50K 46 ranges, mirror scale, 50K/V d.c. 5K/V a.c. D.c.: Volts 0·125, 0·25, 1·25, 2·5, 5, 10, 25, 50, 125, 250, 500, 1,000V. A.c. Volts: 1·5, 3, 5, 10, 25, 50, 125, 250, 500, 1,000V. D.c. Current: 25, 50μA, 2·5, 5, 25, 50, 250, 500mA, 5, 10 amp. Resistance: 10K, 100K, 1 MEG, 10 MEG Ω. Decibels: —20 to +81·5 dB.
£8·50. Post 17p.

MODEL K228A
Taut band suspension. Overload protection. Polarity reversing switch. 30,000 O.P.V.
0/0·5/2·5/15/50/250/500/1,000/2,500V d.c. 0/15/50/150/500/1,000V a.c. 0/50μA/5/50/150/500mA/5A d.c. 0/3K/300K/3meg. **£8·95.** Post 20p.

HIOKI MODEL 700X
100,000 O.P.V. Overload protection. Mirror scale. 0·3/0·6/1·2/1·5/3/6/12/30/60/120/300/600/1,200V d.c.
1·5/3/6/12/30/60/150/300/600/1,200V a.c.
15/30μA/3/6/30/60/150/300mA 6/12 amp. d.c. 2K/200K/2 Meg/20 Meg ohm —20 to +63dB. **£13·50.** Post 20p.

MODEL C-7080 EN
Giant 6in mirror scale. 20,000 O.P.V.
0/0·25/1/2·5/10/50/250/1,000/5,000V d.c. 0/2·5/10/50/250/1,000/5,000V a.c. 0/50μA/1/10/100/500mA/10 amp. d.c. 0/2K/200K/20 meg.
—20 to +50dB.
£13·95. Post 35p.

U4312 MULTIMETER
Extremely sturdy instrument for general electrical use. 667 O.P.V.
0/0·3/1·5/7·5/30/60/150/300/600/900V d.c. and 75mV.
0/0·3/1·5/7·5/30/60/150/300/600/900V a.c.
0/300μA/1·5/6/15/60/150 600MA/1·5/6 amp. d.c.
0/1·5/6/15/60/150/600MA/1·5/6 amp. a.c. 0/200Ω/3k/30kΩ. Accuracy Knife edge pointer, mirror scale. Complete with sturdy metal carrying case, leads and instructions. **£9·50.** Post 25p.

Selected TEST EQUIPMENT

FTC-401 TRANSISTOR TESTER
Full capabilities for measuring A, B and ICO. *npn* or *pnp*. Equally adaptable for checking diodes. Supplied complete with instructions, battery and leads.
£7·50. Post 20p.

Model S-100TR MULTIMETER/TRANSISTOR TESTER. 100,000 O.P.V. mirror scale/overload protection. 0/0·12/0·6/3/12/30/120/600V d.c. 0/6/30/120/600V a.c. 0/12/600μA/12/300mA/12 amp. d.c. 0/10 K/1 MEG/100 MEG. —20 to +50dB. 0·01–2 MFD. Transistor tester measures Alpha, beta and Ico. Complete with batteries, instructions and leads.
£13·50. Post 25p.

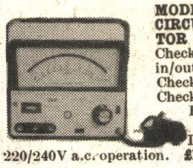

MODEL 449A IN CIRCUIT TRANSISTOR TESTER
Checks true a.c. beta in/out. Checks Icbo. Checks diodes in/out. Checks SCR, etc. Beta HI 10—500 LO 2—50 Icbo 0-5000μA.
220/240V a.c. operation. **£17·50.** Post 25p.

TE-20D RF SIGNAL GENERATOR

Accurate wide range signal generator covering 120 kHz-500 MHz on 6 bands. Directly calibrated Variable R.F. attenuator, audio output, Xtal socket for calibration. 220/240V a.c. Brand new with instructions. **£15.** Carr. 37p. Size 140mm × 215mm × 170mm.

MODEL L-55 FET V.O.M.
Input impedance 10 meg ohms. 0/0·3/1·2/6/30/120/600V d.c. 0/3/12/60/120/600V a.c. 0/120μA/120mA d.c. 0/1K/100K/10 meg/100 meg ohms.
£15·97. Post 25p.

CI-5 PULSE OSCILLOSCOPE
For display of pulsed and periodic waveforms in electronic circuits. VERT. AMP. Bandwidth 10MHz. Sensitivity at 100kHz V RMS/mm. 0·1-25; HOR. AMP. Bandwidth 500kHz. Sensitivity at 100kHz, V RMS/mm. 0·3-25; Pre-set triggered sweep 1-3,000μsec.; free running 20-200,000Hz in nine ranges. Calibrator pips. 220mm × 360mm × 430mm. 115-230V a.c. operation.
£39. Carr paid.

TO-3 PORTABLE OSCILLOSCOPE

3in tube, Y amp. Sensitivity 0·1V p-p/CM. Bandwidth 1·5cps-1·5MHz. Input imp. 2 meg Ω 25pF X amp. sensitivity 0·9V. p-p/CM. Bandwidth 1·5cps-800kHz. Input imp. 2 meg Ω 20pF. Time base. 5 ranges 10cps-300kHz. Synchronisation. Internal/external. Illuminated scale 140mm × 215mm × 330mm. Weight 15½lb. 220/240V a.c. Supplied brand new with handbook. **£40·00.** Carr. 50p.

RUSSIAN CI-16 DOUBLE BEAM OSCILLOSCOPE

5MHz Pass Band. Separate Y1 and Y2 amplifiers. Rectangular 5in × 4in C.R.T. Calibrated triggered sweep from 0·2μ/sec to 100 milli-sec per cm. Free running time base 50 Hz-1MHz. Built-in time base calibrator and amplitude calibrator. Supplied complete with all accessories and instruction manual.
£87. Carr. paid.

TE-16A Transistorised Signal Generator. 5 ranges 400kHz—30MHz. An inexpensive instrument for the handyman. Operates on 9V battery. Wide easy to read scale. 800kHz modulation. 5¾in × 5¾in × 3¾in. Complete with instructions and leads. **£7·97.** Post 25p.

TRANSISTORISED L.C.R. A.C. MEASURING BRIDGE

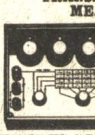

A new portable bridge offering excellent range and accuracy at low cost. Ranges: R. 1Ω–11·1 megΩ 6 Ranges ±1%. L.1 μH — 1 1 1 HENRYS 6 Ranges —2%. C. 10pF ±1110 mFd. 6 Ranges ±2%. TURNS RATIO 1:1/1000–1:11100. 6 Ranges ±1%. Bridge voltage at 1,000cps. Operated from 9V 100μA. Meter indication. Attractive 2 tone metal case. Size 7¾in × 5in × 2in. **£20.** Post 25p.

MODEL TE15 GRID DIP METER

Transistorised. Operates as Grid Dip, Oscillator, Absorption Wave Meter and Oscillating Detector. Frequency range 440kHz–280MHz in 6 coils. 500μA meter. 9V battery operation. Size 180mm × 80mm × 40mm.
£12·50. Post 20p.

BELCO AF-5A SOLID STATE SINE SQUARE WAVE C.R. OSCILLATOR

Sine 18-200,000 Hz; Square 18-50,000 Hz. Output max. +10dB (10 K ohms) Operation internal batteries. Attractive 2-tone case 7¾in × 5in × 2in. Price **£17·50.** Carr. 17p.

MODEL MG-100 SINE SQUARE WAVE AUDIO GENERATOR

Range 19-220,000 Hz. Sine Wave 19 — 100,000Hz. Square Wave. Output Sine or Square wave 10V. P. to P. Size 180mm × 90mm × 90mm. Operation 220/240V a.c.
£17·50. Post 37p.

MODEL AT201 DECADE ATTENUATOR

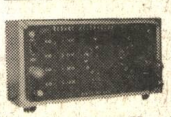

Frequency range 0-200kHz. Attenuator 0-111dB, 0·1dB step. Impedance 600 ohms. Max. input power 30dBm. Size 180mm × 90mm × 55mm.
£12·50. Post 37p.

TE-65 VALVE VOLTMETER

28 ranges. D.c. volts 1·5–1,500V a.c. volts 1·5–1,500V. Resistance up to 1,000 megohms. 200/240V a.c. operation. Complete with probe and instructions.
£17·50. Post 30p. Additional probes available: R.F. **£2·12**; H.V. **£2·50.**

MODEL U4311 SUB-STANDARD MULTI-RANGE VOLT AMMETER

Sensitivity 330 ohms/Volt a.c. and d.c. Accuracy 0·5% d.c. 1% a.c. Scale length 165mm.
0/300/750μA/1·5/3/7·5/15/30/75/150/300/750mA/1·5/3/7·5 amp. d.c. 0/3/7·5/15/30/75/150/300/750mA/1·5/3/7·5 amp. a.c. 0/75/150/300/750mV/1·5/3/7·5/15/30/75/150/300/750V d.c. 0/750mV/1·5/3/7·5/15/30/75/150/300/750V a.c.
Automatic cut out. Supplied complete with test leads, manual and test certificates. **£49.** Post 50p.

G. W. SMITH & CO. (RADIO) LTD.
Also see opposite page and next two pages

UNR-30 RECEIVER

4 Bands covering 550kHz–30MHz. BFO. Built-in Speaker 220/240V a.c. Brand new with instructions. **£15·75.** Carr. 37p.

UR-1A SOLID STATE COMMUNICATION RECEIVER

4 Bands covering 550kHz–30MHz. FET, S Meter. Variable BFO for SSB, Built-in Speaker, Bandspread, Sensitivity Control. 220/240V a.c. or 12V d.c. 12¾in×4¾in×7in. Brand new with instructions. **£25.** Carr. 37p.

SKYWOOD CX203 COMMUNICATION RECEIVER

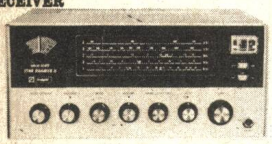

Solid state. Coverage on 5 bands 200–420 kHz and 0·55 to 30MHz. Illuminated slide rule dial. Bandspread. Aerial tuning. BFO, AVC, ANL, "S" meter. AM/CW/SSB. Integrated speaker and phone socket. Operation 220/240V a.c. or 12V d.c. Size 325×266×150 mm. Complete with instructions and circuit. **£32·50.** Carr. 50p.

LAFAYETTE HA-600 SOLID STATE RECEIVER

General coverage 150–400kHz, 550 kHz–30MHz. FET front end. 2 mech. filters, product detector, variable BFO, noise limiter. S Meter, Bandspread. RF Gain. 15in×9¾in×8¾in. 18lbs. 220/240V a.c. or 12V d.c. Brand new with instructions. **£50.** Carr. 50p.

TRIO 9R59DS COMMUNICATION RECEIVER

4 band covering 550kHz–30MHz continuous and electrical bandspread on 10, 15, 20, 40 and 80 metres. 8 valve plus 7 diode circuit. 4/8 ohm output and phone jack. SSB-CW. ANL. Variable BFO. S meter. Sep. bandspread dial. IF frequency 455kHz. Audio output 1·5W. Variable RF and AF gain controls 115/250V a.c. Size 7in×13in×10in with instruction manual. **£49·50.** Carr. paid.

EMI LOUDSPEAKERS

Model 350. 13in×8in with single tweeter/crossover, 20–20,000Hz. 15W RMS. Available 8 or 15 ohms. **£7·25** each. Post 37p.

Model 450. 13in×8in with twin tweeter/crossover. 55–13,000Hz. 8W RMS. Available 8 or 15 ohms. **£3·62** each. Post 25p.

HONEYWELL DIGITAL VOLTMETER VT.100

Can be panel or bench mounted. Basic meter measures 1V d.c. but can be used to measure a wide range of a.c. and d.c. volt, current and ohms with optional plug in cards. Specification: Accuracy: ±0·2, ±1 digit. Resolution: 1mV. Number of digits: 3 plus fourth overrange digit. Overrange: 100% (up to 1·999). Input impedance: 1000 Meg ohm. Measuring cycle: 1 per second. Adjustment: Automatic zeroing, full scale adjustment against an internal reference voltage. Overload: to 100V d.c. Input: Fully floating (3 poles). Input power: 110–230V a.c. 50/60 cycles. Overall size: 5¾in×2⅝in×8⅞in. AVAILABLE BRAND NEW AND FULLY GUARANTEED. **£35·50.** Carr. 50p.

SINCLAIR IC-12

List Price **£2·98**

OUR PRICE **£1·80**

P. & P. 10p.

SINCLAIR EQUIPMENT

Project 60 Package offers.

2×Z30 amplifier, stereo 60 pre-amp, PZ5 power supply. **£15·95.** Carr. 37p. Or with PZ6 power supply. **£18·00.** Carr. 37p.
2×Z50 amplifier, stereo 60 pre-amp, PZ8 power supply. **£20·25.** Carr. 37p.
Transformer for PZ8. **£2·97** extra.
Add to any of the above **£4·45** for active filter unit and **£13·00** for pair of Q16 speakers.
All other Sinclair products in stock.
2000 amp. **£21·95.** Carr. 37p.; 3000 amp. **£28·50.** Carr. 37p.: Neoteric Amp. **£43·95.** Carr. 37p. 1C12. **£1·80.** P. & P. 10p.
NEW PROJECT 605—**£20·97.** Carr. 37p.

WHARFEDALE MID-RANGE HI-FI UNITS

As used in world famous system. 5in dia. Impedance 4/8 ohms. High flux ceramic magnet. 20W RMS. Brand new **£1·50.** Carr. 37p.

SPECIAL OFFER! GOODMANS AXIOM 301

Hi-Fi 12in 20W twin cone full range speaker. 30–16,000Hz. 16,500 gauss. 8 ohm impedance. Brand new and boxed. (List price £21·72). OUR PRICE **£12·50** each. Carr. 50p.

HA-10 STEREO HEADPHONE AMPLIFIER

All silicon transistor amplifier operates from magnetic, ceramic or tuner inputs with twin stereo headphone outputs and separate volume controls for each channel. Operates from 9V battery. Inputs 5MU/100MU. Output 50MW. **£5·97.** Post 15p.

SPECIAL PURCHASE!

NEAT G30J STATIC BALANCE PICK-UP ARMS

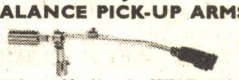

Identical specification to NEAT G30 arm but with two-tone chrome and black finish. Complete with head shell, pick-up rest and plug in phono leads. BRAND NEW—FULLY GUARANTEED. ONLY **£3·95.** Post 25p.

KAMODEN HM-350 TRANSISTOR TESTER

High quality instrument to test Reverse Leak current and D.C. current. Amplification factor of NPN, PNP, transistors, diodes, SCR's, etc. 4"×4" clear scale meter. Operates from internal batteries. Complete with instructions, leads and carrying handle. **£12·50.** Post 30p.

KAMODEN HMG-500 INSULATION RESISTANCE TESTER

Range 0–1,000 Megohms, 500 Volt. Battery operated. Wide range clear meter 4½"×4". Complete with deluxe carrying case, batteries, instructions. **£19·95.** Post 30p.

ARF-300 AF/RF SIGNAL GENERATOR

All transistorised, compact, fully portable. AF sine wave 18 Hz to 220 KHz. AF square wave 18 Hz to 100 KHz. Output sine/square 10v. P-P. RF 100 KHz to 200 MHz. Output 1v. maximum. Operation 220/240v. AC. Complete with instructions and leads. **£29·95.** Post 50p.

AKAI BARGAINS

SUPER MONEY SAVING OFFERS—BUY NOW WHILE STOCKS LAST! ALL BRAND NEW AND FULLY GUARANTEED

1721 Tape Rec.	£73·95	GXC40 Cassette Rec.	£82·95
X5000 Tape Rec.	£99·95	GXC40D Cassette Deck	£67·95
GX370 Tape Deck	£259·95	GXC40T Cassette/Receiver	£123·95
4000DS Tape Deck	£73·95	GXC45D Cassette Deck	£89·95
4000DS Dust Cover	£4·75	GXC46D Cassette Deck	£103·50
X201D Tape Deck	£132·95	GXC46 Cassette Recorder	£115·95
GX221D Tape Deck	£169·95	GXC60D Cassette Deck	£111·25
GX220D Tape Deck	£148·50	GXC65D Cassette Deck	£110·25
GX280D Tape Deck	£249·40	C835D Cassette Deck	£59·50
X1810D Tape/8 track Deck	£169·95	AA6300 Receiver	£79·95
GX1900D Tape/Cass. Deck	£177·95	AA8030 Receiver	£106·95
X2000SD Tape/Cas/8 Rec.	£223·30	AA8080 Receiver	£144·95
CR80DS8 8 track	£121·95	AA8500 Receiver	£175·00
CR81 8 track Rec.	£80·95	ADM11 Microphones (Pair)	£7·50
CR81D 8 track Rec.	£65·95		
CR81T 8 track/Receiver	£118·90		
CR80SS 8 track system	£145·00		

Carriage 50p extra (recorders and decks 75p).

GENUINE BARGAIN!

KOSS SP.3XC STEREO HEADPHONES

Response 10–15,000Hz. Impedance 4–6 ohms. Brand new. Boxed and fully g'teed (List £9·50). OUR PRICE **£6·50.** Post 25p.

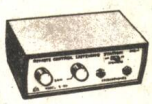

1021 STEREO LISTENING STATION

For balancing and gain selection of loudspeakers with additional facility for stereo headphone switching. 2 gain controls, speaker on-off slide switch, stereo headphone sockets. 6in×4in×2¼in. **£2·25.** Post 15p.

MP7 MIXER PREAMPLIFIER

5 microphone inputs each with individual gain controls enabling complete mixing facilities. Battery operated. 9¼in×5in×3in. Inputs Mics: 3×3mV 50K: 2×3mV 600 ohm. Phono meg. 4mV 50K. Phono ceramic 100mV 1 meg. Output 250mV 100K. **£8·97.** Post 20p.

TE-1035 STEREO HEADPHONES

Low cost high performance stereo headphones. Foam rubber ear cups. Adjustable head-band. 8 ohm impedance. 25–18,000Hz. With lead and stereo jack plug. ONLY **£1·97.** Post 12p.

NEW GARRARD MODULES

Popular range of Garrard decks with Shure cartridge fitted in deluxe plinth with hinged lid.

SP25 III Module/M75-6	£23·50
AP76 Module/M75-6	£33·80
AP96 Module/M75-6	£38·75
Zero 100S Module/M93E	£52·60

Carr. 50p extra any item.

HOSIDEN DH-08S DE-LUXE STEREO HEADPHONES

Features unique mechanical 2 way units and fitted adjustable level controls. 8 ohm impedance 20–20,000cps Complete with spring lead & stereo jack plug **£7·97.** Post 12p.

DOLBY SYSTEM NOISE REDUCTION UNIT

Improves the performance of cassette and semi-professional recorders. Reduces tape hiss by 3dB at 600Hz, 6dB at 1200Hz and 10dB for all frequencies above 3000Hz. Controls for input levels and noise reduction on record and replay. 2 meters for Dolby level. Off tape monitoring. Frequency response: 20Hz to 15kHz±1dB 19kHz—35dB. Size 15⅞in×9in×3¼in. A.c. 200/250V.

OUR PRICE **£32·50** Carr. 50p.

HOSIDEN DHO-2S STEREO HEADPHONES

Wonderful value and excellent performance combined. Adjustable headband. 8 ohm impedance. 20–12,000 cps. Complete with lead and plug. ONLY **£2·37.** Post 12p.

TAPE CASSETTES

Top quality Hi-Fi Low Noise in Library cases.

C60	3 for 75p.	10 for £2·35
C90	3 for £1·05	10 for £3·30
C120	3 for £1·35	10 for £4·20

Tape Head Cleaner **30p** each.
Post 10p extra.

EA.41 REVERBERATION AMPLIFIER

Self contained, transistorised, battery operated. Simply plug in microphone, guitar, etc., and output into your amplifier. Volume control, depth of reverberation control. Beautiful walnut cabinet. 7¼in×3in×4¼in. **£5·97.** Post 15p.

★ **TRANSISTORISED FM TUNER** ★

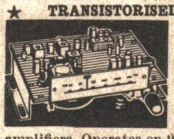

6 TRANSISTOR HIGH QUALITY TUNER, SIZE ONLY 6in×4in×2¼in. 3 I.F. stages. Double tuned discriminator. Ample output to feed most amplifiers. Operates on 9V battery. Coverage 88–108MHz. Ready built ready for use. Fantastic value for money. **£6·37.** Post 12p Stereo multiplex adaptors **£4·97.**

TE 1018 DE-LUXE MONO HIGH IMPEDANCE HEADSET

Sensitive, soft earpads, adjustable headband. Magnetic, impedance 2,600 ohms. **£1·97.** Post 15p.

G. W. SMITH & CO. (RADIO) LTD.
Also see previous pages and opposite page

FANTASTIC OFFER!

NIKKO TRM50 STEREO AMPLIFIER

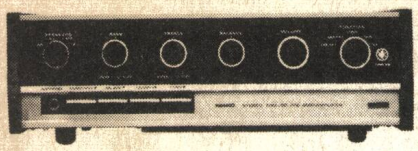

17+17W r.m.s. stereo amplifier with inputs for Magnetic and Crystal phono, Tuner, Tape, Aux and Tape Monitor. Outputs for two pairs of stereo speakers and tape. Stereo headphone socket. Full range of controls including loudness control, scratch filter, etc. Size 13in × 9¼in × 3¾in.
Unrepeatable offer—limited stocks!

List price £59·50
OUR PRICE
£39·95
Carriage 50p

NIKKO TRM 50 SYSTEM

NIKKO TRM50 17+17W rms stereo amplifier, BSR MP60, plinth and cover, Goldring G800 cartridge, pair of Linton 2 speakers and all leads.

OUR PRICE **£104·90** Carr. and Ins. £1·50

LEAK DELTA 30 SYSTEM

Leak Delta 30 stereo amplifier, Goldring GL75, plinth, cover and G800 cartridge. Pair of Leak 150 speakers and all leads.

OUR PRICE **£123·50** Carr. and Ins. £1·50

TELETON SAQ206B SYSTEM

Teleton SAQ206B 8+8W amplifier. BSR MP60, plinth and cover, Goldring G800 cartridge, pair of Apollo speakers and all leads.
OUR PRICE **£54·40** Carr. and Ins. £1·50
Amplifier only, **£22·95**. Carr. 50p.

SUPER BARGAIN!

AUDIOTRONIC ACP 8 8-TRACK CAR STEREO TAPE PLAYER

Tone, volume and balance controls. Track selector. Complete with matched pair of stereo speakers, connections and fittings.

ONLY **£15·95** Post 30p

HOMER INTERCOMS

Ideal for home, office, stores, factories, etc. Supplied complete with batteries, cable and free instructions.

2 Station, **£2·97**, 3 Station **£5·25**, Post 15p.
4 Station **£6·62**. Post 17p.

BH.001 HEAD SET AND BOOM MICROPHONE

Moving coil. Ideal for language teaching, communications. Headphone imp. 16 ohms. Microphone imp. 200 ohms. **£4·62**. Post 15p.

WHARFEDALE LINTON SYSTEM

Wharfedale Linton Amplifier, Linton Turntable, pair of Linton 2 speakers and all leads.

OUR PRICE **£106** Carr. and Ins. £1·25
LINTON RECEIVER SYSTEM £155. Carr. and Ins. £1·50.

AMSTRAD 8000 II SYSTEM

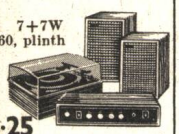

Amstrad 8000 II 7+7W amplifier. BSR MP60, plinth and cover, Goldring G800 cartridge, pair of Apollo speakers and all leads.
OUR PRICE **£48·25** Carr. and Ins. £1
Amplifier only, **£16·95**. Carr. 50p.

MONOTONE 6750 SYSTEM

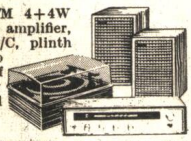

Monotone AM/FM 4+4W stereo tuner amplifier, Garrard 2025 T/C, plinth and cover, stereo cartridge, pair of speakers and all leads.

OUR PRICE **£35·50** Carr. and Ins. £1

AUDIOTRONIC ACR 3500 MW/LW CAR RADIO

Fully transistorised, dual waveband. Size 6¼in × 4¾in × 2in. 12V d.c. Neg. or pos. earth. Complete with fixing kit, speaker and leads.

ONLY **£7·50** Post 20p

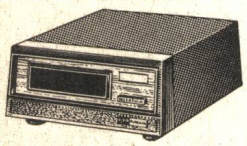

B.S.R. TD8S 8-TRACK STEREO TAPE PLAYER DECK

Integrated preamps (output 125mV) to feed into any stereo amplifier. Automatic and manual programme selector. 4 pole synchronous motor. 210/240V a.c.
OUR PRICE **£16·25**
Carr. 50p.

CREDIT TERMS FOR CALLERS ACCESS & BARCLAYCARD WELCOME

HI-FI EQUIPMENT

SAVE UP TO 33⅓% OR MORE

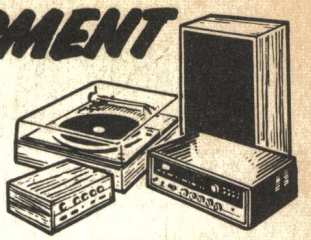

SEND S.A.E. FOR FULL DISCOUNT PRICE LISTS AND PACKAGE OFFERS!

SAVE £££'s PHILIPS GA308 TRANSCRIPTION TURNTABLE

2 speeds 33⅓ and 45 r.p.m. Lightweight tubular counterbalanced arm. Belt driven low speed synchronous motor. Viscous damped pick-up lift/lower device. Complete with teak plinth and hinged cover.
GA308 less cartridge (list £36·55)
OUR PRICE **£24·50**. Post 75p.
GA308 PU with GP400 stereo magnetic cartridge (list £47·65)
OUR PRICE **£29·95**. Post 75p.
LIMITED NUMBER ONLY!

V.A.T. INFORMATION

All mail orders received on or after April 1st will be subject to Value Added Tax.

THIS MUST BE ADDED TO THE TOTAL VALUE OF GOODS ORDERED (INCLUDING POSTAGE/CARRIAGE) AND ENCLOSED WITH ORDER.

ROTEL BARGAINS!
ALL BRAND NEW AND GUARANTEED

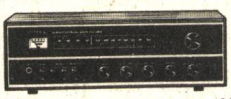

RA210 Amp.	£22·50
RA310 Amp.	£35·95
RA610 Amp.	£51·95
RX150 Receiver	£45·95
RX200 Receiver	£57·50
RX400 Receiver	£70·95

Post 50p extra any item.

SPECIAL OFFER! ROTEL RH700 STEREO HEADPHONES

20–20,000Hz. 8–16 ohm. (List £9·95). OUR PRICE **£6·75**. Post 25p.

SPECIAL OFFER! STEREO SPEAKERS

Matched pair of stereo bookshelf speakers. Deluxe teak veneered finish. Size: 14½in × 9in × 7½in. 8 ohms. 8W RMS. 16W peak. Complete with DIN lead. **£12·95**. Carr. 50p.

RECORD DECKS
(Post 75p)

BSR McDONALD	
C114 Mini	£4·97
C129 Mono	£6·50
C137	£8·35
MP60	£9·50
610	£12·95
810	£31·25
210/TPD3	£8·75
MP60/G800	£12·95
MP60/TPD1	£16·05
MP60/TPD1/G800	£19·50
MP60/TPD2	£14·35
610/TPD1	£18·95
510/TPD1	£17·95
HT 70	£13·99
HT70/G800	£17·25
HT70/TPD1	£20·35
HT70/TPD1 G800	£23·90
810 Plinth/Cover	£9·25
CONNOISSEUR	
BD1 Kit	£10·90
BD1 Chassis	£13·60
BD1/8AU2/Plinth/C	£33·10
BD2/8AU2/Chassis	£25·95
BD2/8AU2/Plinth/C	£33·85
GARRARD	
2025 T/C Stereo	£8·50
SP25 III	£10·25
SP25III/ACOS GP104 Ceramic	£10·25
SP25III/M75-6	£15·95
SP25 III Module/M75-6	£23·50
SL65B	£13·75
AP76	£17·95
AP76 Module/M75-6	£33·80
SL72B	£21·95
SL95B	£32·25
401	£25·95
ZERO 100A	£38·95
ZERO 100S	£36·95
ZERO 100S Mod/M93-E	£52·60
AP96 Module/M75-6	£38·75
GOODMANS	
TD100 Teak	£51·95
GOLDRING	
GL69/2	£18·50
GL72	£20·95
GL72/P	£27·50
Plinth 69/72	£7·02
LID 72	£3·25
GL75	£26·95
GL75P	£35·25
Plinth 75	£7·35
LID 75	£3·60
G99	£19·25
GL85P/C	£56·95
G101P/C	£20·50
LEAK	
Delta	£52·50
MICRO-SEIKI	
MR111	£29·50
MR111 Plinth and Cover	£9·50
PHILIPS	
GA105	£16·95
GA160 Teak	£27·00
GA308 Teak	£24·50
GA308 PU Teak	£29·95
GA212	£56·75
PIONEER	
PL12D	£34·50
PL15C	£51·35
PLA35	£82·65
PL50	£111·85
PL41D	£118·50
PL61	£119·95
THORENS	
TD125 II	£66·50
TD125AB II	£99·95
TX25	£6·95
TD160C	£56·95
TD150A II	£35·95
TD150AB II	£39·95
WHARFEDALE	
Linton	£26·95

PLINTHS AND COVERS
(Post 50p)

Budget SP25, etc.	£3·20
Budget AP76/Zero 100S	£4·50
Budget B.S.R.	£3·25
SME 2000 System	£34·50

RECORD DECK PACKAGES (Post 75p)

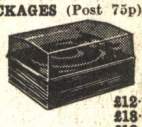

Decks supplied with stereo cartridge ready wired in plinth with cover.

GARRARD	
2025TC/9TAHCD	£12·75
SP25 III/G800	£18·50
SP25 III/M75-6	£18·50
SP25 III/M44-7	£19·75
SP25 III/M44-E	£20·95
SP25 III/M55E	£22·40
AP76/G800	£27·95
AP76/M75-6	£30·25
AP76/M55E	£30·50
AP76/M75EJ	£32·50
AP76/G800E	£30·75
AP76/M44E	£30·50
AP76/M75ED	£38·95
B.S.R. McDONALD	
MP60/G800	£17·50
MP60/M44-7	£18·95
MP60/M44-E	£19·95
GOLDRING	
GL75/G800	£39·50
GL75/G800E	£42·50

G.W.SMITH & CO (Radio) LTD
Personal Callers Welcome – All Branches Open 9–6 Mon. to Sat.

10 TOTTENHAM CT. RD. LONDON, W.1 Tel: 01-637 2232
27 TOTTENHAM CT. RD. LONDON, W.1 Tel: 01-636 3715
257/258 TOTTENHAM CT. RD. LONDON, W.1 Tel: 01-580 0670
3 LISLE STREET, LONDON, W.C.2 Tel: 01-437 8204
34 LISLE STREET, LONDON, W.C.2 Tel: 01-437 9155
311 EDGWARE ROAD, LONDON, W.2 Tel: 01-262 0387

All Mail Orders to—
11-12, Paddington Green, London, W.2
Tel: 01-262 6562

P.E. Sound Synthesiser

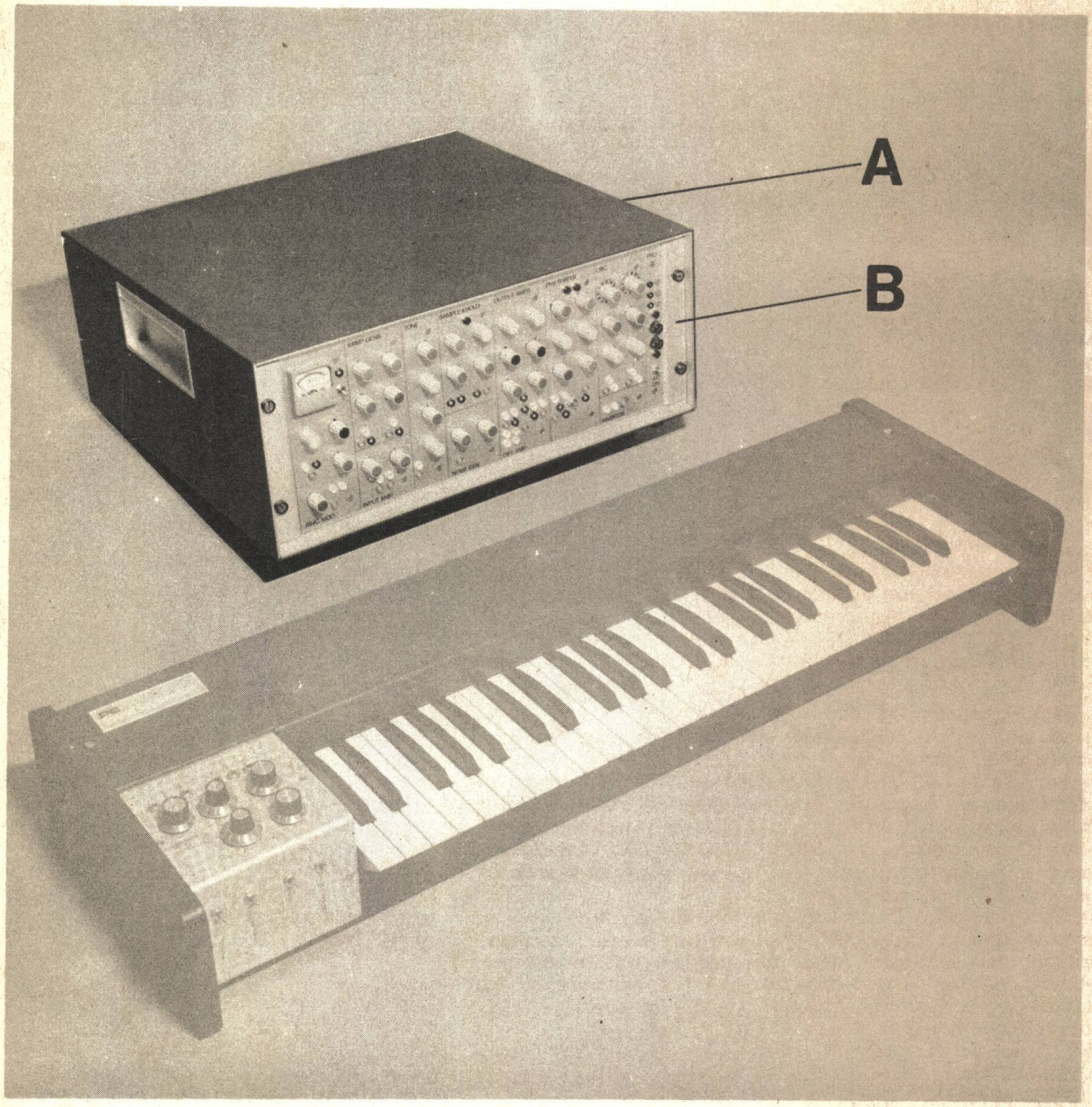

vero

As featured in the current Practical Electronics articles.
Case and framework exclusively available from manufacturers.
Case Part No. 1CD/4U/215 ——— A
Framework Part No. CF/4U/13/D/MR1 ——— B
Total price inclusive of carriage and packing.
Send cash with order for immediate delivery.

£18·31 +VAT

VERO ELECTRONICS LTD.,
Industrial Estate,
Chandlers Ford, Eastleigh,
Hants. SO5 3ZR.

Registered No. 701364

PE

FASHIONS IN BUILDING

As a constructors' magazine PRACTICAL ELECTRONICS is naturally very much concerned with building methods and materials. In its fairly short history, electronics has evolved through three distinct periods represented by different fashions in constructional techniques. First was the wood or original "breadboard" era; then the metal era dominated by the box-like chassis; now the plastics era is here with s.r.b.p. board (in some form or another) providing the main platform for the assembly of circuit components.

In many modern designs metalwork is no longer an essential part of the structure carrying the circuit components. Frequently, metalwork is used in a subservient role, merely to enclose or protect an electronic assembly which exists as a more or less self-contained entity built upon a piece of laminated plastics board.

The "plastics era" dawned soon after the arrival of the transistor. Right at the outset of this momentous technological event, industry was able to accommodate this newcomer by adopting printed circuit techniques. These techniques were already well established and in use with miniature valves. While the printed circuit was an ideal technique for mass production of electronic assemblies, it was not so ideal for the private constructor and his "one-off's". So when transistors became available to the individual, improvisation was called for, and a period of great inventiveness ensued. Many varied (and some quite unexpected) building techniques were tried out.

As a start, existing standard items such as component group boards and tag strips were commonly pressed into service as a platform for a transistorised circuit. Assemblies of varying degrees of elegance were built on odd scraps of s.r.b.p. laminate board, hardboard, and even cardboard. The arrival of perforated s.r.b.p. board helped towards a tidier form of construction and eliminated the drudgery of drilling countless holes. However, there was no universally adopted method for home construction until, some 12 years after the first transistor, there appeared in this country the first purpose-designed proprietary printed wiring board. Like many brilliant and successful ideas, this product was, in essence, beautifully simple and—after the event—so obvious. In due course this printed wiring board, though of course initially conceived with the professional user in mind, was to prove the answer to most private constructors' needs, and in time it rationalised the construction of electronic circuits.

PRACTICAL ELECTRONICS played not an insignificant part in bringing this constructional method to the attention of the amateur. This particular board was introduced to constructors in the very first issue of this magazine, and subsequently has been used in the majority of our projects.

Though very popular, the printed wiring board has no monopoly however, and the constructor has a fair choice of alternative methods, including home-made printed circuits. But practically all methods used today are based on the plastics board, the indispensable material which provides the foundations for modern electronic assemblies.—F.E.B.

Editor
F. E. BENNETT

Editorial
D. BARRINGTON
G. GODBOLD
S. R. LEWIS B.Sc.

Art Dept.
J. D. POUNTNEY *Art Editor*
J. A. HADLEY
R. J. GOODMAN
S. W. R. LLOYD

Advertisement Manager
D. W. B. TILLEARD
Phone: 01-634 4202

P. J. MEW
Phone: 01-634 4210

C. R. BROWN, *Classified*
Phone: 01-634 4301

Editorial & Advertising Offices:
Fleetway House, Farringdon St.,
London EC4A 4AD
Phone: *Editorial* 01-634 4452
Advertisements 01-634 4202

PE Sound Synthesiser 3
VOLTAGE CONTROLLED OSCILLATORS and INVERTER

By G.D.SHAW

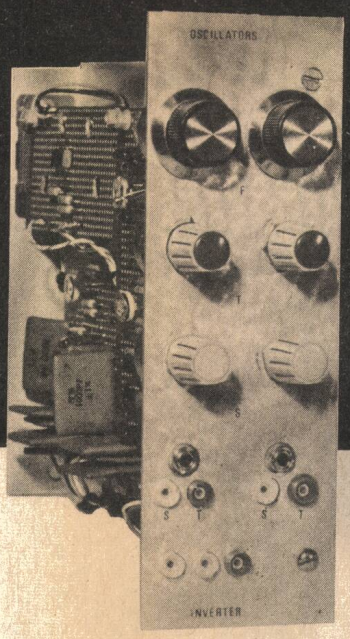

THIS month the voltage controlled oscillator and voltage inverter will be described as well as details for assembling them.

THE VOLTAGE CONTROLLED OSCILLATOR

Perhaps the most important reason for the employment of a voltage controlled oscillator lies in the resultant ability of the oscillator to produce tone patterns by application of varying voltages to its control input. If these voltages are derived from what is essentially another oscillator, or series of oscillators, running at ultra low frequency, then the performance of the tone generating oscillator becomes quite automatic and dependent only on the continued operation of the programming devices.

The oscillators in the Synthesiser are based on the operational linear integrator and the circuit is shown in Fig. 3.1. In this arrangement IC1 acts as the integrator while IC2 is connected as a comparator and serves to switch the direction of integration.

The integrator programming signal is applied across the diode bridge D1–D4 and it is important that the polarities are maintained as shown.

CIRCUIT ACTION

To describe the circuit action assume that the comparator is sitting at its positive saturation level then diodes D1 and D3 in the integrator input bridge are reverse biased. There is a current flow into the integrator summing junction through R1, D2 and similarly a current flow away from the bridge through D4, R2, shown by solid arrows, so that the integrator begins to ramp negatively. The negative excursion of the integrator output voltage will continue until the current driven through R5 is equal to or greater than the current driven through R4 as a result of the output voltage of the comparator. At this time the voltage at point *P* will go negative and the comparator will switch rapidly to its negative saturation level.

Under these conditions diodes D2 and D4 in the integrator input bridge are reverse biased and current flows are established as shown by the dotted arrows. In the case of the current flow away from the integrator summing junction, this causes the integrator to ramp positively.

WAVESHAPES DEVELOPED

Providing that R2 is the same value as R1 and both polarities across the input bridge are at the same potential then the rate of change of integrator output voltage is the same as before and the result is a symmetrical triangular waveform appearing at point *Q*. The oscillogram of Fig. 3.1 shows the phase relationship between the triangular waveform generated by the integrator and the switching waveform generated by the comparator at point *R* in the circuit.

When the integrator output voltage is again equal to or greater than the level of positive feedback set by R4 the comparator switches back to its positive saturation level and the cycle repeats.

FREQUENCY CONTROL

Consideration of the foregoing reveals that R4 actually plays a part in the determination of fre-

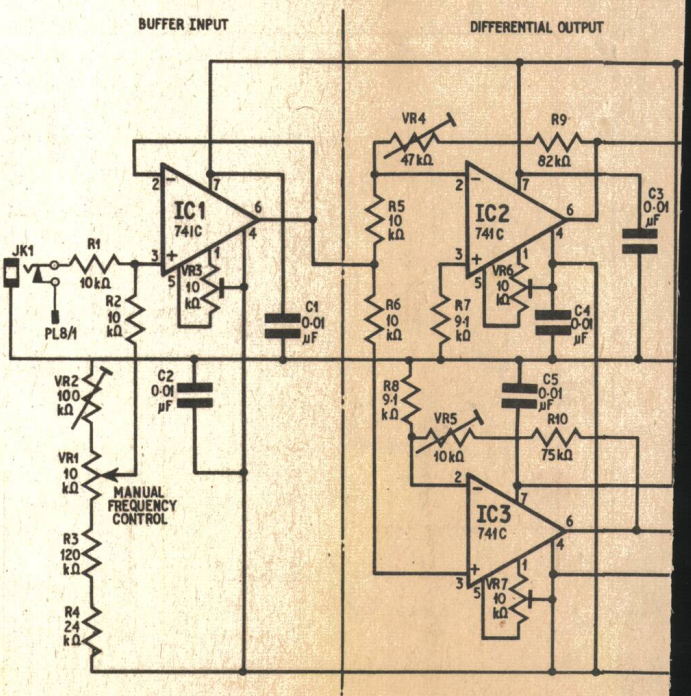

quency by setting the point at which the integrator output causes the comparator to switch.

Lowering the value of this component has the effect of increasing the level of positive feedback to the comparator thereby requiring a higher integrator output voltage to switch the comparator and thus lowering the frequency of operation of the integrator..

Conversely, if the value of R4 is increased the overall frequency of operation is also increased.

PRACTICAL V.C.O.

The circuit shown in Fig. 3.2 is the three stage prototype v.c.o. arrangement. Starting from the output end, the third stage is a practical form of the oscillator shown schematically in Fig. 3.1. The second stage consists of two operational amplifiers arranged to provide a differential output across the oscillator input bridge. This particular stage is necessary since, in order to attain the full frequency range, the oscillator requires a drive potential greater than the individual power supply rails can provide.

The first stage of the circuit is a buffer/follower which serves to reduce the current drive required from the control source and which also provides a test-bed on which to try out various forms of circuit response without the necessity of disturbing the settings of the oscillator and differential driver. The type of input stage used in the v.c.o. is of some importance since it has a bearing, not only on the performance of the oscillator as a whole, but also on the design and operation of other circuits in the synthesiser. The response of the input stage may therefore be either linear or logarithmic and there are advantages and disadvantages attached to both methods.

LOGARITHMIC OSCILLATORS

Most commercially available synthesisers use logarithmic v.c.o.s in which the slope of the response

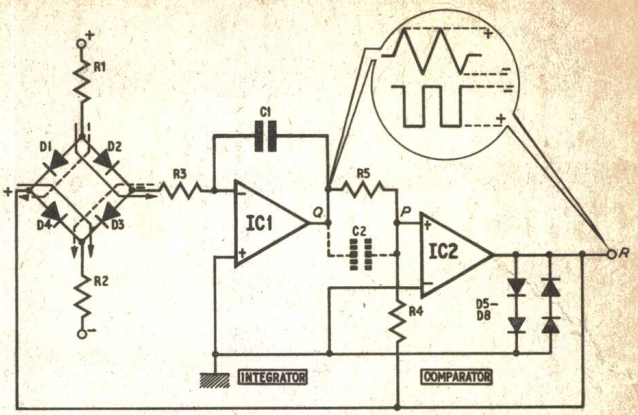

Fig. 3.1. Basic voltage controlled oscillator. Oscillogram shows phase relation between integrator and comparator outputs. The inclusion of the capacitor shown dotted linearises the input voltage/frequency relationship.

is adjusted so that equal increments of input voltage raise the frequency of oscillation by one semitone.

A typical response curve is shown in Fig. 3.3. This has the distinct advantage that if, say, three oscillators are programmed simultaneously by the same control voltage, two of the oscillators may be manually offset by fixed multiples of the semitonal voltage increment so that the effect of the mixed oscillator output is that of producing a chord by the depression of only one key.

The arrangement of having equal voltage increments per semitone also allows for a simplification in the construction of the keyboard divider network and some commercial instruments use a series chain of equal value resistors with a form of "tuning" control which varies the voltage across the chain.

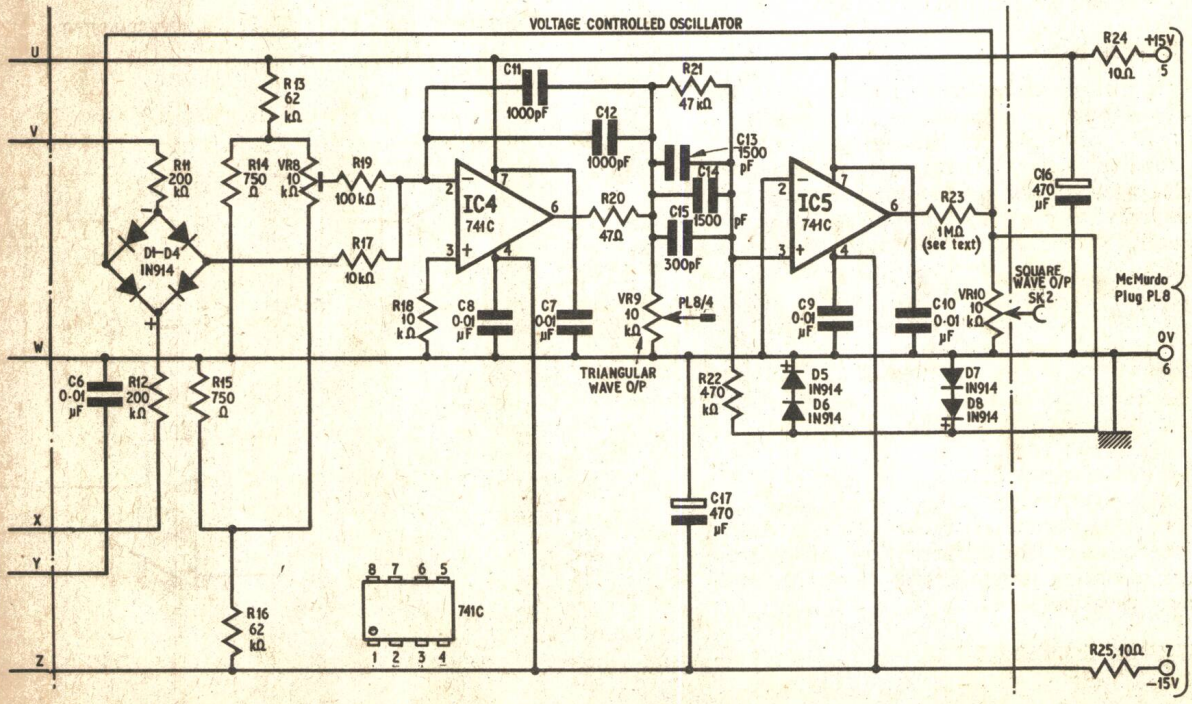

Fig. 3.2. Circuit diagram of the three stage voltage controlled oscillator

LINEAR V.C.O.'s COMPARED

The oscillators in this Synthesiser are arranged with an input stage having a linear performance such that the overall response is as shown in Fig. 3.4.

The resulting loss of the ability to play "chords" was not considered a disadvantage when weighed against the advantages of simplification in building and setting up. Furthermore, the use of linear characteristics in the oscillators provides greater justification for the use of a parallel divider network in the keyboard which, although rather more complex than the series arrangement, means that the accuracy of each semitone is dependent only on the accuracy and stability of its own resistors and not upon the remainder of the chain.

The overall performance of the oscillator, however, is solely dependent upon the response characteristic of the buffer/follower stage and it will be noted that space has been left on circuit board B (Fig. 3.6) for the benefit of constructors who may wish to try out their own ideas of logarithmic response.

The SN76502 manufactured by Texas Instruments is a logarithmic amplifier in integrated circuit form.

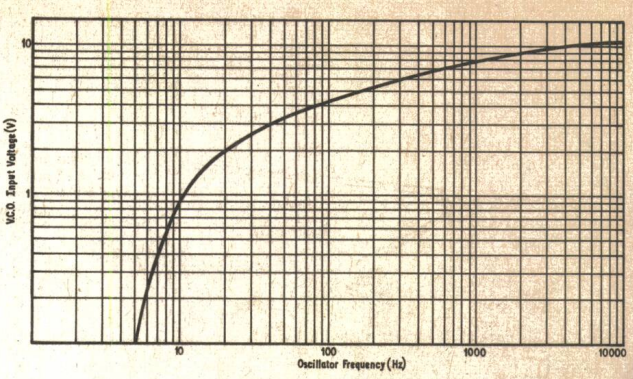

Fig. 3.3. Logarithmic response curve showing the positive exponential relationship obtained when control voltage required is IV/octave

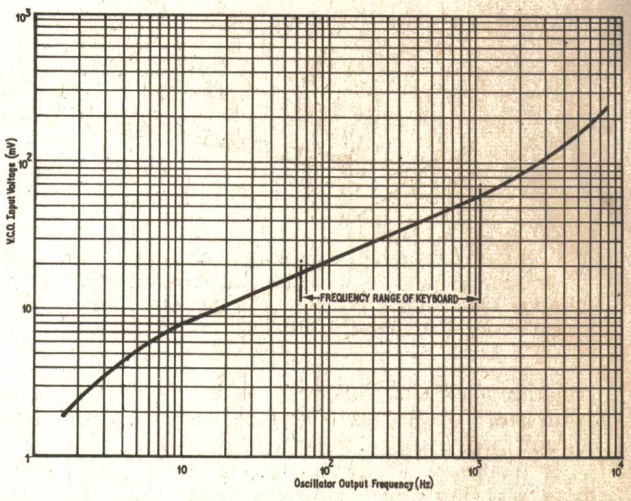

Fig. 3.4. Linear response curve of v.c.o. showing frequency range of keyboard

The advantage of this device is that its response slope may be varied by adjustment of one external component so that performance matching becomes a relatively simple matter.

MAJOR COMPONENTS

The estimated total cost of this project is around £200. Obviously this figure can be reduced if bulk purchase of components which will appear in quantity is made. To make this possible, components in excess of 12 are listed below.

Resistors	Quantity
10kΩ	52
33kΩ	12
All 5% ½ watt carbon	
5·1kΩ	13
7·5kΩ	36
10kΩ	15
All 2% ½ watt metal oxide	

Potentiometers	Quantity
10kΩ carbon linear	19
All 25mm dia. midget moulded carbon types	
10kΩ carbon linear horizontal presets	12
100Ω linear horizontal Cermet presets	53
10kΩ linear horizontal Cermet presets	21

Integrated Circuits	Quantity
741C 8 pin D.I.L.	56

Diodes	Quantity
1N914	39
1SJ50	14

Capacitors	Quantity
470μF elect. 25V	12
0·01μF polyester	46

Sockets	Quantity
3·5mm miniature jack sockets	15
2mm miniature sockets	48

BUILDING THE OSCILLATOR

Due to the restricted space in the finished module construction should start by assembly and wiring of all the components on to the front panel before the panel is mounted to the circuit board support plate. Figs. 3.5 and 3.6 give the front panel drilling details and component layout. The leads from the controls should be formed into a harness which passes down the centre of the panel between the potentiometers as shown, those for routing to the circuit boards being about ten inches long.

Next mount the McMurdo plug to the rear of the circuit board support plate complete with its wire leads already soldered into position. Fit the eight stand-off supports to the plate—transipillars are recommended but six B.A. screws with metallic spacers may be used providing that these are isolated from the conducting strips on the circuit boards.

The front panel should now be fixed to the circuit board support plate using a 4B.A. countersunk screw and nut in the upper hole, and the locking rod and bush in the lower one. If the assembly seems to be

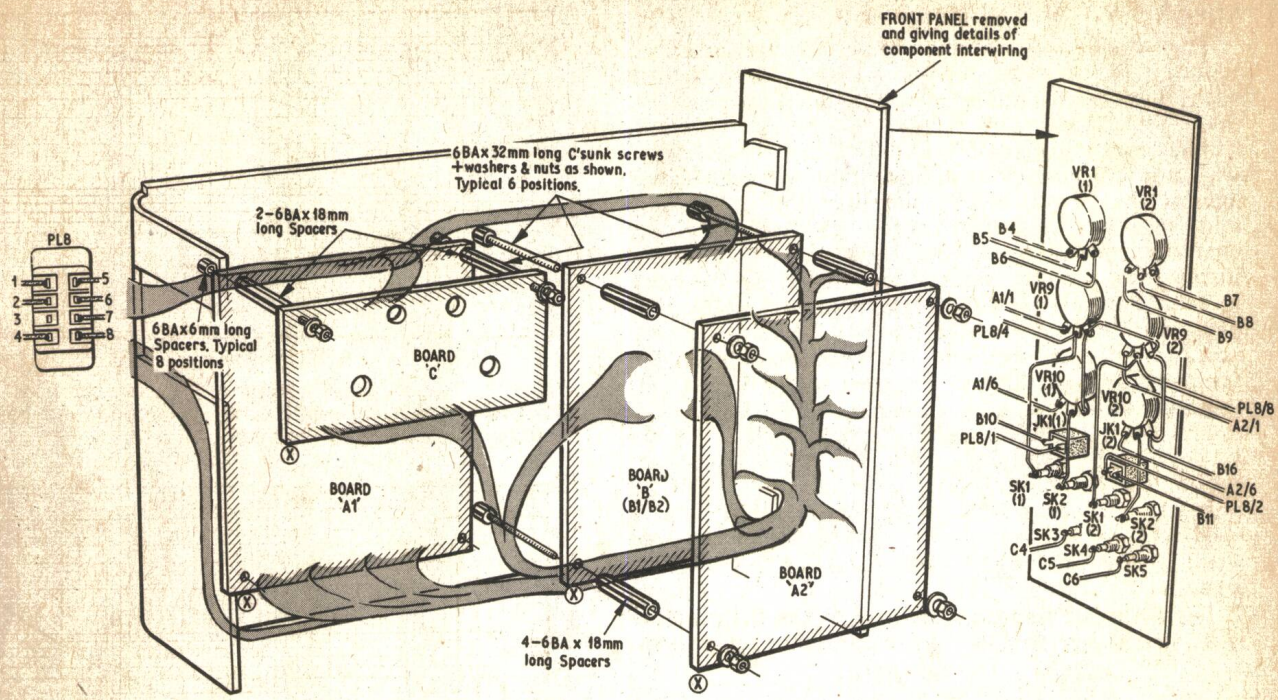

Fig. 3.5. Front panel component assembly and wiring with details of mounting and disposition of boards on the module support plate. The small ringed X at the board edges indicates orientation. (See board details)

on the slack side this may be corrected by fitting a thin steel washer between the bush and lug on the circuit board support plate.

It is useful, at this stage, to make up a jumper lead carrying power supplies from the main busbars so that modules may be tested and set up outside the main frame assembly. The lead should be about 24in (61 cms) in length terminated at one end by a McMurdo plug and at the other by a McMurdo socket wired to match the power supply outputs.

Figs. 3.7 and 3.8 show the circuit board layouts for the oscillator. Board A carries the differential output stage together with the oscillator itself and two of these boards are required.

Board B carries the buffer input stages and power supply decoupling stages for both the other boards.

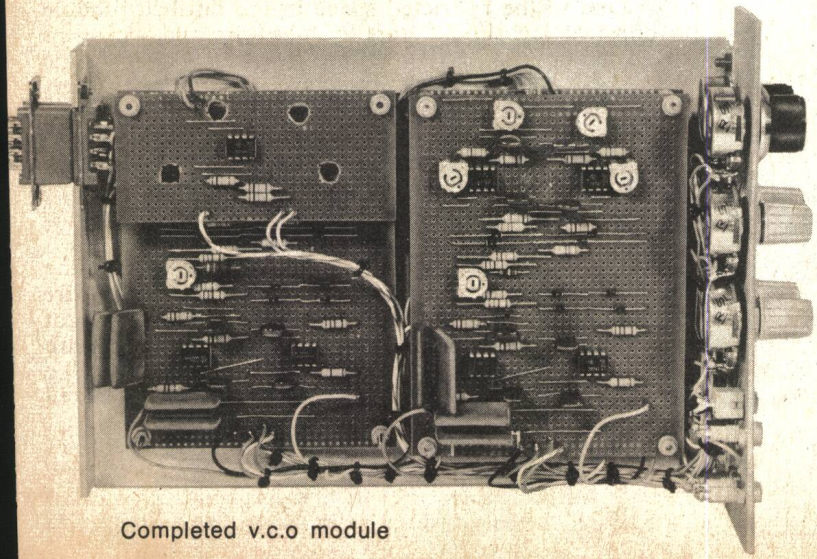

Completed v.c.o module

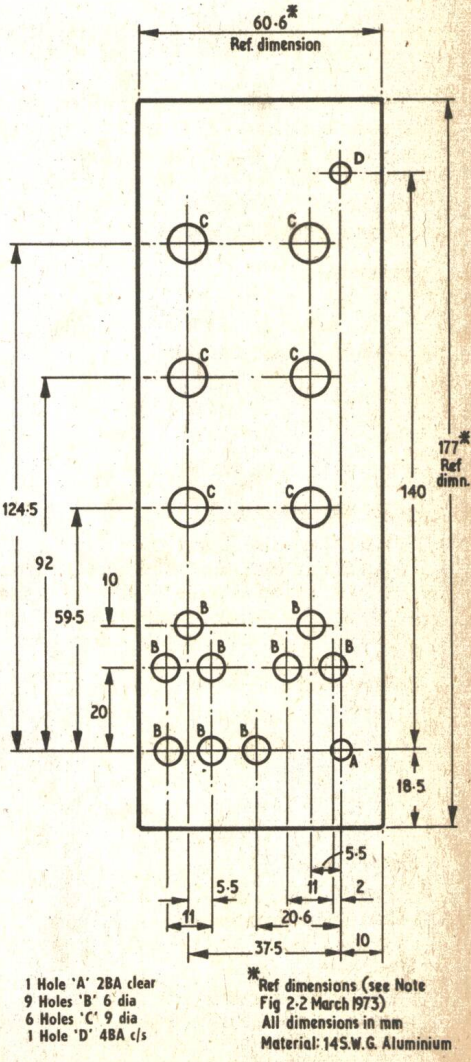

Fig. 3.6. Drilling details for v.c.o. module front panel

BOARD B

The next stage of construction covers assembly of the buffer input stage and power supply decoupling Board B. Fig. 3.7 shows the recommended layout. Wiring of the completed board into the support frame is simplified if single ended Veropins are inserted into the boards at the indicated positions of the lead out wires.

Mount Board B to the support plate adjacent to the front panel and couple up the leads to the power supply, VR1 (manual frequency control) and external input sockets. The leads to Boards A may be omitted at this stage.

COMPONENTS . . .

VOLTAGE CONTROLLED OSCILLATOR (2 REQUIRED)

Resistors

R1	10kΩ	R13	62kΩ
R2	10kΩ	R14	750Ω
R3	120kΩ	R15	750Ω
R4	24kΩ	R16	62kΩ
R5	10kΩ	R17	10kΩ
R6	10kΩ	R18	10kΩ
R7	9·1kΩ	R19	100kΩ
R8	9·1kΩ	R20	47Ω
R9	82kΩ	R21	47kΩ
R10	75kΩ	R22	470kΩ
R11	200kΩ	R23	1MΩ (see text)
R12	200kΩ	R24–R25	10Ω (2 off)

All 2% ½ watt metal oxide

Capacitors

C1–C10	0·01μF Polyester (10 off)
C11–C12	1,000pF Silver Mica (2 off)
C13–C14	1,500pF Silver Mica (2 off)
C15	300pF Silver Mica
C16–C17	470μF elect. 25V (2 off)

Diodes

D1–D8 1N914 (8 off)

Potentiometers

VR1	10kΩ carbon log	
VR2	100Ω horizontal preset	miniature cermet types
VR3	10kΩ horizontal preset	
VR4	47kΩ horizontal preset	
VR5	10kΩ horizontal preset	
VR6	10kΩ horizontal preset	
VR7	10kΩ horizontal preset	
VR8	10kΩ horizontal preset	
VR9	10kΩ midget moulded carbon linear	
VR10	10kΩ midget moulded carbon linear	

Integrated Circuits

IC1–IC5 741C 8 pin dual-in-line (5 off)

Miscellaneous

SK1—3·5mm jack socket, SK2–SK3 2mm miniature socket (2 off) 0·1in matrix Veroboards as required.

CHECK-OUT

Set VR3 to mid position and VR2 to the minimum position and attach the jumper lead. With the power supply switched on and VR1 at minimum position measure the voltage at VR1 wiper. Adjust VR2 on both drivers so that voltages are exactly the same.

The value is not critical at this stage but is preferably in the range −5mV to −10mV. Measure the output voltage of both drivers and adjust VR3 until it is equal to whatever voltage has been set on the wipers of VR1.

Connect a temporary link between the external input and ground on both drivers. The purpose of these links is to simulate a zero-voltage prewired programming connection and they will be removed on completion of the setting up of the oscillators. Finally, set VR1 to its maximum position and measure the voltage at the sliders. This should be about −750mV, depending on the actual potential of the power supply rails, any discrepancy between the two readings being corrected by adjustment of the values of R3 and/or R4.

BOARD A: ASSEMBLY AND CHECK-OUT

Assembly of Board A should commence with the differential output stage which should be constructed up to and including R11 and R12. This stage should now be set up before proceeding with the construction of the oscillator.

Make temporary power supply connections from Board B, attach an input lead to the differential output stage and connect this directly to ground. With VR4 and VR5 at their maximum settings and VR6 and VR7 at their mid positions switch on.

Monitor the output voltages of both halves of the stage and adjust VR6 so that the output of IC2 reads +5mV and VR7 so that the output of IC3 reads −5mV. Now reconnect the input of the differential stage to the output of the driver from which the power supply is being taken and set the output voltage of the driver to −25mV by means of VR1.

Monitor the outputs of IC2 and IC3 and adjust VR4 and VR5 until these read +255mV and −255mV respectively. Repeat the measurements at various settings of VR1 to ensure that the gain of each half of the stage is linear at × 10 throughout the working range. Remember that the actual readings should be, in the case of IC2, + [5mV + (10 × driver output voltage)] and in the case of IC3, − [5mV + (10 × driver output voltage)].

Having set the gain and offset of the differential output stage the assembly of the oscillator section may now be completed (Fig. 3.8).

CHOICE OF CAPACITOR

The type of capacitor used in the integrator is of some importance as far as frequency stability is concerned and it is best to use a type having low leakage and as low a value of inductance as possible. Silver mica is thus the best choice and the value shown may be made up of two or more parallel wired capacitors.

R23 serves to limit the current output of the comparator. With this omitted the comparator has only the forward resistance of D5–8 between its output and ground and, although IC5 is capable of handling the current involved, this means that a substantial ripple will be present on the oscillator power supply rails and could possibly be transmitted through to

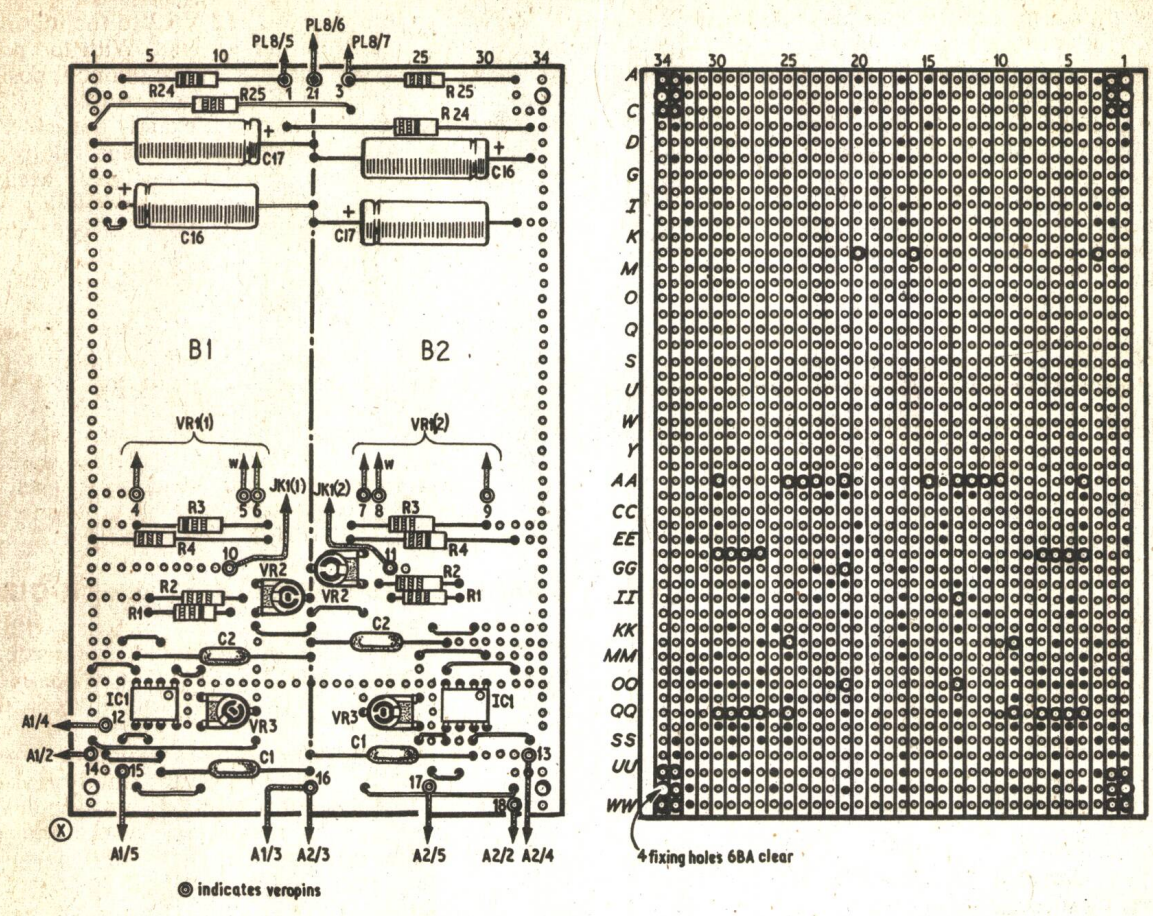

Fig. 3.7. Component layout and wiring for Board B. Since two v.c.o.'s are required, components for each are arranged in board areas B1 and B2

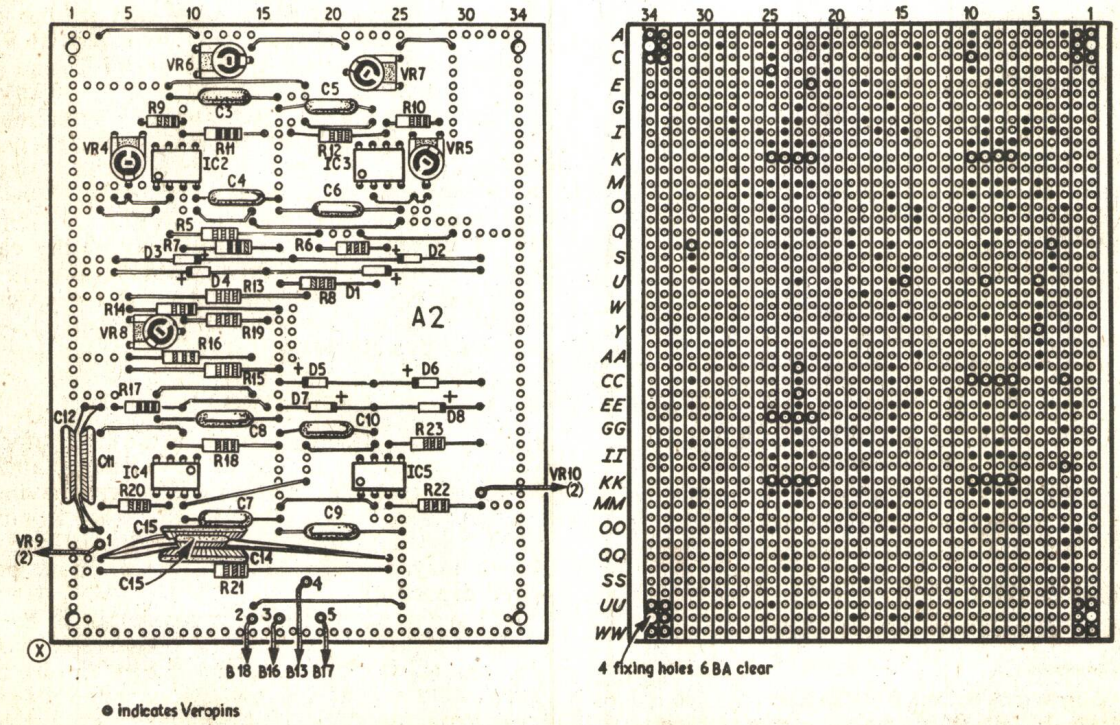

Fig. 3.8. Component layout and wiring for Board A. Two of these are required as shown in Fig. 3.5

the main bus-bars. Thus, where it is intended to use the comparator square wave output as a signal source the value of R23 should be 2·2 kilohms, that is, sufficient to reduce the ripple to an acceptable level. When the square wave output is not to be used, such as in the keyboard oscillators, the value may be increased to 1 Megohm to reduce ripple to negligible proportions. The inclusion of this resistor will however reduce the triangular wave voltage swing to 200mV p-p and limit the maximum frequency of the oscillator to about 8·3kHz.

R13 to R16 and VR8 form a divider network which provides a value of bias current to the summing junction of the integrator.

MOUNTING THE A AND B BOARDS

The completed A boards should be mounted on the support plate such that one is immediately adjacent to the McMurdo plug and the other directly above Board B. It is best to mount and set-up the oscillator boards one at a time. When a board has been fully connected, set VR8 and VR1 to their mid positions and switch on the power supply. Observe the triangular waveform on the oscilloscope —the frequency of oscillation should be about 7kHz.

Gradually reduce the setting of VR1 until the waveform begins to exhibit marked signs of assymmetry. At this point adjust the setting of VR8 *with great care* to restore the symmetry, this latter operation also being seen to cause an increase in the frequency.

Continue reducing the setting of VR1, adjusting VR8 as necessary, until VR1 is at its minimum setting and the output waveform is symmetrical.

At very low frequencies the setting of VR8 is extremely critical, too large a shift in either direction causing IC4 to saturate. If this happens, VR1 should be set to its mid position again and the various steps repeated.

With VR1 in its minimum position final setting of the very low frequency end of the range is accomplished by adjustment of VR2 in conjunction with VR8 as before. If IC4 saturates at or before minimum setting of VR1 the setting of VR2 will have to be increased.

Very low frequency instability can be a problem with this type of oscillator and although it can be made to operate at less than 1Hz with the component values given it is best to set the minimum operating frequency to about 5Hz.

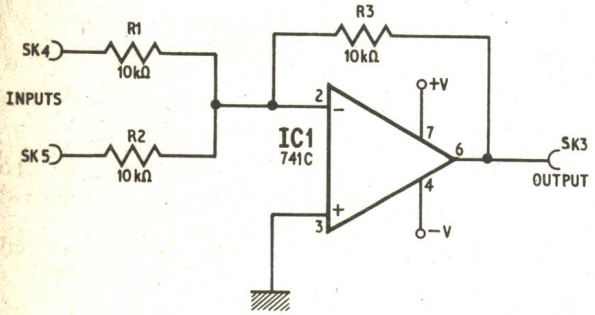

Fig. 3.9. Circuit diagram of voltage inverter

COMPONENTS . . .

INVERTER

Resistors

R1–R3 10kΩ (3 off)

Integrated Circuit

IC1—741C 8 pin D.I.L.

Miscellaneous

SK1–SK3 2mm miniature sockets (3 off) 0·1in matrix Veroboard as required

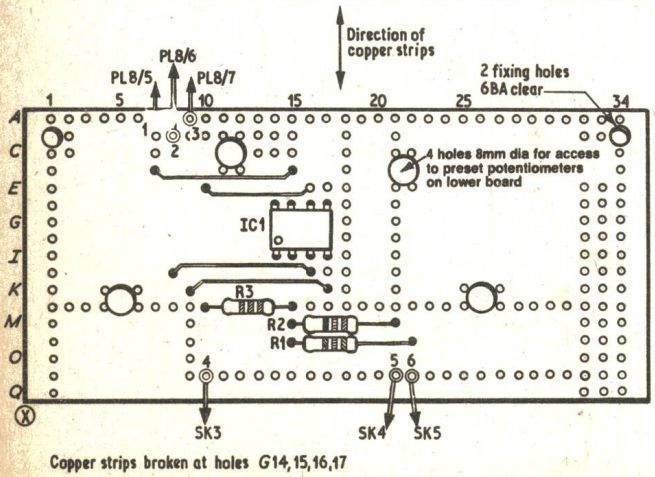

Fig. 3.10. Inverter component Board C layout and wiring

MATCHING THE OSCILLATORS

If the component values and tolerances specified have been adhered to, comparison of performance between both oscillators will show that the input voltage/frequency relationship is substantially similar, any differences in performance characteristic being due to tolerance variations in the components.

Extreme accuracy in the matching of oscillators is not necessary since linear response is involved.

INVERTER

Little need be said concerning the assembly of the voltage inverter which is essentially an inverting unity gain amplifier of the simplest kind. The circuit is shown in Fig. 3.9 while the recommended circuit board layout is shown in Fig. 3.10.

The completed board should be mounted directly over the A board furthest from the front panel.

USING THE MODULE

On completion of the whole module use the voltage inverter to investigate the effects of mixing triangular and square waves at varying frequencies.

The output may be fed to the high level input of most power amplifiers, but bear in mind that the output will be equal to the sum of the voltage swings at the inputs.

Additionally it is possible to carry out some simple experiments in frequency modulation by setting one of the oscillators to modulate the other. A low amplitude modulation at about 7Hz produces a true vibrato to the tone of the modulated oscillator whilst varying the amplitude and frequency of modulation can produce some strange, even bizarre effects.

Next month: the ramp generators and input amplifiers are described.

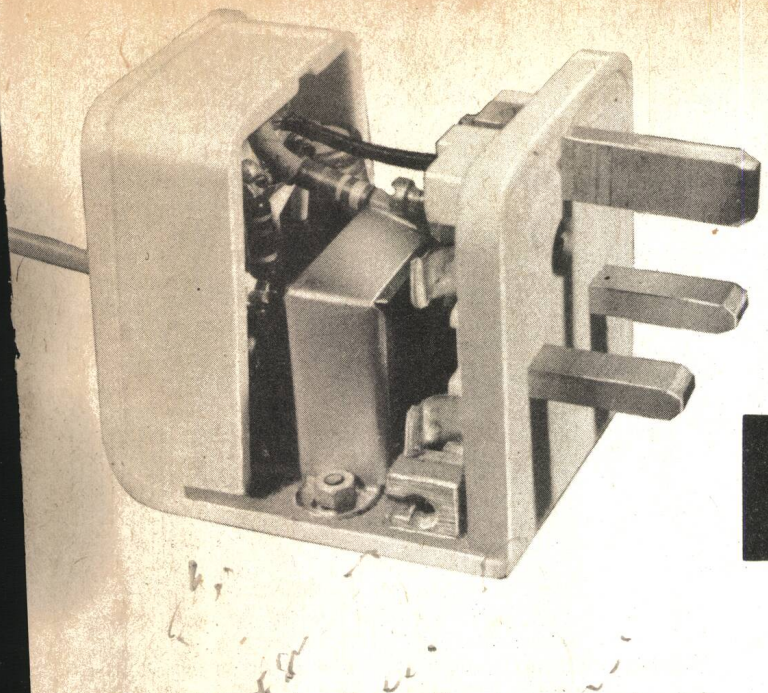

A Novel BATTERY ELIMINATOR

By J. S. GODDARD

THIS article describes a d.c. power supply unit with the unusual feature of being contained in a 13A flat pin mains plug. It will supply 60mA at 9V suitable for radio, cassette or record players.

UNIT ADVANTAGES

One of the disadvantages of conventional battery eliminators is that you are left with a box which must either be strung between plug and unit or replace the batteries in the battery compartment.

This design overcomes both problems. The lead from the mains plug goes directly to the unit and plugs in with a simple jack plug. The batteries of the unit are left in place but simply disconnected when the jack plug is attached. The batteries are reconnected when the plug is removed. The project becomes even easier if the unit has a socket for a battery eleminator.

CIRCUIT

The circuit diagram of the battery eliminator is given in Fig. 1 together with suitable battery cut-out circuit in cases where a socket is not available on the unit to be supplied.

The transformer has a 6-0-6V secondary with the centre tap unconnected. This feeds a four diode bridge rectifier, the output being smoothed by the reservoir capacitor C1 and R2. The Zener diode D5 provides a final 9V regulated output.

MODIFYING THE PLUG

The plug used for housing the circuit components is an Ever-Ready type which has to be modified. This is accomplished by cutting a $\frac{5}{16}$in step at the bottom rear of the plug as in Fig. 2. A piece of $1\frac{7}{8}$in × $1\frac{3}{4}$in × $\frac{1}{8}$in hardboard is cut to form a new base for the plug. This is Araldited into place ensuring that the ends of the plug are upright and parallel.

A $\frac{5}{16}$in hole is drilled and countersunk in the upper half of the plug directly above the brass screw insert for the neon LP1.

For the d.c. leadout pair a $\frac{1}{4}$in hole is drilled $\frac{3}{4}$in up from the base at the centre rear of the plug.

ASSEMBLING THE COMPONENTS

The components may now be mounted in the expanded plug. First, the transformer is loosely held in position by two 6 B.A. screws.

The mains neon is now positioned and connected to the plug terminals together with the transformer primary windings.

With the capacitor and diodes in place the transformer is tightened down. The output lead is connected across the Zener diode after R2 has been added in series, in the positive line, as shown in the circuit diagram.

With all the components mounted in place care should be taken to see that none are touching the mains pins or their screws. If necessary more room can be made by discarding the screws on the back of the mains pins and soldering instead of clamping. Once all appears to be correct inside a cover has to be constructed for the plug.

COMPONENTS . . .

Resistors

R1 220kΩ $\frac{1}{2}$W carbon

R2 82Ω $\frac{1}{2}$ watt 10% carbon

Capacitor

C1 400μF 10V elect.

Diodes

D1–D4 IN4003 (4 off)

D5 9·1V 400mW Zener

Transformer

T1 Eagle miniature mains transformer 240V primary 6-0-6V secondary at 100mA.

Miscellaneous

13A fused mains plug (Ever Ready Type 7032), LP1 mains neon, $1\frac{7}{8}$in × $1\frac{3}{4}$in × $\frac{1}{8}$in hardboard, $\frac{1}{4}$in 6 B.A. countersunk screws (2 off), $\frac{3}{8}$in self tapping (2 off), FS1 fuse to suit equipment. PL1 3·5mm jack plug.

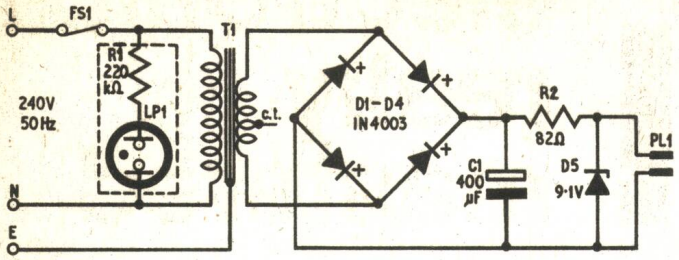

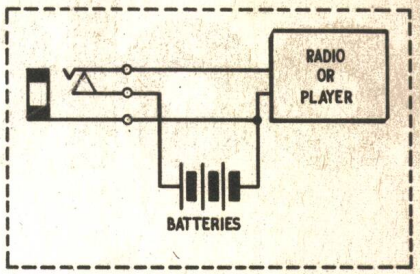

Fig. 1. The circuit diagram of the battery eliminator together with a suitable battery circuit cut-out for the equipment to be supplied

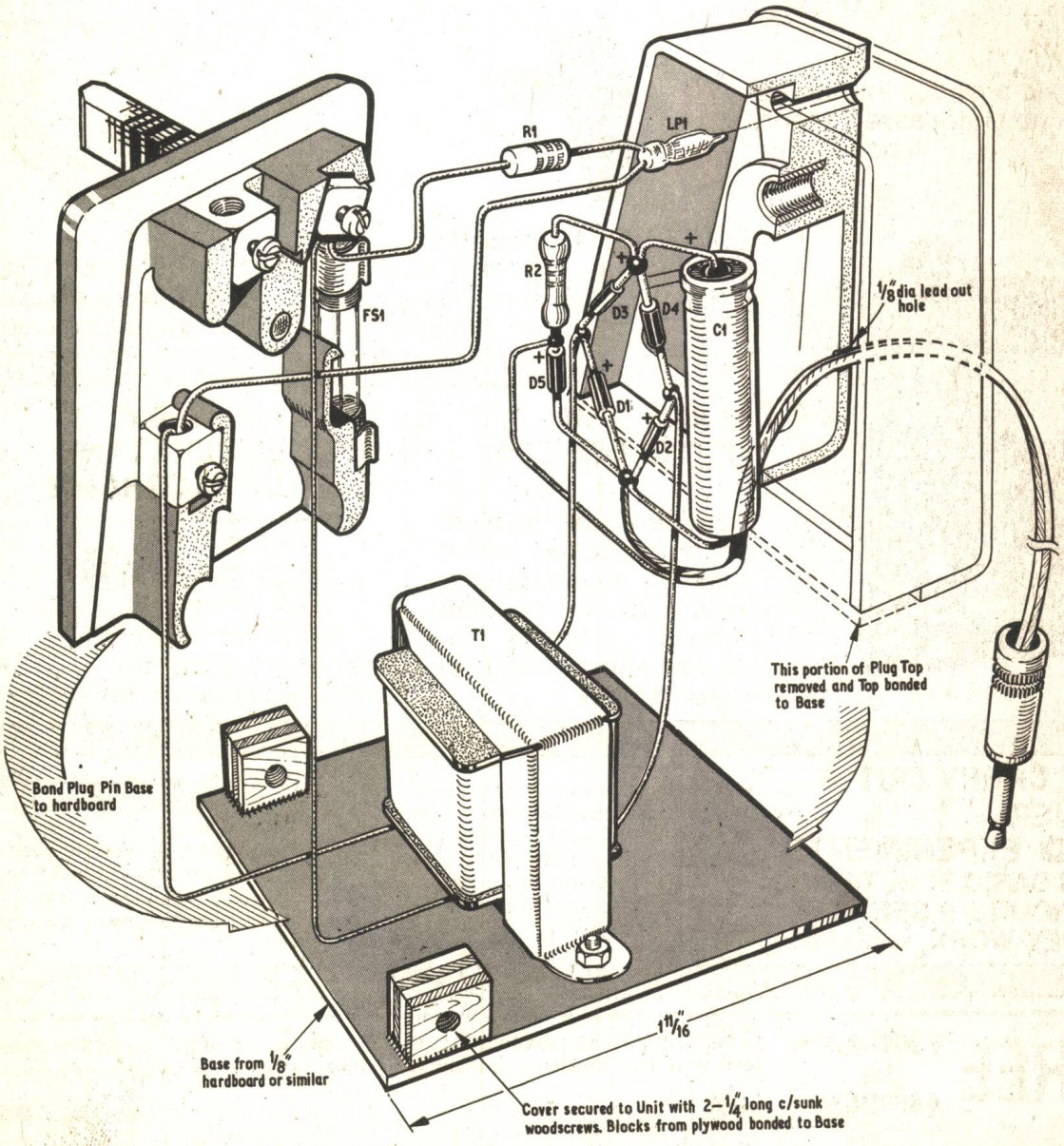

Fig. 2. Assembly and wiring details for the battery eliminator

look! electronics really mastered

... practical
... visual
... exciting!

no previous knowledge
no unnecessary theory
no "maths"

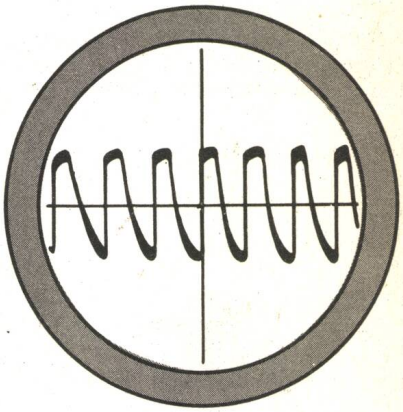

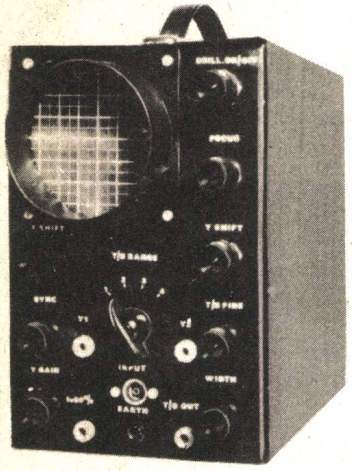

RAPY

BUILD, SEE AND LEARN
step by step, we take you through all the fundamentals of electronics and show how easily the subject can be mastered. Write for the free brochure now which explains our system.

1/ BUILD AN OSCILLOSCOPE

You learn how to build an oscilloscope which remains your property. With it, you will become familiar with all the components used in electronics.

2/ READ, DRAW AND UNDERSTAND CIRCUIT DIAGRAMS

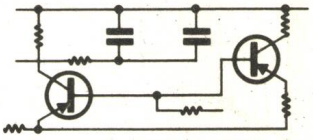

as used currently in the various fields of electronics.

3/ CARRY OUT OVER 40 EXPERIMENTS ON BASIC ELECTRONIC CIRCUITS & SEE HOW THEY WORK, including :

valve experiments, transistor experiments amplifiers, oscillators, signal tracer, photo electric circuit, computer circuit, basic radio receiver, electronic switch, simple transmitter, a.c. experiments, d.c. experiments, simple counter, time delay circuit, servicing procedures.

This new style course will enable anyone to really understand electronics by a modern, practical and visual method—no maths, and a minimum of theory—no previous knowledge required. It will also enable anyone to understand how to test, service and maintain all types of electronic equipment, radio and TV receivers, etc.

FREE **POST NOW for BROCHURE**

or write if you prefer not to cut page

To BRITISH NATIONAL RADIO & ELECTRONICS SCHOOL, P.O. BOX 156, JERSEY. Please send your free brochure, without obligation, to: *we do not employ representatives*

NAME BLOCK CAPS

ADDRESS PLEASE EL43

special free gift also to all our students

TRANNIES

24 WOODHILL, HARLOW, ESSEX
Phone: Harlow 37739
P/P 10p. Price list S.A.E. (No Callers Please)

LOWEST PRICES

Please compare our Prices ! ! !
All our stock are brand *new* with full money *refund* if not *completely satisfied*

74 Series TTL

	1–24	25 plus		1–24	25 plus		1–24	25 plus
7400	15p	14p	7450	15p	14p	7492	67p	64p
7401	15p	14p	7451	15p	14p	7493	67p	64p
7402	15p	14p	7453	15p	14p	7494	77p	74p
7403	15p	14p	7454	15p	14p	7495	77p	74p
7404	15p	14p	7460	15p	14p	7496	77p	74p
7405	15p	14p	7470	29p	25p	74100	£1·75	£1·65
7408	18p	17p	7472	29p	25p	74104	97p	94p
7410	15p	14p	7473	37p	35p	74105	97p	94p
7411	15p	14p	7474	37p	35p	74107	40p	33p
7413	29p	26p	7475	47p	45p	74110	£1·25	£1·25
7420	15p	14p	7476	43p	40p	74111-	£1·00	95p
7430	15p	14p	7480	67p	64p	74118	£1·00	95p
7440	15p	14p	7481	97p	94p	74119	£1·35	£1·25
7441	67p	64p	7482	97p	94p	74121	67p	64p
7442	67p	64p	7483	£1·10	£1·05	74141	67p	64p
7446	97p	94p	7486	32p	30p	74145	£1·50	£1·40
7447	97p	94p	7490	67p	64p	74150	£1·80	£1·70
7443	97p	94p	7491	37p	34p			

* Devices may be mixed to qualify for price breaks
* 100 plus less 10% off 25 plus break

Linear Integrated Circuits

301a	TO99	49p	723c	TO99	87p
301a	DIL	45p	723c	DIL	90p
701c		63p	741c	TO99	38p
702c		63p	741c	DIL	36p
709c	TO99	28p	741c	3 pin DIL	34p
709c	DIL	31p	747c	DIL	42p
710c		53p	743c	TO99	33p
711c		58p	1437		£1·10
			1458		£1·10

Electrolytic Capacitors

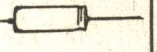

4 volt		16 volt		40 volt	
47µF	6p	15µF	6p	47µF	6p
100µF	6p	33µF	6p	100µF	8p
220µF	6p	68µF	6p	150µF	9p
330µF	6p	150µF	7p	220µF	10p
1,000µF	12p	220µF	8p	470µF	17p
4,700µF	26p	680µF	15p	680µF	23p
		1,000µF	15p	1,000µF	23p
6·3 volt		1,500µF	23p	2,200µF	40p
33µF	6p	2,000µF	39p		
68µF	6p				
150µF	6p	**25 volt**			
470µF	10p	10µF	6p	**63 volt**	
680µF	12p	22µF	6p	1µF	6p
1,500µF	16p	47µF	6p	2·2µF	6p
2,200µF	16p	100µF	7p	4·7µF	6p
3,300µF	24p	150µF	7p	6·8µF	6p
		220µF	9p	10µF	6p
10 volt		470µF	12p	22µF	6p
22µF	6p	680µF	18p	68µF	9p
47µF	6p	1,000µF	20p	100µF	10p
100µF	6p	2,200µF	36p	150µF	12p
220µF	7p	5,000µF	62p	220µF	17p
330µF	9p			330µF	20p
470µF	9p	**40 volt**		470µF	24p
1,000µF	12p	6·8µF	6p	1,000µF	40p
1,500µF	23p	15µF	6p	1,600µF	74p
2,000µF	39p	33µF	6p	2,500µF	93p

BARGAIN PACKS

UNMARKED PACKS

Pack of 25 1N4148 **50p**

Pack of 10
BC108 **50p**
BC107 **50p**
(Plastic can)

Pack of 10 Plastic BC109 **50p**

Pack of 10
BC169 **50p**
(unmarked) but tested

2N2646 (unmarked) **30p each**

Pack of 10
2N2926G **50p**
Unmarked but fully tested

2N3055
1–9 **30p**
10 plus **25p**

FULLY MARKED TYPES
AD161, AD162 M/P
1–9 **54p**
10 plus **48p**

BC107-BC108 BC109
1–9 **8p**
10–99 **7p**
100 plus **6p**

BC 182L:-3-4-212-4
1–9 **8p**
10 plus **7p**

AC127 or AC128
1–9 **12p**
10 plus **11p**
100 plus **9½p**

Transistors

	p		p		p		p		p
AC107	15	BC142	30	BF330	16	OC81	13	2N2905	42
AC126	14	BC143	30	BF390	34	OC83	20	2N2924	16
AC127	12	BC144	26	BFX84	25	OC84	25	2N2926	9
AC128	12	BC145	24	BFX85	32	TIP29A	48	2N3053	24
AC142K	20	BC147	8	BFX86	22	TIP30A	58	2N3054	50
AC141K	18	BC148	8	BFX87	25	TIP31A	58	2N3055	48
AC176	14	BC149	8	BFX88	24	TIP32A	66	2N3405	40
AC187	12	BC153	15	BFY50	19	TIP33A	95	2N3663	52
AC187K	18	BC154	16	BFY51	15	TIP34A		2N3702	8
AC188	12	BC157	12	BFY52	15		£1·40	2N3703	8
AC188K	18	BC158	11	BFY64	35	TIP35A		2N3704	8
ACY17	21	BC159	12	BFY90	65		£2·30	2N3705	8
ACY18	19	BC167	11	BSX20	17	TIP36A		2N3706	8
ACY19	23	BC168	10	C407	20		£2·90	2N3708	8
ACY20	20	BC169	10	C426	30	TIP41A	72	2N3707	8
ACY21	21	BC177	14	C428	28	TIP42A	83	2N3709	8
ACY22	16	BC179	14	C450	15	2N706	12	2N3710	8
ACY39	62	BC182L	8	MP8111	32	2N930	21	2N3711	8
AD140	36	BC183L	8	MP8112	42	2N1131	20		
AD142	40	BC184L	8	MP8113	32	2N1132	25	2N3794	15
AD143	35	BC186	30	MP8121	30	2N1613	20	2N3819	25
AD149	34	BC212L	10	MP8122	40	2N1711	24	40361	45
AD150	55	BC213L	10	MP8123	45	2N2904	36	40362	45
AD161	27	BC214L	10	NKT211	25	2N2904A	40	40636	55
AD162	27	BC258	8	NKT212	25				
M/P	50	BC259	8	NKT214	23				
AF114	14	BC267	12	NKT217	50				
AF115	14	BC268	13	NKT261	21				
AF116	14	BC300	36	NKT271	18				
AF117	14	BC301	29	NKT274	18				
AF118	82	BC302	26	NKT275	23				
AF124	24	BC303	45	NKT403	65	1N914	7	BA145	20
AF139	36	BC304	35	NKT405	79	1N916	7	BA154	12½
AF239	37	BCY70	15	NKY603F		1N4148	7	BAX13	12½
AL100	68	BCY71	33		60	1N4007	20	BAX16	12½
AL102	60	BCY72	15	NKT613F	30	1S44	9	BAY18	17½
AL103	49	BD123	60	NKT674	24	1S113	15	BAY31	7½
ASY26	27	BD130	45	NKT677F	22	1S120	15	BY100	17½
ASY27	36	BD131	62	NKT713	29	1S121	14	BY126	15
AU103	90	BD132	81	NKT773	25	1S130	8	BY127	17½
AU110	97	BD135	38	OC19	50	1S131	10	BYX10	22½
AU111	67	BD136	44	OC20	50	1S132	12	OA5	17½
BC107	8	BD141	£1·70	OC23	30	1S920	7	OA9	10
BC108	8	BD142	45	OC25	25	1S922	8	OA10	22½
BC109	8	BF159	30	OC28	30	1S923	12	OA47	8
BC113	14	BF173	26	OC29	30	1S940	5	OA70	7
BC116	15	BF177	25	OC35	25	AA119	10	OA73	10
BC125	15	BF178	26	OC36	35	AA129	10	OA79	7
BC126	22	BF179	32	OC41	13	AAZ13	10	OA81	8
BC132	14	BF194	14			AAZ15	12½	OA85	10
BC134	14			OC44	13	AAZ17	12½	OA90	7
BC135	14	BF195	15	OC45	13	BA100	15	OA91	7
		BF244	25	OC70	21	BA102	22½	OA95	7
BC137	14	BF260	26	OC71	13	BA115	7½	OA200	10
BC138	24	BF329	16	OC72	13	BA144	12½		

DIODES & RECTIFIERS

MULLARD POLYESTERS

MULLARD POLYESTER CAPACITORS C280 SERIES
250V P.C. mounting: 0·01µF, 0·015µF, 0·22µF, **3p.** 0·033µF, 0·047µF, 0·068µF, **3½p.** 0·1µF, **4p.** 0·15µF, 0·22µF, **5p.** 0·33µF, **6½p.** 0·47µF, **8½p.** 0·68µF, **11p.** 1·0µF, **13p.** 1·5µF, **20p.** 2·2µF, **24p.**

MULLARD POLYESTER CAPACITORS C296 SERIES
400V: 0·001µF, 0·0015µF, 0·0022µF, 0·0033µF, 0·0047µF, **2½p.** 0·0068µF, 0·01µF, 0·015µF, 0·022µF, 0·033µF, **3p.** 0·047µF, 0·068µF, 0·1µF, **4p.** 0·15µF, **6p.** 0·22µF, **7½p.** 0·33µF, **11p.** 0·47µF, **13p.**
160V: 0·01µF, 0·015µF, 0·22µF, 0·033µF, 0·047µF, 0·068µF, **3p.** 0·1µF, **3½p.** 0·15µF, **4½p.** 0·22µF, **5p.** 0·33µF, **6p.** 0·47µF, **7½p.** 0·68µF, **11p.** 1·0µF, **13p.**

VOLUME CONTROLS

Potentiometers
Carbon track 500 Ω to 22·M Ω
Log or Linear
Single **12p.** Dual gang (stereo) **40p**
Single type with D.P. switch **12p** extra.

SLIDE POTENTIOMETERS

58mm, TRACK
SINGLE GANGED, LOG or LIN
1k to 1M. **40p each.**
TWIN GANGED, LOG or LIN
1k to 500k. **60p each.**

CARBON SKELETON PRESETS

Small high quality type (linear only).
All values 100–5megohms.
● 1 watt **5p each.**
● 2·5 watt **6p each.**

VEROBOARD

	0·15 Matrix	0·1 Matrix
2½in × 3¾in	17p	23p
2½in × 5in	25p	25p
3¾in × 3¾in	25p	25p
3¾in × 6in	30p	29p
5in × 17in (plain)	83p	—

Vero Pins (bag of 36), **20p.**
Vero cutter, **45p**; Pin insertion Tools (0·1 and 0·15 matrix) at **55p.**

SLIDE SWITCH
SPST **10p** each. D.P.D.T. **12p** each.
MINIATURE NEON LAMPS
240V or 110V 1–4 **5p**, 5 plus **4½p** each.

MINITRON DIGITAL INDICATOR TYPE 3015F. Reads 0–9 and decimals (Data Sheet on request). Only **£1·50.** 16 DIL Socket, **30p.** Driven by 7447, **95p.**

RECTIFIERS

P.I.V.	1 amp		1·5 amp	
50	IN4001	4p	PL4001	7p
100	IN4002	4p	PL4002	3p
200	IN4003	5p	PL4003	9p
400	IN4004	6p	PL4004	9p
600	IN4005	7p	PL4005	12p
800	IN4006	3p	PL4006	14p
1,000	IN4007	9p	PL4007	18p

BRIDGE RECTIFIERS

P.I.V.	1 amp	2 amp	5 amp	10 amp
50	30p	48p	£1·60	£2·00
100	32p	52p	—	—
200	34p	55p	£1·80	£2·10
400	36p	58p	£1·95	£2·20
600	40p	62p	£2·20	£2·50
800	45p	—	—	—

THYRISTORS

PIV	50	100	200	300	400
1 Amp	25	23	37	40	47
3 Amps	40	45	55	—	60
7 Amps	—	87	92	—	1·12

RESISTORS

¼ watt 5% carbon **1p each**
½ watt 10% carbon **1p each**
1 watt 10% carbon **2½p each**
range 10 ohms to 4·7 meg.
¼ watt m/o 2% **3p each**
range 10–1 meg ohms.

ZENER DIODES

400 M/W 5% Miniature BZY 88 Range
All voltages 3·3–33 Volt
8p each

1 Watt 5%
All voltages 6·8–200 volts
12p each

10 Watt 5%
All voltages 7·5–100 volts
45p each

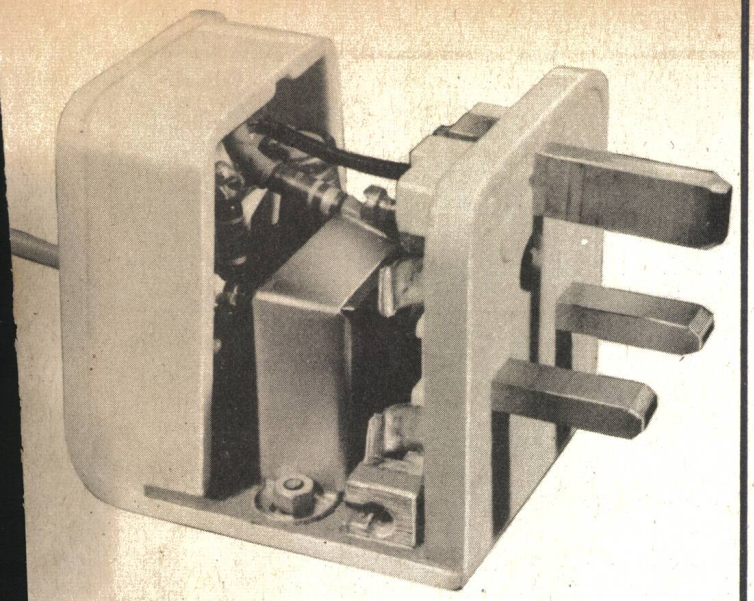

Good results can be obtained by using good quality card about $\frac{1}{16}$in thick. The card is bent to fit around the top and two sides of the plug snugly. The inside of the card may be scored with a knife to make it bend more easily. With the card bent around the plug mark off, with a pencil, the exact dimensions. When cut to shape check to ensure a good fit, if necessary a former may be made to hold the card in the required shape.

The cover is held onto the plug by two self tapping screws. These screws tighten into $\frac{5}{16}$in blocks of plywood about $\frac{3}{8}$in square. The blocks must be drilled to accept the screws and glued in the bottom front of the plug as shown.

Now is the time to fill any gaps between plug and base. A plastic filler is used, which can be sandpapered smooth when dry. The cover and base may be painted to match the plug, sprayed paint gives good results on a suitable primer.

CONNECTING THE UNIT

Consideration now has to be given to the method of connecting the battery eliminator to the unit which it will power. A number of radio and cassette players on the market have facilities for battery eliminators, and in this case it is only necessary to obtain the correct plug. If your unit does not have facilities such as this, or you are unable to obtain the plug, the following will serve as an alternative.

A 3·5mm jack plug is connected to the eliminator's outlet lead with the matching socket in the unit. The jack plug is connected to the outlet lead wire with the positive line going to the tip. The socket may now be fitted to the unit, a suitable position must be found to ensure it will not interfere with any internal workings.

With the hole drilled and socket fitted the supply wiring must be adapted to cater for the new facility. The positive lead to the battery compartment must be broken and the jack socket connected in the break. The negative lead goes to the third contact on the socket as well as the battery compartment.

With the jack plugged into the socket the positive line from battery to unit is broken and connected instead to the outlet of the power supply.

The 400μF electrolytic capacitor may be difficult to obtain, but good results can still be obtained with a smaller one. ★

BOOK REVIEWS

ELECTRONICS IN MUSIC
By F. C. Judd
Published by Neville Spearman
169 pages, 9in × 6in. Price £3·15

MR JUDD has condensed into this book the fruit of many years' experience in electronics. The six main chapter headings cover virtually every aspect of the subject ranging from the application of electronics in the production of music through a survey of electronic musical instruments, the production of synthetic sound and electronic music, the uses of the tape recorder in the field and, finally, a run-down on the parameters involved in the high fidelity reproduction of music.

The text throughout seems designed to guide the reader into this fascinating and ultra-technical subject without once getting bogged down in an excess of detail. Despite this tendency there is sufficient data presented to enable the home constructor to build and experiment with several interesting circuits. The book is well illustrated with sixteen pages of half tone plates and plenty of clear line diagrams and circuits. The author could have perhaps usefully expanded his treatment of the subjects of synthetic sound and electronic music in view of the current high level of interest although the shortfall in this respect does little to mar the overall presentation of the book which is excellent.

"Electronics in Music" is likely to be welcomed enthusiastically by technical and non-technical readers whose interest in the subject matter may be frustrated by the lack of definitive texts.

G.D.S.

TELEVISION INTERFERENCE MANUAL
By B. Priestley, B.Sc., G3JGO
Published by Radio Society of Great Britain
92 pages, 148mm × 210mm. Price 80p

TELEVISION interference from s.w. transmitters is something which many amateur radio enthusiasts find very difficult to eliminate. The Radio Society of Great Britain must therefore be congratulated for attempting to bring this problem to the notice of radio hams and for providing many hints on suppression which, if followed, could greatly reduce the annoyance of TV viewers near to a transmitter.

Television interference can arise from many sources and one of the main problems is tracking down the exact cause. Of course, a well-designed transmitter should include effective circuits for suppressing this unwanted output and transmitter design is included in the book. However, even the best transmitter can have a component failure and the book points out that a careful check on meter readings should be kept and any change in performance noted. R. F. injection into the mains and its suppression is also discussed.

This book has a spiral binding so that the pages lie flat on the bench. The manual may be obtained from RSGB Publications, 35 Doughty Street, London, WC1N 2AE, price 90p including postage.

S.R.L.

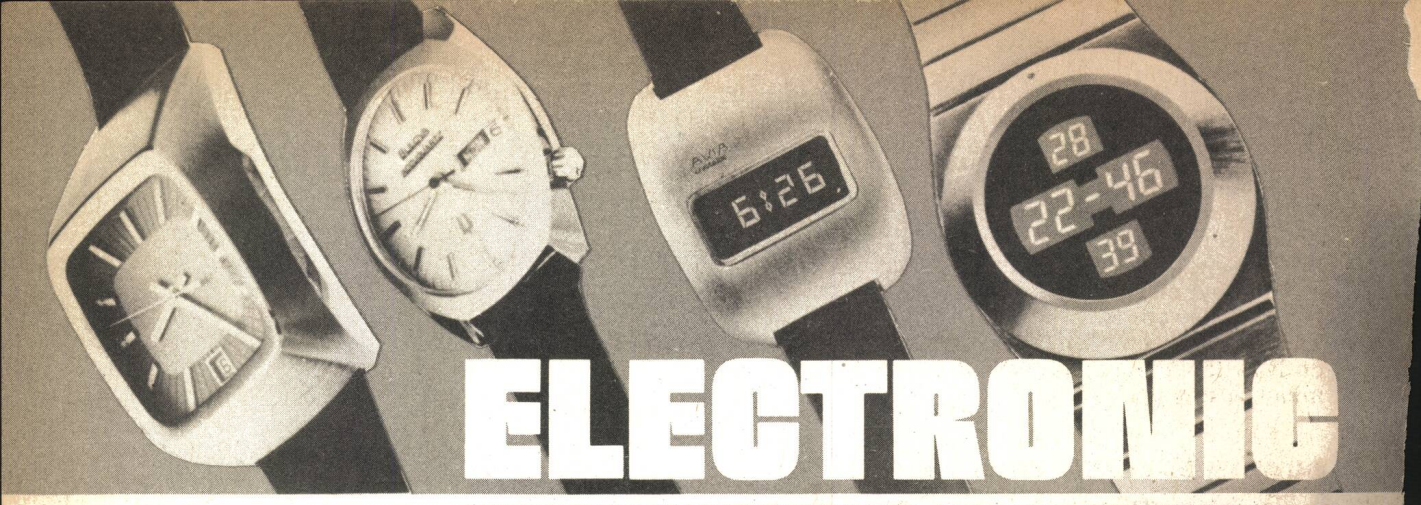

ELECTRONIC TIMEPIECES

By J. B. DANCE, M.Sc.

In this final part, quartz crystal controlled watches and clocks are examined together with various time displays.

QUARTZ TIMEPIECES

Quartz crystal piezo-electric oscillators are now well known for their great frequency stability. Although the piezo-electric effect was discovered by J. and P. Currie in 1880, it was not used for frequency control until 1921 by Cady. Natural quartz can be used, but synthetic quartz often gives a better performance.

CLOCKS

Various clocks using quartz crystal oscillators are available. For example, the General Time Company produce "Quartzmatic" clocks using 262,144Hz crystal oscillators with an integrated circuit to reduce the frequency to 64Hz. The Simplex Company produce quartz controlled master time centres for driving a number of clocks in an establishment with an accuracy of two seconds per month.

The Golay Company produce marine chronometers using a 12kHz oscillator which has a stability of 0·005 second per day at constant temperature or 0·1 second per day over the range 4 to 36°C; this clock employs about 29 transistors.

A quartz clock with a digital display is available from Girard-Perregaux; it is mains driven with stand-by battery power and provides an accuracy of 0·02 second per day. The Junghans 750 quartz movement is powered by a 1·5V battery which lasts a year.

QUARTZ CONTROLLED WATCHES

Quartz crystal controlled wrist-watches have been available since April 1971. Special CMOS (Complementary Metal Oxide Silicon) integrated circuits have been developed which consume a current only during the pulses and which are small enough to be fitted into a normal wrist-watch. In many cases a number of manufacturers have pooled their resources to produce quartz watch movements. The quartz crystals used have to be specially aged so that they provide high accuracy at all times. They are normally sealed in a vacuum enclosure.

The first types of quartz wrist-watches to become available to the public employed the "Beta 21" movement developed by the Centre Electronique Horloger S.A. and marketed in various models under many brand names. The quartz crystal oscillator in this movement operates at 8,192Hz. An integrated circuit divides this frequency by a factor of 32 to produce a 256Hz signal. The current consumption averages about 16μA and the accuracy is about one minute per year.

CYBERNETIC WATCH

The Longines "Ultra-quartz" wrist-watch was first made available on 21st August, 1971. It is especially interesting because it does not contain any integrated circuits, but only a small printed circuit containing miniature electronic components.

The quartz resonator in this watch operates at 9,350Hz and a mechanical vibrator at 170Hz. The signals from the quartz oscillator are used to correct

The Girard-Perregaux quartz watch. The quartz crystal can be seen on the left-hand side, the integrated circuit near the top and the power cell on the bottom right-hand side

the mechanical vibrator 170 times per second. This correction is carried out by a relatively simple circuit employing only 14 transistors, 19 resistors and seven capacitors. The logical deductions made by this circuit are fed to the motor as correction signals. This watch is said to be the first cybernetic watch, since it employs a comparison circuit or "brain".

The vibrator motion is transformed into a rotary motion by means of a pawl system like that of Fig. 6. The toothed wheel rotates once per second. The centre second hand appears to rotate continuously without jumping. The accuracy is about one minute per year.

QUARTZ BALANCE WHEEL WATCH

The "μ-Quartz" or "TS Caliber" watch movement employs an electronically driven balance wheel having four magnets; the exact frequency of this balance wheel (about 4Hz) is controlled by a quartz crystal oscillator. The watch has been developed by B. Golay of Switzerland.

The hair spring fixed to the balance wheel has a special shape which results in the frequency of oscillation being somewhat dependent on the amplitude of movement; the frequency is slightly lower at small amplitudes and vice-versa. This effect is known as the isochronism defect.

The quartz oscillates at 32,768Hz. This frequency is divided down by part of a CMOS integrated circuit containing some 450 components. The strength of the pulse given to the balance wheel depends on the *phase* of its motion relative to the frequency divided signal from the quartz oscillator.

If the balance wheel is running too fast, the pulses to the coil which drives this wheel will be relatively weak, whereas if the wheel is running too slowly, they will be stronger. Thus the frequency of the balance wheel is stabilised at the value determined by the signals derived from the quartz oscillator.

If the isochronism defect amounts to 10 seconds per day for each degree of amplitude variation, the balance wheel frequency need only be adjusted to ± 100 seconds per day if an amplitude variation of $\pm$ 10 degrees is acceptable.

As in other quartz controlled watches, the regulation is effected by means of a trimmer capacitor which adjusts the exact frequency of the quartz oscillator. In this watch the capacitor is adjustable in steps which correspond to a change of 0·25 second per day. The accuracy is about one minute per year.

QUARTZ WATCH WITH STEPPING MOTOR

The Girard-Perregaux "250" quartz watch employs a 32,768Hz quartz oscillator. The pulses from the latter are divided by an integrated circuit to produce 0·5Hz pulses. These operate a miniature stepping motor which causes the centre second hand to jump once per second.

QUARTZ WATCH KITS

The Motorola Company has a section which supplies kits of parts to large watch manufacturers. These kits each comprise a 32,768Hz NT cut quartz crystal, a CMOS integrated circuit and a miniature rotary stepping motor. The additional parts required are a power cell, a trimmer capacitor, a conventional watch dial and hands together with gearing to couple the motor to the hands.

The oscillator frequency chosen is a compromise between the size of the oscillator crystal and the current consumption of the integrated circuit. The use of a higher frequency would enable a smaller quartz crystal to be used, but the increased switching frequency results in a greater power consumption by the divider circuit.

The MC 6061 integrated circuit divides the oscillator frequency by a factor of 65,536 so as to produce 0·5Hz pulses which can drive the motor.

The integrated circuit contains 312 transistors in a six lead ceramic package, but consumes only about 4·5μA from a 1·3V cell or 5μA from a 1·5V cell. Motorola use ion implantation techniques to dope the semiconductor material used in their integrated circuits.

The 6mm diameter motor takes a mean current of about 7·2μA at 1·3V or 8·3μA at 1·5V. The 0·5Hz pulses from the integrated circuit have an amplitude of about 1V and a duration of about 31·25ms, successive pulses being of opposite polarity and separated by one second.

The motor rotates by 180 degrees at intervals of one second, all movements being in the same direction. It has a resistance of about 5 kilohms and contains about 50 metres of wire of a diameter about one-tenth of that of a human hair.

The Golay μ-Quartz movement partially dismantled. The magnets can be seen fixed to the balance wheel in the lower part of the photograph, whilst the driving coil is seen above after it has been swung out from the movement. The quartz crystal, which has been removed, is fitted above this coil

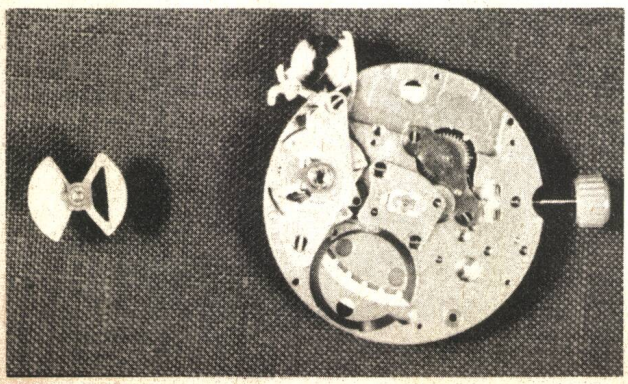

The three parts of the Motorola kit depicted inside an empty watch case. The quartz crystal is shown at the top, the integrated circuit on the left and the stepping motor on the lower right-hand side

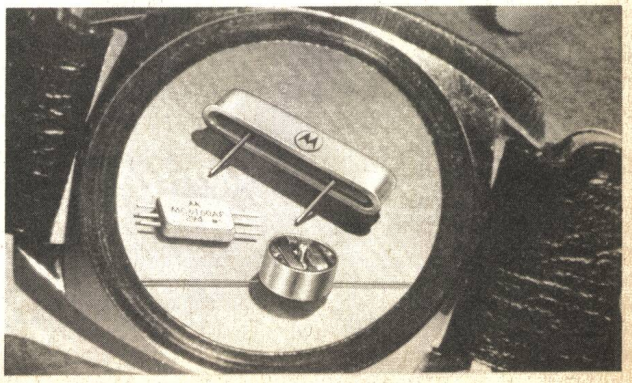

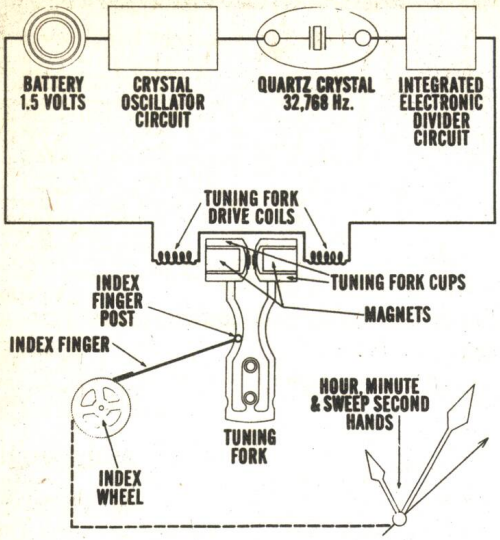

Fig. 8. The operation of the Bulova Accuquartz is depicted here

QUARTZ TUNING FORK WATCHES

The new Bulova "Accuquartz" watch is especially interesting because it contains a quartz oscillator which controls a tuning fork movement. This watch was introduced in the U.S.A. in December 1971 and became available in Europe towards the end of 1972 at prices from £115. It is much thinner than many other quartz models (including an earlier "Accuquartz" model which used the "Beta 21" movement). The new "Accuquartz" range for men and women display the day of the week and the date in addition to the time.

The "Accuquartz" crystal oscillates at 32,768Hz. This frequency is divided by an "Intersil" CMOS integrated circuit containing 126 transistors, etc. The tuning fork oscillates at 341⅓Hz, this being one-third of the frequency 1,024Hz. See Fig. 8.

The Bulova Accuquartz is shown in the foreground together with a much thicker Accuquartz model using the CHE movement

In this watch the tuning fork mechanism advances the gearing 341⅓ times per second by the same type of mechanism as used in the Bulova "Accutron" range. Thus the centre second hand appears to move continuously instead of jumping once per second as in some types of watch.

The "Accuquartz" has an accuracy of about 1 to 2 seconds per week.

THE ASTROQUARTZ

The Junghans "Astroquartz" watch is said to be the smallest quartz watch being manufactured. It employs a 32,768Hz quartz oscillator, but the quartz crystal used is unusual in that it is in the shape of a tuning fork, the prongs of which vibrate like an ordinary tuning fork but at a much higher frequency.

As illustrated in Fig. 9, an integrated circuit acts as oscillator and frequency divider. The 15 cascaded binary stages divide the pulse rate by 2^{15} to produce one output pulse per second. The size of the integrated circuit is only 1·6 × 2·1mm.

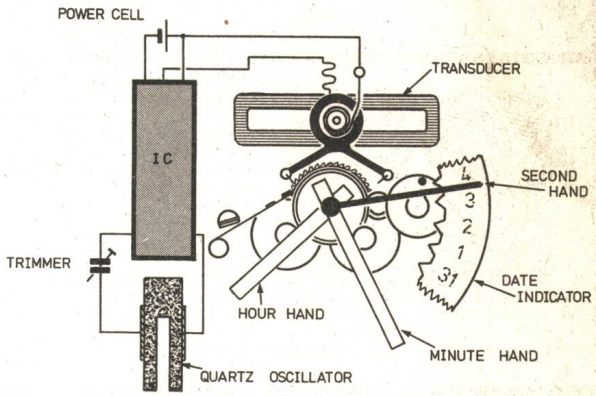

Fig. 9. The above illustration depicts the operation of the Junghans "Astroquartz" watch

The output pulses from this circuit drive an electro-magnetic transducer. The pulses are applied to the coil which turns in a strong magnetic field. The escapement fitted to the axis of this coil engages and turns a wheel with 60 teeth to which a centre second hand is fitted.

THE MEGAQUARTZ

The "Megaquartz" watch is probably the most accurate wrist-watch yet designed, although it is being produced only in small quantities. It has been designed by the Batelle Institute in collaboration with the Omega Watch Company. The accuracy is about 1 second per month.

The main feature of this watch is the use of a circular AT cut quartz crystal oscillating in a shearing mode at 2,359,296Hz—far higher than in any other design. An integrated circuit frequency divider is used.

Omega also offer a quartz watch which has an 8,192Hz oscillator. This frequency is divided by a factor of 32 to produce 256Hz pulses which drive an electro-magnetic motor. The accuracy is about 1 minute per year.

gspk (sales)

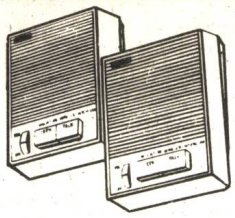

D1075 Wireless Intercom

The great merit of wireless intercoms is that separate connecting wires are not necessary providing the stations are on the same electrical mains circuit. Communication can be up to a distance of ¾ of a mile providing the power lines used are on the same side of the distribution transformer, and several stations can even be operated on the same circuit. Solid state model D1075 is fully transistorised and each unit incorporates a talk–listen button with locking bar; ON/OFF volume control and a pilot light. The fawn moulded cabinets can be desk located or wall mounted and are supplied already fitted with 1·25 metres of heavy duty lead. Operating Frequency: 160kHz. Speaker/Microphone: Dynamic 55mm. Power Output: 120mW. Size: 98 × 40 × 130mm. Printed Circuit: 3 transistors, 1 diode.

£11·60

SOLID STATE TACHOMETER

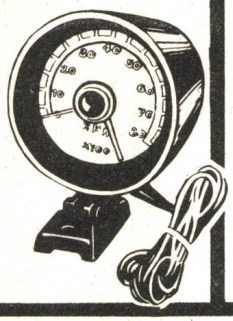

Functionally styled for under or over dashboard installation, this electronic tachometer fits all 4-cycle, 4-cylinder, or 2-cycle, 2-cylinder 12V vehicles. Negative or positive earth. Calibrated white on black 0–8,000 r.p.m. in 100 r.p.m. divisions together with setable "danger" line, simple installation—2 screws, 4 wires. 80mm (3in) dia. dial, 50mm deep. On adjustable angle bracket. Sealed black crackle finish.

£6·86

SPECIAL OFFER !

AUTO BURGLAR ALARM PLUS "POP-OUT" CIGARETTE LIGHTER

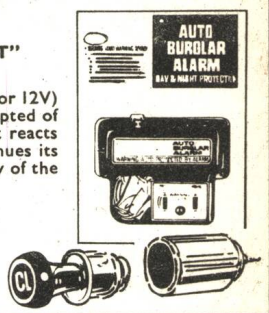

Designed for easy installation on any car (whether 6 or 12V) this device activates the horn when a theft is attempted of equipment or personal belongings. This neat unit reacts when the vehicle is disturbed or rocked and continues its warning for 15 sec. after tampering. The sensitivity of the device is adjustable and controlled by a separate ON/OFF panel which can be located wherever convenient. Supplied with connecting wires and screws in attractive bubble pack, containing installation instructions and diagrams. 150 × 65 × 20mm plus panel 65 × 45 × 20mm.

£2·10 FOR BOTH

FANTAVOX STEREO LOUDSPEAKER SYSTEM

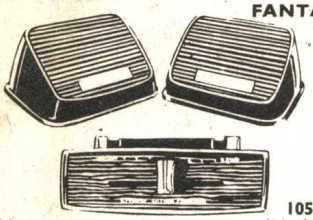

These high quality speaker enclosures are made of tough black moulded plastic and have been designed for fitting on to almost any vehicle surface. The smart louvred fronts are silver trimmed and house heavy duty 5in (125mm) ceramic loudspeakers rated at 3/5 watts. 8 ohms impedance. Already wired with generous length connecting leads and supplied in packs of speaker pairs complete with fixing screws. Each cabinet measures 190 × 105 × 165mm. Weight: 0·55 kg.

1052 FADER CONTROL

Neat, custom-made appearance slide fader control for balance of front and rear speaker volume. Simulated wood finish panel which can be quickly fitted below car dash. Supplied with generous connecting cable and fitting screws. Will suit 4, 8, 16 ohm installations. 100 × 38 × 30mm (including knob but excluding fitting bracket).

All for £4·70

420ES MICROSCOPE

An extremely modestly priced yet efficient microscope capable of magnification up to 750 times with clear sharp images. This model is of the self-illuminating type and incorporates an easily rotable four-position turret magnifying lens with rack and pinion focusing. The crackle black metal body houses the batteries for adjustable illumination. Packed in carton with built-in carrying handle and full notes for user. A sample slide also provided. 105mm at base; 180mm high. Weight: 0·40 kg.

£4·95

G5555 PROFESSIONAL STEREO HEADPHONE

Lightweight materials are skilfully used in the construction of this model in black crackle moulding and kid-soft leathercloth with contrasting bright metal. Each ear pad houses a highly efficient 60mm reproducer unit and features ear muffs removable for cleaning. 10-self-coiled lead plug fitted.
Frequency Response: 20–20,000Hz. Impedance: 4–16 ohms. Sensitivity: 110dB. Power: 0·5W. Weight: 0·39kg.

£9·25

"SPRITE" LIGHTWEIGHT STEREO HEADPHONE

An outstanding achievement following lengthy development by one of the world's leading audio manufacturers, the T.T.C. "Sprite" offers the following specification:
Extreme lightness (only 150 grammes) (5oz);
Instant wearing adjustment with sliding ear-pieces and flexible headband;
Highly efficient Mylar reproducer units;
Removable, washable foam padded ear muffs;
3-metre lightweight lead with stereo plug fitted.
Frequency Response: 30–13,000Hz.
Sensitivity: 105dB. *Power:* 0·2W.
Impedance: 4–16 ohms. *Weight:* 0·15kg.

£2·25

D1019 "Doorphone" with Metal Unit

Three transistor solid state two-way intercom system with specially engineered weatherproof slave unit in heavy gauge metal. Sensible design features include rain protective speaker louvres, simple push-pull button, internal socket connecting lead and removable back plate for wall and door panel mounting. Master unit in high impact white moulding has complementary silver "pinhole" grille and silver/black panels with ON/OFF volume control and push-to-talk switch. 60mm dynamic speaker/microphones are used for both units. 120mW output. 9V internal battery operation. Master unit: 77 × 40 × 105mm. Slave unit: 70 × 32 × 90mm. Supplied with battery, lead and staples.

£3·90

DF100 MICROPHONE

Bijou sized model in matt silver finish with machined capping to insert housing and supplied with unique pocket/lapel clip which also doubles as a desk support. Supplied with lavalier cord, 2 metre lead fitted 3·5mm moulded plug and packed in the latest style click-fast case manufactured from smart durable padded plastic.

Impedance: 200 ohms. Sensitivity: 82dB. Frequency: 100–9,000Hz. Size: 13mm dia. × 92mm.

£3·50

TI-C1000 MINI-METER

£2·70

This is the most compact and reliable multimeter on the market and features easy switch selection, 1,000 ohm/volt 2-jewel meter movement with zero and needle adjustment. Easy to read scale in two colours. Ranges: A.C. Voltage: 0–10V, 50V, 250V, 1,000V. D.C. Voltage: 0–10V, 50V, 250V, 1,000V. D.C. Current: 0–1–100mA. Resistance: 0–150K ohms.

Please fill in the coupon and send with 10p (refundable on ordering) for catalogue. *ALL CALLERS WELCOME*

To G.S.P.K. (Sales) Limited, Dept. P.E.,
Head Office, Hookstone Park, Harrogate, Yorkshire HG2 7BU.
Mon. to Fri. 9 a.m.–5 p.m.

Name.....

Address.....

P.E.

constructing a digital multimeter

– exclusive Wireless World design in the April & May issues

See full construction details of the versatile multiple measurement meter which was first described in our March issue. Intended for both amateur and professional use, the design – based on integrated circuits – is arranged so that you can build either the whole instrument or just the particular measurement facilities you require. Measurements are shown in a "window" on a four digit numerical display.

Survey of the Compatibility of Audio Magnetic Tapes.

With the wide variety of tapes available, it is desirable to establish the compatibility of one type or brand against any other for a particular recording machine. Detailed tests have been made and the results interpreted to produce a table of interchangeable and compatible products.

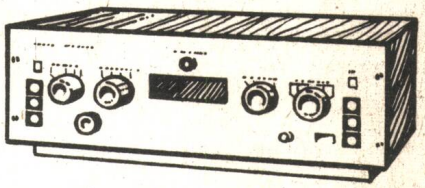

The Wireless World digital multimeter will measure : voltage (199.9 millivolts to 199.9 volts, d.c. and a.c.) resistance (1.999k Ω to 1.999M Ω), capacitance (1999pF to 1.999μF), frequency (0 to 5MHz) and time intervals (20 microseconds minimum).

Wireless World

APRIL ISSUE On sale now 20p

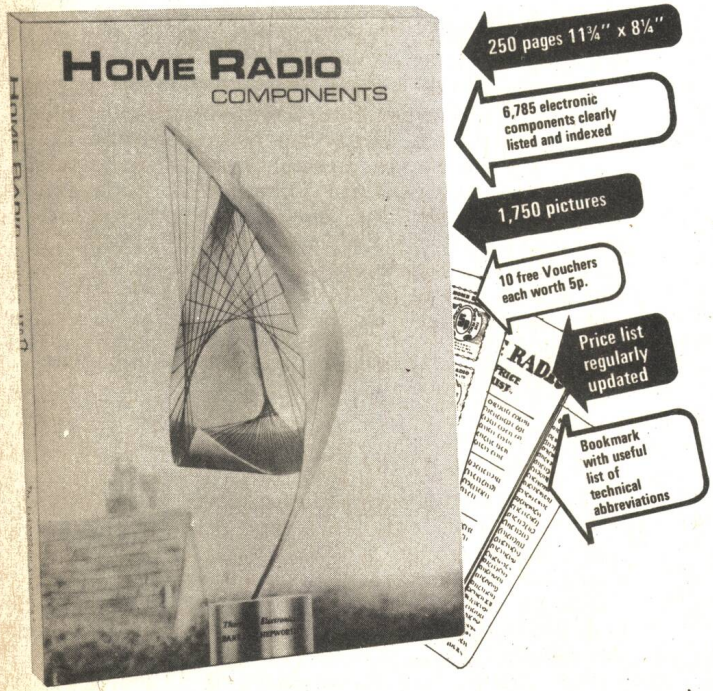
HOME RADIO
COMPONENTS
250 pages 11¾" x 8¼"
6,785 electronic components clearly listed and indexed
1,750 pictures
10 free Vouchers each worth 5p.
Price list regularly updated
Bookmark with useful list of technical abbreviations

The Catalogue you MUST have!

Details of our popular Credit Account Service and our Easy Ordering System are included in the catalogue.

Only 55p.
plus 20p POST AND PACKING

POST THIS COUPON
with cheque or P.O. for 75p.

Name _____

Address _____

_____

HOME RADIO (Components) LTD. Regd. No. 912966 London
Dept. PE, 234-240 London Road, Mitcham CR4 3HD

The price of 75p applies only to catalogues purchased by customers in the UK and to BFPO addresses.

(Right): the Avia watch which employs a liquid crystal display. This is expected to be available in the U.K. at about £135 soon

(Left): the Swissonic 2000 watch. This displays the date, the hours, minutes and seconds continuously by means of a liquid crystal system

DIGITAL WATCHES

Digital watches which employ no moving parts have just begun to appear on the market. They employ quartz oscillators and provide an accuracy of about one minute per year.

Two forms of display have been employed, namely electroluminescent diodes which provide a red display and liquid crystal displays.

ELECTROLUMINESCENT WATCHES

Watches employing gallium arsenide-phosphide electroluminescent diodes provide a display which shows the time in red digits. Unfortunately the display diodes require so much current that it is not possible for the time to be continuously displayed if the power cells are to have a reasonable life. A button on the watch must therefore be pressed each time the user wishes to read the time. The cell life is dependent on the number of times the time is displayed. The display may have to be shaded with the hand if the ambient light level is high.

The "Pulsar" watch manufactured by the Hamilton Company employs light emitting diodes. The brightness of the display is automatically adjusted to suit ambient lighting levels, although it requires shading from direct sunlight when the display is being read.

Each time the button is pressed, the hours and minutes are displayed for 1·25 seconds, but if the button is held down, the seconds are displayed for as long as it is depressed.

The watch employs a 32,768Hz oscillator and a CMOS integrated circuit containing over 1,200 transistors. It is powered by two silver oxide cells which have a life of over one year under normal use (about 25 time readouts per day).

A slight variation of this watch is offered by the Omega Company as their "Time Computer".

LIQUID CRYSTAL DISPLAYS

The other form of digital display used in watches employs liquid crystals. This type of display requires very little power, since it does not emit light. The liquid crystals simply reflect a different proportion of the incident light in regions where an electric field is applied to them. Thus the display cannot be viewed in the dark. A moderately high ambient light intensity is desirable.

The thickness of the liquid crystal material may be about 0·5mm. The special nematic material is placed between two electrodes like a capacitor, but the electrode nearest the face of the watch must be transparent.

In the absence of any field, the liquid is perfectly clear and transparent, any incident light falling on it being absorbed by a black background. When an electric field is applied by suitably shaped electrodes in certain regions (which are in the shape of the digit to be displayed), the liquid becomes opalescent as the crystals come into mutual alignment. They reflect the incident light back from these regions to the observer.

Although watches using liquid crystal displays have the advantage over those using luminescent diode displays in that the digits can be made visible at all times, the life of the present liquid crystal systems seems somewhat doubtful. Even when an alternating voltage is applied, some degradation of the material may occur so that the display gradually becomes less clear. The life should be considerably over one year, but it is too early to estimate it accurately. At least one manufacturer feels that liquid crystals may have an indefinite life if contamination is avoided. The price of replacement units should fall rapidly during the next few years.

THE AVIA WATCH

One watch with a liquid crystal display is marketed by Avia-S.G.T., the liquid crystal system for this watch being produced by the Optel Corporation of the U.S.A. The hours and minutes are continuously displayed, but the seconds are shown by means of two flashing points appearing between the hours and the minutes digits.

The quartz oscillator operates at 32,768Hz. This frequency is divided by a factor of 512 and the 64Hz output operates counters. The latter control the decoders which feed the display.

The 1·5V power cell has a life of 14 months. A circuit is employed to convert the 1·5V from the cell to the 15V required for the decoder-display operation.

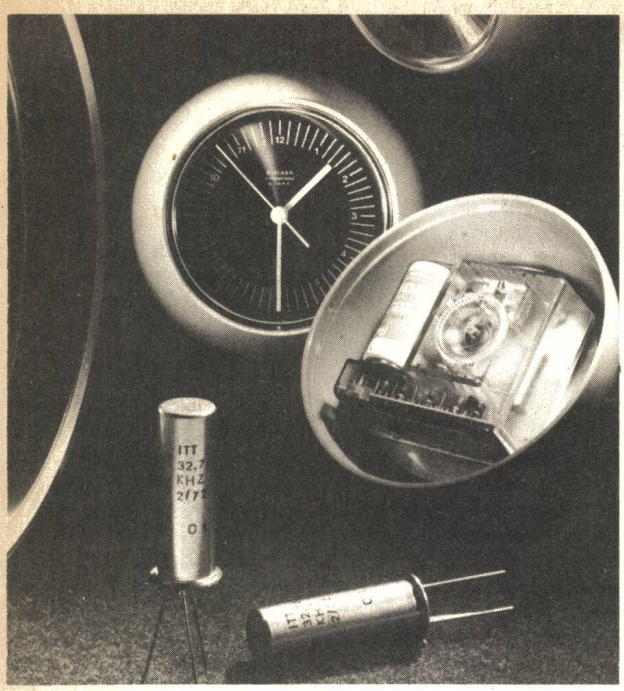

The Staiger 2000 quartz crystal controlled clocks. The ITT crystals used are shown at the front

A DETAILED DISPLAY

Another liquid crystal watch has been developed by Texas Instruments, Ebauches S.A. and Longines. The eight character display provides a continuous readout of the day of the month, hours, minutes and seconds. The accuracy is about 1 minute per year. The watch contains two integrated circuits containing about 700 transistors and is powered by two 1·35V mercury cells.

The hour display can be set by an internal switch to provide either a 12 hour or a 24 hour cycle. The indicated time is set by four micro-switches on the back of the watch which alter the seconds, minutes, hours and date respectively.

Another watch with a liquid crystal display has been produced by the Seiko Company; it displays hours, minutes and seconds.

A Geneva lever movement (about 100 years old) from the Science Museum being compared with an ITT quartz crystal designed for use in a watch

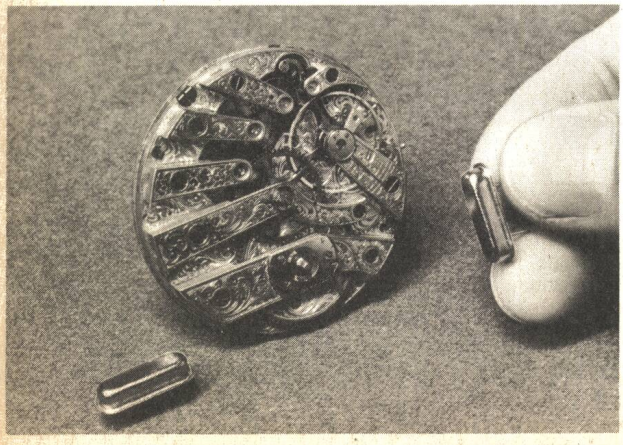

CLOCKS USING LIQUID CRYSTALS

A limited number of clocks with liquid crystal digital displays are available, for example, from the Seiko Company. An impressive digital alarm clock (type S1736) has been constructed on a single chip by American Microsystems; it is interfaced with their liquid crystal readout.

ATOMIC CLOCK

In a totally different sphere it may be mentioned that the standard of time is now based on the frequency of radiation emitted between two hyperfine levels of the caesium-133 atom. The second amounts to 9,192,631,770 cycles of this radiation. This definition provides a more accurate measure of this unit than the motion of the earth.

Ebauches S.A. have made precision time centres using caesium atomic clocks which have an error of less than one microsecond per day (corresponding to one second in about three thousand years!).

POWER CELLS

The cells used to drive electronic watches pose many manufacturing problems. Three of the main manufacturers are Union Carbide, Leclanche and, in England, Mallory.

A new area has recently been opened by Mallory at Crawley for the manufacture of special mercury button cells used in watches. Such cells must give satisfactory service for at least one year after a variable period of storage before sale.

Extreme care must be taken to prevent contamination of the materials used in cell manufacture. All air is filtered before it enters the watch cell manufacturing area at Crawley to prevent dust from being sealed in the power cells. Great care must be taken to prevent the possibility of internal leakage of current.

The electrolyte used in watch cells is chosen for the lowest practical seepage rate, since if it escaped from a cell it would probably damage the delicate watch mechanism.

In conclusion it may be mentioned that the tweezers used to fit new cells into watches should be made of a plastic material, since metal tweezers can easily short the cell. Care should be taken to fit new cells in the correct way so that they provide the circuits with a voltage of the correct polarity.

CONCLUSION

We are in the midst of a revolution in watch design. Although no manufacturer has really broken through the price barrier with a moderately priced quartz controlled watch, it may not be too long before one company does so and the "quartz war" will have begun. The developments in the last few years have been very rapid and it is expected that many of the estimated 300 million watches per annum required by 1980 will be electronic ones.

The traditional place of watch making, Switzerland, has played a large part in the development of electronic watches, but the U.S.A. has initiated much of the work.

The normal skills of the watchmaker will be required to attend to watches employing moving parts, but if digital watches become common, the watch repairer may have to have a very elementary knowledge of electronic engineering with micro-miniature equipment. ★

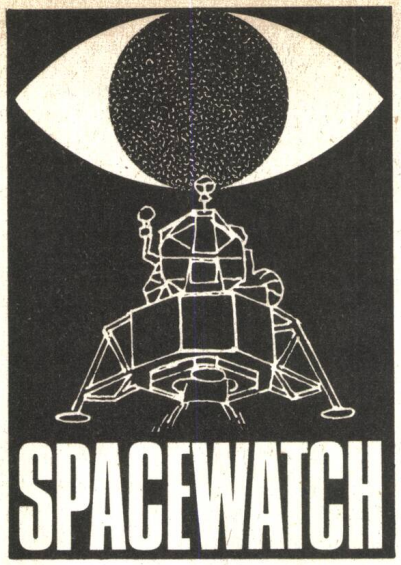

SPACEWATCH

BY FRANK W. HYDE

SPACE BUDGET

The United States space agency will have more money to spend this year, 74 million dollars in fact. A total of 3,136 million dollars is set aside for space matters. This amount will cover a number of NASA projects, for example two new projects as well as the programme for space stations and shuttles.

The two new projects are a new kind of satellite for geodesy known as a Terrestrial Reference Satellite, and an advanced version of the *Nimbus* weather satellite to monitor pollution.

The reference satellite, due for launch in 1976, will use laser beams for the measurement of distances between locations on different continents. The accuracy that can be achieved is of the order of a few inches so that small changes of movement of land masses will be detected.

The new *Nimbus* satellites will monitor both air and ocean pollution. The programme is for the launch of two satellites, one in 1974 and the other in 1976.

The current major projects will continue to be developed, but there will be a phasing out of communications satellite interests. This is because the space agency consider that the viability of these programmes has been proved and the time is now ripe for commercial responsibility for this activity.

The Science Foundation will increase their programme of investigations and some major projects involve visual and radio astronomy. Some 10 million dollars will go to the rail mounted mobile arrays of aerials in New Mexico for the large scale study of distant sources and the detection of signals from any civilisation that may exist in other parts of the Universe.

The visual telescope under construction at the Cerro Tololo inter-American Observatory in Chile, will be given 2·6 million dollars for the completion of the work on what will be the largest optical telescope in the southern hemisphere. The diameter of the mirror is 158 inches and the site offers spectacular advantages over other places for useful viewing time.

LUNOKHOD 2

The Russian moon vehicle, *Lunokhod 2*, which landed on the Moon in January has a special set of programmes. It was landed some 175km from the landing site of *Apollo 17*. The data obtained from the two sources should be complementary.

Landed in the Sea of Serenity, the *Lunokhod 2* task is to examine the boundary area where older rocks may be found. At the boundary area of the highland regions, from which anorthites rise up, the floor of the mare is covered with basalt type lava.

Other experiments will measure and observe the Zodiacal light near the Sun, observe the Milky Way and the centre of the Galaxy with a space photometer. It is hoped also to decide whether there are traces of cosmic dust in the Lunar atmosphere. The possibilities of studying the Universe by optical means from stations on the moon is another experiment which the Soviet team are known to be considering.

The vehicle is also carrying a French laser reflector for measuring the Earth–Moon distance.

The *Lunokhod*, which is of a similar design to the previous vehicle, carries on its outside an orientation device, a lunar surface photometer, soil analysis experiment, a fixed television camera, a steerable television camera, the space photometer, a solar battery, a magnetometer, a photo receiver and aerials which include a corner reflector and a high gain system.

MOON GRAVITY

Analysis of the gravitational variations of the moon recorded by the command module of *Apollo 15* has yielded data about mascons, and the lunar orbiter added to this data when being precisely tracked.

This problem, to which selenologists have devoted considerable time and study, can now be set up as a model. The model now suggested agrees well with the idea that the mascon of Mare Serenetatis is a thin body with well defined boundaries. The previous speculations on this theme have been borne out for Mare Nectaris also.

So far as Serenetatis is concerned the model fits the surface features extremely well. At the moment the data gives support to the volcanic hypothesis.

ORBITING WORKSHOP

As the launch date for the *Skylab*, the first orbiting space station, draws near it may be useful to describe the project and the sequence of events which will be the step in space that many have waited for almost impatiently.

The first crew will be an all Navy one and Charles Conrad, veteran of *Apollo 12*, is the only member of the team who has had astronaut experience. The other two men are J. P. Kerwen, a doctor, and P. J. Weitz, an aeronautical engineer.

Skylab will go into a 270-mile orbit. The sequence is to be the launch of the skylab unit unmanned into the prescribed orbit, the next day, May Day, the launch of the command module with the crew to the calculated rendezvous. When linked up the total length of the units will be 118ft. The diameter will be 22ft at the workshop section.

The arrangement of the airlock and docking sections allow normal joining of the command vehicle to the end of the whole unit. There is also a second docking point on the side of the docking module which could be used for a second command module to attach itself or for rescue purposes.

When the space station is launched the telescope covers the docking section. On attaining its correct location in orbit the telescope will swing to the side and the solar power paddles will open. The ports for docking will then be uncovered.

LIFE SUPPORT SYSTEMS

The station main body is 48ft by 22ft and there is an intermediate section next in the sequence which is 17ft long and is an airlock section. Here all the power control and distribution systems are located.

The air conditioning system, the life support system together with communications control and data management are also arranged there. There is room for two fully suited astronauts with personal life support systems in the section. From here the crew can pass to the docking module to work outside the vehicle or to pass to and from the command module.

The whole assembly with the launcher, a *Saturn 5* rocket, will stand 334 feet high at take off. The combined weight at the time will be 3,110 tons.

Hi-Fi Tape Link

By P. S. EWER

LAST month the circuit of the Tape Link was described in detail. In this the final part, the construction of the Tape Link, the fitting of the heads and the setting up procedure will be described.

TWO ASSEMBLIES

The Tape Link is made up of two assemblies (the amplifier and the power supply) in order to keep the mains transformer away from hum sensitive circuits and enabling the power supply to be positioned where it induces the minimum hum in the replay head.

The folding of the metal should present no problems to a handyman equipped with a vice. Cutting the metal to size is not quite so easy and is best done with a guillotine and a fly press for the cut out parts. Constructors may find it convenient to purchase the metal cut to size from a sheet metal shop.

POWER SUPPLY CONSTRUCTION

Dealing first with the power supply, drill the chassis and bend up as indicated in the photograph.

Next, affix the mains transformer using 4BA × ½in screws and nuts. Do not tighten as they will have to be undone again when the power unit is finally mounted in the case. A tag strip carrying the rectifier diodes should now be assembled and bolted to the chassis.

Wiring between this and the mains transformer is best done at this stage as the tag strip will be difficult to get at once the smoothing capacitors are in place. These and the fuseholder can now be put into position and the wiring completed.

The power lead-out wires and the mains lead are secured by a plastic cable clip bolted down to the mains transformer. Having completed the power supply it can now be tested.

With mains applied and no load imposed upon the outputs, the supplies should read 56 volts and 28 volts respectively. Provided that the voltages measured are within a couple of volts either way and that the mains transformer and capacitors do not get hot after a few minutes' operation, all should be well.

AMPLIFIER CHASSIS

Mark out the front panel to suit components (see Fig. 7). Drill all the holes starting first with an ⅛in drill. Next, open out the holes for the record indicator lamp, the switches and potentiometers with the appropriate drill.

The DIN sockets are mounted beneath the panel and the ⅝in hole required to allow entry of the plugs is most neatly cut with a chassis punch, e.g. a "Q-max cutter". The cut outs for the meters are made by drilling all round just inside the edge with a small drill, pushing out the centre and then truing up to the marked line with a file.

A similar technique should be used for the meter switch cut-out. Drill two holes side by side and open up to the required size with a needle file. Finally countersink all the screw holes.

The strap for mounting the meters, and the U-channel complete the metal work. To make the folding easier, the front panel fixing flanges should be bent over first. The sheet can then be bent up to complete the chassis. Once again, the use of a chassis punch is recommended for the larger holes (see Fig. 4).

The front panel can be finished in any way desired. One method which gives a pleasing appearance is to

satin finish it by stroking lengthwise with a wire brush such as is supplied for cleaning suede shoes. This results in a series of parallel scratches. The panel is then cleaned with a rag soaked in methylated spirit to remove loose material and grease.

Letraset may be used to label the panel, finally protecting the finish with two coats of lacquer.

After fixing the front panel to the chassis the B9A valve holders and the stand-off spacers are mounted and the components assembled to the front panel. The slider switch used by the author for the BIAS/VU selector was supplied with its mounting holes tapped at 8BA.

These were drilled out and retapped at 6BA. However if 8BA screws are used, allowance must be made for this in the front panel drilling.

COIL WINDING

Because many readers find it difficult to obtain specified coils, the author wishes to point out that virtually any 14mm coil is suitable for L1 and L101. Most catalogues specify the number of turns per millihenry and because inductance is proportional to the square of the number of turns, twice this number will give the number of turns required for 4mH. Some easily available pot cores and their turns per millihenry are given in Table 1.

Using 34 s.w.g. enamelled copper wire, wind the required number of turns onto the bobbin. On completion the winding should be secured with a layer of adhesive tape (not Sellotape).

Before assembling the two halves of the pot core, slightly rub the mating surfaces with a sheet of paper to remove any dust which could alter the inductance of the completed coil. The lead wires should be brought out separately through adjacent slots at 90 degrees.

Photograph showing construction of the power supply for the Tape Link. The switch and indicator neon are mounted near the mains input. Positioning of the power supply module within the finished tape deck is best found by trial and error being that which gives minimum hum

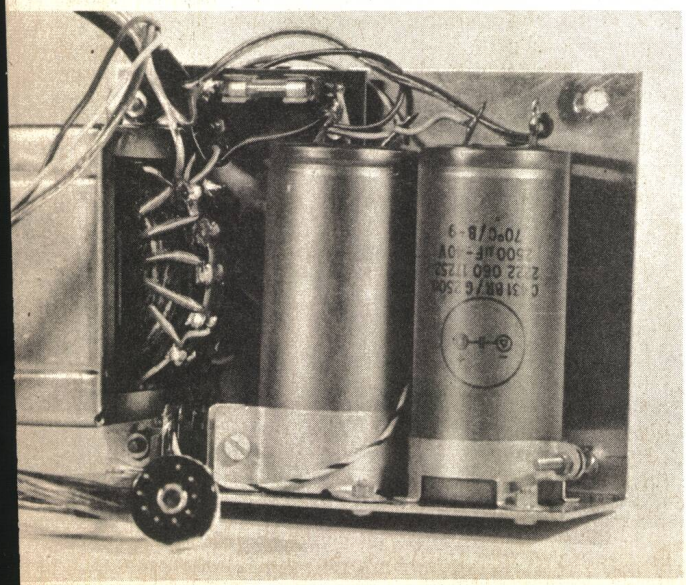

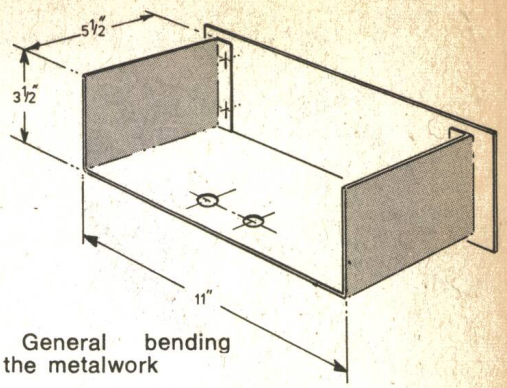

Fig. 4. General bending details of the metalwork

Table 1: ALTERNATIVE POT CORES FOR L1 AND L101

Type	Turns/mH	Turns required for 4mH
LA 2503	52	104
T26/2100R	47·5	95
FX 1636	34·8	70
FX 1011	24·3	49
FX 2236	32	64

Table 2: ALTERNATIVE POT CORES FOR BIAS AND ERASE OSCILLATOR T2

Type	Turns/mH	Turns required Primary	Secondary
LA 2301	53·8	5 + 5	80
LA 2105	54·7	6 + 6	96
LA 2517	42	5 + 5	80
N22/250A	40	5 + 5	80

Fig. 5. Method of winding the primary of the bias and erase oscillator coil

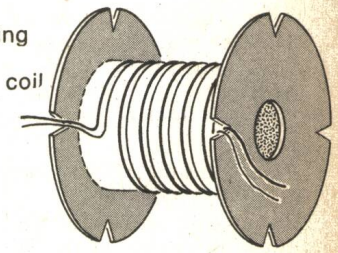

BIAS AND ERASE OSCILLATOR TRANSFORMER

Again the pot core used for this transformer is by no means critical. A 25mm type was used in the prototype but any high frequency 18mm type will do just as well provided the inductance is that specified (see Table 2 above).

Measure off two 20in lengths of 21 s.w.g. wire and twist them lightly together. Allowing a few inches for leadout wires, begin winding the required number of primary turns making sure that the first turn of one half of the primary lies adjacent to the first of the other half and so on (see Fig. 5). After the required turns have been wound the windings should be secured with adhesive tape.

The secondary should then be wound using 30 s.w.g. wire starting in the same place and winding in the same direction. Cover this layer with one layer of tape. Then assemble the pot core with the same precautions as for the previous coil.

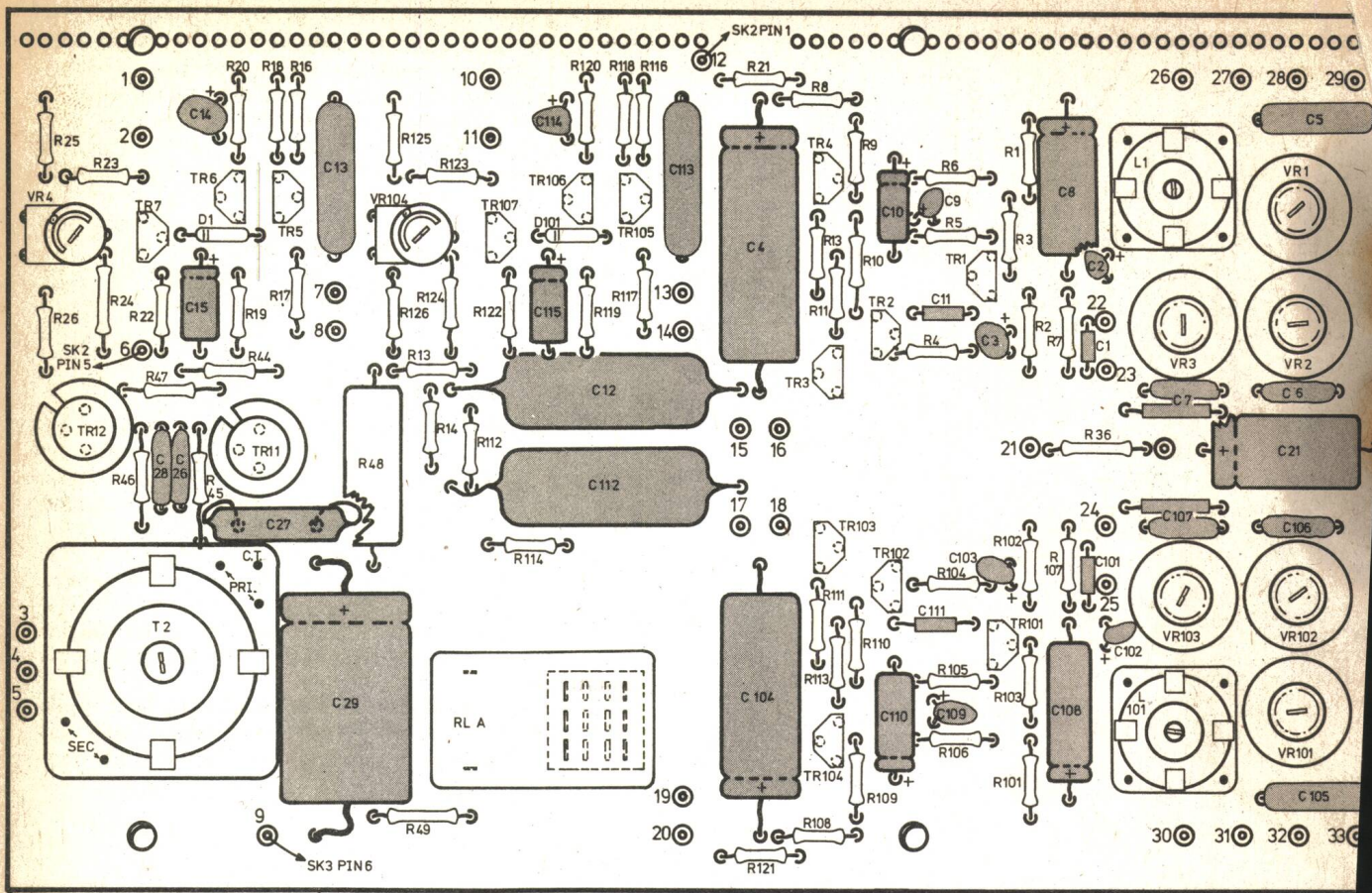
SK2 PIN 1
SK3 PIN 6
SK2 PIN 5
T2
PRI.
SEC.
RL A
TR12
TR11
VR4
VR104
VR1
VR2
VR3
VR101
VR102
VR103
L1
L101
C4
C12
C112
C104
C29
C5
C6
C7
C21
C105
C106
C107
C108
C109
C110
C111
C113
C114
C115
R49
R108
R121
R36

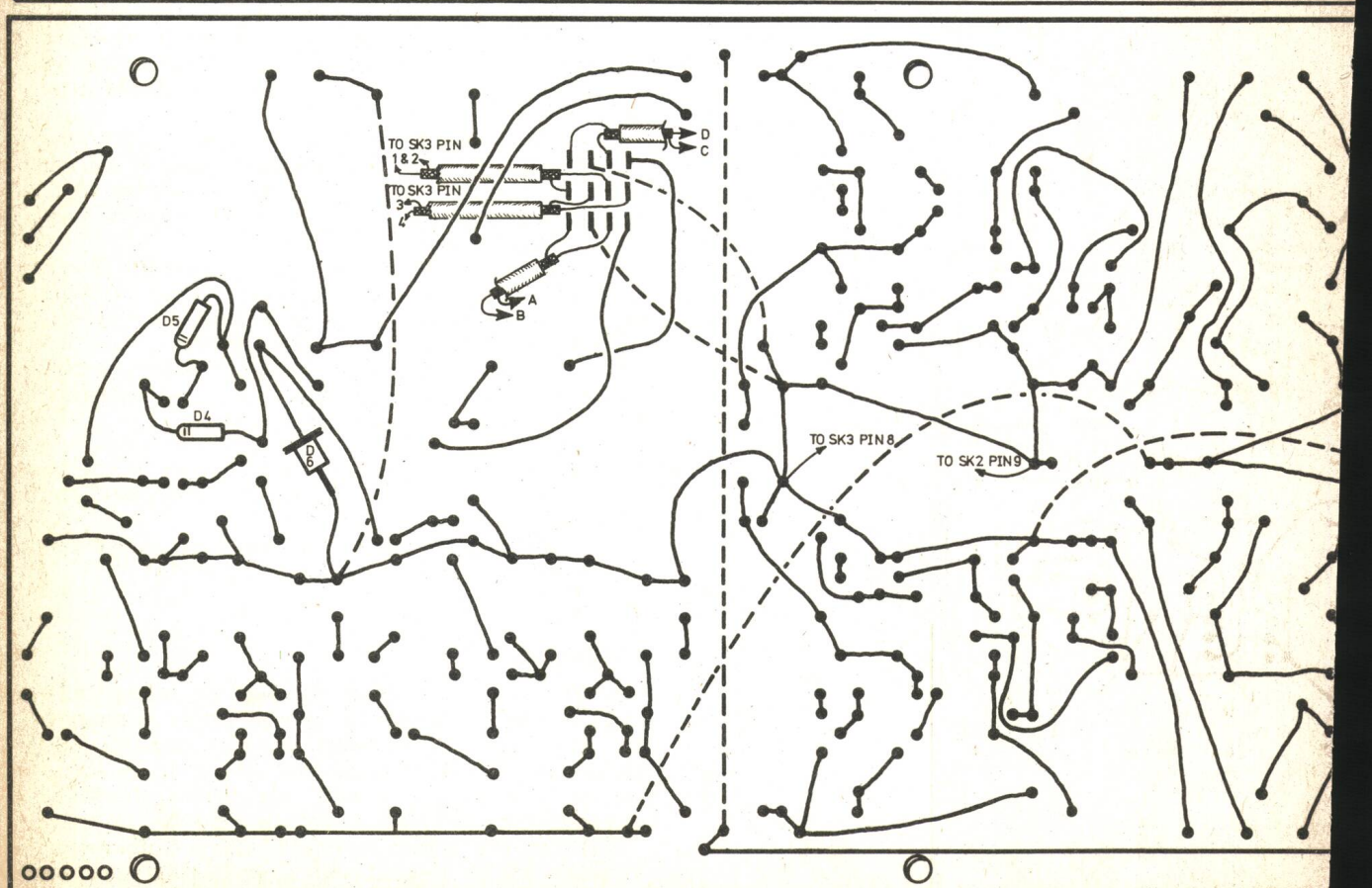
TO SK3 PIN 1&2
TO SK3 PIN 3
TO SK3 PIN 8
TO SK2 PIN 9
D5
D4
D6
A
B
C
D

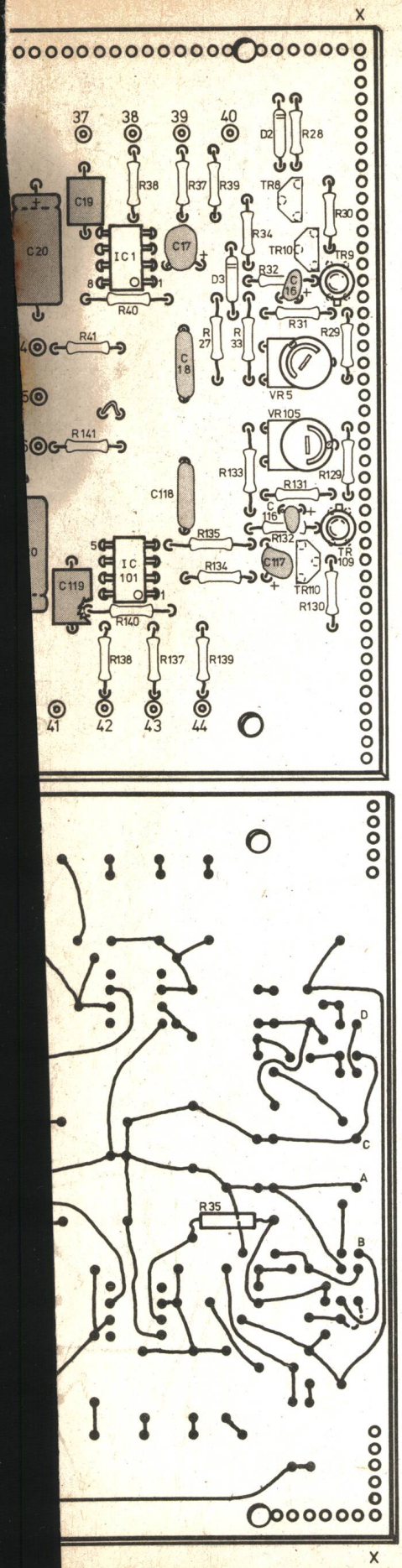

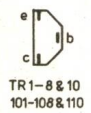

TR1–8 & 10
101–108 & 110

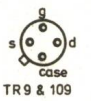

TR9 & 109

TR11 & 12

Fig. 6. Layout of the components on the perforated board. Note that there are some components under the board. C27 should be mounted away from board to avoid heat

The primary windings must now be identified with some form of continuity tester such as a bulb and battery. After scraping the enamel from the four primary wires select one wire and call this the start.

Next find the other end of this wire with the continuity tester. If the method of winding shown is followed then the starts of both primary halves will be at the top of the coil and the other ends at the bottom. The end of the identified wire should then be soldered to the start of the remaining wire, this becoming the centre tap. The remaining wire then becomes the other end of the total primary.

CIRCUIT BOARD

The amplifier is constructed on perforated board which accommodates all the components with the exception of the relay for which a cut-out must be made (Fig. 6). The holes will also have to be opened out for some of the pots and for the fixing screws.

The wiring should proceed logically from one end of the board to the other inserting Veropins where the flying leads are to be soldered to the board. The oscillator tuning capacitor is mounted up in the air on Veropins to keep it away from the hot components near it.

TR11 and TR12 are fitted with clip-on heat sinks (TO5 can). There are four components mounted underneath the board which must not be forgotten.

CONSTRUCTION

Upon completion thoroughly check the board wiring. The connections from the underside of the board to the B9A sockets are then wired, allowing sufficient slack to enable the board to be tilted up through 90 degrees to facilitate servicing should it be required.

The board is next screwed into position and the wiring completed. To facilitate identification, the use of an assortment of colours for the connecting wires is suggested, and screened leads of low capacity *must* be used where indicated (see Fig. 7).

For ease of assembly it is suggested that the switch wafers nearest to the metalwork are wired first. Note the screen between the wafers and the spacers required to give good isolation between the two sections. In the prototype three-pole three-way wafers were used for S1 but the easier to obtain four-pole three-way wafers are perfectly suitable.

Prevention of earth loops is essential with this equipment and the constructor should note that there is only one connection between the chassis and amplifier earth.

At this stage the wiring on the front panel and the chassis should be completed as in Fig. 7.

TESTING

After having thoroughly checked the wiring (mistakes can be expensive) the power supply is plugged into the appropriate socket on the amplifier and mains applied. Providing that there is now no obvious indication of a fault, e.g. smoke, it can be assumed that there are no serious errors.

Measure the supply voltages with a multimeter. These should be 55 volts and 27 to 28 volts approximately. It is then prudent to go around the circuit

Table 3: APPROXIMATE VOLTAGE SETTINGS

Junction of R1 and R2		17·3
TR1	emitter	18·0
	collector	0·7
Junction of R1 and R21		54·0
TR2	collector	25·3
	base	0·7
Junction of R11 and R13		27·0
TR4	base	28·7
	emitter	28·0
TR3	base	25·3
	emitter	26·0
TR5	base	7·7
	emitter	7·0
	collector	18·3
TR6	base	18·3
	emitter	19·0
	collector	7·0
TR7	emitter	6·0
	collector	26·0
VR4 wiper (dependent on setting)		6·0
Junction of R25 and VR4		8·0
Junction of R26 and VR4		4·0
TR8	base	28·0
	emitter	28·7
	collector	20·0
TR10	base	19·4
	collector (dependent on VR4)	12·0
Terminal 6 IC1 (dependent on VR5)		12·0

checking voltages in accordance with Table 3. These are the design figures obtained by calculation and, generally speaking, provided that correlation within plus or minus 20 per cent is obtained all should be well.

When these checks have been made rotate VR4 and VR104 fully clockwise. The meters should now show a reading.

Disconnect the mains and temporarily short pins 5 and 6 of SK3 together. Set the meter switch to BIAS and the function switch to STEREO. Then reconnect the mains. The record indicator light should come on and the meter show an indication which is adjustable by means of the bias control. Failure of the meter to read suggests an oscillator fault and the power should be switched off immediately to prevent damage. Remove the temporary link.

TAPE TRANSPORT

With the old heads and/or electronics stripped out, the new heads have to be fitted to the base plates. Two methods of accomplishing this for the record/replay head are depicted in Fig. 8. It is essential that the tracks interleave correctly and the baseplate may need to be packed up or filed down accordingly.

When correctly positioned, the upper edge of the top track lies just below the edge of the tape (about 0·15mm). With regard to the Collaro deck the slot in the baseplate had to be widened with a file and the

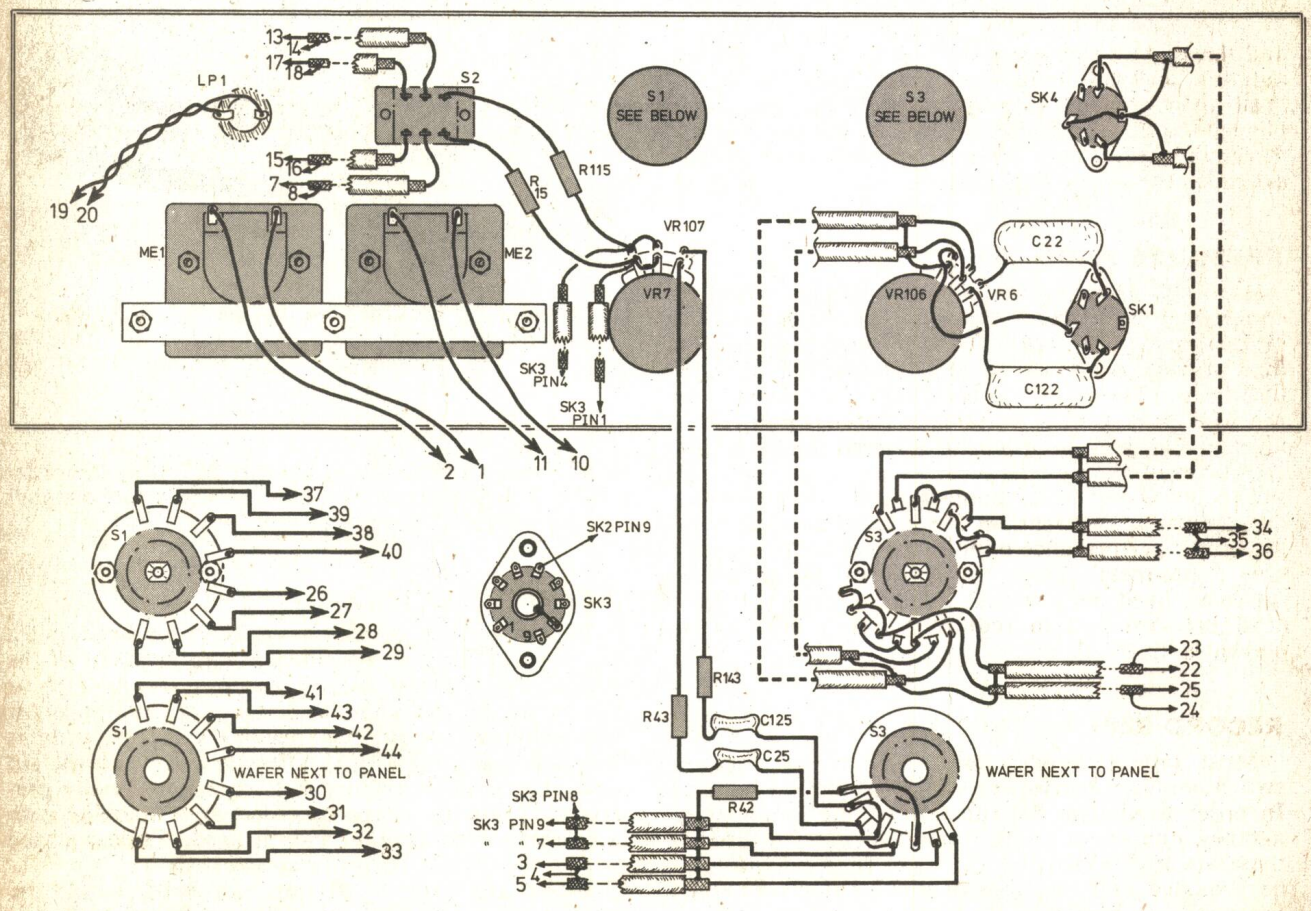

Fig. 7. Interwiring diagram showing the connections between the board and the other components. The numbers indicate the terminal pins on Fig. 6

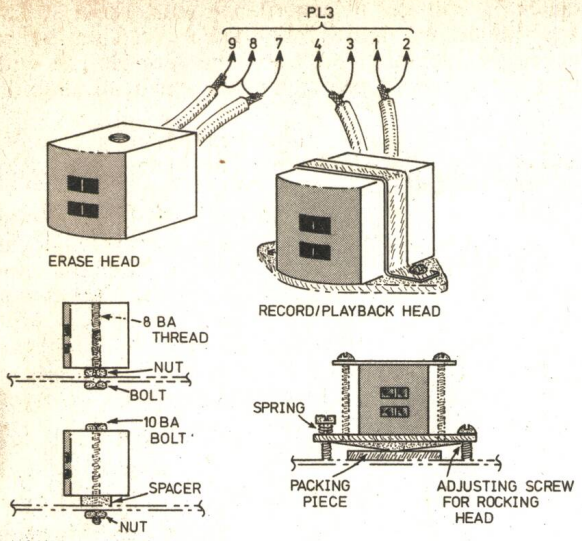

Fig. 8. Methods of fitting the new heads of the tape deck

baseplate packed up to raise the head. The dimensions of the strap are given and it was screwed to the baseplate with self-tapping screws.

The erase head has a single hole through it to clear 10BA, and this is the best means of securing it. The azimuth of the erase head gap is not critical and therefore a rocking plate is not required. On the author's deck this hole was tapped at 8BA and the head then secured directly to the head mounting plate stood-off by an 8BA nut drilled out to clear the thread. The top of the erase head upper track should extend to the edge of the tape.

PRESSURE PADS

A modification made by the author to his deck concerning the pressure pads may be of interest. The original pads were of hard felt requiring quite a high pressure to ensure contact between the tape and the head. These felt blocks were removed and replaced by a pad of composite construction, i.e. a layer of $\frac{1}{8}$in thick foam plastic covered finally with a $\frac{1}{16}$in layer of supple felt.

This gives improved contact at far less pressure thus reducing the wear on the heads and improving the flutter performance of the transport. At the same time a mu-metal screen cut from an old screening can was fixed to the rear of the RECORD/REPLAY head pressure pad to reduce the hum pick-up on playback.

RECORD/REPLAY SWITCH

Most tape recorders have their RECORD/REPLAY switch contacts interlocked with the function buttons. In order to change the function of the amplifier to RECORD, one set of "make" contacts are required. If these are not present on the recorder a switch must be provided and this should have contacts designed for switching capacitive loads.

The heads are wired up to the plug using low capacity screened lead. The deck chassis is earthed to the screens of one of the record/play leads. Care should be taken to ensure that the metalwork of the amplifier does not touch the tape deck. If this is unavoidable the earth link mentioned above must be omitted.

The power supply should not be fixed down yet as its positioning is critical for minimum hum injection. To determine this position the deck should be set in motion as it would be when playing a tape. The power pack is then moved around the cabinet whilst listening to the replay hum level until it is subjectively at its lowest.

The recorder is now complete and ready for setting up.

SETTING UP PROCEDURE

The equipment required to set up the completed recorder is a d.c. voltmeter, an audio sine wave generator and an oscilloscope, or failing this an a.c. millivoltmeter. The setting up should follow the order outlined below as in some cases one stage depends on the setting of the previous.

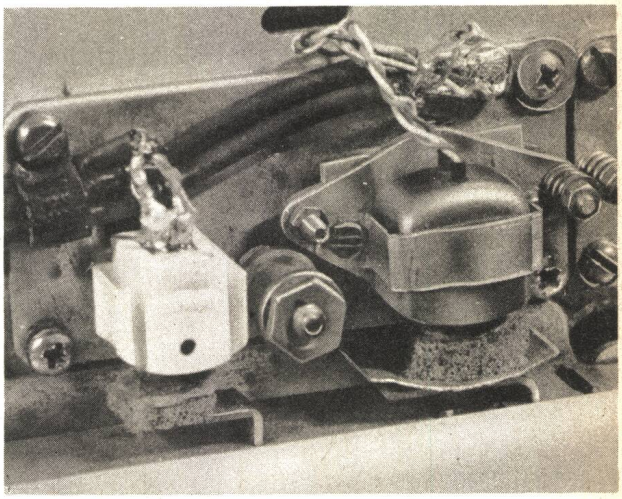

Photograph showing the heads in position on the prototype

AZIMUTH SETTING

Before the electronics are adjusted the heads must be correctly aligned with the tape. Adjustment of the record/replay head gap in relation to the tape is known as azimuth alignment and is essential in order to facilitate the interchangeability of recordings between machines. This is correctly done with the aid of a professional test tape but any commercially pre-recorded tape or a tape recorded on a machine with a known correct azimuth can be used. (Choose a tape with a good high frequency content.)

Whilst the tape is playing the head should be rocked up and down until the maximum high frequency output (measured simply by listening to the output) is obtained, then fixed in this position.

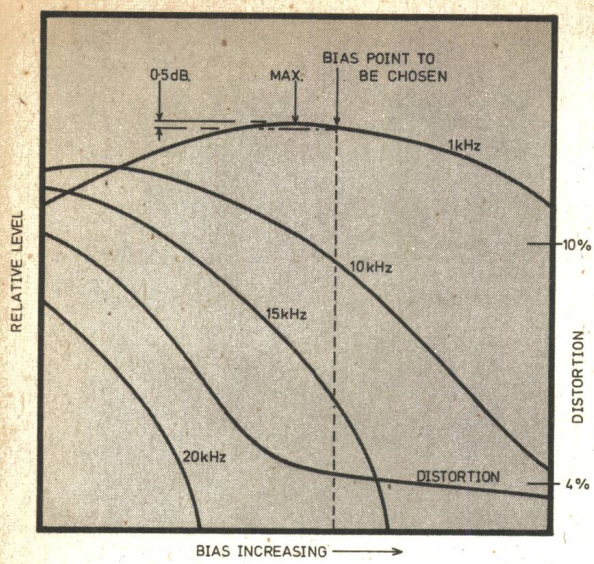

Fig. 9. Graph to show the dependence of frequency response and distortion on the bias level

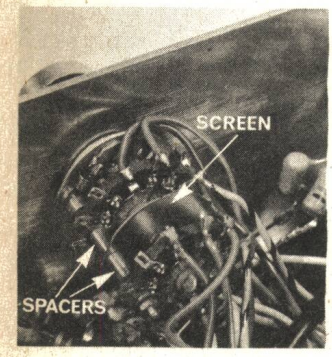

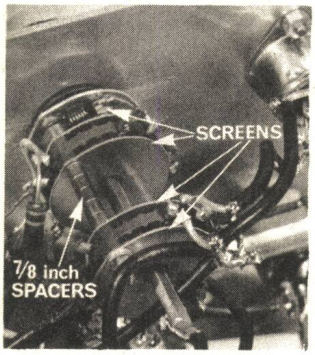

Photographs showing the two wafer switches

Photograph of the completed Tape Link. The meters are held on to the front panel by a strap which is shown

REPLAY AMPLIFIER AND METERING ADJUSTMENTS

Using the voltmeter adjust VR5 and VR105 until the voltage at the emitters of TR9 and TR109 is 12 volts. Next rotate VR4 and VR104 fully clockwise (maximum resistance) then turn back so that the respective meters just read zero.

OSCILLATOR ADJUSTMENT

In the absence of suitable test equipment, a satisfactory result may be obtained by setting the adjuster to its mid position. The exact frequency of operation is not critical and in fact the tolerances of the frequency determining components are wider that the adjustment range.

If an oscilloscope or frequency meter is available then set the oscillator selector switch to STEREO, the bias control to mid range and the machine to the RECORD mode, then adjust the oscillator coil T2 until the frequency is as near to 100kHz as possible.

DETERMINATION OF BIAS SETTING

The correct bias setting is important as it affects many of the parameters of the recorder. The bias setting required depends on the tape speed, the tape in use and the mode of the recorder (MONO or STEREO). The settings should be determined as below and tabulated for reference.

7½ i.p.s.

Record a 1kHz sine wave at a level 6dB below the maximum modulation, adjusting the bias from −3dB to +3dB in ½dB steps. Replay the tape and note the amplitude of the output for each of the bias settings.

A series of results should be obtained which rise to a peak then fall off. The correct setting is that which gives a sensitivity ½dB (approximately 5 per cent) down from the maximum, i.e. slightly more bias than is required for maximum sensitivity (see Fig. 9).

continued on page 341

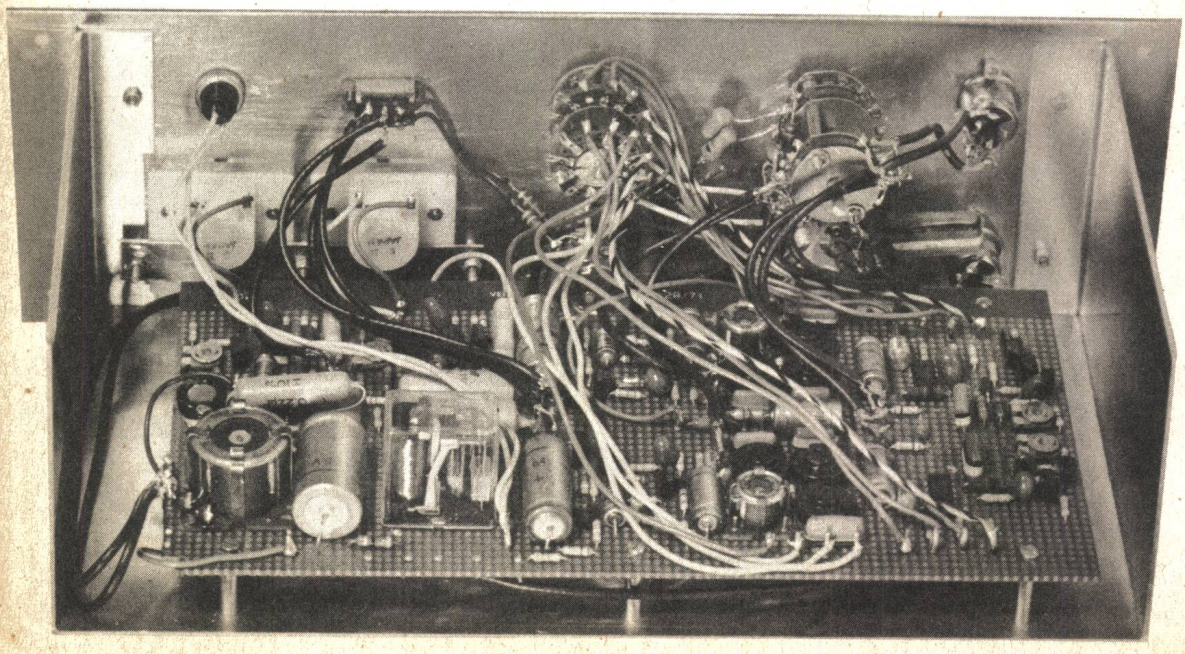

PE

NEXT MONTH...

PUSHBUTTON VARICAP STEREO TUNER

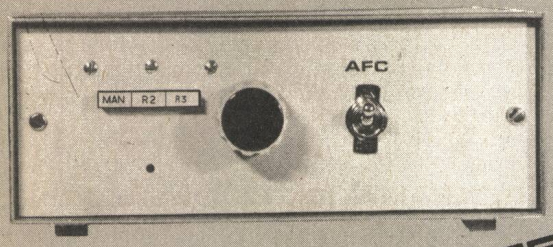

Electronic tuning using varicap diode
Uses ready-built tuner and i.f. modules
I.C. stereo decoder which uses no coils
Pushbutton tuning to preset stations
Can be remotely tuned if desired
Needs no expensive equipment to set up
Compact design uses printed circuit board

Built in only a few hours, this low cost high quality tuner is the perfect unit to complete your hi-fi stereo system

IN THE MAY ISSUE

FREE DISPLAY DEVICE IDENTICHART

At-a-glance information on many types of available readout devices

ALSO IN THIS ISSUE...

PE Sound Synthesiser - 4

RAMP GENERATORS AND INPUT AMPLIFIER

With the completion of this module it is now possible to create an enormous range of exciting sounds!

Don't miss out—Order from your newsagent now!

PRACTICAL ELECTRONICS

MAY ISSUE ON SALE APRIL 13

ELECTRONORAMA

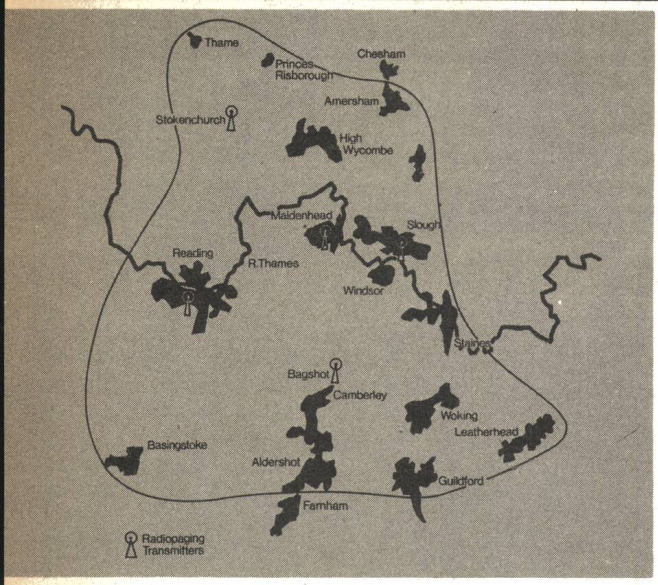

Area covered by the Post Office radio-paging service

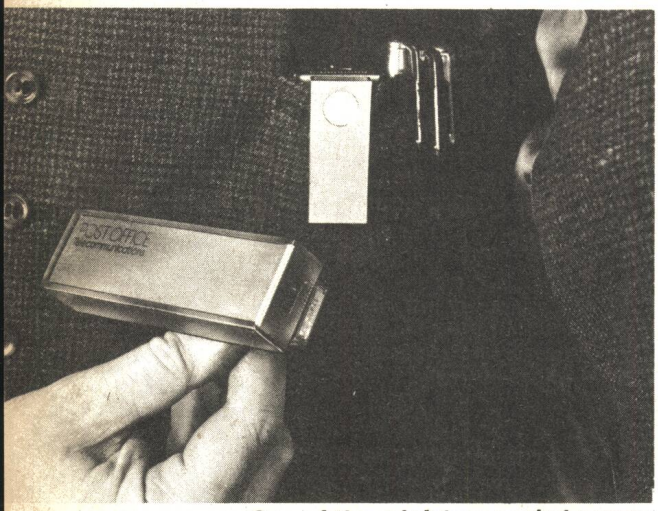

One of the miniature pocket pagers

Computer control complex at Reading Trunk Exchange

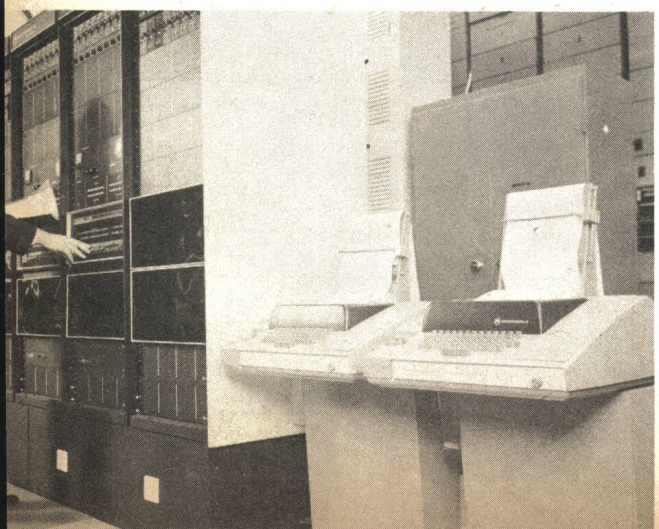

Telephone Paging

WITH the aid of a new Post Office telephone paging system, the businessman, doctor, service engineer and many other people on call within a 500 square mile area of Reading can be easily contacted, even though their whereabouts is not known, simply by dialling a 10-digit telephone number.

The system consists of small "bleeper" pocket receivers; five f.m. transmitters, situated at Reading, Stokenchurch, Bagshot, Slough and Maidenhead; and computer-controlled terminal equipment at the Reading Trunk Exchange.

RECEIVERS

The receivers, small enough to be clipped into a pocket, give a high-pitched 10 second "bleep-bleep" signal when activated by a phone call. Powered by a 1·5V alkaline battery, each receiver will operate for approximately 900 hours, representing three months of average use.

The f.m. receivers are basically a double superhet built around six CMOS integrated circuit modules. Sensitivity is better than 10μV/m and reception is in the 150MHz band. Following detection, the paging tones are decoded by two plug-in active filter modules; 60 frequencies are employed in the range 288·5 to 1,433·5Hz and a two-tone sequence is used to provide a system usable by 3,540 customers. Later the system will cater for 100,000 customers.

Detection of the first coded tone switches the receivers on, reception of the second tone is decoded and once accepted will sound a 2kHz bleep note.

The only control on the receiver is a three position switch: "on", "off" and "memory". In the memory position, used when the person does not want to be disturbed, the incoming signal is stored in a CMOS bistable memory device and when the receiver is switched back to the on position the bleeper will emit its signal.

Each receiver has its own 10-digit number (the first four digits are an STD code common to all receivers) and dialling this number instructs the transmitting equipment to send a signal to activate the bleeper. Communication is one-way only, so the user must prearrange the action to be taken on receipt of a radio-paging call.

COMPUTER CONTROL

The heart of the system is a Digital Equipment, type PDP11, mini-computer with a basic storage capacity of 192,000 bits. Installed at the Reading Trunk Exchange, the computer receives the "telephone calls", converts them (by an interfacer between the telephone network and computer) into a binary-coded format.

The calls are queued and released in batches at 15 second intervals. When the number dialled is recognised and accepted an announcement to replace the telephone handset is given. Once accepted the call is converted to the pager code by the computer, and passed to a frequency synthesiser and then to the relevant transmitters.

The transmitters are switched by command signals from the control complex slightly ahead of the transmission of the pager-code modulation.

Although the system is only a feasibility study, plans have already been made to extend the service to other regions, such as London, Manchester and Birmingham.

More advanced pagers are already being developed and the present receivers are claimed to work inside buildings, cars and on trains. Engineers have, it is claimed, achieved more than a 95 per cent reception in the defined boundary limits.

The radio-paging receivers will cost £5 a month to rent, with an initial fee of £5. Call to a receiver will be free during the introductory service.

THE FREE HEATHKIT CATALOGUE

.....perhaps the most valuable stereo Hifi/Electronics kit publication available today

NEW MULTI-SPEAKER KIT
Features Four KEF Hi-fi Drive Units. Offers monitor quality at lowest cost.

NEW AM/FM STEREO RECEIVER KIT
Solid State FM IF Circuitry, two IC's, two ceramic filters. "Black magic" lighting.

NEW PORTABLE ENGINE ANALYSER KIT
Versatile automotive testing and trouble-shooting.

LOW-PRICED TESTERS AND INSTRUMENTS
for the hobbyist and technician.

PLUS
all the models you have read about in international publications.

NEW 1214 SERIES STEREO HI-FI
Ideal for use for quadraphonic sound.

the HOW AND WHY OF KIT BUILDING
Electronics is fun the HEATHKIT way.

BUILD YOURSELF A PAIR OF SPEAKERS
in an evening – enjoy Stereo sound.

GET THE BEST IN HI-FI
Enjoy worthwhile kit savings.

SOMETHING FOR ALL THE FAMILY
even a battery charger for dad.

LOW COST STEREO RECORD PLAYER
amazing sound value.

It's Free . . . it's the latest Hi-Fi/Electronics catalogue from Heath the world-famous electronic kit manufacturers . . . and it's yours on request. This latest catalogue will appeal to all the family. Stereo Hi-Fi, Transistor portables. Metal detectors, Electronic calculators etc. etc. You name it, Heath can supply. All models offer unbeatable specifications for price.
Excellent continuous credit and no deposit terms available . . . this even includes instruments.
You cannot afford to miss reading this fine publication . . . hurry, send off the coupon for your personal copy today.

Heath (Gloucester) Limited, Gloucester GL2 6EE.

Ask about our No Deposit Terms

Please send me a FREE Heathkit catalogue

Name _____

Address _____

_____

_____

HEATH Schlumberger

Heath (Gloucester) Limited, Dept. PE/4/73
Gloucester GL2 6EE. Telephone 0452 29451

LARGE STOCKS, ATTRACTIVE DISCOUNTS DEPENDABLE SERVICE

ELECTROVALUE

Electronic Component Specialists

TRANSISTORS BY SIEMENS AND NEWMARKET

2N3055 *npn* silicon power	60p
AC153K *pnp* germanium low power	25p
AC176K *npn* germanium low power	23p
AD161 *npn* germanium medium power	42p
AD162 *pnp* germanium medium power	40p
AF139 *pnp* germanium UHF	33p

NPN: BC107 **13p**, BC108 **12p**, BC109 **13p**, BC167 **10p**, BC168 **9p**, BC169 **10p**.

PNP: BC177 **15p**, BC178 **14p**, BC179 **15p**, BC257 **9p**, BC258 **8p**, BC259 **9p**.

Standard groupings available.

BD135 *npn* medium power	26p
BD136 *pnp* medium power	27p

DIODES

OA90, OA91, OA95, **6p** each; OA200, **9p**; OA202, **10p**.

Other semiconductors: AC128, **17p**; AF117, **35p**; BFY51, **19p**. Full lists and technical data will be found in Catalogue No. 6.

SIEMENS' THYRISTORS
0·8A 400V **56p**, 600V **70p**.
3A 400V **60p**, 600V **88p**.

ZENER DIODES full range E24 values: 400mW: 2·7V to 36V, **14p** each; 1W: 6·8V to 82V, **21p** each; 1·5W: 4·7V to 75V, **48p** each. Clip to increase 1·5W rating to 3 watts (type 266F) **4p**.

DIN PLUGS AND SOCKETS

by Hirshmann, 4A rating

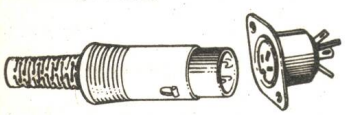

2 way LS —socket **10p**, plug **12p**
3 way scr.—socket **10p**, plug **12p**
5 way scr.—socket **11p**, plug **15p**

TRANSISTOR ACCESSORIES
TO3 cover, **7p**; Heat sinks 1°C/W, type 6W1. undrilled, **60p**.

SWITCHES

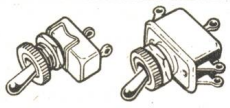

1011 SPST toggle, **20p**; 409 DPDT toggle, **29p** (these are chrome plated, 2·5A rating); 7201 sub-miniature DPDT 250V a.c./2A, **48p**.

ROTARY SWITCHES

Radiospares Miniature Maka-switch (in assembly kit form). Shaft, **48p**. Wafers, MBB-2P5W, 1P11W: BBM1P12W, 2P6W, 3P4W, 4P3W, 6P2W, **6p** each.

WAVECHANGE SWITCHES

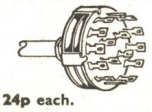

1P12W, 2P6W, 3P4W, 4I3W, **24p** each.

ELECTROLYTIC CAPACITORS AXIAL LEAD

Rated voltage: 3V / Capacity µF	6·3V	10V	16V	25V	40V	63V	100V
0·47	—	—	—	—	—	7p	7p
1·0	—	—	—	—	7p	—	7p
2·2	—	—	—	7p	—	7p	7p
4·7	—	—	7p	—	7p	7p	7p
10	—	7p	—	7p	7p	7p	7p
22	—	7p	7p	—	7p	7p	8p
47	7p	7p	7p	7p	7p	8p	12p
100	7p	7p	7p	7p	8p	12p	18p
220	7p	7p	8p	9p	10p	17p	26p
470	7p	8p	9p	12p	17p	24p	41p
1,000	9p	12p	17p	20p	23p	40p	—
2,200	14p	16p	22p	25p	36p	40p	—
4,700	23p	26p	37p	40p	—	—	—
10,000	37p	40p	—	—	—	—	—

POLYCARBONATE—5% TOLERANCE

250V up to 0·1µF: 100V, 0·1µF and above.
0·01; 0·012; 0·015; 0·018; 0·022; 0·027; 0·033; 0·047; 0·056; **4p** each. 0·068; 0·082; 0·1; 0·12; 0·15; **4p** each. 0·18; 0·22; **5p** each. 0·27; 0·33; **6p**. 0·39 **7p**. 0·47 **8p**. 0·56 **10p**. 0·68 **11p**. 1µF **13p**.

RESISTORS – 10%, 5%, 2%

Code	Power	Tolerance	Range	Values available	1 to 9	10 to 99 (see note below)	100 up
C	1/20W	5%	82Ω–220KΩ	E12	9	8	7·5
C	1/8W	5%	4·7Ω–470KΩ	E24	1	0·9	0.75 nett
C	1/4W	10%	4·7Ω–10MΩ	E12	1	0·9	0·75 nett
C	1/2W	5%	4·7Ω–10MΩ	E24	1·2	1	0·8 nett
C	1W	10%	4·7Ω–10MΩ	E12	2·5	2	1·6 nett
MO	1/2W	2%	10Ω–1MΩ	E24	4	3	2 nett
WW	1W	10% ± 1/20Ω	0·22Ω–3·9Ω	E12	7	7	6
WW	3W	5%	1Ω–10KΩ	E12	7	7	6
WW	7W	5%	1Ω–10KΩ	E12	9	9	8

Codes: C = carbon film, high stability, low noise.
MO = metal oxide, Electrosil TR5, ultra low noise.
WW = wire wound, Plessey.
Values:
E12 denotes series: 10, 12, 15, 18, 22, 27, 33, 39, 47, 56, 68, 82 and their decades.
E24 denotes series: as E12 plus 11, 13, 16, 20, 24, 30, 36, 43, 51 62, 75, 91 and their decades.

Prices are in pence each for quantities of the same ohmic value and power rating. NOT mixed values. (Ignore fractions on total value of resistor order.)

EVERYTHING BRAND NEW, GUARANTEED TO MAKERS' SPEC. NO SECONDS OR REJECTS

KNOBS

All grub screw fitting for ¼in shafts. Black. For other types —see Catalogue No. 6, p. 54.

F.14 (20mm) pack of 2, **32p**; F.13 (26mm) pack of 2, **38p**; F.12 (33mm) pack of 2, **40p**; F.19 (20mm) pack of 2, **32p**; F.18 (26mm) pack of 2, **38p**; F.17 (33mm) pack of 2, **40p**; KB.4 (20mm) pack of 4, **40p**; K30/3 (17mm) aluminium, **24p** each.

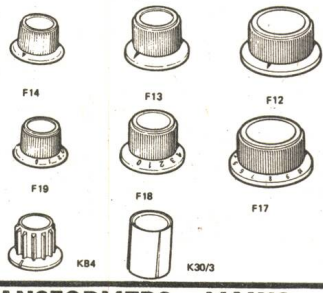

TRANSFORMERS—MAINS

MT3 30V/2A plus 4 taps	£2·85
MT103 50V/1A plus 4 taps	£2·55
MT104 50V/2A plus 4 taps	£3·50
MT127 60V/2A plus 4 taps	£3·80
13TO5 13V/½A, CT	£1·25
28TO5 12–12–2–0–2V/½A	£1·25

IT'S ALL IN THE LATEST ELECTROVALUE CATALOGUE

No. 6 (4th printing) contains details of 100's of semiconductors; ICs with circuit diagrams, R's and C's of practically every kind, accessories, components, tools, materials, etc., information and equivalent tables, etc. Well illustrated (96 pages, 5½in × 8½in) **25p** post free with refund voucher for 25p allowable on orders over £5 or more.

with 25p refund voucher

POTENTIOMETERS

Rotary, carbon track, double wipe

SINGLE P20 lin. 100Ω to 2·2MΩ, **12p**; JP20 Log. 4·7KΩ, to 2·2MΩ, **12p**; **Dual gang** lin. 4·7KΩ to 2·2MΩ, **42p**; Dual log. 4·7KΩ to 2·2MΩ, **42p**; Log/antilog, 10K, 22K, 47K, 1MΩ only, **42p**; Dual antilog. 10K only, **42p**. Any type with 2A D.P. mains switch, **12p** extra.
Only decades of 10, 22 and 47 available in ranges quoted.

TYPE P20

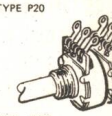
TYPE JP20

DUAL CONCENTRIC DP20 in any combination of P20 values, **60p**; with switch, **72p**.

SLIDER
Lin. or log. 10K to 1 meg. in all popular values, each **26p**.
Control knobs blk./white/red yel./gr./blue/dk. grey/lt. grey, **5p** each.

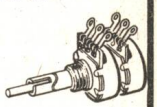
TYPE DP20

CARBON SKELETON PRE-SETS
Small high quality, PR lin. 100Ω, 220Ω, 470Ω, 1K, 2K2, 4K7, 10K, 22K, 47K, 100K, 220K, 470K, 1M, 2M2, 5M, 10MΩ. Vertical or horizontal mounting, **5p** each.

DISCOUNTS

All items offered for sale in accordance with our stated terms of business, copy of which available on request.
Not allowed on nett price items. 10% on orders for **£5** or more. 15% on orders of **£15** or more. *Prices subject to alteration without prior notice.* Prices quoted DO NOT include V.A.T. Orders received after 31st March must be accompanied by an additional 10% of the nett value for V.A.T.

POSTAGE AND PACKING FREE
SURCHARGE 10p on small mail orders under £2. Overseas orders carriage and insurance charged at cost.

ELECTROVALUE

(Dept. PE4), 28 ST. JUDE'S ROAD, ENGLEFIELD GREEN, EGHAM, SURREY TW20 0HB
Hours: 9—5.30. Sat. 1 p.m. Tel.: Egham 3603 Telex 264475
Eng. Reg. No. 1047769 Registered Office: 28 St. Jude's Rd., Englefield Green, Egham, Surrey TW20 0HB

Strictly Instrumental

by K. Lenton-Smith

POPULAR MUSIC is a lucrative and highly competitive field these days and the net is cast to take in an even younger age group each year. Ten-year-olds now have their own idols! To be successful in the "pop" field involves a constant search for new sounds by electronic processes, especially as there is a practical limit to what can be done with the vocal if the lyrics are to remain intelligible. (Some readers may query the use of the word "intelligible" in this context!)

The Survey of Electronic Musical Instruments, published as a supplement to the November 1972 edition (issues unobtainable), showed how manufacturers are catering for this search for new tonal ideas. Though initially featured by recording artists, new effects are copied by local groups as they struggle to keep abreast of the times. Amateur musicians, who prefer "pop" music though never play publicly, like to re-create at home some of the sounds they hear on radio, tape and discs. The younger generation has always, as a tradition, looked for change and new experience, the popular music field being no exception. Over the years, the specification of available electronic musical instruments has taken this into account increasingly.

LIGHT MUSIC TODAY

A certain line in "Fings ain't wot they used to be", referring to the light music scene at that time, mentioned musicians "backing themselves with three chords only". When that song was written, there was an element of truth in Lionel Bart's cynicism: a number of performers only seemed able to strum the tonic, sub-dominant and dominant seventh chords on their highly-amplified guitars. This deficiency was often covered up by a show of vocal and physical gymnastics!

The advent of the Beatles brought more tuneful melodies and the use of less closely related chords. Though the Beatles, as a group, no longer exist they underlined the fact that, if a song is to survive, the melody must be original and tuneful. Many modern "pop" numbers will be forgotten a few months hence, but the Lennon and McCartney compositions have already taken their place with those of the established Old Masters such as George Gershwin, Cole Porter, Jerome Kern and Richard Rodgers.

Burt Bacharach is today's prime example of a composer who writes enjoyable music which will be remembered many years hence: Antonio Carlos Jobim is in the same category, specialising in the Latin-American field. The reader who plays their music, or attempts the transcriptions of Dave Brubeck or Dudley Moore, will appreciate that the days of "three chords only" have long passed and things certainly ain't what they used to be! These composers frequently use complex chord sequences which demand a high degree of musical ability to perform them.

Whereas our sphere of electronics —especially integrated circuitry— has enjoyed a spin-off from space research, classically trained musicians who have turned to lighter music have also benefited that field. The music for a number of West End shows running currently has come from composers with classical backgrounds, whilst we have previously commented on Walter Carlos, Robert Moog and the music for "Clockwork Orange".

RETROGRADE

Today's standard of compositions and the requisite musicianship in light music is higher than it was a generation ago. At the same time, the true standard of many electronic musical instruments has fallen. Manufacturers appear to be attempting to get the proverbial quart into a pint pot, especially where organs are concerned. Perhaps this is understandable where many instruments are sold to be installed in clubs, or other public places, where the audience expects a really professional performance—by their standards.

The organ studio demonstrator will show convincingly what a wonderful instrument you are about to purchase. It will no doubt have many extras such as a built-in rhythm unit, waa waa, percussion, arpeggiator, automatic chord unit, Leslie speaker, cassette tape recorder and perhaps a small synthesiser keyboard, to name but a few. Underneath all this, how much real organ is there? All these additions are expensive and the makers are probably working to a given price range, so something has to give.

The accompaniment manual is usually the victim, and the buyer is lucky if he is offered more than one pitch on that keyboard. We should perhaps remember that not all users of electronic organs are light music orientated or require the help of automatic chord/rhythm units. No serious organist would consider a single-pitch manual, or for that matter a short spinet manual of 44 notes and a set of stub-pedals. A number of users are primarily interested in baroque music or are simply church organists who require a home organ for practice purposes which will produce conventional pipe-organ tonal quality.

SOUND SYNTHESISER

For those who wish to experiment with unusual effects, the synthesiser is ideal. Mr Shaw's P.E. Sound Synthesiser should prove to be a fascinating project for readers seeking new musical sounds: we hope it will also alert organ makers to the fact that organs should sound as such and not attempt to compete with the synthesiser. Both are separate and distinct musical devices with identities of their own.

Incidentally, readers who went to the Audio Fair to hear Mr Shaw's synthesiser last year might also have listened to some of the stereo demonstrations on various stands. One of the records used for this purpose was "Moog Indigo" (VSD 6549) featuring Jean Jacques Perrey, is recommended to those who like the Moog and can appreciate the performer's skill and have a strong sense of humour.

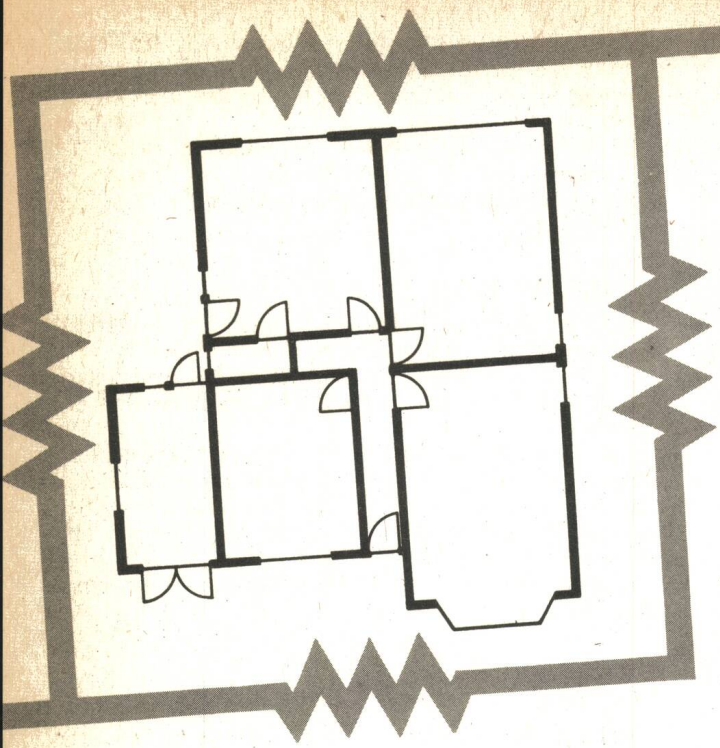

Simple All-Around SECURITY ALARM

By J. Andrews

THIS alarm system was developed to protect the house and buildings remote from it, for example, garage, workshop, etc., which might be subject to burglary or vandalism. It can of course be used to protect all other types of property.

SEARCH LOOP SYSTEM

Many alarms use the search loop system in which the doors and windows have micro-switches fitted. The switches are wired in series and should any one switch be opened the circuit is broken. When the loop is connected to a simple alarm breaking the search loop will cause a bell or other device to sound. However, if the loop can be shorted out before the switches the alarm can be rendered inoperative.

This is particularly easy if the building protected is remote from the house as the search loop wires may be run back together and offer an opportunity for short circuit. Short circuits could be caused in a number of ways, by accident, fire or deliberately.

BALANCED BRIDGE

To overcome these problems a simple bridge was devised for the prototype security alarm as seen in Fig. 1.

Here, one arm is made up of the search loop wire resistance Rx. With the bridge balanced, that is, when Rx × R2 = R1 × R3, no voltage will appear at the alarm input points XY. If the search loop is made either open or short circuit, outputs will appear at these points but of opposing polarity.

POLARISING DIODES

To overcome this and to provide voltages of a single polarity for the open and short circuit conditions, a diode bridge was arranged so that any change of balance in the resistance bridge provides a negative going input to the alarm circuit as in Fig. 2.

In this, the finalised circuit of the Security Alarm, the resistance bridge is made up of R1, R2, R3, VR1 and the loop resistance Rx.

Arm resistances are made 150 kilohms so that the standing current is low. VR1 is included to balance any difference in the bridge arms and also provides a test facility as described later.

LATCH CIRCUIT

As the output resistance of the bridge is relatively high it is necessary to multiply the input impedance

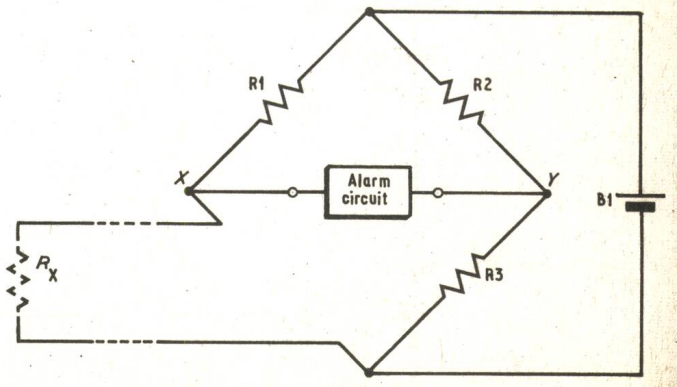

Fig. 1. Basic bridge system

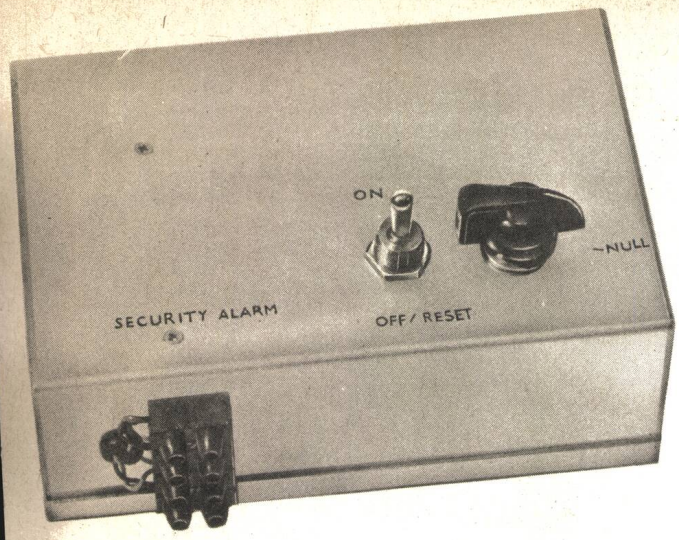

The completed security alarm control unit

of any device connected across it. In the latch circuit this is achieved by connecting TR1 and TR2 as a Darlington pair.

TR2 output drives TR3 which is a higher power device suitable for driving a relay or lamp up to 800 milliamps when saturated.

Latching or hold on is achieved as follows. When TR3 is turned on by TR2 the collector voltage falls due to the drop across the relay and when TR3 is saturated is approximately 0·3V.

As TR3 collector goes negative, this turns TR2 on harder and positive feedback holds TR2 and TR3 in saturation regardless of input current to TR1.

The current to TR3 base is limited by R5. Once tripped the circuit will stay on until the supply is interrupted. C2 is included to ensure the circuit resets.

In the prototype a relay was used to switch on an external bell. It could also be used to turn on lights or activate other warning systems.

CONSTRUCTION

Most of the small components given in the circuit diagram can be assembled on a piece of 3in × 1½in Veroboard as is Fig. 3. When assembled and wired, 6in sleeved flying leads should be connected where indicated.

The choice of housing for the board and ancillary pieces was a 4in × 6in × 2½in standard aluminium chassis. First the mounting holes for VR1 are drilled together with those for the double-pole switch and Veroboard spacers.

With these items fitted interwiring can be completed as in Fig. 4.

TESTING

To test the assembled alarm connect up batteries B1 and B2 only and fit a 200 kilohm resistor across the loop terminal. If a high impedance multimeter is available connect across capacitor C1 as seen in Fig. 2.

Set the meter to the ten volt range, and switch the unit on. If now VR1 is rotated from end to end a null should be found.

If all is in order, connect B3 and switch on. The relay should stay out. If this is not so check that the null balance is correct.

Now rotate VR1 in a clockwise direction and the relay should pull in. If the null is now reset the relay should remain in.

Now reset the alarm by flicking switch S1 off and on, then rotate VR1 anticlockwise when the

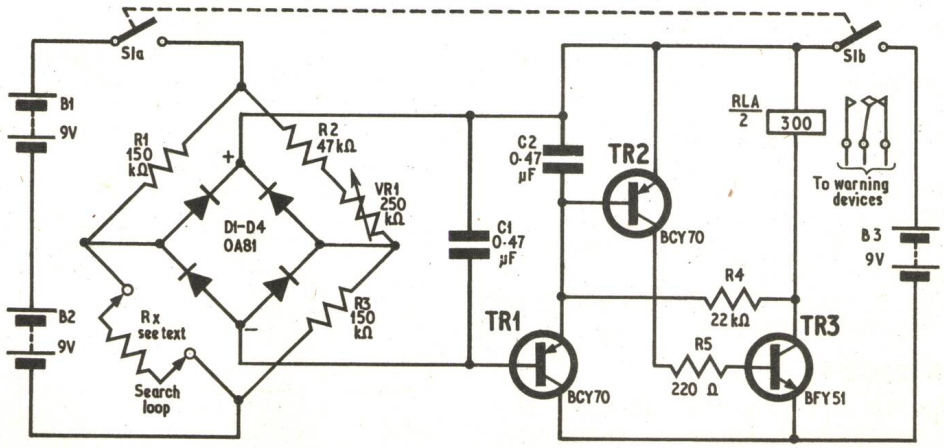

Fig. 2. Circuit diagram of the security alarm

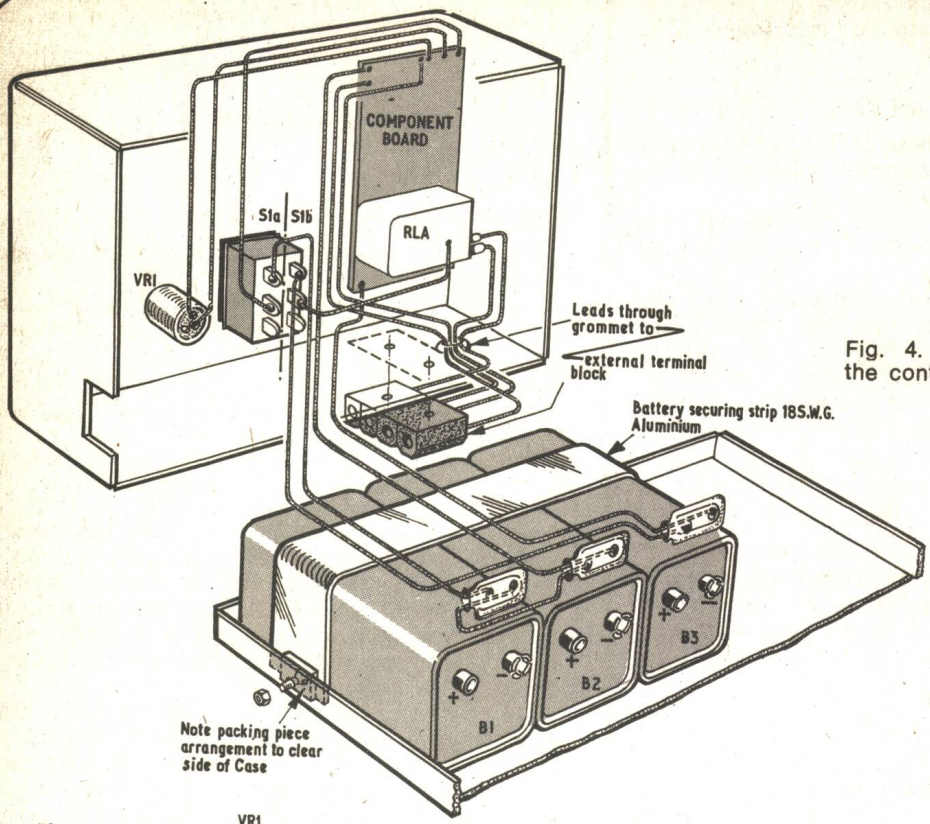

Fig. 4. Interwiring details of the control unit

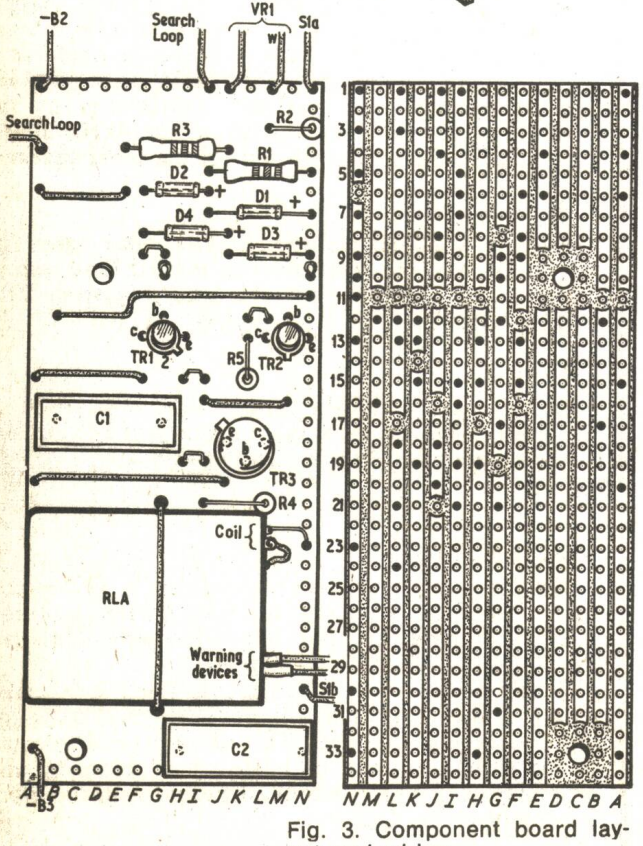

Fig. 3. Component board layout and wiring

COMPONENTS . . .

Resistors

R1 150k Ω R4 22k Ω
R2 47k Ω R5 220 Ω
R3 150k Ω
All ½ watt 10% carbon

Capacitors

C1 0·47uF C2 0·47uF

Potentiometer

VR1 250k Ω carbon lin.

Transistors

TR1–TR2 BCY70 (2 off) TR3 BFY51

Diodes

D1–D4 OA81 (4 off)

Switch

S1 Double-pole, single throw mains on/off

Relay

RLA 100–300 Ω coil, 6V with contacts to suit application

Miscellaneous

B1–B3 9V Vidor VT6 (3 off), aluminium chassis 4in × 6in × 2½in, Veroboard and wire to suit

relay should again pull in. Return VR1 to null and reset the alarm with the switch.

Note that the relay cannot be reset unless VR1 is at null.

TESTING WITHOUT A METER

Disconnect R4 from the base of TR2 and connect a 200kΩ resistor across the loop terminals as before. Connect all batteries and switch on.

Rotate VR1 until the relay pulls in, then back off until the relay drops out. Note the point at which the relay pulled in.

Rotate VR1 in the opposite direction until the relay pulls in again, and note this point. The centre of the two points at which the relay pulled in is the null point of the bridge.

Reconnect R4 and check that when VR1 is rotated in either direction the relay pulls in and remains when VR1 is set to null.

FINISH

Once the instrument has been checked and the null and test points have been determined, Letraset may be used to apply a legend to the front panel. A coat of clear varnish will ensure the case stays bright.

INSTALLATION

As explained previously the search loop resistance must total 150kΩ–200kΩ. This is extremely high and any amount of wire used to make up the search loop will not affect this figure, therefore it is necessary to insert resistance in the form of two 100kΩ resistors in the loop

Arrangement of switches in the loop need not be confined to microswitches on doors and windows. Switches can be placed under carpets, etc., depending on the amount of security required. One further idea to protect windows apart from microswitches, is to fix a screen of fine copper with tape or clear varnish directly to the glass. This is included in the search loop; should the window be broken, the alarm will sound.

The alarm control unit would normally be installed in some part of the house, perhaps in a cupboard or concealed behind furniture. However, when siting the alarm, bear in mind the wires will have to run to parts of the house or outbuildings to be protected.

WARNING DEVICE

No actual warning device is shown as this will be governed by personal requirements, possibly only a warning light will be required, however the relay could turn on house lights or ring a large bell.

Once installed and assuming the alarm has been tested as above, no difficulty should be encountered. Before connecting the search loop check with an ohmmeter for continuity and correct resistance. Connect the search loop to the control unit and set VR1 to null; switch on the alarm and check that both shorting and open-circuiting the search loop cause the alarm to operate.

When in use periodically check the alarm by rotating VR1 first clockwise and then anticlockwise. In both cases the alarm should sound. This forms a test of battery condition. Batteries should operate the unit for their shelf life. ★

HI-FI TAPE LINK

continued from page 332

3¾ i.p.s.

Repeat as for 7½ i.p.s. using a test frequency of 500Hz.

1⅞ i.p.s.

As for 7½ i.p.s. but using 250Hz.

The bias must be determined separately for mono and stereo modes.

PRE-EMPHASIS

Adjustment of the pre-emphasis gives a maximally flat overall frequency response.

7½ i.p.s.

Apply an input signal from a signal generator at 15·4kHz and adjust L1 until peak output is obtained at the output of the replay amplifier (junction of R11 and R13). Next set the generator frequency to 4kHz and record at a level of −10dB. Replay the tape and note its output as this is to be used as a reference.

Reset the frequency to 15·4kHz and make another recording leaving the level control untouched. Note the playback level and then make successive recordings adjusting VR1 to give a playback level at 15·4kHz which is ½dB greater than at 4kHz. The overall response should now be reasonably flat. However, a check should be made at a number of points between 4kHz and 15·4kHz adjusting VR1 so that the undulations in the response curve lie equally about the 4kHz figure.

Then repeat this procedure for the other channel.

3¾ i.p.s.

Record a 800Hz reference level once again at −10dB. Set the generator to 9·6kHz and repeat the above procedure but this time adjusting VR2 then VR102.

1⅞ i.p.s.

In this case a 200Hz reference level is used at −10dB. The generator is set initially to 6·0kHz and VR3 then VR103 are set up as above.

MODIFICATIONS

Readers wishing to save the expense of two meters can parallel the outputs of the meter drive amplifiers into one storage capacitor. The meter will then show the larger of the two input signals.

If this design is to be used with the P.E. Gemini amplifier then it is advisable to fit attenuators to the input and output sockets. This allows reasonable use of the gain control to be made when recording and on playback gives an output consistent with the input sensitivity of the Gemini. ★

Correction: In the first part (March 1973) Figs. 2b and 2c should be transposed.

PE Digi-Cal

By R.W. COLES

PART 10

M COUNTER BOARDS

THIS month's article deals with the M(COUNTER) boards which are the last of the arithmetic unit plug-in cards to be described.

M COUNTER FUNCTION

The basic system used to enable the MULTIPLICATION and DIVISION operations to be carried out was described in Part 1, where it was mentioned that the successive additions and subtractions carried out were counted in a counter circuit.

It is this counter which is housed on the two identical M boards, together with the COMPARATOR circuit required during MULTIPLICATION to register an equality between the count and the contents of the E REGISTER.

BLOCK DIAGRAM

A block diagram of the COUNTER/COMPARATOR circuits and their related data paths is shown in Fig. 10.1, which can be placed in context by reference to the overall system block diagram, Fig. 1.3 of Part 1.

The counter itself consists of a serial string of six, four-bit, decade counter units which have a maximum count capacity of 999999.

The COUNTER can be cleared or preset by appropriate control signals from the programme, and is triggered by the PLUS/MINUS COMPLETE signal from board CB, which is produced during each addition and subtraction.

The six, four-bit, B.C.D. outputs from the counter are fed to the comparator circuit and also to the A REGISTER into which they can be entered at the end of a DIVISION sequence as required.

When the COMPARATOR registers an equality between the count and the E REGISTER contents during a multiplication, it sets a latch which produces the COMPARATOR EQUAL signal, which in turn stops the arithmetic clock.

Before a MULTIPLICATION sequence, the EQUALS LATCH is cleared by a signal from the PROGRAMME.

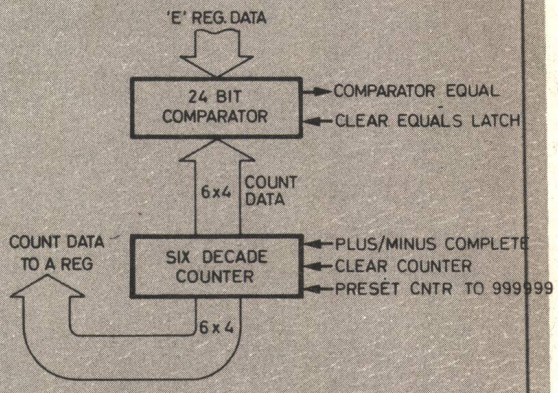

Fig. 10.1. Block diagram of the COUNTER/COMPARATOR circuits and their related data paths

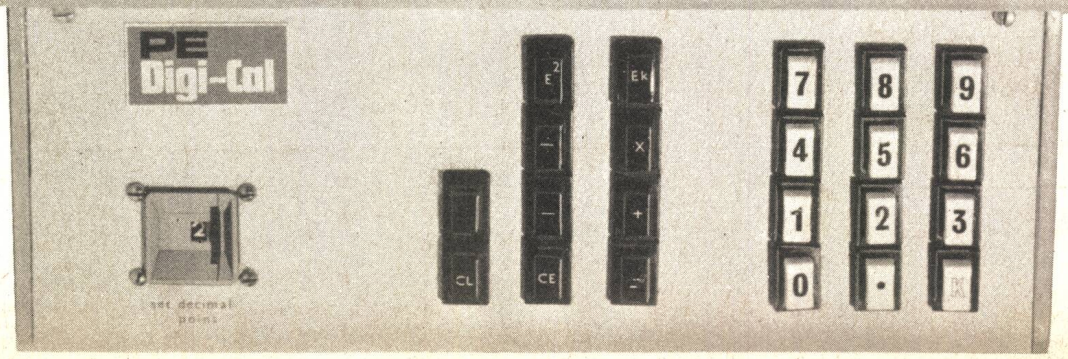

PARTITIONING

A six decade counter and comparator requires too many i.c.s, even when using M.S.I. devices, for it to be housed on a single DL109 card, so the circuit is split into two identical sections, each comprising a three decade counter and a commensurate amount of comparator circuitry. This is described more fully in Fig. 10.2.

Only one EQUALS LATCH is required, but in practice a latch is incorporated on each board to ensure interchangeability, which is an advantage in fault finding, and initial testing.

The latch in use is determined by the external edge connector wiring, no connection being made to the latch inputs and outputs on the board in the M2 position.

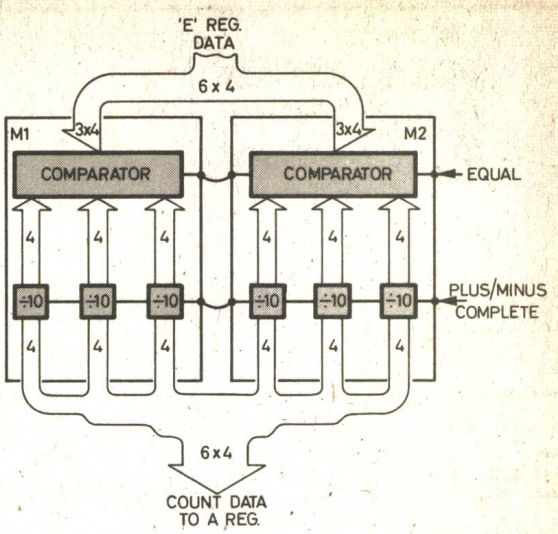

Fig. 10.2. Partitioning of the COUNTER/COMPARATOR between the two M boards

FULL CIRCUIT

The full circuit of one of the M COUNTER boards is shown in Fig. 10.3. The counter chain is easily identified as IC's 123, 124 and 125 which are SN7490 devices connected to count in a B.C.D. code by connection on the A output to the B input.

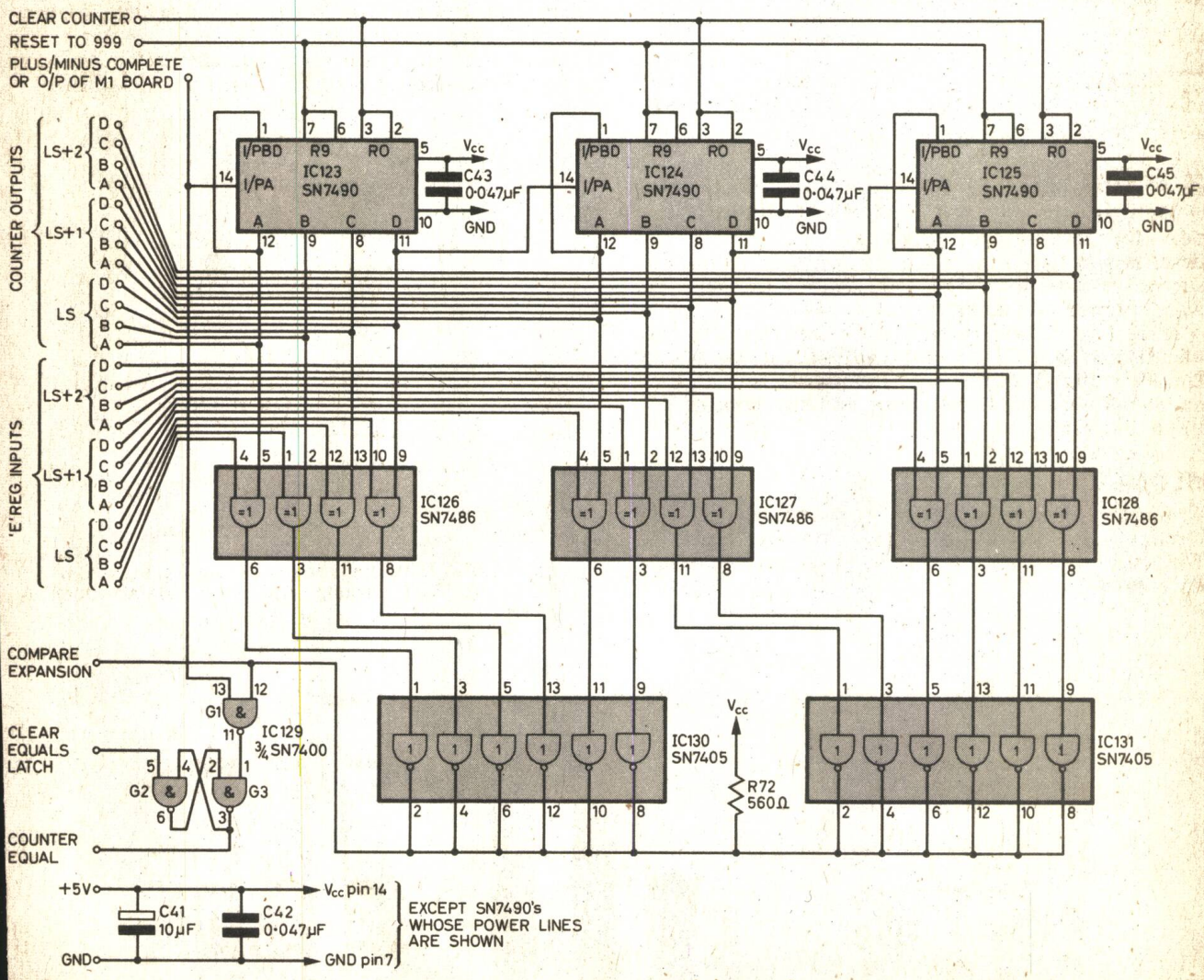

Fig. 10.3. Circuit diagram of one of the M boards. The other board is identical to this, both being built on DL109/44 boards

The count input to the board comes either from the PLUS/MINUS COMPLETE line (in the case of M1) or from the LS+2, D output of board M1 (in the case of M2).

Each of the SN7490 devices has a decoupling capacitor connected between its power supply lines, in addition to the two standard board decoupling capacitors C41 and C42.

LINE DRIVING

Special precautions are necessary for absolute integrity of the count, without false triggering or commutation, because the ABCD counter outputs are taken off the board as inputs to the A REGISTER.

Line driving from counters in this way can cause problems due to the high peak current required to charge the stray capacitance of the line during a 0 to 1 transition. Having an extra reservoir of charge available directly across the i.c. power pins goes a long way toward preventing the mistriggering problems which could result.

COUNTER PRESETS

The RESET 0 (R0) and RESET 9 (R9) inputs to the SN7490 set the COUNTER outputs to 0000 or 1001 respectvely.

The R0 inputs are connected together to form the CLEAR COUNTER line, controlled by the PROGRAMME, and the R9 inputs together make up the RESET to 999 line.

As mentioned in Part 1, it is necessary to preset the M COUNTER to 999999 before a division so that the final number of subtractions counted when the A REGISTER contents go negative and stop clock generation, is not the full number of subtractions performed, but the full number minus one.

Setting the count to 999999 is the same as starting to count from minus one, since on the first PLUS/MINUS COMPLETE pulse, the count will change to 000000, the number registered by the counter always being one behind the true number of subtractions performed.

During MULTIPLICATION the true number of additions performed has to be counted—the PROGRAMME ensuring this by energising the CLEAR COUNTER input and not the RESET to 999 input.

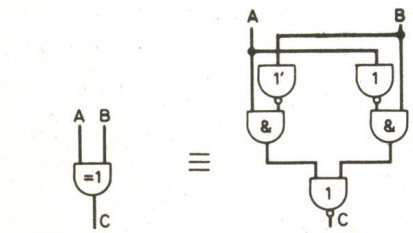

A	B	C
0	0	0
1	0	1
0	1	1
1	1	0

A	B	C
0	0	1
1	0	0
0	1	0
1	1	1

Fig. 10.4. Equivalent logic for an EXCLUSIVE-OR gate and truth tables for both positive and negative logic conventions

COMPONENTS . . .

Resistors

R72, R73 560Ω ¼W ±10% (2 off)

Capacitors

C41, C46 10μF 15V elect. (2 off)

C42–45, C47–50 0·047μF (8 off)

Integrated Circuits

IC123–125, IC132–134	SN7490 (6 off)
IC126–128, IC135–137	SN7486 (6 off)
IC129, IC138	SN7400 (2 off)
IC130, IC131, IC139, IC140	SN7405 (4 off)

Printed Circuit Boards

Type DL109/44 Shirehall (2 off)

In each case components are divided equally between the two M boards

COMPARATOR

The COUNTER as described is all that is needed to allow the DIVISION operation to take place, but during MULTIPLICATION comparison of the count with the E REGISTER contents is required.

The COMPARATOR is made up of the remaining i.c.s on each board and is concerned solely with detecting the equality of E REGISTER and COUNTER outputs so that a control signal can be produced to stop the clock at this point.

The 24 bits of E REGISTER data and the 24 bits of COUNTER data are individually compared on a one-to-one basis in a series of 24 EXCLUSIVE-OR gates formed from six SN7486 packages, housed three to a board.

EQUIVALENCE GATE

The SN7486 package is a member of the M.S.I. family and is described as a quad EXCLUSIVE-OR gate in TTL literature. The very useful EXCLUSIVE-OR function has its own logic symbol, but is in fact made up of a series of simpler gates, as has its own logic symbol, but is in fact made up of a series of simpler gates, as shown in Fig. 10.4.

Readers may recognise the equivalent logic as being simply the common AND-OR-INVERT function together with a couple of inverters to produce the NOT version of the A and B inputs.

The reason for the EXCLUSIVE-OR name becomes obvious when the basic (positive logic) truth table is examined. The output from the gate is a logic 1 if either input A OR input B is a logical 1 but *not* if both are logical 1's.

This response is that of a non-equivalence gate since a logic 1 output is produced only when the inputs are different, but the situation is changed when the gate is examined in operation as a negative logic system, as the second truth table demonstrates.

NEGATIVE LOGIC

In the second truth table we can see that when a low voltage is interpreted as a logic 1, rather than as a logic 0, the output of an SN7486 gate is a logic 1 when the inputs are identical, giving the equivalence function.

M COUNTER BOARDS

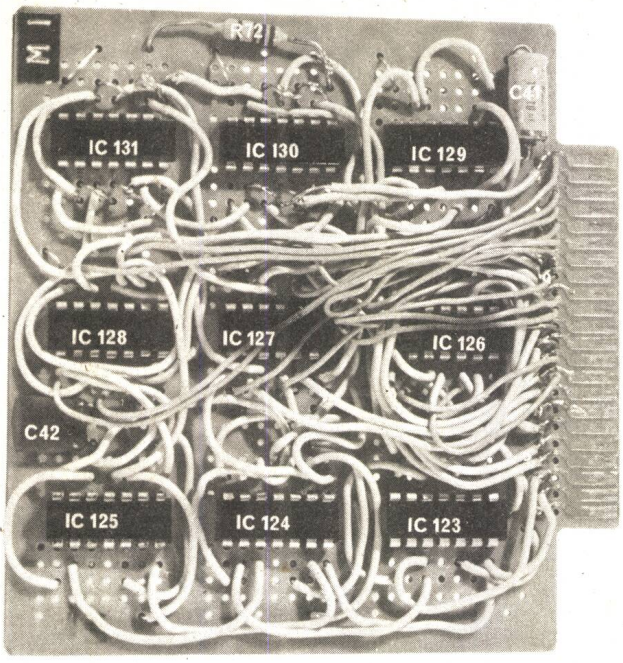

M2/1	1	23	A2/35
not used	2	24	A2/36
not used	3	25	A1/35
not used	4	26	A1/36
E2/35, M2/22	5	27	A2/37
E2/36	6	28	A2/38
E2/37	7	29	A1/37
E2/38	8	30	A1/38
E1/29	9	31	A2/39
E1/30	10	32	A2/40
E1/31	11	33	GND
E1/32	12	34	+5V
E1/35	13	35	A1/39
E1/36	14	36	A1/40
E1/37	15	37	not used
E1/38	16	38	not used
CB/31	17	39	not used
not used	18	40	not used
CL = LATCH (fr prog)	19	41	not used
CL CNTR (fr prog)	20	42	not used
RESET to 999 (fr prog)	21	43	not used
CB/41	22	44	not used

1	COMPARE EXPANSION	
2	not used	
3	not used	
4	not used	
5	D	LS + 2
6	C	LS + 2
7	B	LS + 2
8	A	LS + 2
9	D	LS + 1
10	C	LS + 1
11	B	LS + 1
12	A	LS + 1
13	D	LS
14	C	LS
15	B	LS
16	A	LS
17	COUNTER EQUAL	E REG INPUTS
18	not used	
19	CL EQUALS LATCH	
20	CL CNTR	
21	RESET to 999	
22	COUNT INPUT	

Layout of components on upper side of M COUNTER board, and interconnection details of the M1 edge connector. See Fig. 6.9 for disposition of edge connectors

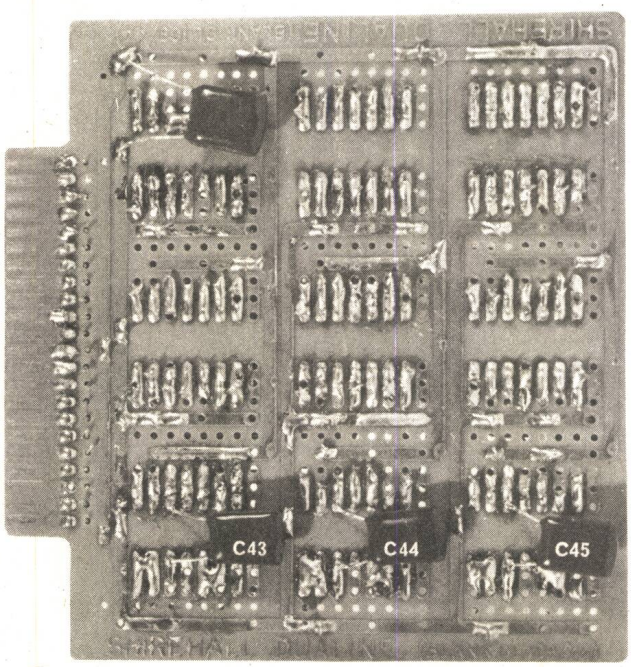

CNTR OUTPUTS	LS + 2	D	23	
		C	24	
		B	25	
		A	26	
	LS + 1	D	27	
		C	28	
		B	29	
		A	30	
	LS	D	31	
		C	32	
		GND	33	
		+5V	34	
	LS	B	35	
		A	36	
		not used	37	
		not used	38	
		not used	39	
		not used	40	
		not used	41	
		not used	42	
		not used	43	
		not used	44	

M2

M1/1	1	23	A2/27
not used	2	24	A2/28
not used	3	25	A1/27
not used	4	26	A1/28
E3/29	5	27	A2/29
E3/30	6	28	A2/30
E3/31	7	29	A1/29
E3/32	8	30	A1/30
E3/35	9	31	A2/31
E3/36	10	32	A2/32
E3/37	11	33	GND
E3/38	12	34	+5V
E2/29	13	35	A1/31
E2/30	14	36	A1/32
E2/31	15	37	not used
E2/32	16	38	not used
not used	17	39	not used
not used	18	40	not used
not used	19	41	not used
CL CNTR (fr prog)	20	42	not used
RESET to 999 (fr prog)	21	43	not used
M1/5	22	44	not used

Layout of capacitors on underside (ignore unmarked capacitor) and interwiring details of M2 socket

To disbelievers, all this talk of switching logic conventions to suit the circumstances can be confusing, and really it is only a convenient way of looking at things.

In practical terms, the output of an SN7486 gate will go low when its inputs are identical, so to determine when all 24 gates have low outputs, i.e. when M equals E, we need a 24 input NAND gate which responds to negative logic inputs.

NEGATIVE LOGIC NAND GATE

No such gate is available in the standard TTL range, but if it were, it would be listed as a NOR gate because TTL is described in the positive logic convention.

All is not lost however since by using an open-collector inverter connected in the input of each SN7486, and then joining all the open collectors through a single common resistor to V_{CC}, i.e. by performing the WIRED-OR function at their outputs, a negative logic NAND gate of virtually unlimited size can be formed (Fig. 10.5).

The way a gate operates is fairly straightforward: if all SN7486 outputs are low, i.e. if M equals E, then the output of all inverters will be high, and the common resistor ensures a high voltage output.

If any one or more of the SN7486 outputs is high, however, one or more of the inverter outputs will go low and pull the common output to a low level.

INVERTERS

The inverters used on the M boards are type SN7405, which have the required open collector output circuitry. Note that the SN7404 devices are not suitable for use in this position due to their standard totem-pole outputs.

Although only one "pull-up" resistor is required for the full 24 inverters, electrically speaking in fact a separate resistor is used on each board to allow the boards to operate autonomously when required.

The inverter outputs from the two boards are united by means of the COMPARE EXPANSION input/output line, so that the two resistors are effectively in parallel.

LATCH FUNCTION

When an equality is registered by the comparator, the common output line rises to a high level and this signal is used to set the simple latch flip-flop made from cross-coupled SN7400 gates G2 and G3.

Setting the latch is carried out via another gate G1, which is controlled by the clock input line to

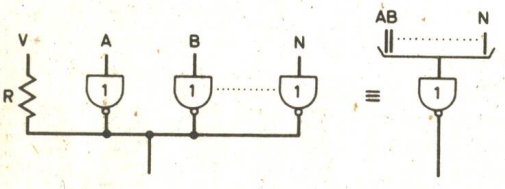

Fig. 10.5. The use of inverters to form a 24 input NOR gate

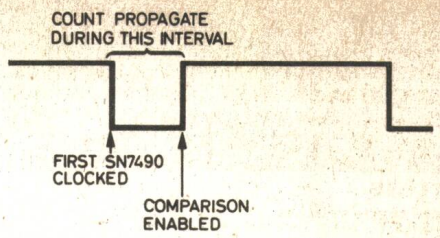

Fig. 10.6. PLUS/MINUS COMPLETE waveform from the COUNTER board

the first SN7490. In practice this line will carry the PLUS/MINUS COMPLETE waveform, since only the latch on the M1 board is wired into circuit.

The reason for this gated latch input circuit is explained in Fig. 10.6, which shows the PLUS/MINUS COMPLETE waveform from the COUNTER board.

The SN7490 counters are triggered from the negative going signal, but because these devices operate in the ripple count mode, there will be a significant count propagation delay time down the chain which can and will lead to transient spurious outputs from the COMPARATOR gating.

Using the PLUS/MINUS COMPLETE signal to gate the COMPARATOR output prevents the spurious outputs from setting the EQUALS LATCH until count propagation is complete, since G1 is enabled by the positive going edge of the waveform.

EQUALITY

When a genuine state of equality exists between the COUNTER and E REGISTER the latch is set, energising the COUNTER EQUAL line which in turn stops the supply of clock pulses to the A, Z and ADDER boards.

Before a further MULTIPLICATION sequence is initiated, the PROGRAMME clears the EQUALS LATCH ready for a new comparison.

CONSTRUCTION

Construction of the two M boards follows the by now familiar pattern, two DL109/44 cards being used. All wiring should be kept as short as possible whilst avoiding "bird's nests".

Speed problems decrease by a factor of ten for each stage of the COUNTER meaning in effect that only the first stage could be a problem in this respect. For this reason it is best to select which board is to be installed in the M1 position during test calculations, since the first stage of one board might perform better than the other at speed.

TESTING

The M boards are easy to check in isolation if required, but if the recommended sequence of construction has been followed and the calculator is operational on ADD/SUBTRACT, it is easier to test the boards in situ, using the MULTIPLY/DIVIDE programmes—but more of this next month.

Next month: E² Logic, Error Detection and Testing

MAIL ORDERS: Some items have a postage and handling charge shown against them. Where p. & p. is not shown the charge is 13p for any selection. When both classes of goods are ordered the charge is 13p plus any p. & p. charges shown. (Overseas extra). Telephone 01-692 4412.

GARLAND BROS. LTD.

DEPTFORD BROADWAY, LONDON, SE8 4QN

SWITCHES

Standard toggle switches:
SW20—S.P.S.T. 20p; SW21—D.P.D.T. 25½p.
Miniature toggle switches:
SW18—S.P.S.T. 51p; SW19—D.P.D.T. 64p.
Slider switches, SW3—D.P.D.T. 15½p.
Wafer switches
(rotary)—26½p each
SW4—1 pole, 12 way.
SW5—2 pole, 6 way.
SW6—3 pole, 4 way.
SW7—4 pole, 2 way.
SW8—4 pole, 3 way.

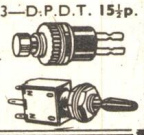

MINIATURE SPEAKERS

2½in 8Ω
2½in 8Ω
2½in 80Ω
All at 68p each.

GROOV-KLEEN

de luxe model 42. £2·15

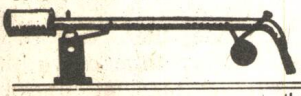

STEREO HEADPHONES

Eagle SE5. 8Ω
40–16,000Hz
Complete with cable and stereo jack plug.
£3·43 Plus 24p p.&p.

PLINTH

to suit Garrard 2025, SP25 etc. Teak finish, complete with Perspex cover. Very attractive appearance.
£3·95 plus 55p p. & p.

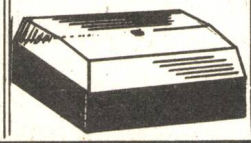

V.A.T.

Prices in this advertisement include V.A.T. If ordering before April 1st please deduct 10% from total order.

10 WATT AMPLIFIER module

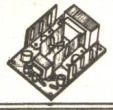

Input: 30mV into 10kΩ for 10W, 40 – 16,000 Hz.
Output: 3-8-16Ω
Power Supply 12V
£4.70 plus 24p p. and p.

J-BEAM FM4S AERIAL

4 element, all channel aerial for stereo radio. £6·10 plus 50p p. & p.

BATTERY HOLDERS

for 4 x HP7.
Long or short—22p.

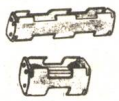

Press studs, ready wired PP3 size—10p; PP9 size—13p.

CONSOLE CASES

in plain aluminium, ideal for mixers, instruments, etc.

Type	W. in	A in	B in	C in	D in	Price p. & p.
GB20	8	9	3½	2	3	£1·56 33p
GB21	10	9	3½	2	3	£1·74 33p
GB22	12	9	3½	2	3	£1·89 33p

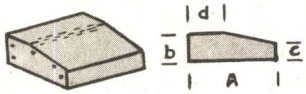

PLASTIC BOXES

for constructional projects. White, with lid and screws.
BP1 4½ins x 3ins x 1½ins—37p.
BP2 6ins x 4ins x 2½ins—37p.

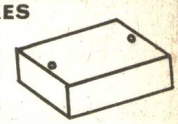

EQUIPMENT CASES

in plain aluminium with sloping front panel.

Type	H.	W.	D.	Price	p. & p.
SF1	2in	5½in	2½in	50p	13p
SF2	2in	7½in	3½in	66p	17½p
SF3	2in	9½in	4½in	83p	20p

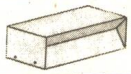

ALUMINIUM BOXES

with lids and screws

Type	L.	W.	D.	Price	p. & p.
GB7*	5½in	2½in	1½in	42p	16p
GB8*	4in	4in	1½in	42p	16p
GB9*	4in	2½in	1½in	42p	14p
GB10*	5½in	4in	1½in	49p	19p
GB11	4in	2½in	2in	42p	14p
GB12	3in	2in	1in	36p	15p
GB13	6in	4in	2in	57p	20p
GB14	7in	5in	2½in	69p	21p
GB15	8in	6in	3in	89p	29p
GB16	10in	7in	3in	£1·00	29p

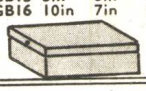

* These sizes fit standard veroboards

DYNAMIC MICROPHONE UD130HL

This sensitive, quality microphone is uni-directional and is complete with mute switch and 20 feet of cable and plug. 100–12,000Hz. Dual impedance 600Ω and 50kΩ.

£6·60 plus 24p p. & p.

MICROPHONE HOLDER

with swivel (as supplied with the mic. above). Fits most tubular mics. and stands. 57p.

MICROPHONE FLOOR STAND

Professional, heavy quality with folding, tripod base. Telescopic stem extends to 59ins. Chrome finish.
£6·25 plus 45p p. & p.

TAPE ERASER

erases a whole reel of tape in seconds. 240V. A.C. Full instructions.
£2·20 plus 22p p. & p.

CATALOGUE

15p

POST FREE

SCREENED CABLES

Single for mics, audio leads, etc. 5½p yd.
Twin, as above, common screen 10p yd.
Stereo, two cores, individually screened 11p yd.
Four core with common screen 23p yd.
Four core, individually screened 30p yd.
Coiled screened leads, 20 feet long £1·05 each.

PLUGS

Car aerial	15½p
Co-axial	10p
D.I.N. 2 pin (speaker)	11p
D.I.N. 3 pin	15p
D.I.N. 4 pin	15½p
D.I.N. 5 pin, 180°	14½p
D.I.N. 5 pin, 240°	16½p
D.I.N. 6 pin	16½p
Jack, 2½mm unscreened	10p
Jack, 2½mm screened	11p
Jack, 3½mm unscreened	9p
Jack, 3½mm screened	13p
Jack, ¼in unscreened	13p
Jack, ¼in screened	22p
Jack, stereo, unscreened	22p
Jack, stereo, screened	38p
Phono, plastic top	5½p
Phono, plated metal	13p
Wander, red or black	3½p
Banana 4mm, red or black	6½p

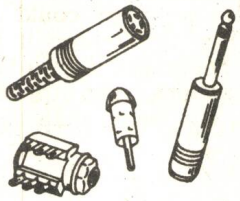

LINE SOCKETS

Car aerial	15½p
Co-axial	19p
D.I.N. 2 pin (speaker)	16½p
D.I.N. 3 pin	17½p
D.I.N. 5 pin, 180°	17½p
D.I.N. 5 pin, 240°	17½p
Jack, 3½mm	16½p
Jack, ¼in screened	54p
Jack, stereo, screened	37p
Phono, plated metal	15½p

SOCKETS

Car aerial	9p
Co-axial, surface	9p
Co-axial, flush	10p
D.I.N. 2 pin (speaker)	11p
D.I.N. 3 pin	10p
D.I.N. 5 pin, 180°	10p
D.I.N. 5 pin, 240°	10p
Jack, 2½mm	11p
Jack, 3½mm	11p
Jack, ¼in unswitched	16½p
Jack, ¼in switched	18½p
Jack, stereo, switched	26p
Phono, single	5½p
Phono, 2 on a strip	7½p
Phono, 3 on a strip	10p
Phono, 4 on a strip	11p
Wander, single, red or black	5½p
Wander, twin strip	7½p
Banana 4mm red, or black	6½p

MINIATURE ELECTROLYTICS

1·0μF	63V	7p	150μF	25V	8p
1·5μF	63V	7p	150μF	40V	13p
2·2μF	63V	7p	150μF	63V	15p
3·3μF	63V	7p	220μF	4V	7p
4·7μF	63V	7p	220μF	10V	7p
6·8μF	40V	7p	220μF	16V	8p
6·8μF	63V	7p	220μF	25V	13p
10μF	25V	7p	220μF	40V	15p
10μF	63V	7p	220μF	63V	22p
15μF	16V	7p	330μF	4V	7p
15μF	40V	7p	330μF	10V	8p
15μF	63V	7p	330μF	16V	13p
22μF	10V	7p	330μF	63V	26p
22μF	25V	7p	470μF	6·3V	8p
22μF	63V	7p	470μF	10V	13p
33μF	6·3V	7p	470μF	25V	15p
33μF	16V	7p	470μF	40V	22p
33μF	40V	7p	680μF	6·3V	13p
47μF	4V	7p	680μF	16V	15p
47μF	10V	7p	680μF	25V	22p
47μF	25V	7p	680μF	40V	26p
47μF	40V	7p	1000μF	4V	13p
47μF	63V	8p	1000μF	10V	15p
68μF	6·3V	7p	1000μF	16V	22p
68μF	16V	7p	1000μF	25V	26p
68μF	63V	13p	1500μF	6·3V	15p
100μF	4V	7p	1500μF	10V	22p
100μF	10V	7p	1500μF	16V	26p
100μF	25V	7p	2200μF	6·3V	22p
100μF	40V	8p	2200μF	10V	26p
100μF	63V	15p	3300μF	6·3V	26p
150μF	6·3V	7p	4700μF	4V	26p
150μF	16V	7p			

TRANSFORMERS

all with 0-250 Volt primaries.

Miniature
MM6 6V, 500mA+6V, 500mA.
MM12 12V, 250mA+12V, 250mA.
MM20 20V, 150mA+20V, 150mA.
£1·42 plus 14p p. & p.

L.T.
LT1 6·3V, 1·5A—82p plus 20p p. & p.
LT2 6·3V, 3A—96p plus 28p p. & p.
LT3 12V, 1·5A—96p plus 28p p. & p.
LT4 12V, 3A—£1·45 plus 33p p. & p.
LT5 9–0–9V, 0·5A—83p plus 23p p. & p.
LT6 12–0–12V, 1A—£1·04 plus 29p p.&p.

Multi-tapped
MT30/2 0–12–15–20–24–30V, 2A— £2·15 plus 33p p. & p.
MT60/1 0–5–20–30–40–60V, 1A—£2·31 plus 33p p. & p.
MT60/2 0–5–20–30–40–60V, 2A—£3·25 plus 37p p. & p.

Speaker Matching 3–8–16Ω
Example: 16Ω speaker to 8Ω amplifier.
99p plus 22p p. & p.

Charger
CT/01 1A—£1·16 plus 28p p. & p.
CT/02 2A—£1·43 plus 33p p. & p.
CT/03 4A—£1·76 plus 33p p. & p.
Secondaries 0–5–11–17V.

VEROBOARD

Size	0·1 Matrix	0·15 Matrix
2½in x 3½in	25½p	18½p
2½in x 5in	28½p	28½p
3½in x 3½in	28½p	28½p
3½in x 5in	32p	35p
17in x 2½in	87p	66p
17in x 3½in	£1·18	94p

Spot face cutter—43p
Pins, either size, pack of 36—21p
Edge connectors:
24 way, 0·1 —37½p
24 way, 0·15—37½p
36 way, 0·1—48½p
16 way, 0·15—25p

BONDED ACRYLIC FIBRE

B.A.F. wadding, 18in wide, 1in thick. The ideal lining for speaker enclosures. 33p per yard. P. & p. 1yd 14p; each extra yard 4p.

CONTROLS

Log. or Lin.
Single, less switch, 15p
Single, D.P. switch, 26p
Tandem, less switch, 44p
5kΩ, 10kΩ, 25kΩ, 50kΩ, 100kΩ, 250kΩ, 500kΩ, 1MΩ, 2MΩ

BATTERY ELIMINATORS

suitable for transistor radios and similar light current equipment. Input 240V. A.C.
Output: PP6—6V D.C.; PP9—9V D.C.
Price £1·65 plus 15p p. & p.

CASSETTE OWNERS!

For Philips and similar cassette recorders.
PU12 power unit for connection to 12V + or — E cars, giving 7½V stabilised output—£3·55+16p p. & p.
PP75 mains power supply, output 7½V D.C.—£2·15 + 16p p. & p.
Both units are complete with cables and 5 pin D.I.N. plug.

CASSETTE MICROPHONE

Low impedance dynamic with remote control switch. Fitted 2½mm and 3½mm plugs. £2·20 plus 15p p. & p.

ELECTROLYTICS

1μF	450V	21p	1000μF	50V	46p
2μF	450V	22p	2000μF	25V	43p
4μF	350V	15½p	2000μF	50V	58p
8μF	450V	18½p	2500μF	25V	50p
16μF	450V	20p	2500μF	50V	66p
25μF	25V	7½p	3000μF	25V	53p
25μF	50V	11p	5000μF	25V	66p
32μF	450V	30p	5000μF	50V	£1·21
50μF	50V	11p	8–8μF	450V	20p
100μF	50V	12p	8–16μF	450V	22p
250μF	25V	15½p	16–16μF	450V	30p
250μF	50V	19p	16–32μF	450V	69p
500μF	25V	20p	32–32μF	450V	54p
500μF	50V	27½p	50–50μF	350V	42p
1000μF	25V	30p			

Build yourself a TRANSISTOR RADIO

WITH AFTER SALES SERVICE

ROAMER 10 WITH VHF INCLUDING AIRCRAFT

10 TRANSISTORS. 9 TUNABLE WAVEBANDS, MW1, MW2, LW, SW1, SW2, SW3, TRAWLER BAND, VHF AND LOCAL STATIONS ALSO AIRCRAFT BAND.

Built-in ferrite rod aerial for MW/LW. Retractable, chrome plated 7 section telescopic aerial, can be angled and rotated for peak short wave and VHF listening. Push-pull output using 600mW transistors. Car Aerial and tape record sockets. 10 transistors plus 3 diodes. Fine tone moving coil speaker. Ganged tuning condenser with VHF section. Separate coil for Aircraft Band. Volume/on/off, wave change and tone controls. Attractive case in black with silver blocking. Size 9in × 7in × 4in.

Easy to follow instructions and diagrams. Parts price list and easy build plans 30p (FREE with parts). Earpiece with plug and switched socket for private listening 30p extra.

TOTAL BUILDING COSTS **£8·50** P.P. & INS. 50p (OVERSEAS P. & P. £1)

ROAMER EIGHT Mk. I

NOW WITH VARIABLE TONE CONTROL

7 TUNABLE WAVEBANDS: MW1, MW2, LW, SW1, SW2, SW3 AND TRAWLER BAND. Built-in ferrite rod aerial for MW and LW. Retractable chrome plated telescopic aerial for short waves. Push-pull output using 600mW transistors. Car aerial and tape record sockets. Selectivity switch. 8 transistors plus 3 diodes. Fine tone moving coil speaker. Air spaced ganged tuning condenser. Volume/on/off, tuning, wave change and tone controls. Attractive case in rich chestnut shade with gold blocking. Size 9in × 7in × 4in approx. Easy to follow instructions and diagrams. Parts price list and easy build plans 25p (FREE with parts). Earpiece with plug and switched socket for private listening 30p extra.

TOTAL BUILDING COSTS **£6·98** P. P. & INS. 45p (OVERSEAS P. & P. £1)

ROAMER SEVEN Mk. IV

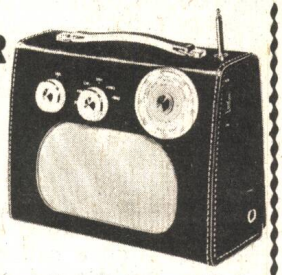

7 TUNABLE WAVEBANDS: MW1, MW2, LW, SW1, SW2, SW3 AND TRAWLER BAND. Extra medium waveband provides easier tuning of Radio Luxembourg, etc. Built-in ferrite rod aerial for MW and LW. Retractable 4 section 24in chrome plated telescopic aerial for SW. Socket for car aerial. Powerful push-pull output. 7 transistors and 2 diodes, including micro-alloy R.F. transistors. Fine tone moving coil speaker. Air spaced ganged tuning condenser. Volume/on/off, tuning and wave change controls. Attractive case with carrying handle. Size 9in × 7in × 4in approx. Easy to follow instructions and diagrams. Parts price list and easy build plans 25p (FREE with parts). Earpiece with plug and switched socket for private listening 30p extra.

TOTAL BUILDING COSTS **£5·98** P. P. & INS. 45p (OVERSEAS P. & P. £1)

ROAMER SIX

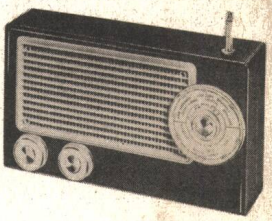

6 TUNABLE WAVEBANDS: MW, LW, SW1, SW2, TRAWLER BAND PLUS AN EXTRA MW BAND FOR EASIER TUNING OF LUXEMBOURG, ETC. Sensitive ferrite rod aerial and telescopic aerial for short waves. 3in speaker. 8 stages—6 transistors and 2 diodes including micro-alloy R.F. transistors, etc. Attractive black case with red grille, dial and black knobs with polished metal inserts. Size 9in × 5¼in × 2¾in approx. Easy build plans and parts price list 25p (FREE with parts).

TOTAL BUILDING COSTS **£3·98** P. P. & INS. 30p (OVERSEAS P. & P. £1)

POCKET FIVE

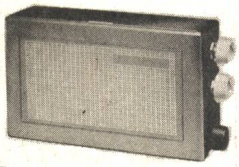

3 TUNABLE WAVEBANDS: MW, LW, TRAWLER BAND WITH EXTENDED MW BAND FOR EASIER TUNING OF LUXEMBOURG, ETC. 7 stages—5 transistors and 2 diodes, supersensitive ferrite rod aerial, fine tone moving coil speaker. Attractive black and gold case. Size 5¼in × 1¾in × 3¼in. Easy build plans and parts price list 10p (FREE with parts).

TOTAL BUILDING COSTS **£2·29** P. P. & INS. 23p (OVERSEAS P. & P. 63p)

TRANSONA FIVE

5 TRANSISTORS AND 2 DIODES

3 TUNABLE WAVE BANDS: MW, LW AND TRAWLER BAND. 7 stage—5 transistors and 2 diodes, ferrite rod aerial, tuning condenser, volume control, fine tone moving coil speaker. Attractive case with red speaker grille. Size 6¼in × 4¼in × 1¼in. Easy build plans and parts price list 10p (FREE with parts).

TOTAL BUILDING COSTS **£2·50** P. P. & INS. 24p (OVERSEAS P. & P. 63p)

TRANS EIGHT

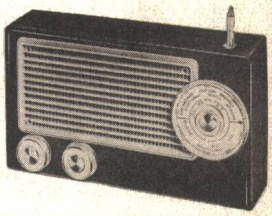

8 TRANSISTORS AND 3 DIODES

6 TUNABLE WAVEBANDS: MW, LW, SW1, SW2, SW3 AND TRAWLER BAND. Sensitive ferrite rod aerial for MW and LW. Telescopic aerial for short waves. 3in speaker. 8 improved type transistors plus 3 diodes. Attractive case in black with red grille, dial and black knobs with polished metal inserts. Size 9in × 5¼in × 2¾in approx. Push-pull output. Battery economiser switch for extended battery life. Ample power to drive a larger speaker. Parts price list and easy build plans 25p (FREE with parts).

TOTAL BUILDING COSTS **£4·48** P. P. & INS. 32p (OVERSEAS P. & P. £1)

NEW! "EDU-KIT"

BUILD RADIOS, AMPLIFIERS, ETC., FROM EASY STAGE DIAGRAMS. FIVE UNITS INCLUDING MASTER UNIT TO CONSTRUCT. Components include: Tuning Condenser: 2 Volume Controls: 2 Slider Switches: Fine tone moving coil Speaker: Terminal Strip: Ferrite Rod Aerial: 2 Plugs and Sockets: Battery Clips: 4 Tag Boards Balanced Armature Unit: 10 Transistors: 4 Diodes: Resistors: Capacitors: Three ¼in Knobs. Units once constructed are detachable from Master Unit, enabling them to be stored for future use. Ideal for Schools, Educational Authorities and all those interested in radio construction. Parts price list and easy build plans 25p (FREE with parts).

ALL PARTS INCLUDING CASE AND PLANS **£5·50** P. P. & INS. 32p (OVERSEAS P. & P. £1)

FULL AFTER SALES SERVICE

★ Callers side entrance "Lavell" Shop
★ Open 10-1, 2.30-4.30 Monday-Friday, 9-12 Saturday
★ VAT PRICE ADJUSTMENTS AS FROM APRIL 1, 1973

RADIO EXCHANGE LTD

61a HIGH ST., BEDFORD MK40 1SA. Tel. 0234 52367

I enclose £..... please send items marked

ROAMER TEN	☐	ROAMER SEVEN	☐
ROAMER EIGHT	☐	TRANS EIGHT	☐
TRANSONA FIVE	☐	ROAMER SIX	☐
POCKET FIVE	☐	EDU-KIT	☐

Parts price list and plans for.....

Name .....

Address .....

..... P.E. 52

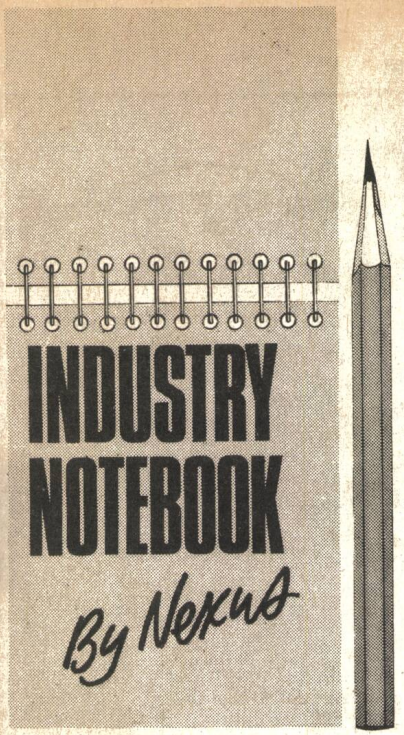

FIRST AWARDS

The Society of Radio and Electronic Technicians, now almost 6,000 strong, has awarded its first three Honorary Fellowships. Proud recipients were Lord Orr-Ewing, Edwin Spreadbury and Kenneth Tempest, all of whom have played a major role in establishing the Society.

The awards were made at a dinner in The Cholmondeley Room, House of Lords, with this year's SERT president, James Redmond, director of engineering BBC, in the chair. Among the distinguished guests were Sir Eric Eastwood, chief scientist and director of research GEC, and Sir Cyril English, director general of the City and Guilds of London Institute.

Of the three Honorary Fellows it was probably "Spread" who enjoyed the distinction most keenly for it was he who helped in the formation of the Radio Trades Examination Board back in 1941 and, later, as chairman of RTEB, he was instrumental in founding SERT of which he became first chairman.

Lord Orr-Ewing, top man in Ultra Electronics, was first president of SERT in 1966 and gave influential support. Immediate past chairman Kenneth Tempest had the satisfaction of seeing membership pass the 5,000 mark during his term of office.

SERT has not wavered in its policy of insisting on good qualifications for members and thus has helped raise the status of technicians and brought them into the professional class of employment.

The properly qualified electronic technician engineer deserves his professional status and quite clearly the work of SERT and the IEETE (which caters more broadly for the electrical technician engineer although many members are in electronics) is important in establishing a better business and industrial status for members.

MAGIC MILLION

A million pounds is a nice round figure for turnover—indeed a magic figure to aim at for those with the guts to go it alone without benefit of shelter from working within a big group.

Bill Coates, top man in Leicester-based component distributor Townsend-Coates gets his taste of magic this year. He started up in 1961 with a first year sales turnover of £2,500, largely to local concerns. Now he has a staff of 46, stocks 16,000 different items from nearly a dozen manufacturers and sells on a nation-wide basis.

Two go-it-aloners who are working on the magic million, although still with some way to go, are Ray Vincent and Jim Griffith. In 1966 they took over ailing Plastronics Ltd., at Watford, a moulding and sub-assembly shop serving the electronics industry. Staff today is 40 after a move to new premises in 1969 and, says Jim, it will be necessary to make another move for expansion before long.

Among the more important customers for Plastronic moulded products are Garrard, BSR, British Radio Corporation, Lotus cars and Scammell lorries. The computer industry is also a big customer.

EXHIBITION NEWS

The first commercial full scale exhibition and conference on Automatic Testing Equipment—fastest growing sector of the instrument industry—will take place at the popular Metropole Convention Centre, Brighton, opening on November 26. Stands are already being booked by leading manufacturers and a call for papers has gone out.

Microwave 73, also at the Metropole is a sell-out. It will be opened officially on June 19 by His Royal Highness the Duke of Kent in his capacity as a member of the National Electronics Council and a Companion of the IERE.

Sir Gerald Narbarro is to hop over to the USA to open Coil Winding-Chicago 73 organised by British-based Electromation Exhibitions Ltd. and opening on March 27. Sir Gerald is first president of the International Coil Winding Association.

The International London Electronic Components Show opening at Olympia on May 22 is to have 350 exhibitors. Biggest stand is occupied by a consortium of French companies who are clearly determined to cash in on the opportunities of the enlarged EEC.

The Soviet Union will be showing valves, passive components and test gear through British agents Z & I Aero Services. Previous showings of Russian components both in the UK and France have left me totally unimpressed—perhaps there will be more of interest this year.

BIPOLAR PROCESS

Plessey's Bipolar Process III technology for integrated circuits has now moved from pilot production at the Allen Clark Research Centre at Caswell, to full production at the main semiconductor plant at Swindon.

Whole families of new devices have been planned and with higher speeds now available a new range of applications has been opened up. Among the first commercially available products are high speed dividers capable of accepting an input of 1·2GHz, and a range of logic circuits compatible with Motorola's MECL III range. Selected variants, say Plessey, have a considerable performance gain over standard MECL III.

The production technique uses an epitaxial layer only 4 microns thick with emitter-base and base-collector junctions well under a micron deep. This is obviously not a cheap process but every milestone on the path to improved performance must exact its price.

HALF CENTURY

Eddystone Radio is approaching its 50th birthday with record growth and a firmer policy than it has had for years. Eddystone's Big Three, managing director Dick Carroll, chief engineer Bill Cooke, and sales manager Ken Wilkins are now dedicated to total solid state equipment and minimum production targets of 10,000 receivers on any new models.

The last of the Eddystone valve receivers, the popular 830, has been delivered and is being superseded by the new solid state 1830 range of general purpose receivers which have already won full approval from the British and a number of other PTT administrations.

During a visit to Eddystone's Birmingham works, I was told that the 958 Series of high-stability receivers, of which over 1,000 have now been delivered, is now available in nine versions. What has given Eddystone this flexibility in production is a big switch to modular construction and this has also had its effect on manufacturing and testing methods.

Designing with Integrated circuits

BY A.FOORD

7 Counters and Displays

WE HAVE spoken in general about digital instrumentation and counters and this month will consider how the counters can be constructed. We will first examine in detail the individual integrated circuits used in a typical decade counter.

SN7490N DECADE COUNTER

The SN7490N consists of four master-slave bistables internally interconnected to provide a divide-by-five and a divide-by-two counter. There are also gated direct reset lines to inhibit the count inputs and return all the outputs to a logical 0 or binary coded decimal (BCD) count of nine.

The output from the first bistable is not internally connected to the next stage, and so three different count modes are possible, Fig. 7.1.

1. The BD input is externally connected to the A output, and the A input receives the incoming count. A count sequence is obtained as shown in the truth table. The outputs can be reset to a conventional zero or to a BCD count of nine for nines complement decimal applications.

2. Where a symmetrical divide-by-ten count is required (the previous arrangement divides by ten, but not symmetrically) the D output is connected to the A input. The input count is applied to the BD input and a divided-by-ten symmetrical square wave is obtained at the A output. The circuit thus divides by five first and then by two.

3. For divide-by-two and divide-by-five operations the two counters can be used independently. Bistable A is used to divide-by-two while the BD input is used to obtain a divide-by-five operation at the B, C, and D outputs. However the

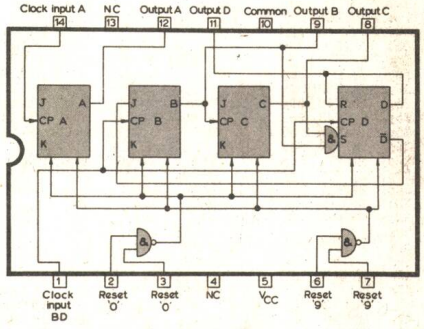

MODE 1 BCD			
A	B	C	D
0	0	0	0
1	0	0	0
0	1	0	0
1	1	0	0
0	0	1	0
1	0	1	0
0	1	1	0
1	1	1	0
0	0	0	1
1	0	0	1

MODE 2 SYMMETRICAL ÷10			
A	B	C	D
0	0	0	0
0	1	0	0
0	0	1	0
0	1	1	0
0	0	0	1
1	0	0	0
1	1	0	0
1	0	1	0
1	1	1	0
1	0	0	1

MODE 3 ÷5		
B	C	D
0	0	0
1	0	0
0	1	0
1	1	0
0	0	1

Fig. 7.1. The three count modes possible with the SN7490N

GLOSSARY

BINARY CODED DECIMAL

A binary numbering system for coding decimal numbers in groups of four bits. The binary value of these four-bit groups ranges from 0000 to 1001 and codes the decimal digits 0 to 9. To count to 9 takes four bits, to count to 99 takes two groups of four bits, etc.

RESET

Also called clear. It is an input which makes the output go to a desired state, usually 0 or 9.

Henry's

YOUR COMPLETE AUDIO-ELECTRONIC STORES

More of everything at the right price. All your electronic requirements within 200 yards – call and see for yourself.

INTEGRATED CIRCUITS

Why buy alternatives when you can buy the genuine article from us at competitive prices from stock. BRANDED FROM TEXAS I.T.T FAIRCHILD

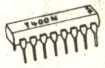

Type	1/11 p	12/24 p	25/99 p
SN7400	0·20	0·18	0·16
SN7401	0·20	0·18	0·16
SN7402	0·20	0·18	0·16
SN7403	0·20	0·18	0·16
SN7404	0·20	0·18	0·16
SN7405	0·20	0·18	0·16
SN7406	0·30	0·27	0·25
SN7407	0·30	0·27	0·25
SN7408	0·20	0·19	0·18
SN7409	0·45	0·42	0·35
SN7410	0·20	0·18	0·16
SN7411	0·23	0·22	0·20
SN7412	0·42	0·40	0·35
SN7413	0·30	0·27	0·25
SN7416	0·30	0·27	0·25
SN7417	0·30	0·27	0·25
SN7420	0·20	0·18	0·16
SN7422	0·48	0·44	0·40
SN7423	0·48	0·44	0·40
SN7425	0·48	0·40	0·35
SN7427	0·42	0·39	0·35
SN7428	0·50	0·45	0·42
SN7430	0·20	0·18	0·16
SN7432	0·42	0·39	0·35
SN7433	0·70	0·61	0·44
SN7437	0·65	0·60	0·50
SN7438	0·65	0·60	0·50
SN7440	0·20	0·18	0·16
SN7441AN	0·75	0·72	0·70
SN7442	0·75	0·72	0·70
SN7443	1·00	0·95	0·90
SN7445	2·00	1·75	1·60
SN7446	2·00	1·75	1·60
SN7447	1·75	1·60	1·45
SN7448	1·75	1·60	1·45
SN7450	0·20	0·18	0·16
SN7451	0·20	0·18	0·16
SN7453	0·20	0·18	0·16
SN7454	0·20	0·18	0·16
SN7460	0·20	0·18	0·16
SN7470	0·30	0·27	0·25
SN7472	0·30	0·27	0·25
SN7473	0·40	0·37	0·35
SN7474	0·40	0·37	0·35
SN7475	0·55	0·52	0·50
SN7476	0·45	0·42	0·39
SN7480	0·80	0·75	0·67
SN7481	1·25	1·15	1·10
SN7482	0·87	0·80	0·70
SN7483	1·00	0·90	0·85
SN7484	0·90	0·85	0·80
SN7486	0·45	0·41	0·38
SN7490	0·75	0·70	0·65
SN7491AN	1·00	0·95	0·90
SN7492	0·75	0·70	0·65
SN7493	0·75	0·70	0·65
SN7494	0·80	0·75	0·70
SN7495	0·80	0·75	0·70
SN7496	1·00	0·97	0·95
SN7497	6·25	5·50	5·00
SN74100	2·50	2·30	2·00
SN74104	1·45	1·35	1·20
SN74105	1·45	1·35	1·20
SN74107	0·50	0·45	0·40
SN74110	0·80	0·70	0·60
SN74118	1·00	0·95	0·90
SN74119	1·90	1·78	1·65
SN74121	0·60	0·55	0·50
SN74122	1·35	1·25	1·10
SN74123	2·70	2·55	2·47
SN74141	1·00	0·95	0·90
SN74145	1·50	1·40	1·30
SN74150	3·35	2·95	2·15
SN74151	1·10	0·95	0·90
SN74153	1·35	1·27	1·20
SN74154	2·00	1·75	1·55
SN74155	1·55	1·47	1·35
SN74156	1·55	1·47	1·35
SN74157	1·80	1·70	1·50
SN74160	2·60	2·40	2·25
SN74161	2·60	2·40	2·25
SN74162	3·40	3·25	2·70
SN74163	3·40	3·25	2·70
SN74164	2·75	2·30	2·10
SN74165	4·00	3·50	3·00
SN74166	4·00	3·50	3·00
SN74167	6·25	5·60	5·10
SN74170	4·10	3·55	3·05
SN74174	2·00	1·75	1·30
SN74175	1·35	1·27	1·15
SN74176	1·60	1·35	1·20
SN74177	1·60	1·35	1·20
SN74180	1·55	1·30	1·20
SN74181	7·00	6·00	5·50
SN74182	2·00	1·80	1·60
SN74184	2·40	2·00	1·80
SN74185A	2·40	2·00	1·80
SN74190	1·95	1·85	1·75
SN74191	1·95	1·85	1·75
SN74192	2·00	1·90	1·80
SN74193	2·00	1·90	1·80
SN74194	2·50	2·25	1·90
SN74195	1·85	1·70	1·60
SN74196	1·50	1·40	1·30
SN74197	1·50	1·40	1·30
SN74198	4·60	3·70	3·35
SN74199	4·60	3·70	3·35

PRICES OF 7400 SERIES ARE CALCULATED ON THE TOTAL NUMBER ORDERED REGARDLESS OF MIX

LARGER QUANTITY PRICES PHONE (01) 402 4891

HIGH POWER SN 74 HOO } Now in stock—send
LOW POWER SM 74 LOO } for list No. 36

A SELECTION OF SEMI-CONDUCTORS FROM STOCK

AAY30	10p	BC147	12p	BU105	2·25	OC44	15p
AAY42	15p	BC169C	12p	BY100	15p	OC45	15p
AAZ13	10p	BC182	10p	BY126	15p	OC57	50p
AC107	35p	BC214	15p	BY127	15p	OC71	15p
AC126	25p	BCY32	75p	BYZ13	35p	OC72	25p
AC127	25p	BCY34	35p	C106D	65p	OC77	45p
AC128	25p	BCY39	1·00	GET111	55p	OC81	25p
AC176	25p	BCY42	30p	GET115	55p	OC83	25p
AC187	25p	BCY43	25p	GET880	45p	OC140	55p
AC188	25p	BCY55	2·50	LM309K (T03)	1·87	OC170	25p
ACY17	30p	BCY70	15p	MAT121	25p	OC171	30p
ACY20	20p	BCY71	20p	MJE340	50p	OC200	45p
ACY21	20p	BCY72	15p	MJE370	70p	OC201	75p
ACY39	55p	BCY87	2·99	MJE520	75p	OC202	80p
AD140	50p	BCZ11	50p	MJE2955	1·10	OC203	50p
AD149	50p	BD124	80p	MJE3055	75p	OCP71	1·25
AD161	35p	BD131	75p	MPF105	40p	ORP12	50p
AD162	35p	BD132	80p	NKT214	20p	ORP60	40p
AF117	20p	BF115	25p	NKT216	40p	P346A	20p
AF118	50p	BF167	25p	NKT217	40p	RAS310AF	45p
AF124	25p	BF173	25p	NKT403	70p	RAS508AF	55p
AF139	30p	BF179	30p	NKT404	50p	TAA263	75p
AF186	40p	BF180	30p	OA5	50p	TIL209	39p
AF239	40p	BF194	15p	OA10	35p	TIP29A	50p
ASY27	30p	BF195	15p	OA81	10p	TIP30A	60p
ASY28	25p	BF861	25p	OA91	7p	TIP31A	60p
BA102	30p	BF898	25p	OA200	7p	TIP32A	70p
BA115	7p	BFX13	25p	OA202	10p	TIP33A	1·00
BA145	15p	BFX34	75p	OC16	75p	TIP34A	1·50
BAX13	5p	BFX37	30p	OC20	95p	TIP35A	2·50
BAX16	7p	BFX88	20p	OC23	85p	TIP36A	3·00
BC107	10p	BFY50	20p	OC25	40p	TIP41A	75p
BC108	10p	BFY51	20p	OC28	65p	TIP42A	85p
BC109	10p	BFY52	20p	OC35	50p	2N3054	50p
BC109C	12p	BFY64	50p	OC36	65p	2N3055	55p
BC113	15p	BFY90	59p	OC42	40p	2N3440	75p
BC117	20p	BLY36	8·00			2N3442	1·25
BC143	35p	BSX20	15p			2N3525	75p
		BSY27	15p			2N3614	59p
						2N3615	75p
						2N3702	10p
						2N3704	10p
						2N3705	10p
						2N3714	1·80
						2N3771	1·75
						2N3773	2·00
						2N3790	2·25
						2N3819	35p
						2N3820	50p
						2N3866	85p
						2N3903	15p
						2N3906	12p
						2N4061	12p
						2N4062	12p
						2N4126	15p
						2N4871	35p
						2N5457	30p
						2N5777	55p
						28001	1·00
						28012	10·00
						28018	6·25
						28026	8·90
						28301	50p
						28303	65p
						28324	95p
						40250	50p
						40360	40p
						40361	40p
						40362	50p
						40408	50p
						40486	75p
						40636	1·10
						40430	1·00

VAT

Prices DO NOT include Value Added Tax. From 1st April 10% must be added and shown separately to your total order (inclusive post/packing). Help us help you receive your order without delay.

QUANTITY DISCOUNTS

10% 12+ ; 15% 25+ ANY ONE
20% 100+ ; 25% 250+ TYPE

From above sections except Integrated Circuits and Special Offers where discounts are included.

Minimum order value £1 please.
Postage 7p on all orders.

SPECIAL OFFERS! SEMI-CONDUCTORS

BFY90 59p
1000 MC/S
25 + 20p
100 + 17p
500 + 15p

AF117 Mullard 25p
25 + 17p
100 + 15p
500 + 12p

OC170 Mullard 25p
25 + 20p
100 + 18p
500 + 15p
1000 + 13p

BY127 Mullard 15p
25 + 12p
100 + 10p
500 + 9p
1000 + 8p

OA202 10p
25 + 8p
100 + 7p
500 + 6p
1000 + 5p

OC35 Mullard 50p
25 + 45p
100 + 40p
500 + 35p
1000 + 30p

2N2926 10p
All Colours
25 + 9p
100 + 8p
500 + 6p
1000 + 5p

2N3819 Texas 35p
25 + 30p
100 + 25p
500 + 20p
1000 + 15p

BC107, BC108, BC109 10p each
All Makes
25 + 8p
100 + 7p
500 + 6p
1000 + 5p

AD161, AD162 35p each
25 + 32p
100 + 28p
500 + 25p
1000 + 22p

2N3053 20p
25 + 18p
100 + 15p
500 + 12p
1000 + 10p

2N3055 55p
25 + 50p
100 + 45p
500 + 38p
1000 + 33p

ZENER DIODES

400 M/W 5% Miniature
BZY 88 Range

All voltages 3·3 – 33 Volt
10p each.

25+	9p
100+	8p
500+	6·5p
1000+	5p

Any one type.

1½ Watt 5% Wire Ends Metal Case
All voltages 6·8 – 100 Volts
20p each

25+	18p
100+	16p
500+	12p
1000+	10p

Any one type.

3 Watt Plastic Wire Ends 5%
3EZ Range

All voltages 6·8 – 100 Volts
30p each.

SILICON RECTIFIERS WIRE ENDED PLASTIC

Type	P.I.V.	1-11
1 amp miniature		
IN4001	50	6
IN4002	100	7
IN4003	200	8
IN4004	400	8
IN4005	600	10
IN4006	800	12
IN4007	1000	15
1·5 amp miniature		
PL4001	50	8
PL4002	100	9
PL4003	200	10
PL4004	400	10
PL4005	600	12
PL4006	800	15
PL4007	1000	16

LINEAR (O/P AMPS)

702C	TO5	75p
709C	TO99	35p
709C	D.I.L.	35p
723C	TO99	£1·00
723C	D.I.L.	95p
725C	TO99	£4·50
741C	TO99	55p
741C	D.I.L.	55p
747C	TO99	£1·10
747C	D.I.L.	£1·10
72741P	D.I.L.	60p
72748P	D.I.L.	60p

SINCLAIR IC12 £1·80

TOSHIBA TH9013P

20 WATT AMP £4·47 POST PAID

TH9014P Pre Amp £1·50

DATA AND CIRCUITS REF. 42 10p

FREE WITH PURCHASES

TRANSISTORS, IC's, TRIACS, BRIDGES, SCR's, LDR's

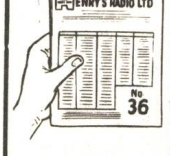

NEW FREE BOOKLET (No. 36) OVER 1500 TYPES—

Send for yours today!

PLESSEY INTEGRATED CIRCUIT
3 Watt Amplifier SL403 D
Complete with 8-page booklet, circuits and data
£1.50 each

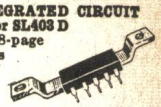

TRIACS

STUD WITH ACCESSORIES

Type	Volts P.I.V.	Price 1-11
3 AMP RANGE		
SC35A	100	75p
SC35B	200	79p
SC35D	400	85p
6 AMP RANGE (TO48)		
SC40A	100	85p
SC40B	200	90p
SC40D	400	£1·00
SC40E	500	£1·20
10 AMP RANGE (TO48)		
SC45A	100	95p
SC45B	200	£1·00
SC45D	400	£1·25
SC45E	500	£1·45
15 AMP RANGE (TO48)		
SC50A	100	£1·25
SC50B	200	£1·35
SC50D	400	£1·65
SC50E	500	£1·85
DIAC D32	25p	
TRIACS—		
Additional Types		
40430	(TO66)	85p
40669	(Plastic)	£1·00
40486	(TO5)	80p

NEW BRIDGE RECTIFIERS

SMALL SIZE AND LOW COST

Type	Volts P.I.V.	Price 1-11
HALF AMP		
BO5/05	50	20p
BO5/10	100	25p
ONE AMP ¼ × ¾ H TUBULAR		
B1/05	50	25p
B1/10	100	25p
B1/20	200	30p
B1/60	600	35p
ONE AMP (G.I.) TUBULAR		
W005	50	30p
W01	100	35p
W02	200	40p
W06	600	45p
TWO AMPS ½ H × ½ L × ⅛		
B2/05	50	35p
B2/100	100	40p
B2/200	200	45p
B2/600	600	50p
B2/1000	1000	60p
FOUR AMPS ½H × ½L × ⅛		
B4/100	100	60p
B4/200	200	65p
B4/400	400	70p
B4/600	600	75p
B4/800	800	£1·00
SIX AMPS ½H × ½L × ⅛		
B6/100	100	70p
B6/200	200	75p
B6/400	400	90p
B6/600	600	£1·00

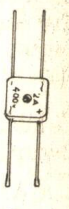

SILICON CONTROLLED RECTIFIERS

Type	Volts P.I.V.	Price 1-11
ONE AMP		
CRS 1/05	50	25p
CRS 1/10	100	30p
CRS 1/20	200	30p
CRS 1/40	400	35p
CRS 1/60	600	45p
THREE AMP (TO48)		
CRS 3/05	50	30p
CRS 3/10	100	30p
CRS 3/20	200	35p
CRS 3/40	400	45p
CRS 3/60	600	55p
FIVE AMP (TO66)		
CRS 5/400	400	60p
SEVEN AMP (TO48)		
CRS 7/100	100	60p
CRS 7/200	200	65p
CRS 7/400	400	70p
CRS 7/600	600	95p
SIXTEEN AMP		
SCR 16/100	100	65p
SCR 16/200	200	70p
SCR 16/400	400	80p
SCR 16/600	600	£1·00

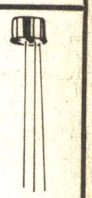

Henry's RADIO LIMITED

EDGWARE ROAD, W2

404-406 Electronic Components and Equipment 01-402 8381
354-356 High Fidelity and Tape Equipment 01-402 5854/4736
309 PA-Disco-Lighting High Power Sound 01-723 6963
303 Special offers and bargains store
All mail to 303 Edgware Road, London W2 1BW

Open:- 9 am-6 pm 6 days a week (309 closed Thursday) All stores open all day Saturday

"Where can I get exclusive units at lowest prices?"...

ROC ELECTRONICS!

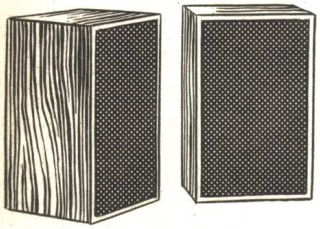

R.088 MATCHED STEREO LOUD SPEAKERS. Here's real value in stereo speakers! Each unit comes complete with 10-foot lead and phono plug, and look really smart. Power handling per speaker: 4 watts rms, 8 watts peak. Frequency range: 40-16,000 Hz. Flux density: 8,500 gauss. Impedance: 8 ohms. Dimensions: 9" high, 5¼" wide, 4¼" deep. Finish: oiled walnut.
ROC PRICE £9·50 pair.
Normal Price £10·75

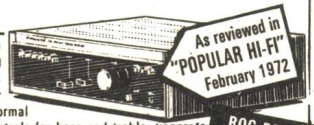

REALISTIC 30 WATT STEREO AMPLIFIER MODEL SA-500
A superb hi-fi amplifier with all the features you've ever wanted – for under £46·00. Saving over £10·00 on the normal retail value. Up-to-the-minute slider controls for bass and treble. Separate volume and balance controls. Headphone socket on front panel. Push-button input controls – magnetic phono (high/low) tuner, aux, mono, monitor. Loudness push-button control for perfect sound at low output levels. Left and right push-button on/off switches for speakers. Noise filtering and tape monitoring facilities. Two auxiliary AC outlets. Frequency response 20-20,000 Hz ± 1 db at full power. 15 watts rms per channel. Walnut cabinet with satin aluminium trims. Inputs: phono 2·5mV and 5mV RIAA; tuner/aux 250mV. Hum and noise: phono – 50db; tuner/aux – 65db. How's that for a specification! Size 14¼" wide, 3½" high, 10½" deep.
ROC PRICE £35.20
Normal Price £55·50

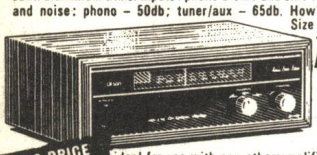

OLSON RA-310 AM/FM/MPX STEREO TUNER
This ROC Tuner is especially designed to match the Olson AM-395 Stereo Amplifier. In price and value, as well as it's good looking design! But of course it's also ideal for use with any other amplifier. The RA-310 costs £10·00 less than the normal retail value, and yet it is a highly sophisticated unit, incorporating the latest solid state techniques. Operation is drift free for supreme station-holding capability. You can connect this Tuner to a stereo amplifier, to a tape deck or a tape recorder. And of course it covers all the stations in the AM and FM bands. FM: 87-108 MHz; AM: 525-1605 kHz. FM Sensitivities: FM, 3μV; AM, 250μV. Stereo separation 30dB at 1kHz, image rejection 60dB. Size: 11⅞" wide, 4" high, 7½" deep.
ROC PRICE £31.20
Normal Price £50·00

REALISTIC SA-1008 6-WATT STEREO AMPLIFIER
Here's fabulous, exciting value in miniature! This high quality stereo amplifier measures only 9" wide × 3" high × 5¾" deep. And yet it has separate ganged volume, balance and tone controls. Plus speaker in/out, mono/stereo, phono/tuner and power on/off slide switches. The ends are oiled walnut, with matching enamelled metal top. The front panel is satin aluminium and walnut-brown enamel. Frequency response is 50 to 10,000 Hz ± 3dB. Output 3 watts r.m.s. per channel into 8 ohms. Inputs are 100mV for both phono and tuner.
ROC PRICE £12.45
Normal Price £21·00

SPECIAL OFFER!

TEC HR-007 HEADPHONE RADIO
When you want to listen to the radio all by yourself. Then this will solve the problem. Separate volume and tuning controls with easy-to-use knobs. Frequency range is 535 to 1605 kHz medium wave band. Maximum output is 300 mW.
Normal Price £7·65 **ROC PRICE £5.80**

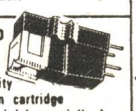

EAGLE LC.07 STEREO MOVING-MAGNET CARTRIDGE
Here's your opportunity to own a transcription cartridge for the price of a ceramic! Is specially designed to match top quality tone arms, and to get the very best from your hi-fi amplifier. 0·7 mil diamond stylus. Output: 7mV per channel. Frequency range: 20-21,000 Hz. Channel balance: ± 1dB. Channel separation: 28dB. Compliance: 12 × 10-6 cm/dyne.
ROC PRICE £6·37

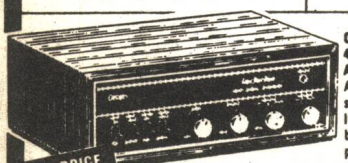

OLSON AM-395 40-WATT STEREO AMPLIFIER
An ideal unit for your new stereo separate system. It is more than £10·00 below the normal retail price! Making the AM-395 one of Britain's best hi-fi buys. It takes in signals from magnetic or ceramic pick-ups, tuners (see Olson RA-310) and tape decks. And it's got outputs for taping and for headphones. There are separate bass and treble controls, separate Left and Right channel volume controls. And a loudness switch for boosting the bass and treble notes when listening at low output levels. Frequency response: 20-20,000 Hz ± 3dB. Output: 20 watts r.m.s. per channel into 8 ohms. Inputs: magnetic phono 3·0mV RIAA, crystal phono 100mV; tape 160mV; tuner 160mV. Size 11⅞" wide, 4" high, 7½" deep. The specification reads well – sounds even better!
ROC PRICE £24.10
Normal Price £39·60

A-3000 36-WATT SOLID STATE STEREO AMPLIFIER
The A-3000 looks as good as it sounds! Giving you a big performance this superb audio amplifier has a full range of facilities on the front and rear panels. On the front – all the controls you're ever likely to need plus a headphone socket. On the rear – signal inputs, speaker outputs and a line fuse for circuit protection.
Specifications: 18 watts rms per channel into 8 ohms. Frequency response 20-35,000 Hz (± 2db) Inputs Magnetic, Ceramic, Tuner, Tape, Aux. Tape Play. Size: 345mm × 300mm × 130mm.
ROC PRICE £28.00
Normal Price £35·70

CONSTRUCTORS' KITS

TWO TRANSISTOR RADIO KIT
Complete with solar cell
£2·50

10 PROJECT INTEGRATED CIRCUIT KIT
Build a radio, morse key, etc.
£3·50

SOLAR ELECTRONIC KIT
20 ways of harnessing the sun's energy
£4·50

TWO OCTAVE ELECTRONIC ORGAN KIT
Make your own music. Complete with speaker
£4·50

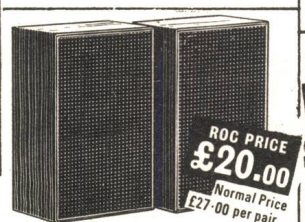

R.446 3-WAY MATCHED SPEAKERS
These will do justice to your amplifier – and to your pocket. At only £20·00 a pair, they are real value-for-money. Each cabinet is heavily lagged and teak finished. They handle 16 watts rms (8 watts rms each). Each loudspeaker contains a 6½" base unit plus tweeter. Frequency range: 40 to 19,000 Hz. Size 14" high, 9" wide, 6½" deep.
ROC PRICE £20.00
Normal Price £27·00 per pair.

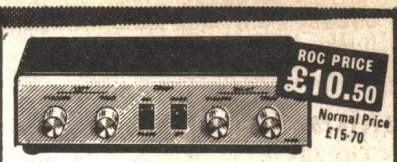

OLSON AM400 4-WATT STEREO AMPLIFIER
Here's marvellous value for someone just starting to set themselves up in audio! At only £10·50, you get a fine amplifier in a scratch resistant metal cabinet, with a smart brushed aluminium front panel. It incorporates separate tone and volume controls for each channel. Inputs are provided for turntable (ceramic cartridge), tuner and tape deck or recorder. Frequency response: 70-20,000 Hz ± 3dB. Output: 2 watts r.m.s. per channel into 8 ohms. Inputs: phono 80mV; tuner/aux 80mV. Size 8" wide, 2½" high, 4½" wide.
ROC PRICE £10.50
Normal Price £15·70

25-WATT 3-WAY CRYSLER 'LIVING AUDIO' SPEAKER CE-5b
This high quality speaker has its own built-in 3-way sound response switch, giving you the ideal frequency response for hi-fi, natural or mood music listening. Its beautiful, heavy, oiled walnut cabinet incorporates two separate speaker units an 8" woofer, and a 5" mid-range with 2" concentric tweeter. Power handling capacity: 25 watts r.m.s into 8 ohms. Overall frequency response: 35-20,000 Hz. Cabinet size: 10½" × 7½" × 8¾". Exactly right for matching the most modern decor.
ROC PRICE £27.25
Normal Price £39·95 each.

PALACE AM/FM/MPX STEREO TUNER AMPLIFIER SSA-16
This is one of the lowest priced stereo tuner amplifiers on the market. It covers the full range of both AM and FM broadcast frequencies. And when you're switched to FM, an indicator lights up when a stereo signal is received – that's the time to switch to 'Stereo'! The SSA-16 has all the facilities you'd expect to find on tuners costing twice as much – separate volume, bass, treble, balance and tuning controls. Selector switch for tape, phono, AM, FM, stereo. Jack socket on front panel for stereo headphones. Frequency range: FM 88-108 MHz. AM 535-1605 kHz. Frequency response: 50-10,000 Hz ± 3dB. Power output: 4 watts total music power into two 8 ohm speakers. Size: 16" wide, 4½" high, 8" deep.
ROC PRICE £27.55
Normal Price £42·00

ROC 7-WATT STEREO AMPLIFIER CHASSIS SK-317
This exclusive ROC Stereo Chassis is completely self-contained, and it costs £2·25 less than the normal retail value! The SK-317 is a really compact unit measuring only 5½" wide, 1⅞" high and 6¾" deep. It contains its own mains power supply, and has a ganged volume control and separate treble controls for each channel. Specification: frequency response 40-17 000 Hz ± 3dB; output 3·5 watts music power per channel into 8 ohms; input, phono, 600mV; signal-to-noise ratio better than 45dB.
ROC PRICE £5.50
Normal Price £7·75

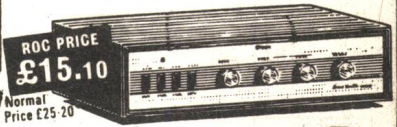

OLSON AM-372 16-WATT STEREO AMPLIFIER
Here's a really good amplifier at a really down-to-earth price – nearly £7 less than the normal retail value! Just look at what the AM-372 will do for you – reproduce signals from ceramic or crystal cartridges, AM and FM tuners, and tape recorders. And it gives you outputs for two sets of speakers, headphones and tape recorders. Frequency response is 30 to 20,000 Hz ± 3dB. Output 3 watts r.m.s. per channel music power into 8 ohm speakers. Phono input 200mV. Tuner input 200mV. Size: 12¼" wide, 3¼" high, 7¼" deep.
ROC PRICE £15.10
Normal Price £25·20

ROC ELECTRONICS LTD

N. JORY Esq. 193 EDGWARE RD, LONDON, W2 1ET. 01-723 6211
CALLERS WELCOME 9–6 MON. TO SAT.
ALSO AT 87 TOTTENHAM COURT RD. LONDON W1
TEL: 01-580 3739 OPEN 9–6 MON.–FRI. SAT. 9–1

Buy it with your BARCLAYCARD

Return-of-post mail order service from Edgware Road. Orders over £10 post free (UK only). Add 25p for p & p to orders under £10. HP terms available for callers

counters are reset simultaneously because the reset lines are common.

SN7475N QUADRUPLE BISTABLE LATCH

The SN7475N is a bistable latch which is used as a temporary store for binary information, Fig. 7.2. Information which is present at a data input (D) is transferred to the Q output while the clock is high. The Q output follows the data for as long as the clock is high but the last information is retained at the data output when the clock goes low.

SN74141N DECODER-DRIVER

The SN74141N is one of several decoder-drivers available in the TTL range and is designed to drive

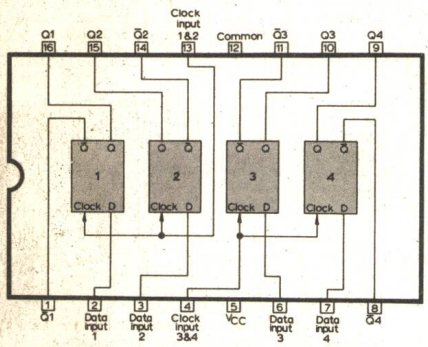

TRUTH TABLE (Each Latch)	
t_n D	t_{n+1} Q
1	1
0	0

Fig. 7.2. The SN7475N quadruple bistable latch (t_n = bit time before clock negative-going transition, t_{n+1} = bit time after clock negative-going transition)

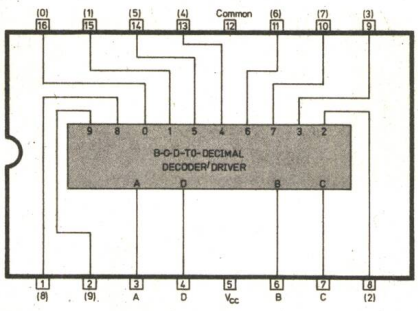

Fig. 7.3. The SN74141N decoder-driver for cold cathode indicators

TRUTH TABLE

INPUT				OUTPUT ON
D	C	B	A	
O	O	O	O	O
O	O	O	I	I
O	O	I	O	2
O	O	I	I	3
O	I	O	O	4
O	I	O	I	5
O	I	I	O	6
O	I	I	I	7
I	O	O	O	8
I	O	O	I	9
I	O	I	O	NONE
I	O	I	I	NONE
I	I	O	O	NONE
I	I	O	I	NONE
I	I	I	O	NONE
I	I	I	I	NONE

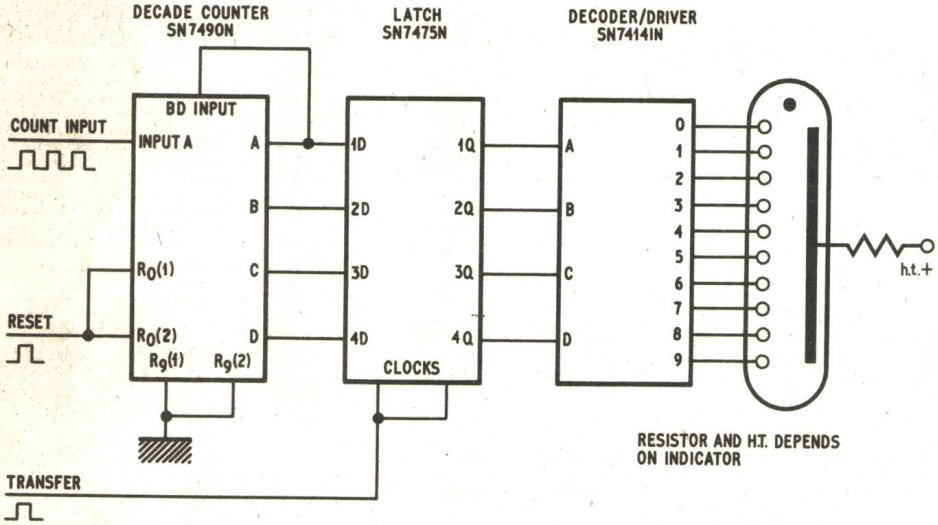

Fig. 7.4a. A typical counting module

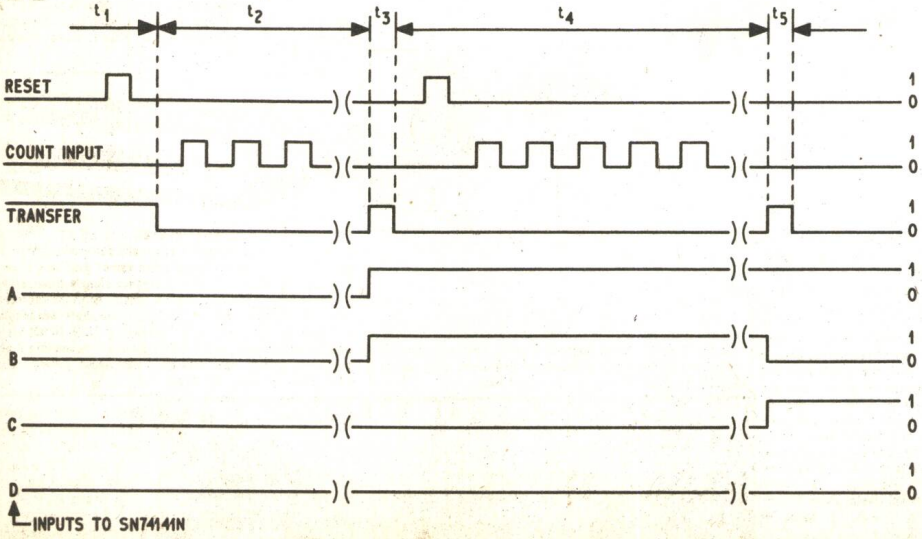

Fig. 7.4b. Typical waveforms in the circuit above

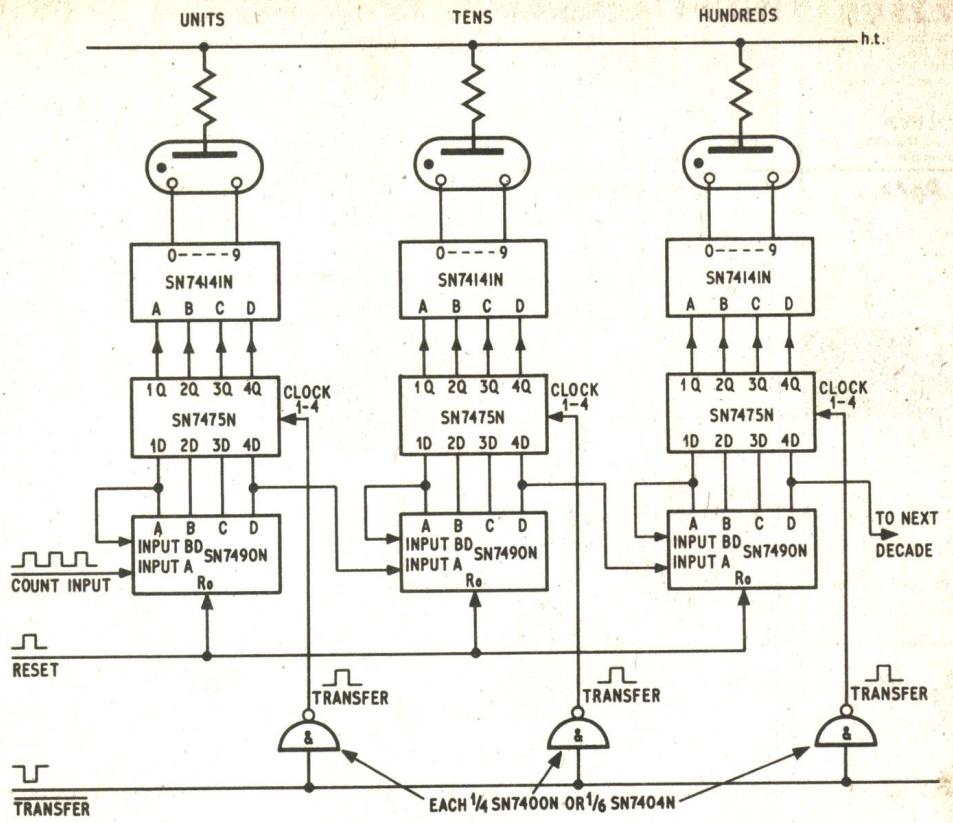

Fig. 7.5. Cascading the modules for multi-decade operation

cold cathode indicator tubes. It accepts a BCD input which it decodes to drive the cathodes of an indicator tube without the need for external components, as in Fig. 7.3.

SINGLE COUNTER MODULE

A typical application for a single counting module is shown in Figs. 7.4a, b, with the counting sequence.

(a) During t_1 the decade counter is reset to 0.

(b) During t_2 a BCD count of three is available at the output of the SN7490N, but the indicator still displays 0.

(c) At the start of t_3 the indicator will display 3, and at the end of t_3 the BCD count of three is committed to the memory of the SN7475N. The decade counter is free to count again.

(d) During t_4 the decade counter is reset to 0 and will then repeat the cycle to display five.

For multi-decade operations the modules may be cascaded as shown in Fig. 7.5.

PRACTICAL DETAILS

For those constructors who wish to experiment with these applications, R.S. Components produce the three integrated circuits, a printed circuit board, and the indicator tube.

The 5V logic supply and the h.t. can be derived from a transformer which gives 6·3 volts and 250 volts.

For testing purposes the reset and transfer lines may be derived from switches, and the input signal derived from a Schmitt trigger SN7413N oscillator.

FAN-IN PROBLEMS

(a) RESET (SN7490)

The reset line of the SN7490 can have a fan-in of one if the other reset input is returned to V_{CC}, so that an SN7400 (fan-out of 10) can drive an adequate number of decades.

(b) COUNT INPUTS (SN7490)

The A or BD inputs of the SN7490 can be driven from an SN7400.

(c) TRANSFER CLOCK (SN7475)

The transfer line of each SN7475 has a fan-in of eight (two per latch). The solution is to use one quarter of an SN7400 for each SN7475 package or to use a buffer (such as the SN7437 or SN7440) which has a fan-out of 30.

CONCLUSION

This article has shown how three integrated circuits can be used to interface with cold cathode indicator tubes. Where the intermediate outputs are not required the new SN74142N combines these three circuits into one 16 pin dual-in-line package, with a considerable space saving.

For driving displays other than cold cathode indicators the SN74141N would be replaced by one of the other drivers in the range. Although seven segment indicators (for example) are popular because they only need a 5V rail, cold cathode indicator tubes are still preferred by many people, since the required h.t. is not difficult to provide.

2N414 £1.25 POST FREE

The I.C. Radio in a TO18 can. Supplied complete with data sheet No. 10 which contains specification, circuit and details and prices of components such as ferrite rods, compression trimmers etc.

I.C. Sockets

Dual-in-line or Zig-Zag (Quil), 14 and 16 pin
Our Price 1p per pin

Slider Pots

Single	Dual	log
10K	10 + 10K	or
25K	25 + 25K	lin
50K	50 + 50K	
100K	100 + 100K	Knobs
30p	50p	10p.

NEW LISTS

LOUDSPEAKERS	No. 4
COILS AND INDUCTORS	No. 5
TRANSFORMERS	No. 6

(postage 5p)

Diodes & Rectifiers

AA119	9p	BA156	15p	BY176	£1·50
AA120	9p	BA243	56p	BY182	£1·50
AA129	9p	OA47	10p	BY250	23p
BA102	25p	OA79	9p	IN4001	6p
BA115	17p	OA90	7p	IN4002	7p
BA130	10p	OA91	7p	IN4003	8p
BA145	20p	OA200	10p	IN4004	8p
BA148	20p	BY100	15p	IN4005	10p
BA154	13p	BY126	15p	IN4006	12p
BA155	14p	BY127	15p	IN4007	15p

FM TUNER chassis fully transistorised 9 volt operation. **OUR PRICE £6·25**
Matching stereo decoder **£4·97**
Ask for model list No. 11.

VDR's & Thermistors

A15B	75p	GL23	£1·00	VA1005	15p
CZ1	15p	R53	£1·32	VA1026	13p
CZ4	13p	R54	£1·46	VA1033	13p
CZ13A	13p			VA1040	10p
E298 ED/A258	10p			VA1053	10p
E298 ZZ/06	10p			VA1055S	10p
GL16	£1			VA1034	10p

Resistors

½ watt 5% Carbon Film – low noise Hi-Stabs
All E24 values 1p each plus p. & p. 7p for up to 50 Resistors and a further 2p for each additional 50. Deduct 33⅓% for 100 of one type or 25% for mixed orders over £1 in value.

1 W	10% Carbon Composition	3p each
2 W	10% Carbon Composition	6p each
2½ W	5% Wire wound	9p each
5 W	Wire wound	9p each
10 W	Wire wound	10p each

plus p. & p. 7p for up to 25 resistors plus 1p for each additional 25.

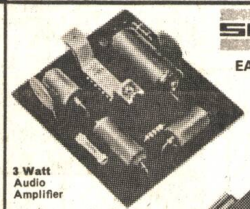

3 Watt Audio Amplifier
Our Price inc. handbook **£2·49**

10+ less 15%
25+ less 25%
100+ less 33⅓%

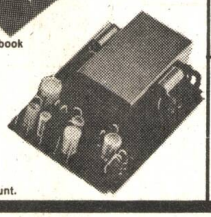

5 Watt Audio Amplifier
Our Price **£3·99**
Less quantity discount.

Potentiometers

5KΩ	50KΩ	500KΩ
10KΩ	100KΩ	1MΩ
25KΩ	250KΩ	2MΩ

log or lin less switch (& 1KΩ lin)	12p
log or lin with switch	24p
dual less switch	40p
dual with switch 10K, 100K & 1M log only	52p
10K log + 10K antilog less switch	40p

Eliminators

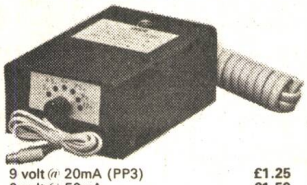

9 volt @ 20mA (PP3)	£1.25
6 volt @ 50mA	£1.50
9 volt @ 50mA	£1.50
6 + 6 volt, 50mA	£2.50
9 + 9 volt, 50mA	£2.50
7½ volt for cassette recorders	£2.00
6, 7½ or 9 volt	£3.00
3, 4½, 6, 7½, 9, 12 @ 500mA (illus.)	£3.99

Car Battery Converter **fully stabilised** to provide 6, 7½ or 9 volts £4.99
(p. & p. **15p** on all types)

Presets

Vertical or Horizontal

0·1 watt **5p**	0·25 watt **7p**			
100	1K Ω	10K Ω	100K Ω	1M Ω
250	2·5K Ω	25K Ω	250K Ω	2·5M Ω
500	5K Ω	50K Ω	500K Ω	5M Ω

Capacitors

dise ceramic		low voltage	
·01μF 18v	5p	0·1μF 30v	5p
·022μF 18v	5p	0·22μF 6v	5p
·047μF 12v	5p	0·47μF 3v	5p
ceramic plate		**30V**	
1000pf	10p	4700pf	10p
2200pf	10p	10,000pf	10p

Ceramic – plate			63V (C333)	
1·8pf	8·2pf		33pf	120pf
2·2pf	10pf		39pf	150pf
3·3pf	12pf		47pf	180pf
3·9pf	15pf		56pf	220pf
4·7pf	18pf		68pf	270pf
5·6pf	22pf		82pf	330pf
6·8pf	27pf		100pf	

all 5p. each

mylar film		100V			
1000pf	2p	·01μF	3p	·068μF	4p
2000pf	2p	·02μF	3p	·1μF	4p
5000pf	2p	·04μF	3p	·2μF	5p
		·05μF	3p		

polystyrene 160V
10pf to 10,000pf in multiples of 10, 15, 22, 33, 47 & 68. **3p each**

metallised polyester	250V (C280)				
·01μF	3p	·068μF	3½p	·47μF	8p
·015μF	3p	·1μF	4p	·68μF	11p
·022μF	3p	·15μF	4p	1μF	13p
·033μF	3p	·22μF	5p	1·5μF	20p
·047μF	3p	·33μF	6½p	2·2μF	24p

metallised polyester	400V (C281)				
·01μF	4½p	·047μF	6p	·22μF	10p
·015μF	4½p	·068μF	6p	·33μF	14p
·022μF	4½p	·1μF	7p	·47μF	15p
·033μF	5½p	·15μF	8p		

silvered mica 1% (>50pf) 500V			
2·2pf—820pf	7p	4·7nF—5600pf	19p
1nF—2·2nf	9p	6800pf—·01μF	29p
2·7nF—3·6nF	16p		

mixed dielectric	600V		
·01μF	7p	·047μF	7p	·22μF	16p
·022μF	7p	·068μF	8p	·47μF	24p
·033μF	7p	·1μF	8p	1μF	33p

mixed dielectric	1000V				
1000pf	6p	6800pf	9p	·1μF	12p
2200pf	6p	·01μF	9p	·22μF	22p
3300pf	6p	·022μF	9p	·47μF	30p
4700pf	6p	·047μF	12p		

Ceramic					
12KV.d.c.		8KV.d.c.		HI-K 750V.	
10pf	9p	200pf	9p	1000pf	5p
15pf	9p	220pf	9p	1500pf	5p
22pf	9p	250pf	9p	2000pf	5p
68pf	9p	270pf	9p	3000pf	5p
82pf	9p	300pf	9p	5000pf	5p
100pf	9p	750V DISC		10,000pf	5p
120pf	9p	470pf	5p	feed-through	
140pf	9p	1000pf	5p		
150pf	9p	5000pf	5p		
180pf	9p	10,000pf	5p	1000pf	5p

CHROMASONIC electronics

MAIL ORDERS: Where no p. & p. charge is shown, a minimum of 7p applies, p. & p. on overseas orders is charged at cost.
ADDRESS TO: **M. O. Dept.**
56, Fortis Green Road, London, N10 3HN.
Telephone 01-883 3705

Heat Sinks

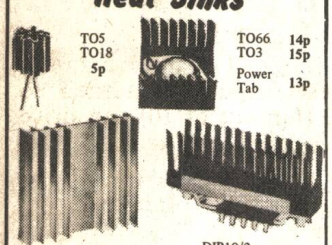

TO5 TO18 5p
TO66 TO3 14p 15p
Power Tab 13p
10D 50p
DIP10/2 for SL403D 15p

Veroboard

	Copperclad 0.1"	Copperclad 0.15"	Plain 0.15"
2½" x 1"	6p	6p	–
2½" x 3¾"	20p	16p (9)	10p
2½" x 5"	24p	21p (7)	12p
3¾" x 3¾"	24p	21p (8)	–
3¾" x 5"	27p	27p (10)	17p
17" x 2½"	67p	50p	37p
17" x 3¾"	90p	70p	52p
17" x 5"	–	–	75p

Spot-face Cutter 36p
Pin Insertion Tool 47p
Terminal Pins 18p per pack of 36

NEW LISTS

BOXES, CHASSIS, etc.	No. 7
TRANSISTORS, I.C.'s, etc.	(soon)

(postage 5p)

Aluminium Boxes

Including baseplate and screws

No.	L.	W.	D.	Price	p. & p.
(7)	2¾"	x 5¼"	x 1½"	35p	8p
(8)	4"	x 4"	x 1½"	35p	8p
(9)	4"	x 2¾"	x 1½"	35p	8p
(10)	4"	x 5¼"	x 1½"	40p	8p
11	4"	x 2½"	x 2"	35p	8p
12	3"	x 2"	x 1"	32p	9p
13	6"	x 4"	x 2"	50p	10p
14	7"	x 5"	x 2½"	58p	12p
15	8"	x 6"	x 3"	75p	18p
16	10"	x 7"	x 3"	85p	20p

Transistors & Integrated Circuits

AC107	25p	BC147	10p	BF196	15p	OC81	19p	2N1304	22p	2N5172	15p
AC126	17p	BC148	10p	BF197	15p	OC140	20p	2N1711	25p	BZY88 ZENERS SERIES	10p ea.
AC127	15p	BC149	10p	BF272	53p	OC170	23p	2N1893	30p		
AC128	15p	BC157	12p	BFY50	24p	OC171	30p	2N2926, all	10p	LO05TI	£1.50
AC176	15p	BC158	10p	BFY51	21p	ZTX107	15p	2N3053	23p	LO36TI	£1.50
AC187	25p	BC159	12p	BRY39	38p	ZTX108	12p	2N3054	50p	LO37TI	£1.50
AC187K	25p	BC169	15p	BSX21	26p	ZTX109	15p	2N3055	49p	MC1303L	£1.75
AC188	25p	BC268	15p	BSY95A	14p	ZTX300	12p	2N3702	12p	MC1330	80p
AC188K	25p	BD115	67p	BU105/02	£1.75	ZTX301	15p	2N3703	12p	MC1350	75p
ACY20	20p	BD131	70p	MJE340	67p	ZTX302	20p	2N3704	10p	MC1351	£1.00
AD140	40p	BD132	70p	MPF192	40p	ZTX303	20p	2N3705	10p	MC1352	£1.00
AD149	40p	BD131/2M.P.	149p	MPF103	37p	ZTX304	25p	2N3706	10p	MFC4000B	49p
AD161 AD162	60p	BF160	21p	MPF104	37p	ZTX341	20p	2N3707	15p	MFC4010A	55p
AF114	18p	BF167	20p	MPF105	40p	ZTX500	15p	2N3708	12p	LM380	£1.45
AF115	18p	BF173	20p	MPF106	45p	ZTX501	15p	2N3709	12p	SL403D	£1.50
AF116	18p	BF180	25p	OC35	40p	ZTX502	20p	2N3710	12p	TAD100	£1.50
AF117	18p	BF181	30p	OC44	15p	ZTX503	17p	2N3711	12p	FILTER LP1175	£1.50
AF139	28p	BF184	25p	OC45	15p	ZTX504	50p	2N3819	35p		
BC107	10p	BF185	25p	OC71	11p	ZTX531	25p	2N3903	15p	μA709C	45p
BC108	10p	BF194	15p	OC72	17p	2N697	18p	2N3904	17p	μA710	45p
BC109	10p	BF195	15p	OC76	15p	2N706	12p	2N3905	21p	μA723C	£1.05
						2N708	15p	2N3906	12p	μA741C	50p

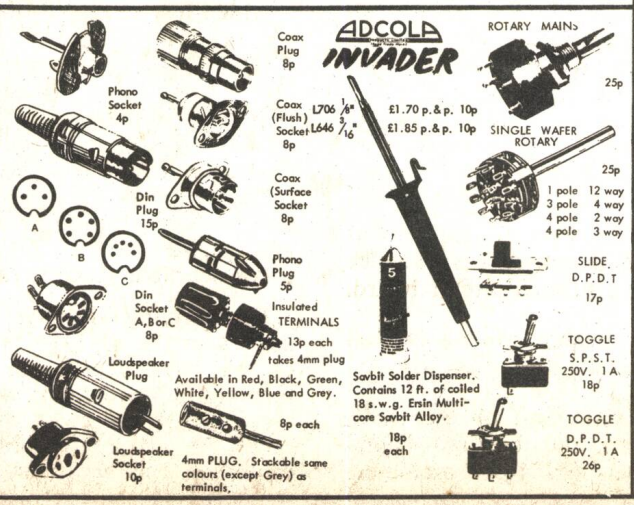
Phono Socket 4p
Coax Plug 8p
Coax (Flush) Socket 8p
L706 L646
Coax (Surface Socket 8p
Din Plug 15p
Phono Plug 5p
Din Socket A, B or C 8p
Insulated TERMINALS 13p each takes 4mm plug
Loudspeaker Plug
Loudspeaker Socket 10p
8p each
4mm PLUG. Stackable same colours (except Grey) as terminals.
Available in Red, Black, Green, White, Yellow, Blue and Grey.
ADCOLA INVADER
£1.70 p.& p. 10p
£1.85 p.& p. 10p
Savbit Solder Dispenser. Contains 12 ft. of coiled 18 s.w.g. Ersin Multicore Savbit Alloy.
18p each
ROTARY MAINS
25p
SINGLE WAFER ROTARY
25p
1 pole 12 way
3 pole 4 way
4 pole 2 way
4 pole 3 way
SLIDE D.P.D.T 17p
TOGGLE S.P.S.T. 250V. 1A 18p
TOGGLE D.P.D.T. 250V. 1A 26p

Mullard ß Siemens Electrolytics

CAP μF	VOLTAGE 4	6.3	10	16	25	40	63
1	—	—	—	—	—	—	6p
1·5	—	—	—	—	—	—	6p
2·2	—	—	—	—	—	—	6p
3·3	—	—	—	—	—	—	6p
4·7	—	—	—	—	—	—	6p
6·8	—	—	—	—	6p	—	6p
10	—	—	—	6p	—	6p	6p
15	—	—	6p	—	6p	6p	6p
22	—	—	6p	—	6p	—	6p
33	—	6p	—	6p	—	6p	—
47	6p	—	6p	—	6p	6p	6p
68	—	6p	—	6p	—	—	10p
100	6p	—	6p	—	6p	6p	12p
150	—	6p	—	6p	6p	10p	12p
220	6p	—	6p	6p	10p	12p	18p
330	6p	—	6p	10p	—	—	21p
470	—	6p	10p	—	12p	18p	40p
680	—	10p	—	12p	18p	21p	—
1000	10p	—	12p	18p	21p	40p	60p
1500	—	12p	18p	21p	—	—	—
2200	—	18p	21p	40p	45p	55p	93p
3300	—	21p	—	—	—	—	—
4700	21p	—	—	60p	75p	93p	—

CAP μF	VOLTAGE 16	25	40	64
500			33p	40p
1250			50p	—
1600			—	75p
2000		40p	50p	—
2500		—	—	93p
3200		50p	—	—
4000		75p	93p	—
6400		75p	93p	—

Quantity Prices on application.

Hi-Volt Electrolytics

1; 2; 4; 8μF	450V	14p	32μF	450V	20p
16μF	450V	15p	50μF	350V	20p
8+8μF; 450 V.W		18p	32+32μF; 350 V.W		25p
8+16μF; 450 V.W		20p	32+32μF; 450 V.W		43p
16+16μF; 450 V.W		25p	50+50μF; 350 V.W		35p

BSR LATEST SUPERSLIM STEREO & MONO

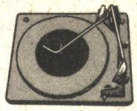

Plays 12", 10" or 7" records.
Auto or Manual. A high quality unit backed by BSR reliability with 12 months' guarantee. AC 200/250v.
Size 13¼ × 11¼in.
Above motor board 3¾in.
below motor board 2¼in.

with STEREO and MONO XTAL **£8·75** Post 25p

RCS BARGAIN 4 TRANSISTOR MONO AMPLIFIER

Powerful 3 watts output, 15 ohm. AC mains operated with transformer. 3-Controls, volume, treble, bass and On/Off switch with knobs. Ready made on printed circuit board. Fused inputs and outputs. Famous make, size 8" wide × 4" deep × 3" high.

PRICE **£5·50** Post 25p

RCS DE-LUXE 3 WATT AMPLIFIER. Ready made, tested. Printed circuit. 3 watts output. Tone and volume controls. Complete with output valve and rectifier, two knobs, and high performance loudspeaker. Double wound fully isolated mains transformer. A.C. mains 200/250V. Response 50-12,000 cps. Sensitivity 300mV. **£4** Post 25p

BSR JUNIOR SINGLE PLAYER

Heavy duty 4-speed motor with separate pick-up arm fitted LP/78 turnover mono cartridge **£4·50** Post 25p

HI-FI PICK UP CARTRIDGES.
Stereo/Mono 9TA £2·50; GP94 £2·50; GP93 £2.
Sapphire Mono GP91 £1·50; Powerpoint LP/78 60p.

GARRARD DECCA DISCO DECK

Single play Stereo/Mono Deram transcription head and arm.
Four speeds.
10½in. turntable.
Anti-rumble filter.
Bias compensation.
Laboratory motor.

SPECIAL PRICE **£18·50** Post 25p

METAL PLINTH AND PLASTIC COVER

Cut out for most Garrard or B.S.R. Most will play with cover in position. Latest Design. Covered in black leatherette. Antimagnetic.
12½ × 14½ × 7½in. high. **£4·50** Post 35p

ALSO AVAILABLE IN SOLID NATURAL MAHOGANY WAX POLISHED FINISH—AT SAME PRICE

SPECIAL OFFER! SMITH'S CLOCKWORK 15 AMP TIME SWITCH

Single pole two-way. Surface mounting with fixing screws. Will replace existing wall switch to give light for return home, garage, automatic anti-burglar lights, etc. Variable knob. Turn on or off at full or intermediate settings. Two types available 0 to 60 minutes or 0 to 6 hours. Fully insulated. Makers last list price £4·50. Brand new and fully guaranteed.
OUR PRICE **£1·50** P. & P. 15p or £3 pair Post Free. (Please state type when ordering)

BLANK ALUMINIUM CHASSIS. 18 s.w.g. 2½in. sides 6 × 4in. 45p; 8 × 6in. 53p; 10 × 7in. 65p; 12 × 8in. 85p; 14×9in. 90p; 16×6in. 90p; 12 × 3in. 50p; 16 × 10in. £1.
ALUMINIUM PANELS 18 s.w.g. 6 × 4in. 9p; 8 × 6in. 15p; 14 × 3in. 16p; 10 × 7in. 19p; 12 × 5in. 20p; 12 × 8in. 28p; 16×6in. 28p; 14×9in. 34p; 12×12in. 40p; 16×10in.. 50p

RADIO BOOKS (Post 3p)

Handbook of transistor equivalents	40p
Radio valve guide, Book 1, 2, 3, 4, 5 (each)	30p
Master colour code folder	15p
Boys' book of crystal sets and simple circuits	18p
Universal gram motor speed indicator	8p
High fidelity loudspeaker enclosures	40p
Practical Stereo handbook	30p
Sound and Loudspeaker Manual	50p
Coil design and construction manual	30p
Radio, TV and electronics data book	25p
Transistor circuits manual, No. 4	15p
Practical transistor audio amplifier Book 1	40p
Transistor subminiature receivers	32p
Practical Transistor Novelty Circuits	40p
Resistor colour code disc calculator	10p
Engineers' and Machinists' reference tables	20p
TV fault finding	50p

R.C.S. STABILISED POWER PACK KITS

All parts and instructions with Zener Diode, Printed Circuit, Bridge Rectifiers and Double Wound Mains Transformer input 200/240V a.c. Output voltages available 6 or 9 or 12 or 15 or 18 or 20V d.c. at 100mA or less
PLEASE STATE VOLTAGE REQUIRED.
Details S.A.E. Size 3½×1½×1½in. **£2** Post Free

R.C.S. GENERAL PURPOSE TRANSISTOR PRE-AMPLIFIER BRITISH MADE

Ideal for Mike, Tape, P.U., Guitar, etc. Can be used with Battery 9-12v. or H.T. line 200-300v. D.C. operation. Size 1¾"×1½"×¾". Response 25 c.p.s. to 25 Kc/s, 26 db gain.
For use with valve or transistor equipment. **90p** Post 10p
Full instructions supplied. Details S.A.E.

MAINS TRANSFORMERS

All post 25p each

250-0-250 80 mA. 6.3 v. 4 amp.	£1·50
250-0-250 80 mA. 6.3 v. 3.5 a. 6.3 v. 1 a, or 5 v. 2 a.	£2.50
350-0-350 80 mA. 6.3 v. 3.5 a. 6.3 v. 1 a, or 5 v. 2 a.	£3
300-0-300 v. 120 mA., 6.3 v. 4 a. C.T.; 6.3 v. 2 a.	£3·25
MINIATURE 200 v. 20 mA., 6.3 v. 1 a. 2½×2½×2in.	75p
MIDGET 220 v. 45 mA., 6.3 v. 2 a. 2¾×2½×2in..	90p
HEATER TRANS. 6.3 v. 3a.	60p
GENERAL PURPOSE LOW VOLTAGE. Tapped outputs at 2 amp., 3, 4, 5, 6, 8, 9, 10, 12, 15, 18, 24 and 30 v.	£2·25
1 amp., 6, 8, 10, 12, 16, 18, 20, 24, 30, 36, 40, 48, 60.	£2·25
2 amp., 6, 8, 10, 12, 16, 18, 20, 24, 30, 36, 40, 48, 60.	£3·25
5 amp., 6, 8, 10, 12, 16, 18, 20, 24, 30, 36, 40, 48, 60	£8·75
3 amp. 5, 8 and 13V	£1·00
5 amp. 5, 8 and 13V	£1·20
3 amp. 3, 5, 8, 10, 13 and 5-0-5V	£1·30
5 amp. 3, 5, 8, 10, 13 and 5-0-5V	£1·50

AUTO TRANSFORMERS. 115v to 230v or 230v to 115v. 150w. £2·25; 500w. £6·25; 750w. £10; 1000w. £15.
CHARGER TRANSFORMERS. Input 200/250v. for 6 or 12v., 1½ amp. £1·50; 2 amp. £1·80; 4 amp. £2·50
BATTERY CHARGERS—Ready built with leads and clips 1½ amp. £2; 4 amp. £4; 5 amp. £4·50.
FULL WAVE BRIDGE CHARGER RECTIFIERS: 6 or 12v. outputs. 1½ amp. 40p; 2 amp. 55p; 4 amp. 85p.
LUCAS 2DS500 Full wave Bridge 70v. 5 amp 95p.

MAINS ISOLATING TRANSFORMER

Primary 0–110–240v. Secondary 0–240v. 3 amps. 720 watts. Insulated terminals. Varnish impregnated. Fully enclosed in steel case with fixing feet. **£10** Carr. 50p
Famous make. (Value £19) OUR PRICE
Can be used as 800 watt auto transformers 240-110V.

NEW TUBULAR ELECTROLYTICS

2/350V	14p	250/25V	14p	50+50/350V	35p
4/350V	14p	500/25V	20p	60+100/350V	58p
8/450V	14p	1000/25V	35p	32+32/250V	18p
16/450V	15p	1000/50V	47p	32+32/450V	33p
32/450V	20p	8+8/450V	18p	350+50/325V	50p
25/25V	10p	8+16/450V	20p	32+32+32/350V	43p
50/50V	10p	16+16/450V	25p	100+50+50/350V	48p
100/25V	10p	32+32/350V	25p		

LOW VOLTAGE ELECTROLYTICS.
1, 2, 4, 5, 8, 16, 25, 30, 50, 100, 200mF 15V 10p.
500mF 12V 15p; 25V 20p; 50V 30p.
1000mF 12V 17p; 25V 35p; 50V 47p; 100V 70p.
2000mF 6V 25p; 25V 42p; 50V 57p.
2500mF 50V 62p; 3000mF 25V 47p; 50V 65p.
5000mF 6V 25p; 12V 42p; 25V 75p; 35V 85p; 50V 95p.

CERAMIC, 1pF to 0·01mF, 4p. Silver Mica 2 to 5000pF, 4p.
PAPER 350V-0·1 4p, 0·5 13p; 1mF 15p; 2mF 150V 15p.
500V-0·001 to 0·05 4p; 0·1 5p; 0·25 8p; 0·47 25p.
SILVER MICA. Close tolerance 1%. 2·2-500pF 8p; 560-2,200pF 10p; 2,700-5,600pF 20p; 6,800pF-0·01, mfd 30p each.
TWIN GANG. "0-0" 208pF+176pF, 65p; Slow motion drive 365pF+365pF with 25pF+25pF, 50p; 500pF standard 45p; single gang 500pF 75p; small 3-gang 500 pF £1·60.
SHORT WAVE SINGLE. 10pF, 30p, 25pF, 55p, 50pF, 55p.

SHORT WAVE SINGLE GANG. Precision Silver Plated Gangable Tuning Condensers. **50p** each
Values up to 100pF.
Section Couplers supplied FREE with two or more gangs.

NEON PANEL INDICATORS 250V AC/DC Amber 20p.
RESISTORS. ¼ w., ½ w., 1 w., 20% 1p; 2 w. 5p. 10Ω to 10M. HIGH STABILITY. ½ w. 2% 10 ohms to 6 meg., 10p. Ditto 5%. Preferred values 10 ohms to 10 meg., 4p.
WIRE-WOUND RESISTORS 5 watt, 10 watt, 15 watt, 10 ohms to 100K 10p each; 2½ watt, 1 ohm to 8·2 ohms 10p.
TAPE OSCILLATOR COIL. Valve type, 35p.

WEYRAD P50 — TRANSISTOR COILS

RA2W Ferrite Aerial	72p	Spare Cores	3p
Osc. P50/1AC	33p	Driver Trans. LFDT4	58p
I.F. P50/2CC 470 kc/s	36p	Printed Circuit, PCA1	58p
3rd I.F. P50/3CC	36p	J.B. Tuning Gang	65p
P51/1 or P51/2	36p	Weyrad Booklet	10p
P50/3V	36p	OPT1	58p

Mullard Ferrite Rod 8 × ⅜in. 20p. 6 × ⅜in. 20p.

VOLUME CONTROLS

Long spindles. Midget Size 5 K. ohms to 2 Meg. LOG or LIN. L/S 15p. D.P. 25p.
STEREO L/S 55p. D.P. 75p.
Edge 5K. S.P. Transistor 25p.

80Ohm Coax 4p yd.

BRITISH AERIALITE AERAXIAL-AIR SPACED
40 yd. £1·40; 60 yd. £2.
FRINGE LOW LOSS **10p yd**
Ideal 625 and colour

1¼inch DIAMETER WAVECHANGE SWITCHES. 25p.
2 p. 2-way, or 2 p. 6-way, or 3 p. 4-way 25p each.
1 p.1 2-way, or 4 p. 2-way, or 4 p. 3-way 25p
TOGGLE SWITCHES, sp. 14p; dp. 22p; dp. dt. 22p.
Sub-miniature, sp. 30p; dp. 37; dp. dt. 45p.

E.M.I. 13½ × 8in. SPEAKER SALE!

With twin tweeters. And crossover. 10 watt. State 3 or 8 or 15 ohm. As illustrated. **£3·95** Post 25p

With flared tweeter cone and ceramic magnet. 10 watt. Bass res. 45-60 cps. Flux 10,000 gauss. State 3 or 8 or 15 ohm. **£2·25** Post 25p

TEAK CABINET

16×10×9in. Modern design **£5** Post 25p

GOODMANS 6½in. HI-FI WOOFER

8 ohm, 10 watt. Large ceramic magnet. Special Cambric cone surround. Frequency response 30–12,000 cps. Ideal P.A. Columns. Hi-Fi Enclosure Systems, etc. Suitable cabinet 12×8×6 £4.
£4

ELAC CONE TWEETER

The moving coil diaphragm gives a good radiation pattern to the higher frequencies and a smooth extension of total response from 1,000 cps to 18,000 cps. Size 3½ × 3½ × 2in. deep. Rating 10 watt. 3 ohm or 15 ohm models. Crossover 95p. **£1·90** Post 10p

GOODMANS 8 in WOOFER

8 ohm 12 watt. Deep cone. Heavy ceramic magnet. Bass resonance 35 cps. Frequency response 30-8,000 cps.
£4·50

LOUDSPEAKERS P.M. 3 OHMS. 7×4in. £1·25; 6½in. £1·50; 8×5in. £1·60; 8in. £1·75; 10×6in. £1·90; 10in. £2.
SPECIAL OFFER! 80 ohm. 2½in. 2½in. 35 ohm, 2in.; 3 in. 5in. 25 ohm, 2½in. dia.; 3in. dia.; **£1** EACH TYPE
15 ohm, 3½in. dia. 5in; 6×4in; 7×4in; 8×5in.
3 ohm, 2½in. 2½in, 3½in, 5in dia. (6×4in., 8 ohm, £1·50).
RICHARD ALLAN TWIN CONE LOUDSPEAKERS 8in. diameter 4 watt; 10in. diameter 5 watt; 12 in. diameter 6 watt, 3 or 8 or 15 ohm models £2·20 each. Post 15p.
SPEAKER COVERING MATERIALS. Samples Large S.A.E.
Horn Tweeters 2-16Kc/s, 10W 8 ohm or 15 ohm £1·95.
De Luxe Horn Tweeters 2-18 Kc/s, 15W, 15 ohm £3.
TWO-WAY 3,000 c.p.s. CROSSOVERS 3 or 8 or 15 ohm 95p.

TWO-WAY CROSSOVER NETWORK 3,000 c/s

With variable tweeter attenuator giving accurate high/low frequency balance. Mounted on panel 5½in. × 4in. with control knob, tweeter and woofer leads and input terminals. Suitable for 3 to 8 ohm impedance. **£1·90** Post 10p

VALVE OUTPUT TRANS. 25p. MIKE TRANS. mu metal 100-1 £1·25. 5 WATT MULTI RATIO, 3, 8 and 15 ohms 80p.
PUSH-PULL VALVE OUTPUT TRANSFORMERS.
50 watt ..... £9·50 100 watt ..... £12·50

STEREO/MONO HEADPHONES

New model with new type slider volume controls. Stereo/Mono switch. 8 ohms. £10.
High Quality with tweeters and volume controls. 8 ohm. £7.
Budget Model. 8 ohm. £3·25.
HEADPHONE JUNCTION BOX with switch £1·75.
Mono Stethoscope 8 ohms. 65p.
EAR PIECES. Crystal 25p.
Magnetic 8 ohms. 13p.
Magnetic 250 ohms. 23p.
ACOS 1000 ohms. 53p.

BRITISH MADE STEREO MULTIPLEX DECODER

Brand New. 7 transistors plus integrated circuit. Fibre glass printed circuit board. Size 2½ × 6½ × ¾in. Pre-aligned. Complete with stereo beacon indicator. 12V d.c. operation. 400mV output for 100μV input. Full instructions for any FM Tuner. Some technical experience essential. **£6·50**
DIPOLE LOFT AERIAL £1·50. Post 15p
CABLE 4p yard.

COAXIAL PLUG 10p, PANEL SOCKETS 10p, LINE 18p
OUTLET BOXES. SURFACE OR FLUSH 25p.
BALANCED TWIN RIBBON FEEDER 300 ohms. 5p yd
JACK SOCKET Std. open-circuit 14p, closed circuit 23p
Chrome Lead Socket 45p. Phono Plugs 5p. Phono Socket 5p
JACK PLUGS Std. Chrome 15p; 3·5mm Chrome 12p. DIN
SOCKETS Chassis 3-pin 10p; 5-pin 10p. DIN SOCKETS Lea
3-pin 18p; 5-pin 15p. DIN PLUGS 3-pin 18p; 5-pin 25p
VALVE HOLDERS, 5p; CERAMIC 8p; CANS 5p.

ALL PRICES INCLUDE ANY V.A.T. MINIMUM POST AND PACKING 15p.

RADIO COMPONENT

Illustrated Colour Brochure, Radio Books & Component Lists 10p. Written guarantee.

E.M.I. WOOFER AND TWEETER KIT

£5·75 THE PAIR Post 25p. (Available separately. Woofer £4·25; Tweeter £1·90).

Comprising a fine example of a Woofer 10¾×6¾in. with a massive Ceramic Magnet, 44oz, Gauss 13,000 lines. Aluminium Cone centre to improve middle and top response. Also the E.M.I. Tweeter 3¼in. square has a special lightweight paper cone and magnet flux 10,000 lines. Crossover condenser and full instructions supplied.

Impedance Standard	8 ohms
Maximum power	12 watts
Useful Response	35 to 18,000 cps
Bass Resonance	45 cps

SUITABLE ENCLOSURE 20 x 13 x 9in. MODERN DESIGN. TEAK WOOD FINISH **£9** Post 25p

8in. or 10in. ELAC HI-FI SPEAKER

Dual cone plasticised roll surround. Large ceramic magnet. 50–16,000 cps. Bass resonance 55 cps. 8 ohm impedance. 8in. 10 watts, 10in. 12 watts music power. **£3·75** Post 25p

TEAK VENEER SPEAKER CABINET

Fluted Wood Front

MODEL "A". 20 × 13 × 9in. For 12in. dia. or 10in. speaker. **£9** Post 25p

MODEL "B". 16 × 10 × 9in. For 13 × 8in. or 8in. speaker **£5** Post 25p

MODEL "C". 16 × 8 × 6in. For 10 × 6in. or 6in. speaker. **£4** Post 25p

LOUDSPEAKER CABINET WADDING 18in. wide, 15p ft

BARGAIN AM TUNER. Medium Wave. Transistor Superhet Ferrite aerial. 9 volt. **£4·95**

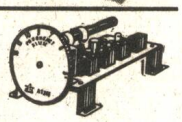

BARGAIN 4 CHANNEL TRANSISTOR MONO MIXER. Add musical highlights and sound effects to recordings. Will mix Microphone, records, tape and tuner with separate controls into single output. 9 volt. battery operated. **£3·95**

STEREO VERSION OF ABOVE £5·95

BARGAIN FM TUNER 88-108 Mc/s Six Transistor. 9 volt. Printed circuit. Calibrated slide dial tuning. Walnut Cabinet, Size 7 × 5 × 4in. **£14·85**

BARGAIN FM TUNER as above less cabinet **£9·85**

BARGAIN 3 WATT AMPLIFIER. 4 Transistor Push-Pull Ready built, with volume control. 9 volt battery operated. **£4·50**

THE "INSTANT" BULK TAPE ERASER & HEAD DEMAGNETISER. Suitable for cassettes, and all sizes of tape reels. A.C. mains 200/250V. Leaflet S.A.E. **£2·50** Post 15p

WAFER THIN HEATING ELEMENTS

OFFERING 1001 USES for every type of heating and drying applications in the home, garage, greenhouse, factory (available in manufacturing quantities). Approx. size 10⅝ × 8¼ × 1/16in. Operating voltage 200/250V. a.c. 250 watts approx. Printed circuit element enclosed in asbestos fitted with connecting wires. Completely flexible providing safe Black heat. British-made for use in photo-copiers and print drying equipment.

Ideal for home handymen and experimenters. Suitable for Heating Pads, Food Warmers, Convector Heaters, etc. Must be clamped between two sheets of metal or asbestos, etc., to make efficient clothes dryers, towel rails—ideal for airing cupboards. Ideal for anti-frost device for the garage—preventing frozen radiators or acting as oil sump heater. Use in the green house for seed raising and plant protection. Invaluable aid for bird houses, incubators, etc., etc. Can be used in series for lower heat. Or in parallel for higher heat applications.

ONLY **40p** EACH (FOUR FOR £1·50)

ALL POST PAID—Discounts for quantity.

BAKER 12in MAJOR £9

Post 25p

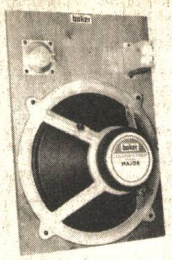

30-14,500 c.p.s., 12in. double cone, woofer and tweeter cone together with a **BAKER** ceramic magnet assembly having a flux density of 14,000 gauss and a total flux of 145,000 Maxwells. Bass resonance 40 c.p.s. Rated 20 watts. State 3 or 8 or 15 ohm. Post Free.

Module kit, 30-17,000 c.p.s. with tweeter, crossover, baffle and instructions. **£11·50** Post 25p

BAKER "BIG-SOUND" SPEAKERS

Robustly constructed to stand up to long periods of electronic power. As used by leading groups. Useful response 30-13,000 cps. Bass Resonance 55 cps.

GROUP "25" 12in. 25 watt 3, 8 or 15 ohms. **£8** Post 25p

GROUP "35" 12in. 35 watt 3, 8 or 15 ohms. **£9** Post 25p

GROUP "50" 15in. 50 watt 8 or 15 ohms. **£20** Post 25p

MAJOR 100 WATT ALL PURPOSE TRANSISTOR AMPLIFIER

4 inputs speech and music. 4-way Mixing. Response 10–30,000 cps. Matches all loudspeakers. 8/15 ohm A.C. 200/250V. Separate Treble and Bass controls. Guaranteed. Details S.A.E. **£49** Post Free

CALLERS ONLY! DE-LUXE 100 WATT AMPLIFIER CHASSIS. 7 Valve version, 4 inputs, 10 wide range controls. For Mikes, Discos, Organs, Guitars, etc. 4, 8 and 15 ohm matching. **£55**

Q MAX CHASSIS CUTTERS

A die, punch and Allen Screw

¾in. Round	68p	1⅛in. Round	98p	Key "B" for above	8p
7/16in. Round	75p	1in. Round	98p	2in. Round	£2·05
Key "T" for above	5p	1 1/16in. Round	98p	2 3/16in. Round	£2·30
½in. Round	83p	1¼in. Round	98p	Key "C" for above	12p
9/16in. Round	83p	1 3/16in. Round	£1·05	2¼in. Round	£4.10
5/8in. Round	83p	1 7/16in. Round	£1·05	2⅜in. Round	£5·25
11/16in. Round	88p	1⅜in. Round	£1·05	3in. Round	£8·10
¾in. Round	88p	1 5/16in. Round	£1·10	Key "E" for above	18p
13/16in. Round	90p	1½in. Round	£1·10	1in. Square with key	£1·93
⅞in. Round	90p	1⅝in. Round	£1·25		
Key "A" for above	5p	1¾in. Round	£1·43		
		1 7/8in. Round	£1·50		

SLIDER VOLUME CONTROLS

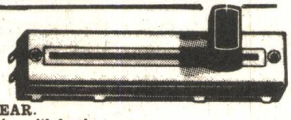

MONO LOG or LINEAR. Size 3 7/16 × ⅜ × 7/16in. with knobs. 5K, 10K, 25K, 50K, 100K. 250K, 500K, 1 MEG, 2 MEG. **65p** EACH

E.M.I. TAPE MOTORS. 120v. or 240v. AC. 1,200 r.p.m. 4 pole 135mA. Spindle 0·187 × 0·75in. Size 3½ × 2½ × 2½in. (illustrated). Post 15p. **£1·25**

BALFOUR GRAM. MOTORS. 120v. or 240v. AC. 1,200 r.p.m. 4 pole 50mA. Spindle ¼ × 3/20. Size. 2½ × 2¼ × 1¼in. Post 15p **85p**

E.M.I. GRAM MOTORS. 120V or 240V a.c. 2,400 rpm. 2-pole 70mA. Spindle ⅜ × 7/16in. Size 2⅞ × 2½ × 2⅜in. **75p** Post 15p

BAKER HI-FI SPEAKERS

HIGH QUALITY — BRITISH MADE

REGENT

12in. 15 watts

An inexpensive unit for the beginner in high fidelity and for general purposes. May be used to improve any Radio, Amplifier, Hi-Fi or Television receiver.

Bass Resonance	45cps
Flux Density	12,000gauss
Useful response	45-13,000cps
3 or 8 or 15 ohm models	

£8 Post 25p

DE-LUXE Mk II

12in. 15 watts

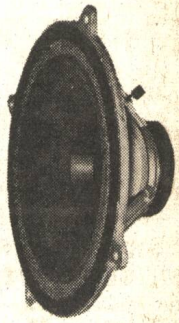

Especially designed to provide full range reproduction at an economical cost. Suitable for use with any high fidelity system. Built-in concentric tweeter cone.

Bass Resonance	30cps
Flux Density	14,000gauss
Useful response	25-16,000cps
8 or 15 ohms models	

£10 Post 25p

SUPERB

12in. 20 watts

A high quality loudspeaker, its remarkable low cone resonance ensures clear reproduction of the deepest bass. Fitted with a special copper drive and concentric tweeter cone resulting in full range reproduction with remarkable efficiency in the upper register.

Bass Resonance	25cps
Flux Density	16,500gauss
Useful response	20-17,000cps
8 or 15 ohms models	

£15 Post 25p

AUDITORIUM

12in. 25 watts

A full range reproducer for high power Electric Guitars, public address, multi-speaker systems, electronic organs. Ideal for Hi-Fi and Discotheques.

Bass Resonance	35cps
Flux Density	15,000gauss
Useful response	25-16,000cps
8 or 15 ohms models	

£14 Post 25p

AUDITORIUM

15in. 35 watts

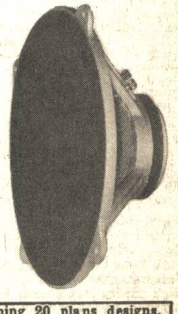

A high wattage loudspeaker of exceptional quality with a level response to above 8,000 cps. Ideal for Public Address, Discotheques, Electronic instruments and the home.

Bass Resonance	35cps
Flux Density	15,000gauss
Useful response	20-14,000cps
8 or 15 ohms models	

£20 Post 25p

Hi-Fi Enclosure Manual containing 20 plans designs, crossover data and cubic tables. 42p. Post Free.

ALL PRICES INCLUDE ANY V.A.T. OPEN 9-6 p.m. WEDNESDAYS 9-1 p.m., SATURDAYS 9-5 p.m. (Closes for Lunch 1.15-2.30)

SPECIALISTS 337 WHITEHORSE ROAD • CROYDON

(Export: Remit cash and extra postage.)

Buses 50, 68, 159. Rail Selhurst

Telephone 01-684-1665

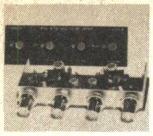

3W STEREO AMPLIFIER £3·90;

10W AMPLIFIER, £3·75.

R.F. FIELD INDICATOR Model FL-30HA Frequency Range (5 ranges) 1M/cs to 250M/cs, **£3.**

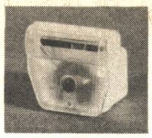

TAPE RECORDER LEVEL METER 500μA, 50p.

MINIATURE INDICATOR LAMPS (5 colours), **11p;** 6·3V or 12V Bulbs for above, **4p. MAINS NEONS** with long leads, **6p;** Panel mounting (red, green, clear), **15p. CARTRIDGES:** Compatible ACOS GP91-3SC, **90p;** Stereo GP93-1, **£1·15. HEADPHONES:** High Impedance (2,000 ohm), **90p;** Stereo 8 ohm, **£1·95;** Stereo/Mono 8/16 ohm, **£2·10. MICROPHONES:** Lapel, **28p;** ACOS Mic 60, **£1;** Cardioid Dynamic Microphone Dual Impedance 600 ohm and 50K, **£4·50. CONDENSER** Microphone, **£8·62. JUNCTION BOXES** JB3, **£1·20.**

Please note there will be 10% V.A.T. charge as from April 1.

Large S.A.E. for list No. 5. Special Prices for quantity quoted on request. Please add 10p for P. & P. on orders under £5.

M. DZIUBAS

158 Bradshawgate, Bolton, Lancs. BL2 1BA

GUNTON ELECTRONIC IGNITION KIT £9·35 INC. VAT

READY BUILT UNIT GUARANTEED 5 YEARS £11·55 INC. VAT

Patents Pending. 12 volt only—state pos. or neg. earth.
Capacitive discharge ignition is recognised as being the most efficient system and will give you:

- ★ **Continual Peak-Tuned Performance**
- ★ **Up to 20% reduced fuel consumption**
- ★ **Easier All-weather Starting**
- ★ **Increased Acceleration and Top Speed**
- ★ **Longer Spark Plug Life**
- ★ **Increased Battery Life**
- ★ **Elimination of Contact Breaker Burn**
- ★ **Purer Exhaust Gas Emission**

Kit includes absolutely everything for assembly: Ready drilled Case and Hardware Printed Circuit Board, Cables, Coil Connectors, Silicon Grease Nuts and Bolts, etc. 8 page illustrated instructions cover fitting of all types of tachometers. Call in for a workshop demonstration. S.A.E. all enquiries please, or Phone 33652. (Many letters from satisfied customers.)

SCORPIO: Transformer **£2·42.** Printed Circuit Board **83p**

All prices include carriage and V.A.T.

ALUMINIUM BOXES

Complete with baseplate and screws

AT DIRECT FROM MANUFACTURERS' PRICES WITH RETURN OF POST SERVICE

Type No	L	W	D	Price
7*	5¼	2¾	1½	44p
8*	4	4	1½	44p
9*	4	2¾	1½	44p
10*	5¼	4	1½	53p
11	4	2½	2	44p
12	3	2	1	39p
13	6	4	2	59p
14	7	5	2½	68p
15	8	6	3	88p
16	10	7	3	96p

* These sizes accept standard veroboard range.
All prices include carriage and V.A.T. 20% discount on 10 or more boxes. 30% discount on orders over £10.

Dept. PE4, ELECTRONICS DESIGN ASSOCIATES
82 BATH STREET, WALSALL WS1 3DE

WATFORD ELECTRONICS

35 CARDIFF ROAD, WATFORD

C.W.O. Please. P. & P. please add 10p to order under £2.

RESISTORS
High stability, low noise, carbon film resistors. Tubular miniature high power resistors.

Power Watts	Tolerance	Range	Values Available	Price 1–99	Price 100+
¼	5%	2·2–2·2MΩ	E12	1p	0·8p
½	5%	2·2–10MΩ	E12	1p	0·8p
1	5%	2·2–10MΩ	E12	2p	1·5p
4	10%	1–10 ohm	E12	6p	—

Quantity prices available for any selection. Ignore fractions on total order.

CAPACITORS
Electrolytics, general purpose, miniature, axial lead. Mullard 015, 016, 017 series.

1μF	63V	6p	22μF	63V	6p
1·5μF	63V	6p	47μF	63V	6p
2·2μF	63V	6p	100μF	40V	6p
3·3μF	63V	6p	150μF	25V	6p
4·7μF	63V	6p	220μF	25V	11p
6·8μF	63V	6p	470μF	25V	13p
10μF	63V	6p	680μF	25V	20p
15μF	63V	6p	1,000μF	25V	25p

POLYESTER FILM CAPACITORS
Mullard C296 series
400V d.c.: μF: 0·001, 0·0015, 0·0022, 0·0033, 0·0047, 0·0068, 0·01, 0·015, 0·022, 2½p each. μF: 0·033, 0·047, 0·068, 0·1, 4p each. μF: 0·15, 6p. μF: 0·22, 7p. μF: 0·33, 10p. μF: 0·47, 13p.
160V d.c.: μF: 0·1, 0·15, 4p. 0·22, 5p. 0·33, 6p. 0·47, 7p. 0·68, 10p. 1·0, 13p.

Mullard C280 series. P.C. mounting
400V d_c.c.: μF: 0·01, 0·015, 0·022, 3p each. 0·033, 0·047, 4p each.
250V d.c.: μF: 0·068, 0·1, 0·15, 4p each. μF: 0·22, 0·33, 5p each. μF: 0·47, 7p. μF: 0·68, 10p. μF: 1·0, 11p.

CERAMIC DISC CAPACITORS
Working voltage 50V d.c., Plaquette body with 25mm leads. Range: 22μF–10,000μF. 2p each.

SLIDER POTENTIOMETERS
Single, 10kΩ, 25kΩ, 50kΩ, 100kΩ, log or linear, 35p.
Dual gang, 10kΩ + 10kΩ, etc., above values, log or linear, 50p.
Knobs for above, 10p.

PRESET POTENTIOMETERS SKELETON
Horizontal or vertical mounting, 0·25W Miniature, 5½p each.

SEMICONDUCTORS

TRANSISTORS

AC126	10p	BC148	10p	OC42	11p
AC127	10p	BC149	10p	OC44	11p
AC128	10p	BD131	70p	OC45	11p
AD161	30p	BD132	70p	2N2926R	9p
AD162	30p	BFY50	22p	2N29260	9p
AF117	10p	BFY51	22p	2N2926V	9p
BC107	7p	BFY52	22p	2N2926G	10p
BC108	7p	OC26	40p	2N3054	55p
BC109	7p	OC27	40p	2N3055	55p
BC147	10p	OC35	40p		

LINEAR INTEGRATED CIRCUITS
709 35p; 741 40p; 723 80p; DIL sockets 14 and 16 pin, 20p
All IC's are in DIL package.

ZENER DIODES
BYZ88 series. Power rating: 400mW. 5% tolerance. Values available: 3·3V–30V, 12p.

DIODES

OA85	7p	OA91	5p	IN4004	7p
OA90	5p	IN4001	6p	IN4007	7p

SILICON BRIDGE RECTIFIER WO1 30p (1 amp—100V)

POTENTIOMETERS
Carbon track, 1kΩ–2MΩ, log or linear, single Gang, 12p. 5kΩ–2MΩ log or linear, dual gang, 37p. 5kΩ–2MΩ, log or linear, single gang with switch, 24p. Knobs for above: 10p each.

VEROBOARD

	0·1 matrix	0·2 matrix		0.1 matrix	0.2 matrix
2½in × 3¾in	22p	16p	17in × 2½in	75p	57½p
2½in × 5in	24p	24p	17in × 5in (plain)	—	82p
3¾in × 3¾in	24p	24p	17in × 3¾in (plain)	—	60p
3¾in × 5in	27p	27p	17in × 2½in (plain)	—	42p

Pin insertion tool, 52p. Spot face cutter, 42p. Packet of 50 pins, both sizes, 20p.

JACK PLUGS AND SOCKETS

Standard screened	12p	2·5mm screened	8p
Stereo screened	30p	3·5mm screened	10p
Standard socket	12p	2·5mm sockets	7p
Stereo sockets	15p	3·5mm sockets	7p

DIN PLUGS AND SOCKETS
2 pin, 3 pin, 5 pin (180 or 240). Plugs, 12p. Sockets, 8p.

Post this Coupon for Catalogue

Please enclose 10p postage stamps for a copy of the catalogue which gives details of listed items listed in this advert, and more.

NAME.....
(BLOCK CAPITALS PLEASE)
ADDRESS.....
.....

AUTO—ELECTRIC CAR AERIAL

with dashboard control switch—fully extendable to 40in or fully retractable. Suitable for 12V positive or negative earth. Supplied complete with fitting instructions and ready wired dashboard switch. **£5·75** plus 25p post and insurance.

TAPE HEADS

We are gradually obtaining more information about the Truvox tape heads we have, we are told that these have been wound in a very ingenious way so that winding may be coupled either in parallel or in series depending whether high or low impedance is required. We also have matching erase heads and now offer these in pairs. 1 record and 1 erase head. Price of the 2 track **45p** per pair. 4 track **75p** per pair. Pair mounted on plate **45p** extra.

MAINS OPERATED CONTACTOR

220/240V 50 cycle solenoid with laminated core so very silent in operation. Closes 4 circuits each rated at 10A. Extremely well made by a German Electrical Company. Overall size 2½ × 2 × 2in. **£1·50** each.

TELESCOPIC AERIAL

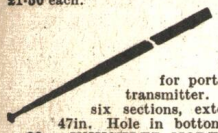

for portable, car radio or transmitter. Chrome plated—six sections, extends from 7½ to 47in. Hole in bottom for 6BA screw. **38p.** KNUCKLED MODEL FOR F.M. **50p.**

MAINS CLOCK & TIME SWITCH

Smith's main's driven clock with 15A programmable switch also notes showing how you can use this to wake up with music playing, kettle boiling or come home to a warm house, warn-off burglars, keeps pets warm, halves your heating bills etc., etc. **£1·75** +20p p. & p.

WATERPROOF HEATING ELEMENT

26 yards length 70W. Self-regulating temperature control. **50p** post free.

IMMERSION HEATERS BY REMPLOY

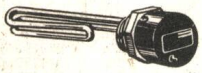

Standard fitting for domestic water tanks, made by the famous Remploy Company. Complete with sealing washers suitable for 200–240V a.c. Depth into tank 11in. 2kW or 3kW. **£1·50** plus 40p each post and insurance.

NEED A SPECIAL SWITCH?

Double Leaf Contact. Very slight pressure closes both contacts. **6p** each, **60p** doz. Plastic pushrod suitable for operating, **5p** each, **45p** doz.

THERMOSTAT

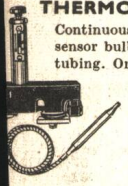

Continuously variable 30°–90°C. Has sensor bulb connected by 33in of flexible tubing. On operation a 15A 250V switch is opened and in addition a plunger moves through approx. ½in. This could be used to open valve on ventilator, etc. **£1·50** plus 23p p. & ins.

HIGH ACCURACY THERMOSTAT

Uses differential comparator I.C. with thermistor as probe. Designer claims temperature control to within 1/7th of a degree. Complete kit with power pack **£5·50.**

NUMICATOR TUBES

For digital instruments, counters, timers, clocks, etc. Hi-vac. XN. 3. Price **£1·45** each. 10 for **£13.**

12-WAY SUB-MINIATURE MULTI-CORE CABLE

7·0076 copper cores each core. P.V.C. insulated and of different colour. P.V.C. covered overall and approx. 3/16in thick. Price **20p** per yard.

VAT From April 1st VAT must be added to total orders.

STANDARD WAFER SWITCHES

Standard size 1½" wafer—silver-plated 5-amp contact, standard ¼" spindle 2" long—with locking washer and nut.

No. of Poles	2 way	3 way	4 way	5 way	6 way	8 way	9 way	10way	12way
1 pole	40p	40p	40p	40p	40p	40p	40p	40p	40p
2 poles	40p	40p	40p	40p	40p	40p	40p	70p	70p
3 poles	40p	40p	40p	40p	70p	70p	70p	95p	95p
4 poles	40p	40p	40p	70p	70p	70p	70p	£1·20	£1·20
5 poles	40p	40p	70p	70p	95p	95p	95p	£1·45	£1·45
6 poles	40p	70p	70p	70p	95p	95p	95p	£1·70	£1·70
7 poles	70p	70p	70p	95p	£1·20	£1·20	£1·20	£1·95	£1·95
8 poles	70p	70p	70p	95p	£1·20	£1·20	£1·20	£2·20	£2·20
9 poles	70p	70p	95p	95p	£1·45	£1·45	£1·45	£2·45	£2·45
10 poles	70p	70p	95p	£1·20	£1·45	£1·45	£1·45	£2·70	£2·70
11 poles	70p	95p	95p	£1·20	£1·70	£1·70	£1·70	£2·95	£2·95
12 poles	70p	95p	95p	£1·20	£1·70	£1·70	£1·70	£3·20	£3·20

THYRISTOR LIGHT DIMMER

For any lamp up to 250W. Mounted on switch plate to fit in place of standard switch. Virtually no radio interferences. Price **£2·95** plus 20p post and insurance. Industrial model 5A with control knob but not mounted on switch plate **£3.**

HORSTMANN "TIME AND SET" SWITCH

(A 30A Switch.) Just the thing if you want to come home to a warm house without it costing you a fortune. You can delay the switch on time of your electric fires, etc., up to 14 hours from setting time or you can use the switch to give a boost on period of up to 3 hours. Equally suitable to control processing. Regular price probably around £5. Special snip price **£1·50**, p. & ins. 23p.

13 AMP TWIN GANG SOCKETS

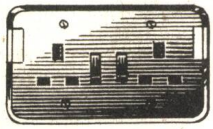

Offered at less than wholesale price your opportunity to replace those dangerous adaptors—brown bakelite flush mounting—standard fitting. Unswitched **20p** each, separately switched **30p** each. Less 10% ten or more +20p postage if order under £5.

4 WATT AUDIO AMPLIFIER £1·45

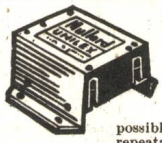

Works off dry batteries, car battery or mains power pack. Only **£1·45.** This low price possible only because the make is over-produced. Unrepeatable once stocks are cleared. Made by the famous Mullard company and carries their full guarantee. Complete in dustproof case, amplifier may be used for Mono or Stereo, music or speech. Hundreds of applications. Frequency response 50H3-16KH3. Supplied complete with connection diagram and operating notes. Postage & Ins. 20p.
FREE All purchasers receive Mullard booklet "Do It Yourself Stereo" tells all you need to know to build your own stereo system. Write today to avoid missing this terrific offer.

HONEYWELL PROGRAMMER

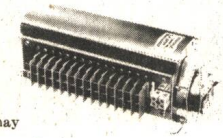

This is a drum type timing device, the drum being calibrated in equal divisions for switch setting purposes with trips which are infinitely adjustable for position. They are also arranged to allow 2 operations per switch per rotation. There are 15 changeover micro switches each of 10A type operated by the trips thus 15 circuits may be changed per revolution. Drive motor is mains operated 5 revs per min. Some of the many uses of this timer are Machinery control, Boiler firing, Dispensing and Vending machines, Display lighting animated and signs, Signalling, etc. Price from makers probably over £10 each. Special snip price **£5·75** plus 25p post and insurance. Don't miss this terrific bargain.

MIGHTY MIDGET

Probably the tiniest possible radio, as described in Practical Wireless, January 73. All electronic parts **£2** post paid.

DIGITAL COUNTER TIMER

Very stable and reliable crystal controlled circuit. Capable of work in excess of 15MHz. Construction simplified by use of 15 integrated circuits. Complete kit with case **£39·50** or construction data and price list **50p.**

INTEGRATED CIRCUIT BARGAIN

A parcel of integrated circuits made by the famous Plessey Company. A once-in-a-lifetime offer of Micro-electronic devices well below cost of manufacture. The parcel contains 5 ICs all new and perfect, first-grade device, definitely not sub-standard or seconds. 4 of the ICs are single silicon chip GP amplifiers. The 5th is a monolithic NPN matched pair. Regular price of parcel well over £5. Full circuit details of the ICs are included and in addition you will receive a list of many different ICs available at bargain prices **25p** upwards with circuits and technical data of each. Complete parcel only **£1** Post paid.
DON'T MISS THIS TERRIFIC BARGAIN.

EXTRACTOR FAN

Cleans the air at the rate of 10,000 cubic ft per hour. Suitable for kitchens, bathrooms, factories, changing rooms, etc., it's so quiet it can hardly be heard. Compact 5½in casing with 5½in fan blades. Kit comprises motor, fan blades, sheet steel casing, pull switch, mains connector, and fixing brackets, **£2·50** plus 30p post and ins.

QUICK CUPPA

Mini Immersion Heater, 350W 200/240V. Boils full cup in about two minutes. Use any socket or lamp holder. Have at bedside for tea, baby's food, etc. **£1·25,** post and insurance 14p. 12V car model also available same price. Jug heater **£1·50** plus p. & p. 14p.

MAINS TRANSISTOR POWER PACK

Designed to operate transistor sets and amplifiers. Adjustable output 6V, 9V, 12V for up to 500mA (class B working). Takes the place of any of the following batteries: PP1, PP3, PP4, PP6, PP7, PP9, and others. Kit comprises: mains transformer, rectifier, smoothing and load resistor condensers and instructions. Real snip at only **£1** plus 20p postage.

TREASURE TRACER

Complete Kit (except wooden battens) to make the metal detector as the circuit in Practical Wireless, August issue. **£2·95** plus 20p post and insurance.

WINDSCREEN WIPER CONTROL

Beat dirty roads, drizzle, fog, etc. Kit of parts to make this useful accessory with circuit details. **£2·25.**

12 VOLT 1½ AMP POWER PACK

This comprises double-wound 230/240V mains transformer with full wave rectifier and 2000 m/f/d" smoothing. Price **£2** plus post & packing.

ONE CHIP RADIO

Ferranti's latest device ZN414—gives results better than superhet. Supplied complete with technical notes and circuits. **£1·25** each. 10 for **£11.**

HI-Q TUNER COMPONENTS

For experimenting with the ZN414
Kit No. 1—Plessey Miniature Tuning Condenser with built in LW switch and 3in Ferrit slab and litz wound MW coil. **65p.**
Kit No. 2—Air spaced tuning condenser 6in ferrite rod, litz wound MW and LW coils, **85p.**
Kit No. 3—Air spaced TC with slow motion drive 8in ferrite rod, with Litz wound LW and MW coils, **£1.**
Kit No. 4—Permeability tuner with fast and slow motion drive and LW loading coils, **45p.**

6 VOLT CLOCK MOTOR

Works from 50 cycle mains through condenser, resistor or step-down transformer. This is a synchronous motor made by Smiths, so it is an extremely accurate speed controller. Very small in size (2W) and with a polythene cover. Price **30p each.** 10 for **£2·70.**

SOLDER GUN

A must for every busy man, gives almost instant heat also illuminated job. 100W **£2·25** plus post and ins. 20p. BIG JOB 250W model **£4·75** plus post and ins. 40p.

MAINS OPERATED SOLENOIDS

Model 772—small but powerful 1in pull—approx. size 1½in × 1½in × 1¼in **60p.**
Model 400/1 ¾in pull. Size 2¾in × 2in × 1¾in **75p.**
Model TT10 1¼in pull, size 3 × 2½ × 2in **£1·80** plus 20p post and insurance.

3 STAGE PERMEABILITY TUNER

Made originally for Radiomobile car radios. This is a medium wave tuner with a frequency coverage 16kc–525kc. Aerial, RF and oscillator sections (long wave coil available) small size, only 2¾ × 2 × 1in. Can be used with our IF module and AF modules and a few inter connection components to make a complete compact receiver. Circuit supplied. Price **65p** less 10% for 10.

TERMS:—10% discount if ten of an item ordered, send postage where quoted—other terms post free if order for these over £6 otherwise add 20p.

J. BULL (ELECTRICAL) LTD.

(Dept. P.E.), 7 Park Street, Croydon CRO 1YD
Callers to 102/3 Tamworth Road, Croydon

Don't miss

SOUND 73 international

BLOOMSBURY CENTRE HOTEL

Coram Street, Russell Square
London W.C.1

13-15 MARCH 1973
Tues/Wed 10.00-18.00 hrs.
Thurs 10.00-17.00 hrs.

THE ONLY EXHIBITION IN EUROPE EXCLUSIVELY FEATURING

PUBLIC ADDRESS
&
ALLIED EQUIPMENT

There will also be Lectures and Demonstrations

Tickets and information from the organisers

THE ASSOCIATION OF PUBLIC ADDRESS ENGINEERS
6 Conduit Street, London
WIR 9TG ENGLAND
TEL. 01-493 5256

PRACTICAL ELECTRONICS "SCORPIO" ELECTRONIC IGNITION SYSTEM

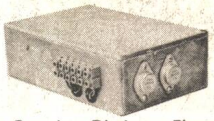

This Capacitor-Discharge Electronic Ignition system was described in the November and December issues of Practical Electronics. It is suitable for incorporating in any 12V ignition system in cars, boats, go-karts, etc., of either pos. or neg. earth and up to six cylinders. The original coil, plugs, points and contact-breaker capacitor fitted in the vehicle are used. No extra or special components are required.
Helps to promote easier starting (even under sub-zero conditions), improved acceleration, better high-speed performance, quicker engine warm-up and improved fuel economy. Eliminates excessive contact-breaker point burning and the need to adjust point and spark-plug gaps with precision.
Construction of the unit can easily be completed in an evening and installation should take no longer than half an hour. A complete complement of components is supplied with each kit together with ready-drilled roller-tinned professional quality fibre-glass printed-circuit board, custom-wound transformer and fully-machined die-cast case. All components are available separately. Case size 7¼in × 4¼in × 2in. approx.
Complete assembly and wiring manual **25p**, refundable on purchase of kit. Price: **£10·50** plus 50p P. & P.

PSYCHODELIC LIGHTING UNIT Mk. 3

This unit represents a natural progression from our phenomenally successful Mk. 1 and 2 Units. As before the drive voltage is derived directly from the amplifier output or across the speakers. The unit converts the audio frequency signals into a three-coloured light display; the colour depending on the frequency of the signal and the intensity on the loudness of the audio source.
The unit is constructed on professional fibre-glass printed-circuit board material and uses latest full-wave triac circuitry. There is a master-level control, together with independent sensitivity controls for each channel. The original minimum ambient light level controls have been redesigned permitting their use as faders; allowing dimming from max. to zero at the turn of a knob. R.F.I. suppression is now incorporated as standard as well as provision for D.J. "Pulse-Flash" controls. The choice of two inputs enables operation from both high and low power amplifiers. Max. power 1·5kW per channel at 240V a.c.
Complete assembly built and tested. Size 9in × 7in × 3in. Price **£25** carr. paid.

PLEASE NOTE ALL THE ABOVE PRICES ARE SUBJECT TO V.A.T. ADJUSTMENT

DABAR ELECTRONIC PRODUCTS
98a Lichfield Street, Walsall, Staffs. WS1 1UZ
TELEPHONE: WALSALL 34365 TELEGRAMS: DABELEC Walsall Staffs.

ERSIN
Multicore
5 CORE SOLDER

for fast, easy reliable soldering

Ersin Multicore Solder contains 5 cores of non-corrosive flux, instantly cleaning heavily oxidised surfaces. No extra flux is required.

EASY-TO-USE DISPENSERS

Size 5 Savbit alloy 18 swg, **18p** (illustrated).
Size 19A 60/40 alloy 18 swg, **18p**
Size 15 60/40 alloy 22 swg, **22p**

IDEAL FOR HOME CONSTRUCTORS

Size 1 cartons in 40/60, 60/40 and Savbit alloys in 7 gauges **25p**

Size 12 for Service Engineers and Electricians. 75ft of 18 swg Savbit alloy. **75p**

NEW! BIB WIRE STRIPPER AND CUTTER

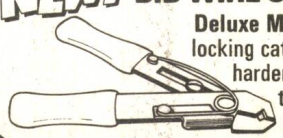

Deluxe Model 9 Automatic opening spring, locking catch, plastic-covered handles. Case hardened and precision ground. Adjusts to most wire sizes. Cuts and strips flex, splits plastic twin flex. **75p**

Prices shown are recommended retail, excluding V.A.T.
From Electrical and Hardware Shops. If unobtainable, send 10p p&p direct to:
Multicore Solders Ltd., Hemel Hempstead, Hertfordshire HP2 7EP

YATES ELECTRONICS

(FLITWICK) LTD.

ELSTOW STORAGE DEPOT
KEMPSTON HARDWICK
BEDFORD

C.W.O. PLEASE. POST AND PACKING PLEASE ADD 10p TO ORDERS UNDER £2.

Catalogue which contains data sheets for most of the components listed will be sent free on request. 10p stamp appreciated.

OPEN ALL DAY SATURDAYS

RESISTORS

¼W Iskra high stability carbon film—very low noise—capless construction.
¼W Mullard CR25 carbon film—very small body size 7·5 x 2·5mm.
½W 2% ELECTROSIL TR5

Power watts	Tolerance	Range	Values available	Price 1–99	Price 100+
¼	5%	4·7Ω–2·2MΩ	E24	1p	0·8p
¼	10%	3·3MΩ–10MΩ	E12	1p	0·8p
½	2%	10Ω–1MΩ	E24	3·5p	3p
½	10%	1Ω– 3·9Ω	E12	1p	0·8p
½	5%	4·7Ω–1MΩ	E12	1p	0·8p
4	10%	1Ω–10Ω	E12	6p	5·5p

Quantity price applies for any selection. Ignore fractions on total order.

DEVELOPMENT PACK

0·5 watt 5% Iskra resistors 5 off each value 4·7Ω to 1MΩ.
E12 pack 325 resistors **£2·40**. E24 pack 650 resistors **£4·70**.

POTENTIOMETERS

Carbon track 5kΩ to 2MΩ, log or linear (log ¼W, lin ½W).
Single, **12p**. Dual gang (stereo), **40p**. Single D.P. switch **24p**.

SKELETON PRESET POTENTIOMETERS

Linear: 100, 250, 500Ω and decades to 5MΩ. Horizontal or vertical P.C. mounting (0·1 matrix).
Sub-miniature 0·1W, **5p** each. Miniature 0·25W, **6p** each.

TRANSISTORS

AC107	15p	AF125	20p	BD132	75p	OC28	50p	2N3702	13p
AC126	12p	AF126	20p	BD133	75p	OC35	50p	2N3703	12p
AC127	12p	AF127	20p	BF115	25p	OC42	12p	2N3704	13p
AC128	12p	AF139	32p	BF173	20p	OC44	12p	2N3705	12p
AC131	12p	AF178	32p	BF177	28p	OC45	12p	2N3706	11p
AC132	12p	AF180	40p	BF178	32p	OC70	12p	2N3707	12p
AC176	12p	AF181	40p	BF179	32p	OC71	12p	2N3708	10p
AC187	22p	BC107	9p	BF180	32p	OC72	12p	2N3709	11p
AC188	22p	BC108	9p	BF181	32p	OC81	12p	2N3710	11p
AD140	50p	BC109	9p	BF194	15p	OC82D	12p	2N3711	11p
AD149	45p	BC147	13p	BF195	15p	2N2904	20p	2N4062	12p
AD161	33p	BC148	13p	BF197	15p	2N2926R	9p	40360	35p
AD162	36p	BC149	13p	BF200	32p	2N2926O	9p	40361	35p
AF114	20p	BC157	14p	BFY50	20p	2N2926Y	9p	40362	40p
AF115	20p	BC158	14p	BFY51	20p	2N2926G	10p	40408	40p
AF116	20p	BC159	14p	BFY52	20p			ZTX302	15p
AF117	20p	BC187	22p	BU105	225p	2N3054	58p	ZTX500	15p
AF117	38p	BD131	75p	OC26	45p	2N3055	60p	ZTX502	20p
AF124	22p								

ZENER DIODES

400mW 5% 3·3V to 30V, **12p**.

WIRE WOUND POTS, 3W, 10, 25, 50Ω and decades to 100kΩ, 35p.

DIODES

RECTIFIER			
BY127	1250V	1A	12p
BZV10	800V	6A	25p
BZY13	200V	6A	20p
IN4001	50V	1A	7p
IN4004	400V	1A	8p
IN4007	1000V	1A	10p

SIGNAL	
OA85	7p
OA90	5p
OA91	5p
OA202	7p
IN4148	5p
BA114	8p

BRUSHED ALUMINIUM PANELS

12in × 6in=**25p**; 12in × 2½in=**10p**; 9in × 2in=**7p**

SLIDER POTENTIOMETERS

86mm × 9mm × 16mm, length of track 59mm.
SINGLE 10K, 25K, 100K log. or lin. **40p**.
DUAL GANG, 10K + 10K etc. log. or lin. **60p**.
KNOB FOR ABOVE **12p**.
FRONT PANEL **65p**.
18 Gauge panel 12in × 4in with slots cut for use with slider pots. Grey or matt black finish complete with fixings for 4 pots.

THERMISTORS

VA1055S	15p
VA1066S	15p
VA1077	15p
R53	£1·35

COMPACT CASSETTES—IN PLASTIC LIBRARY BOX

C90	65p
C120	85p

MULLARD POLYESTER CAPACITORS C296 SERIES

400V: 0·001μF, 0·0015μF, 0·0022μF, 0·0033μF, 0·0047μF, **2½p.** 0·0068μF, 0·01μF, 0·015μF, 0·022μF, 0·033μF, **3p.** 0·047μF, 0·068μF, 0·1μF, **4p.** 0·15μF, **6p.** 0·22μF, **7½p.** 0·33μF. **11p.** 0·47μF, **13p.**
160V: 0·01μF, 0·015μF, 0·022μF, 0·033μF, 0·047μF, 0·068μF, **3p.** 0·1μF **3½p.** 0·15μF **4½p.** 0·22μF, **5p.** 0·33μF, **6p.** 0·47μF, **7½p.** 0·68μF, **11p.** 1·0μF, **13p.**

MULLARD POLYESTER CAPACITORS C280 SERIES

250V P.C. mounting: 0·01μF, 0·015μF, 0·022μF, **3p.** 0·033μF, 0·047μF, 0·068μF, **3½p.** 0·1μF, **4p.** 0·15μF, 0·22μF, **5p.** 0·33μF, **6½p.** 0·47μF, **8½p.** 0·68μF, **11p.** 1·0μF, **13p.** 1·5μF, **20p.** 2·2μF, **24p.**

MYLAR FILM CAPACITORS 100V

0·001μF, 0·002μF, 0·005μF, 0·01μF, 0·02μF, **2½p.** 0·04μF, 0·05μF, 0·068μF, 0·1μF, **3½p.**

CERAMIC DISC CAPACITORS

100pF to 10,000pF, **2p** each.

ELECTROLYTIC CAPACITORS—MULLARD 015/6/7 RANGE REPLACES C426, C457 RANGES.

(μF/v) 1·0/63, 1·5/63, 2·2/63, 3·3/63, 4·7/63, 6·8/40, 10/25, 10/63, 15/16, 15/40, 15/63, 22/10, 22/25, 22/63, 33/6·3, 33/40, 47/4, 47/10, 47/25, 47/40, 47/63, 68/6·3, 68/16, 100/4, 100/10, 100/25, 100/40, 150/6·3, 150/16, 150/25, 220/4, 220/10, 220/16, 330/4, 330/10, 470/6·3, **5p** each. 68/63, 150/40, 220/25, 330/16, 470/10, 680/6·3, 1,000/4, **9p.** 100/63, 150/63, 220/40, 470/25, 680/16, 1,000/10, 1,500/6·3, **12p.** 220/63, 470/40, 680/25, 1,000/16, 1,500/10, 2,200/6·3, **15p.** 330/63, 680/40, 1,000/25, 1,500/16, 2,200/10, 3,300/6·3, 4,700/4, **18p.**

SOLID TANTALUM BEAD CAPACITORS 12p

0·1μF	35V	2·2μF	35V	22μF	16V
0·22μF	35V	4·7μF	35V	33μF	10V
0·47μF	35V	6·8μF	25V	47μF	6·3V
1·0μF	35V	10μF	25V	100μF	3V

ELECTROLYTIC CAPACITORS Miniature P.C. mounting 5p each.

(μF/V): 10/12, 50/12, 100/12, 200/12, 5/25, 10/25, 25/25, 100/25.

VEROBOARD

	0·1	0·15
2½ × 3¾	22p	16p
2½ × 5	24p	24p
3¾ × 3¾	24p	24p
3¾ × 5	27p	27p
17 × 2½	75p	57½p
17 × 3¾	100p	78p
17 × 5 (plain)	—	82p
17 × 3¾ (plain)	—	60p
17 × 2½ (plain)	—	42p
2½ × 5 (plain)	—	12p
2½ × 3¾ (plain)	—	11p
Pin insertion tool	52p	52p
Spot face cutter	42p	42p
Pkt. 50 pins	20p	20p

JACK PLUGS AND SOCKETS

Standard screened	18p	2·5mm insulated	8p
Standard insulated	12p	3·5mm insulated	8p
Stereo screened	35p	3·5mm screened	13p
Standard socket	15p	2·5mm socket	8p
Stereo socket	18p	3·5mm socket	8p

D.I.N. PLUGS AND SOCKETS

2 pin, 3 pin, 5 pin 180°, 5 pin 240°, 6 pin
Plug 12p. Socket 8p.
4 way screened cable, **15p**/metre.
6 way screened cable **22p**/metre.

BATTERY ELIMINATOR £1·50

9V mains power supply. Same size as PP9 battery.

LARGE (CAN) ELECTROLYTICS

1600μF	64V	74p	2500μF	64V	80p	4500μF	16V	50p
2500μF	40V	74p	2800μF	100V	£2·60	4500μF	25V	£1·68
2500μF	50V	58p	3200μF	16V	50p	5000μF	50V	£1·10

HIGH VOLTAGE TUBULAR CAPACITORS—1,000 VOLT

0·01μF	10p	0·047μF	13p	0·22μF	20p
0·022μF	12p	0·1μF	13p	0·47μF	22p

POLYSTYRENE CAPACITORS 160V 2½%

10pF to 1,000pF E12 Series Values **4p each.**

SMOKE AND COMBUSTIBLE GAS DETECTOR—GD1 £2

The GD1 is the worlds first semiconductor that can convert a concentration of gas or smoke into an electrical signal. The sensor decreases its electrical resistance when it absorbs deoxidizing or combustible gases such as hydrogen, carbon monoxide, methane, propane, alcohol, North Sea gas, as well as carbon-dust containing air or smoke. This decrease is usually large enough to be utilized without amplification. Full details and circuits are supplied with each detector.

PRINTED BOARD MARKER 97p

Draw the planned circuit onto a copper laminate board with the P.C. Pen, allow to dry, and immerse the board in the etchant. On removal the circuit remains in high relief.

LARGE RANGE ITT/TEXAS IC's NOW IN STOCK

PRICES ARE CALCULATED ON TOTAL NUMBER ORDERED REGARDLESS OF MIX

INTRODUCTORY OFFER: 15% DISCOUNT ON THE PRICES OF IC's ON ALL ORDERS RECEIVED BEFORE THE END OF MARCH, 1973

	1–11 p	12–24 p	25–99 p	100+ p
7400	18	16	14	13
7401	18	16	14	13
7402	18	16	14	13
7403	18	16	14	13
7404	20	18	16	14
7405	20	18	16	14
7406	50	45	40	35
7407	56	50	44	38
7408	36	30	27	23
7409	36	30	27	33
7410	18	16	14	13
7411	23	21	20	18
7412	36	30	27	23
7413	34	28	26	22
7416	45	43	39	34
7420	18	16	14	13
7421	36	30	27	23
7426	32	29	23	20
7430	20	18	16	14
7432	40	36	32	28
7440	20	18	16	14
7441	80	75	70	65
7442	80	75	70	65
7443	125	120	115	115
7447	175	165	150	120
7448	185	175	170	165
7450	18	16	14	13
7451	18	16	14	13
7453	18	16	14	13
7454	18	16	14	13
7460	18	16	14	13
7470	30	28	25	24
7472	30	28	27	23
7473	40	38	36	30
7474	40	36	32	28
7475	55	52	50	49
7476	40	36	32	30
7480	100	95	90	85
7481	125	115	110	105
7482	100	96	90	85
7483	100	97	95	92
7484	120	115	110	105
7485	250	245	240	230
7486	45	42	37	33
7490	75	67	60	52
7491A	100	92	85	79
7492	75	70	65	60
7493	75	68	60	52
7494	95	90	85	80
7495	105	100	95	90
7496	100	95	90	85
74100	250	240	235	230
74118	100	82	73	64
74121	43	40	38	36
74141	100	95	90	85
74145	150	140	135	130
74150	330	280	250	220
74151	110	100	95	89
74153	120	110	105	95
74154	200	180	170	160
74155	150	120	100	86
74156	130	120	100	96
74180	155	136	112	105
74190	195	190	185	180
74191	195	190	185	180
74192	200	190	180	164
74193	200	180	170	150
74196	200	190	180	170
74197	200	195	180	170

LINEAR IC's

709	14 pin DIL	32p
741	8 pin DIL	34p
741	14 pin DIL	28p
723	14 pin DIL	95p
747	14 pin DIL	85p
748	8 pin DIL	35p
DIL socket,	14 pin and 16 pin	16p

Sinclair Project 60

Now—the Z.50 Mk.2

with built-in automatic transient overload protection

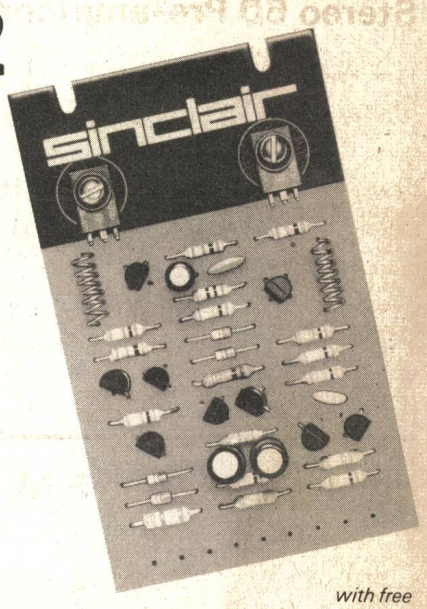

with free manual
£5.48

When originally introduced, the Sinclair Z.50 proved how it was possible to design and produce a popularly priced modular power amplifier having characteristics to challenge the world's costliest amplifiers. Many thousands of Z.50's are now giving excellent service day in, day out. But we have also learned that constructors do not always use their Z.50's ideally. That is why we have introduced modifications whereby risk of damage through mis-use is greatly reduced and performance further enhanced. The Z.50 Mk.2 has improved thermal stability, more accurately regulated D.C. limiting to ensure more symetrical output voltage swing and clipping and still less distortion at lower power. Z.50 Mk.2 is compatible with all other Project 60 modules, and may be incorporated to advantage in existing systems. Eleven silicon epitaxial planar transistors are now used, two more than in the original Z.50; circuitry has been re-designed, making this versatile high performance amplifier better than ever.

Z.30 the power amplifier for quality and economy

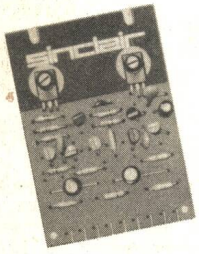

with free manual
£4.48

The Z.30 provides excellent facilities for the constructor requiring a high fidelity audio system of less power than that available from Z.50's. Using a power supply of 35 volts, Z.30 will deliver 15 watts RMS into 8 ohms, or 20 watts RMS into 3 ohms using 30 volts. Total harmonic distortion is a fantastically low 0.02% at 15 watts into 8 ohms with signal to noise ratio better than 70 dB unweighted. Input sensitivity 250mV into 100K ohms. Size 80 x 57 x 13 mm ($3\frac{1}{8}$ x $2\frac{1}{4}$ x $\frac{1}{2}$) Z.30, Z.50 and Z.50 MK.2 modules are compatible and interchangeable.

Brilliant new technical specifications

Input impedance 100 KΩ
Input (for 30w into 8Ω) 400mV
Signal to noise ratio, referred to full o/p at 30v HT 80dB or better
Distortion 0.02% up to 20W at 8Ω. See curve
Frequency response 10Hz to more than 200 KHz ±1dB
Max. supply voltage 45v (4Ω to 8Ω speakers) (50v 15Ω speakers only)
Min. supply voltage 9v
Load impedance – minimum : 4Ω at 45v HT
Load impedance – maximum : safe on open circuit

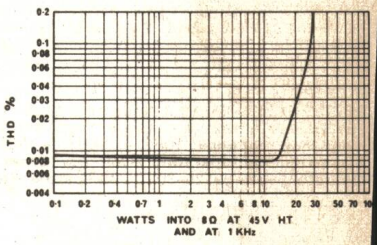

Guarantee

If, within 3 months of purchasing any product direct from Sinclair Radionics Ltd., you are dissatisfied with it, your money will be refunded at once. Many Sinclair appointed Stockists also offer this same guarantee in co-operation with Sinclair Radionics Ltd.

Each Project 60 module is tested before leaving our factory and is guaranteed to work perfectly. Should any defect arise in normal use, we will service it at once and without any charge to you, if it is returned within two years from the date of purchase. Outside this period of guarantee a small charge (typically £1.00) will be made. No charge is made for postage by surface mail. Air Mail is charged at cost.

sinclair

Typical Project 60 applications

System	The Units to use	together with	Units cost
Simple battery record player	**Z.30**	Crystal P.U., 12V battery volume control, etc.	**£4.48**
Mains powered record player	**Z.30, PZ.5**	Crystal or ceramic P.U. volume control, etc.	**£9.45**
12W. RMS continuous sine wave stereo amp. for average needs	**2 x Z.30s, Stereo 60; PZ.5**	Crystal, ceramic or mag. P.U., F.M. Tuner, etc.	**£23.90**
25W. RMS continuous sine wave stereo amp. using low efficiency (high performance) speakers	**2 x Z.30s, Stereo 60; PZ.6**	High quality ceramic or magnetic P.U., F.M. Tuner, Tape Deck, etc.	**£26.90**
80W. (3 ohms) RMS continuous sine wave de luxe stereo amplifier. (60W. RMS into 8 ohms)	**2 x Z.50s, Stereo 60; PZ.8, mains transformer**	As above	**£34.88**
Indoor P.A.	**Z.50, PZ.8, mains transformer**	Mic., guitar, speakers, etc., controls	**£19.43**

F.M. Stereo Tuner **(£25)** & A.F.U. **(£5.98)** may be added as required.

the world's most advanced high fidelity modules

Stereo 60 Pre-amp/control unit

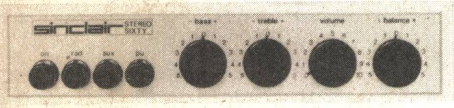

Designed specifically for use on Project 60 systems, the Stereo 60 is equally suitable for use with any high quality power amplifier. Since silicon epitaxial planar transistors are used throughout, a really high signal-to-noise ratio and excellent tracking between channels is achieved. Input selection is by means of press buttons, with accurate equalisation on all input channels. The Stereo 60 is particularly easy to mount.

SPECIFICATIONS—Input sensitivities: Radio – up to 3mV. Mag. p.u. 3mV: correct to R.I.A.A. curve ±1dB:20 to 25,000 Hz. Ceramic p.u. – up to 3mV: Aux – up to 3mV. **Output:** 250mV. **Signal to noise ratio:** better than 70dB. **Channel matching:** within 1dB. **Tone controls:** TREBLE+12 to —12dB at 10KHz: BASS +12 to —12dB at 100Hz. **Front panel:** brushed aluminium with black knobs and controls. **Size:** 66 x 40 x 207mm.

Built, tested and guaranteed. **£9.98**

Project 60 Stereo F.M. Tuner

The phase lock loop principle was used for receiving signals from space craft because of its vastly improved signal to noise ratio. Now, Sinclair have applied the principle to an F.M. tuner with fantastically good results. Other advanced features include varicap diode tuning, printed circuit coils, an I.C. in the specially designed stero decoder and switchable squelch circuit for silent tuning between stations. In terms of high fidelity this tuner has a lower level of distortion than any other tuner we know. Stereo broadcasts are received automatically, a panel indicator lighting up as the stereo signal is tuned in. This tuner can also be used to advantage with most other high fidelity systems.

SPECIFICATIONS—Number of transistors: 16 plus 20 in I.C. **Tuning range:** 87.5 to 108MHz. **Sensitivity:** 7μV for lock-in over full deviation. **Squelch level:** Typically 20μV. **Signal to noise ratio:** >65dB. **Audio frequency response:** 10Hz – 15KHz (±1dB). **Total harmonic distortion:** 0.15% for 30% modulation. **Stereo decoder operating level:** 2μV. **Cross talk:** 40dB. **Output voltage:** 2 x 150mV R.M.S. maximum **Operating voltage:** 25–30VDC. **Indicators:** Stereo on; tuning. **Size:** 93 x 40 x 207mm.

Built and tested. Post free. **£25**

Super IC.12 Integrated circuit high fidelity amplifier

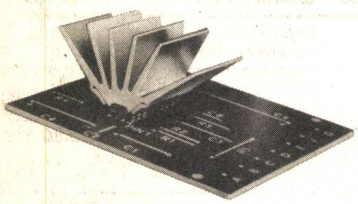

Having introduced Integrated Circuits to hi-fi constructors with the IC.10, the first time an IC had ever been made available for such purposes, we have followed it with an even more efficient version, the Super IC.12, a most exciting advance over our original unit. This needs very few external resistors and capacitors to make an astonishingly good high fidelity amplifier for use with pick-up, F.M. radio or small P.A. set up, etc. The free 40 page manual supplied, details many other applications which this remarkable IC. make possible. It is the equivalent of a 22 transistor circuit contained within a 16 lead DIL package, and the finned heat sink is sufficient for all requirements. The Super IC.12 is compatible with Project 60 modules which would be used with the Z.50 and Z.30 amplifiers. Complete with free manual and printed circuit board.

SPECIFICATIONS

Output power: 6 watts RMS continuous (12 watts peak). 6–8Ω. **Frequency Response:** 5Hz to 100KHz±1dB. **Total Harmonic Distortion:** Less than 1%. (Typical 0·1%) at all output powers and frequencies in the audio band (28V). **Load Impedance:** 3 to 15 ohms. **Input Impedance:** 250 Kohms nominal. **Power Gain:** 90dB (1,000,000,000 times) after feedback. **Supply Voltage:** 6 to 28V. **Quiescent current:** 8mA at 28V. **Size:** 22×45×28mm including pins and heat sink..

Manual available separately 15p post free.

With FREE printed circuit board and 40 page manual.
£2.98 Post free

Power Supply Units
The new PZ.8 Mk.3

The most reliable power supply unit ever made available to constructors. Brilliant circuitry makes failure from over load and even direct shorting of the output impossible. This is due to an ingenious re-entrant current limiting principle which, as far as we know has never before been available in any comparable unit outside the most expensive laboratory equipment. Ripple and residual noise have been reduced to the point of almost total elimination. This is, of course, the perfect unit for Project 60 assemblies, particularly where the new Z.50 MK.2 amplifiers are used. Nominal working voltage – 45.

PZ.8 Mk.3—£7.98
(Mains transformer, if required) £5.98
PZ.5 30v. unstabilised
(not suitable for Project 60 tuner) **£4.98**
PZ.6 35v. stabilised
(not suitable for IC. 12) **£7.98**

Project 605

the easy way to buy and build Project 60 without soldering

Project 605 in one pack contains: one PZ.5, two Z.30's, one Stereo 60 and one Masterlink, which has input sockets and output components grouped on a single module and all necessary leads cut to length and fitted with clips to plug straight on to the modules thus eliminating all soldering.

Complete with comprehensive manual, post free **£29.95**
All you need for a superb 30 watt high fidelity stereo amplifier

Order form

Please send _____
I enclose cash/cheque/money order.

Name _____

Address _____

_____

_____ **PE/4/73**

SINCLAIR RADIONICS, Business Reg. No. 699483:
London Rd, St. Ives, Hunts. PE17 4HJ

sinclair

CRESCENT RADIO LTD

11 & 40 MAYES ROAD, LONDON N22 6TL 888 3206

MAIL ORDER DEPT. No. 11 MAYES RD. LONDON N22 6TL

COMPONENTS AND HI FI FOR THE HOME CONSTRUCTOR

OUR SHOPS ARE OPEN ALL DAY FROM 9 A.M. TO 6 P.M. 6.30 P.M. ON FRIDAY (WE CLOSE ALL DAY THURSDAY)

13 SOUTH MALL, EDMONTON, N.9 803 1685

LOW VOLTAGE AMPLIFIER

5 transistor amplifier complete with volume control, is suitable for 9V d.c. and a.c. supplies. Will give about 1W at 8 ohm output.
With high IMP input this amplifier will work as a record player, baby alarm, etc., amplifier.

£1·75 plus 13p P. & P.

TRI-VOLT BATTERY ELIMINATOR

Enables you to work your Transistor Radio, Amplifier or Cassette, etc., from the a.c. mains through this compact Eliminator. Just by moving a plug you can select the voltage you require, 6, 7½ or 9 volt. This means all your transistor power pack applications can be handled by this one unit. Approx. size 2¾in × 2¼in × 3¼in. Our Price **£2·75** plus 10p P. & P. Same model suitably wired for the Philips Cassette **£3** plus 10p P. & P.

DIGITAL CLOCK KIT

24-hr. Nixie dig. clock kit. We supply: a complete set of components; a complete set of easy to follow instructions; printed circuits made to make construction as simple as possible; a cabinet and front panel to give a professional finish. All for the price of the components. **£22·50** + 50p P. & P. Please send S.A.E. if you require more information.

EA1000 3 WATT AUDIO AMPLIFIER

An Audio Amplifier designed around the TAA621 Linear I.C.:—

Supply Voltage	9–24V
Speaker Imp.	8–16 ohm
Frequency	50Hz–25kHz
Overall Size	2in × 3in × ¾in

Ideal Amplifier for radios, record players, stereo units, etc.
Full technical data and diagrams with each module. All guaranteed and a bargain at **£2·63** + 5p P. & P.

V.A.T.
From 1st April, 1973, will you please include on your Total (Goods plus Postage and Packing) Value Added Tax at the Standard Stated Rate.

MINI LOUDSPEAKERS

2¼in 8 ohm	50p
2¼in 80 ohm	50p
2¼in 40 ohm	50p

Please include 5p P. & P. on each L.S.

MAINS TRANSFORMER

Fused Primary 240V. Secondary 220V @ 50mA. 6·3V @ 1A. This transformer is made to a very high standard and is a small size: 2in × 2¼in × 2¼in. **63p** plus 15p P. & P.

S. G. BROWN "DIPLOMAT" MONO/STEREO HEADSET. Finest quality British made Lightweight Headphones. Incorporate ceramic piezo electric transducers. *Specification:*—Frequency—20–17,500 CPS. Impedance—Predominantly capacitive, at ·001MFD per earpiece can be regarded as 150K at 1kcs. Weight—3·5oz. (98 grams). Please include 10p per set P.P. A Bargain at **£1·50** each set.

TRI-VOLT CAR SUPPLY

Enables you to work your Transistor Radio, Amplifier or Cassette, etc. from the 12 volt car supply. Positive or negative earth. Approx. size = 2in. × 3¼in. × 1¼in. This converter supplies 6, 7½ or 9 volts and is transistor regulated. A real money saving device for **£2·50** plus 10p P. & P.

MINIATURE RELAY

6 volt 70 ohm.
Single Pole Changeover **40p** plus 5p P. & P.
Approx. size = 1½in. × 1in. × ¾in.

ADD LUXURY TO YOUR CAR

WITH A MOTOR DRIVEN CAR AERIAL

Spec.: 5 Section
Extended Length 100cm
Length under Fender 40cm
Cable Length 120cm

Supplied complete with Fixing Bracket and Control Switch. **£5·75** plus 25p P. & P.

EMI LOUDSPEAKER 450

10W 13in × 8in ± two 2·2½in tweeters and cross-over. All wired and ready for use. This ever-popular 450 in 3–8–15 ohm imp. **£3·75** plus 38p P. & P. each.

CRESCENT CASSETTES

Top quality cassettes at unbeatable prices (complete with standard storage case): C60 **28p**, C90 **38p**, C120 **48p** plus 5p P. & P.

PSYCHEDELIC LIGHT CONTROL UNIT

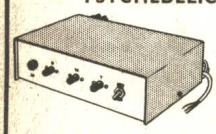

Three Channel: Bass—Middle—Treble. Each channel has its own sensitivity control. Just connect the input of this unit to the loudspeaker terminals of an amplifier, and connect three 250V up to 500W lamps to the output terminals of the unit, and you produce a fascinating sound-light display. (All guaranteed) **£18·50** plus 38p P. & P.
If you require more information please send S.A.E.

"CRESCENT" 100 WATT R.M.S. ALL PURPOSE AMPLIFIER U.BUILD.IT

We supply the three modules for you to build this Disco-Group-P.A. amplifier into the cabinet of your choice.

★ **THE POWER AMP MODULE TP100W**
170W r.m.s. sq. wave 300W instantaneous peak into 8 ohm (60W into 16 ohm). **£14·28** carr. 45p

★ **THE PRE-AMP MODULE**
Four control pre-amp, Vol, Bass, Treble. Middle controls. Designed to drive most amplifiers using F.E.T. first stage. **£3·96** carr. 25p

★ **THE POWER SUPPLY MODULE PS100**
Is supplied complete with the mains transformer. **£9·66** carr. 50p
Complete fixing instructions are supplied and no technical knowledge is required to connect the three ready wired modules.
A fantastic bargain. If you purchase all three modules. **£25** carr. 75p
Send S.A.E. for further details on this or our ready built amplifiers.

BRIGHTNESS CONTROL

Full control over 300 watts of incandescent lighting. Thyristor light dimmer mounted on a standard switch block ready to fit into a MK. Box. Enjoy the pleasure of having the precise amount of light you require at any time. Our Price **£2·75** plus 8p P.& P. each.

PHOTOELECTRIC KIT

CONTENTS. P.C. Chassis Board, Chemicals, Etching Manual, Infra-Red Photo-transistor, Latching Relay, 2 Transistors, Diode, Resistors, Gain Control, Terminal Block, Elegant Case, Screws, etc. In fact everything you need to build a Steady-Light Photo-Switch/Counter/Burglar Alarm, etc. (Project No. 1) which can be modified for modulated-light operation with a few additional components.

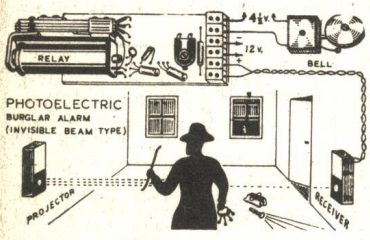

PHOTOELECTRIC KIT
£2·85
Postage and Pack. 15p (U.K.)
Commonwealth
SURFACE MAIL 25p
AIR MAIL £1·40
Australia, New Zealand, S. Africa, Canada and U.S.A.
Also Essential Data Circuits and Plans for Building
10 Advanced Designs

INVISIBLE BEAM OPTICAL KIT

Everything needed (except plywood) for building: 1 Invisible-Beam Projector and 1 Photocell Receiver (as illustrated). Suitable for all Photoelectric Burglar Alarms, Counters, Door Openers, etc.
CONTENTS: 2 lenses, 2 mirrors, 2 45-degree wooden blocks. Infra-red filter, projector lamp holder, screws, nails, brackets, building plans, etc. Price **£1·45**. Postage and Pack. 10p (U.K.). Commonwealth: Surface Mail 20p, Air Mail 50p.

LONG RANGE INVISIBLE BEAM OPTICAL KIT

CONTENTS: As above. Twice the range of standard kit. Larger Lenses, Filter, etc. Price **£2·10**. Postage 15p (U.K.). Commonwealth: Surface 20p, Air Mail £1·15.

BIOFEEDBACK AMPLIFIER KIT

Tunable, General-Purpose, Interference-Rejecting Differential Amplifier for experimental investigation of signals produced by the brain, heart and muscles. When used with an oscilloscope, or aural indicator, it enables you to monitor your brain-waves, learn to relax, meditate, etc.
CONTENTS: All Capacitors, Resistors, Pots, Semiconductors, I.C., Electrodes, Leads, Chassis, Case, Batteries, Plans and Instructions. Price **£4·75** postage and pack. 25p (U.K.). Commonwealth: Surface 30p. Air Mail £1.

ALPHA-BETHA-THETA BRAINWAVE MONITOR KIT

Aural Brainwave Indicator for use with a Biofeedback Amplifier. Converts subsonic brain frequencies into audible signals for easy recognition.
CONTENTS: Resistors, Pots, Capacitors, Transistors, Diodes, Leads, Chassis, Case, Earphone, Battery, Plans and Instructions. Price **£3·25**, postage and pack. 15p (U.K.). Commonwealth: Surface 25p. Air Mail 75p.

YORK ELECTRICS Mail Order Dept.
335 BATTERSEA PARK ROAD, LONDON, S.W.11
Send S.A.E. for full details, a brief description of all Kits and Projects

COMPARE OUR PRICES

Speaker Bargains	£p
E.M.I. 13in × 8in 3, 8 & 15 ohms plain	2·00
with tweeter	2·25
twin tweeter	3·50
Type 350 ·20 watt with tweeter 8 ohms. P.P. 37p.	7·25
8in × 5in 3, 8 & 15 ohms	1·30
7in × 4in 3 & 8 ohms	1·05
FANE 8in 8 ohm, dual cone	2·30
CELESTION 8in 15 ohm	1·50
BAKER GROUP 25 12in 25W 8 or 15 ohm	5·75
Postage 25p per speaker	
2¼in 8 or 64 ohm P.P. 10p	50

Kit-form cabinets, teak	
(17in × 10in × 6in) with a 13in × 8in or 8in cut out	2·75
(12in × 12in × 6in) with a 8in × 5in or 8in cut out. (please specify cut out)	2·25

Add 35p per Cabinet for post & packing

Microphone Bargains	£p
MIC45 "ACOS" metal case, crystal hand	95
CM 20 Crystal Hand	45
DX143 Dynamic, cassette-type stick	1·00
MIC60 "ACOS" stick crystal	1·00
CM70 PLANET stick metal, switch crystal	1·45
DM160 Dynamic uni-dir, ball metal	3·75
UD130 50K/600 ohm uni-dir, ball metal	4·50
TW209 Lesson dual imp ball metal uni-dir	5·75
Condenser Mike uni-dir 600 ohm	7·95
Guitar mike	45
Lapel type, crystal	40
Postage 17p each	

Cartridges—with standard fittings & stylii	£p
GOLDRING G850	3·25
GOLDRING G800	4·95

ACOS GP91/2SC or GP91/3SC stereo compatible	1·05
ACOS GP94 stereo ceramic	1·75
ACOS GP95 stereo crystal	1·35
ACOS GP96 stereo ceramic	1·75
9THAC Sonotone stereo ceramic (diamond)	1·95
9THAC/G Sonotone stereo ceramic (diamond) slimline	1·95
ACOS GP67/2C mono crystal	65
ACOS GP101 compatible crystal	75
19-TI Sonotone stereo crystal	90
Postage 5p per cartridge	

Battery Eliminators	
240v input 6 or 9v d.c. output at 150 mA	1·99
240v input 6, 7½ or 9v output at 300 mA	2·99
12v d.c. input (for cars) 6, 7½ or 9v d.c. output at 300 mA	2·99
P. & P. 10p	

Tapes—"MYLAR" base finest quality British made.

5in	600ft 36p	5¼in	1800ft 85p
5in	900ft 45p	7in	1200ft 55p
5in	1200ft 60p	7in	1800ft 80p
5¼in	900ft 49p		
5¼in	1200ft 55p	7in	2400ft 95p

Postage 9p each

Plastic Library Cases for
5in Reels 16p
5¼in Reels 19p
7in Reels 21p
P. & P. 5p each

THIS MONTH'S SPECIAL OFFER
Amstrad Stereo Headphones
Model HPS 5A with v. controls. Recommended retail price **£6·95**. Our price **£3·95**. P. & P. 25p

Slight price alterations due to V.A.T. will effect certain of our items after April 1st.

RIVERSDALE ELECTRONICS
Mail Order Dept. E4/73, P.O. Box 470, Manchester M60 4BU
SEND 25p FOR COMPLETE CATALOGUE
ALL OUR MERCHANDISE IS FULLY GUARANTEED

BRITAIN'S FASTEST SERVICE!

A SELECTION FROM OUR COMPREHENSIVE CATALOGUE

ALL ITEMS ARE BRAND NEW AND FULLY GUARANTEED

AA119	6p	BCY58	18p	CA3043	£1·73	OA81	8p	1N4007	19p	2N6027(D13T1)	45p
AC107	30p	BCY70	15p	CA3044	£1·42	OA90	8p	1N4148	4p		
AC126	20p	BCY71	30p	CA3046	86p	OA91	5p	1N5400	14p	3N84	£1·30
AC127	25p	BCY72	15p	CA3048	£2·34	OA95	5p	1N5404	18p	3N128	88p
AC128	24p	BD124	75p	CA3052	£1·80	OA200	6p	1N5408	25p	3N140	£1·05
AC128/AC176	36p	BD131	75p	CA3065	£1·80	OA202	7p	1S44	4p	3N152	£1·05
AC151	12p	BD132	75p	CA3088E	£1·38	OC20	97p	1S920	7p	3015F	£2·00
AC152	15p	BD131/132	£1·50	CA3090Q	£4·70	OC25	37p	1S940	6p	3015G	£2·00
AC153	19p	BDY20	92p	CD4001AE	72p	OC28	70p	1S5009	80p	7400	16p
AC153/176K	32p	BF115	23p	CD4009AE	£1·56	OC29	76p	1S5012	80p	7401	20p
AC176	16p	BF163	35p	CD4011AE	72p	OC35	60p	1S5015	75p	7402	20p
AC187	17p	BF173	19p	CD4012AE	£1·16	OC36	63p	1S5018	75p	7403	20p
AC188	23p	BF177	25p	CD4013AE	£1·48	OC41	40p	1S5024	75p	7404	25p
AC187/188K	40p	BF178	31p	CD4015AE	£3·90	OC42	40p	1S5047	75p	7405	25p
ACY17	27p	BF180	35p	CD4017AE	£3·90	OC44	20p	2N404	23p	7408	25p
ACY18	20p	BF194	15p	CD4018AE	£3·90	OC45	20p	2N696	15p	7409	25p
ACY19	20p	BF195	15p	CD4020AE	£4·34	OC71	20p	2N697	17p	7410	20p
ACY20	20p	BF196	15p	CD4024AE	£2·78	OC72	20p	2N698	30p	7413	30p
ACY21	19p	BF200	35p	CR1/051C	45p	OC75	25p	2N706	10p	7420	20p
ACY22	10p	BF254	14p	CR1/401C	60p	OC76	25p	2N706A	12p	7425	30p
AD140	55p	BF255	15p	CRS3/05AF	£1·08	OC77	40p	2N708	16p	7430	20p
AD149	50p	BFX13	25p	CRS3/40AF	£1·53	OC81	20p	2N911	50p	7440	24p
AD161	35p	BFX29	25p	CZ6	15p	OC81D	20p	2N914	20p	7442	£1·16
AD162	38p	BFX84	25p	D10 (NTGD10)	40p	OC83	23p	2N918	42p	7443	£1·45
AD161/162	70p	BFX85	34p	IRT84	£2·90	OC84	25p	2N929	25p	7444	£1·45
AF106	24p	BFX86	25p	LIC709C/5	42p	OC139	25p	2N930	28p	7445	£2·06
AF114	25p	BFX87	30p	LIC709C/8	42p	OC140	35p	2N1131	24p	7446	£1·45
AF115	25p	BFX88	24p	LIC723C/5	£1·02	OC170	25p	2N1132	24p	7447	£1·25
AF116	25p	BFY50	15p	LIC723C/14	£1·00	OC171	30p	2N1302	17p	7450	20p
AF117	25p	BFY51	15p	LIC741C/5	45p	OCP71M	42p	2N1303	17p	7451	20p
AF118	44p	BFY52	15p	LIC741C/8	40p	ORP12	50p	2N1304	24p	7453	20p
AF124	25p	BFY53	17p	MC1303L	£1·75	ORP60	40p	2N1305	24p	7454	20p
AF125	24p	BFY90	£1·05	MC1305P	£2·80	ORP61	40p	2N1306	30p	7460	20p
AF126	17p	BP101	75p	MC1307P	£1·65	ORP69	50p	2N1307	30p	7470	45p
AF139	30p	BPX66	£1·35	MC1310P	£2·95	PN70	9p	2N1308	34p	7472	32p
AF186	40p	BRY39	40p	MC1312P	£2·75	PN71	9p	2N1309	34p	7473	45p
AF239	36p	BSX19	16p	MC1330P	£2·95	PN107	7p	2N1559 (CR1/401C)	60p	7474	46p
AF279	47p	BSX20	16p	MC1352P	£2·00	PN108	7p	2N1613	15p	7475	45p
ASY26	25p	BSX21	20p	MC1352P	£2·00	PN109	7p	2N1711	15p	7476	45p
ASY27	30p	BSY27	20p	MC4024P	£2·20	PN3819(2N3819)	20p	2N1893	54p	7480	67p
ASY28	22p	BSY29	25p	MC4044P	£2·20	ST2	28p	2N2218	33p	7482	87p
ASY29	30p	BSY95A	12p	MC4044P	£2·20	SL103A	50p	2N2218A	44p	7483	£1·32
BA138	15p	BY100	20p	MFC6030	£1·63	SL403A (Rect)	60p	2N2219	38p	7486	33p
BAX16	8p	BY127	22p	MFC6040	£1·15	SL803A	80p	2N2219A	53p	7490	60p
BB103	16p	BTY79/400R	92p	MFC8010	£1·38	SL403D		2N2368	17p	7491A	£1·28
BB104	28p	BT106	£1·20	MFC8040	£1·24	(IC Amp.)	£1·50	2N2369	17p	7492	85p
BB105	32p	BZY88C3V3	13p	MFC9020	£2·12	TAA263	75p	2N2369A	17p	7493	75p
BC107	10p	BZY88C3V6	13p	MJE371	68p	TAA293	97p	2N2484	42p	7494	£1·13
BC107/BC177		BZY88C3V9	13p	MJE520	65p	TAA310	£1·25	2N2646	45p	7495	80p
	24p	BZY88C4V3	13p	MJE521	62p	TAA320	75p	2N2904	44p	7496	£1·48
BC108	10p	BZY88C4V7	13p	MJE2955	£1·06	TAA861	45p	2N2904A	49p	74100	£1·64
BC108/BC178		BZY88C5V1	13p	MJE3055	66p	TAD100	£1·97	2N2905	65p	74107	52p
	23p	BZY88C5V6	13p	MJ480	97p	TAD110	£1·97	2N2905A	75p	74121	43p
BC109	10p	BZY88C6V2	13p	MJ481	£1·25	TIL112	£2·00	2N2924	18p	74141	£1·00
BC109/BC179		BZY88C6V8	13p	MJ491	£1·35	TIL209	35p	2N2925	20p	74150	£3·35
	24p	BZY88C7V5	13p	MJ802	£4·12	TIP31A	60p	2N2926	10p	74151	£1·10
BC109C	11p	BZY88C8V2	13p	MJ802/MJ4502	£8·56	TIP32A	70p	2N3053	27p	74153	£1·35
BC140	30p	BZY88C9V1	13p	MJ900	£1·80	TIP41A	85p	2N3054	50p	74154	£2·00
BC147	10p	BZY88C10V	13p	MJ1000	£1·50	TIP42A	£1·00	2N3055	50p	74155	£1·55
BC148	9p	BZY88C11V	13p	MJ4502	£4·44	TIS43	30p	2N3391A	29p	74156	£1·55
BC149	10p	BZY88C12V	13p	MPF102	37p	VA1066s	15p	2N3525	£1·04	74190	£1·80
BC157	12p	BZY88C13V	13p	MPF103(2N5457)	49p	VA1039	15p	2N3702	9p	74191	£1·80
BC158	11p	BZY88C15V	13p	MPF104(2N5458)	49p	VA1040	15p	2N3703	9p	74192	£1·74
BC159	12p	BZY88C16V	13p	MPF105(2N5459)	49p	VA1077	15p	2N3704	9p	74193	£1·74
BC147/157	22p	BZY88C18V	13p	NKT0033	46p	W005	30p	2N3705	9p	74196	£1·50
BC148/158	20p	BZY88C20V	13p	NKT211	96p	W01	31p	2N3706	9p	74197	£1·50
BC149/159	22p	BZY88C22V	13p	NKT212	25p	W02	32p	2N3707	9p	40250	66p
BC167	11p	BZY88C24V	13p	NKT213	25p	W04	33p	2N3708	7p	40309	40p
BC168	10p	BZY88C27V	13p	NKT216	25p	W06	35p	2N3709	9p	40310	60p
BC169	11p	BZY88C30V	13p	NKT217	46p	W08	44p	2N3710	9p	40311	42p
BC169C	12p	BZX61C7V5	23p	NKT218	50p	ZTX107	12p	2N3711	9p	40312	62p
BC177	14p	BZX61C8V2	23p	NKT223	25p	ZTX108	11p	2N3819	25p	40320	42p
BC178	13p	BZX61C9V1	23p	NKT271	27p	ZTX300	13p	2N3820	60p	40360	56p
BC179	14p	BZX61C10V	23p	NKT274	18p	ZTX302	18p	2N3823E	20p	40361	45p
BC182	10p	BZX61C11V	23p	NKT275	18p	ZTX303	15p	2N3826	30p	40362	45p
BC182L	10p	BZX61C12V	23p	NKT279A	20p	ZTX304	23p	2N3866	£1·10	40406	52p
BC183	9p	BZX61C13V	23p	NKT281	12p	ZTX314	11p	2N3904	28p	40407	40p
BC183L	10p	BZX61C15V	23p	NKT351	29p	ZTX320	30p	2N3906	28p	40408	54p
BC184	13p	BZX61C16V	23p	NKT401	75p	ZTX500	18p	2N4058	13p	40409	62p
BC184L	12p	BZX61C18V	23p	NKT402	71p	ZTX501	14p	2N4060	11p	40410	62p
BC212	12p	BZX61C20V	23p	NKT403	77p	ZTX502	15p	2N4061	11p	40430	£1·22
BC212L	12p	BZX61C22V	23p	NKT404	65p	ZTX503	18p	2N4062	11p	40432	£1·60
BC238	10p	BZX61C24V	23p	NKT405	60p	ZTX504	17p	2N4444	£2·20	40468A	52p
BC238/308	20p	BZX61C27V	23p	NKT406	79p	1N914	45p	2N4871	40p	40512	£1·95
BC257	9p	BZX61C30V	23p	NKT713	62p	1N3754	4p	2N5245	45p	40576	£1·70
BC258	8p	CA3004	£2·25	NKT773	29p	1N4001	20p	2N5457(MPF103)	49p	40600	70p
BC259	9p	CA3005	£1·50	NKT781	25p	1N4002	7p	2N5458(MPF104)	49p	40601	70p
BC307	12p	CA3011	92p	NTGD10	29p	1N4003	7p	2N5459(MPF105)	46p	40602	45p
BC308	10p	CA3013	£1·30	OA47	40p	1N4004	10p	2N5777	45p	40603	70p
BCY30	25p	CA3014	£1·52	OA79	8p	1N4005	10p			40669	£1·20
BCY31	48p	CA3018	88p			1N4006	12p			40673	68p
BCY32	50p	CA3018A	£1·19				15p			40739	£1·50
BCY33	20p	CA3020	£1·55								
BCY34	25p	CA3028A	88p								
BCY38	30p	CA3035	£1·52								

ELECTROLYTIC AXIAL LEADS

Mfd.	Working Voltage	Price	Mfd.	Working Voltage	Price
1·0	40v	7p	100	16v	6p
1·0	100v	5p	100	25v	6p
2·2	25v	7p	100	40v	7p
2·2	63v	5p	100	63v	10p
4·7	40v	5p	220	25v	8p
10	25v	5p	220	40v	9p
10	63v	6p	470	25v	12p
22	25v	6p	1000	25v	16p
22	40v	6p	2200	25v	30p
47	25v	6p	4700	16v	33p
47	40v	6p			

CAPACITORS—METALLISED POLYESTER

Stock values: MFD	Price each
0·01, 0·015, 0·022, 0·033	3p
0·047, 0·068, 0·10	4p
0·150, 0·220	5p
0·33	7p
0·47	8p
0·68	11p
1·0	14p
1·5	20p
2·2	24p

Order as "Polyesters" + Capacitance.

CAPACITORS—POLYSTYRENE

Axial leads, Clear encapsulation, 5% Tolerance. 160 volt working.

Stock values	Price each
100pF, 150pF, 220pF, 330pF, 470pF, 560pF, 680pF, 820pF, 1000pF, 1500pF, 2200pF, 3300pF, 4700pF, 5600pF, 6800pF,	3p

Order as: "Polystyrenes" + Capacitance.

ALUMINIUM HEAT SINKS

10DN **34p** (Plain Al undrilled)
10DDR **43p** (Plain Al drilled 2 x To3)

LOW PRICED DIL IC HOLDERS

DRD 7 14 Pin DIL **15p** DRD 8 16 Pin DIL **17p**

NYLON NUTS AND BOLTS

Cheese head screw bolts. Nuts with integral washer. Moulded in high density nylon. Ideal for mounting "live" assemblies, power transistors, etc.
Each pack consists of four nuts and four screw bolts.

Pack No.	Thread	Length	Quantity	Pack Price
HSN1	6BA	½"	4	10p
HSN3	6BA	¾"	4	10p

Order as "Nuts and Bolts" + Pack No.

OPTO ELECTRONICS—3 devices

from our range—OCP71—**42p**, ORP12—**50p**, TIL209 Red led **35p**

TEST PROBES

Probably the best test probes ever made. When you push a plunger a spring steel forked tongue pushes out and holds the components, wires etc., while you take readings etc. It won't let go until you release it.

KLEPS 30 Black and Red, per pair **£1·20**

RESISTORS—METAL OXIDE

Metal Oxide resistors by Electrosil. Ultra low noise, ¼ Watt, 2%. Available in the range E24 between 10 ohms and 1 Meg.
E24 series=1·0, 1·1, 1·2, 1·3, 1·5, 1·6, 1·8, 2·0, 2·2, 2·4, 2·7, 3·0, 3·3, 3·6, 3·9, 4·3, 4·7, 5·1, 5·6, 6·2, 6·8, 7·5, 8·2, 9·1, and their decades.
Type No. TR5 Price: **4p** each
Order as "Metox" + value.

RESISTORS—CARBON FILM

A range of miniature high stability resistors with very low noise characteristics and long life. Tolerances, ranges and wattages as indicated. (Wattage ratings are at max. limiting voltage).

Type No.	Wattage	Tol.	Range	Series	Price
UPM050	0·5	5%	10E-1M	E12	1p each
UPM050	0·5	10%	1M -4·7M	E12	1p each
UPM075	0·75	5%	10E-1M	E12	1p each
UPM075	0·75	10%	1M -4·7M	E12	1p each
UPM100	1·00	10%	10E-1M	E12	2½p each

ARROW SERVICE PLUS

10% DISCOUNT OVER £4
NO POSTAGE AND PACKING
TOP QUALITY PRODUCTS
ALWAYS BY RETURN
COMPREHENSIVE CAT. ⟹

EDUCATIONAL ORDERS A SPECIALITY

ARROW ELECTRONICS LTD.

Dept. PE 6

7 COPTFOLD ROAD
BRENTWOOD
ESSEX

I enclose PO/Cheque for 10p
Name .....
Address .....
Arrow Electronics Limited
Dept. PE 6
7 Coptfold Road
Brentwood,
Essex

TRANSFORMERS

MAINS ISOLATING SERIES
Primary 200-250 Volts Secondary 240 Volts Centre Tapped (120V) and Earth Shielded
ALSO AVAILABLE WITH 115/120V SEC. WINDING

Ref. No.	VA (Watts)	Weight lb	oz	Size cm.	P & P £	p
07	20	1	11	7·0 × 6·0 × 6·5	1·61	30
100	60	3	8	8·9 × 8·0 × 7·7	2·39	36
61	100	5	12	10·2 × 8·9 × 8·3	2·62	52
30	200	9	8	12·0 × 10·3 × 10·0	4·39	52
62	250	12	4	9·5 × 12·7 × 11·4	5·80	67
55	350	15	0	14·0 × 10·8 × 12·4	7·77	82
63	500	27	0	17·1 × 11·4 × 15·9	11·20	*
92	1000	40	0	17·8 × 17·1 × 21·6	20·63	*
128	2000	63	0	24·1 × 21·6 × 15·2	34·10	*

AUTO SERIES (NOT ISOLATED)

Ref. No.	VA (Watts)	Weight lb	oz	Size cm.	Auto Taps	P & P £	p
113	20		11	7·3 × 4·3 × 4·4	0-115-210-240	0·85	22
64	75	1	14	7·0 × 6·4 × 6·0	0-115-210-240	1·66	30
4	150	3	0	8·9 × 6·4 × 7·6	0-115-200-220-240	2·00	36
66	300	6	0	10·2 × 10·2 × 9·5	,, ,,	3·89	52
67	500	12	8	14·0 × 10·2 × 11·4	,, ,,	5·78	67
84	1000	16	0	11·4 × 14·0 × 14·0	,, ,,	10·49	82
93	1500	28	9	13·5 × 14·9 × 16·5	,, ,,	15·20	*
95	2000	40	0	17·8 × 16·5 × 21·6	,, ,,	19·84	*
73	3000	45	8	17·4 × 18·1 × 21·3	,, ,,	26·99	*

TOTALLY ENCLOSED 115V AUTO TRANSFORMERS
115V 500 Watt totally enclosed auto transformer, complete with mains lead and two 115V outlet sockets, **£7·87.** P & P 67p.
Also available a 20 Watt version. **£1·67.** P & P 22p.

LOW VOLTAGE SERIES (ISOLATED)
PRIMARY 200-250 VOLTS 12 AND/OR 24 VOLT RANGE

Ref. No.	Amps. 12V	24V	Weight lb	oz	Size cm.	Secondary Windings	P & P £	p
111	0·5	0·25		12	7·6 × 5·7 × 4·4	0-12V at 0·25A × 2	0·85	22
213	1·0	0·5	1	0	8·3 × 5·1 × 5·1	0-12V at 0·5A × 2	1·01	22
71	2	1	1	0	7·0 × 6·4 × 5·7	0-12V at 1A × 2	1·33	22
18	4	2	2	4	8·3 × 7·0 × 7·0	0-12V at 2A × 2	1·86	36
70	6	3	3	12	10·2 × 7·6 × 8·6	0-12V at 3A × 2	2·24	42
108	8	4	5	4	10·0 × 8·3 × 8·2	0-12V at 4A × 2	2·48	52
72	10	5	6	3	7·9 × 10·8 × 10·2	0-12V at 5A × 2	2·94	52
17	16	8	7	8	12·1 × 9·5 × 10·2	0-12V at 8A × 2	4·54	52
115	20	10	11	13	12·1 × 11·4 × 10·2	0-12V at 10A × 2	5·78	67
187	30	15	16	12	13·3 × 12·1 × 12·1	0-12V at 15A × 2	10·67	82
226	60	30	34	0	17·0 × 14·5 × 12·5	0-12V at 30A × 2	19·61	*

30 VOLT RANGE

Ref. No.	Amps.	Weight lb	oz	Size cm.	Secondary Taps	P & P £	p
112	0·5	1	4	8·3 × 3·7 × 4·9	0-12-15-20-24-30V	1·01	22
79	1·0	2	0	7·0 × 6·4 × 6·0	,, ,,	1·35	36
3	2·0	3	2	8·9 × 7·0 × 7·6	,, ,,	2·01	36
20	3·0	4	6	10·2 × 8·9 × 8·6	,, ,,	2·48	42
21	4·0	6	0	10·2 × 10·0 × 8·6	,, ,,	2·94	52
51	5·0	6	8	12·1 × 10·0 × 8·6	,, ,,	3·66	52
117	6·0	7	8	12·1 × 10·0 × 10·2	,, ,,	4·36	52
88	8·0	10	0	14·0 × 11·7 × 10·0	,, ,,	5·64	67
89	10·0	12	2	14·0 × 10·2 × 11·4	,, ,,	7·14	67

50 VOLT RANGE

Ref. No.	Amps.	Weight lb	oz	Size cm.	Secondary Taps	P & P £	p
102	0·5	1	11	7·0 × 7·0 × 5·7	0-19-25-33-40-50V	1·33	30
103	1·0	2	10	8·3 × 7·3 × 7·0	,, ,,	1·94	36
104	2·0	5	0	10·2 × 8·9 × 8·6	,, ,,	2·69	42
105	3·0	6	0	10·2 × 10·2 × 8·3	,, ,,	3·65	52
106	4·0	9	4	12·1 × 11·4 × 10·2	,, ,,	4·83	52
107	6·0	12	4	12·1 × 11·1 × 13·3	,, ,,	7·14	67
118	8·0	18	9	13·3 × 13·3 × 12·1	,, ,,	9·32	97
119	10·0	19	12	16·5 × 11·4 × 15·9	,, ,,	11·68	97

60 VOLT RANGE

Ref. No.	Amps.	Weight lb	oz	Size cm.	Secondary Taps	P & P £	p
124	0·5	2	4	8·3 × 9·5 × 6·7	0-24-30-40-48-60V	1·35	36
126	1·0	3	0	8·9 × 7·6 × 7·6	,, ,,	1·88	36
127	2·0	5	6	10·2 × 8·9 × 8·6	,, ,,	2·94	42
125	3·0	8	8	11·9 × 9·5 × 10·0	,, ,,	4·48	52
123	4·0	10	6	11·4 × 9·5 × 11·4	,, ,,	5·78	67
120	6·0	16	12	13·3 × 12·1 × 12·1	,, ,,	8·37	82
122	10·0	23	2	16·5 × 12·7 × 16·5	,, ,,	13·85	*

LEAD ACID BATTERY CHARGER TYPES

Ref. No.	Amps.	Weight lb	oz	Size cm.		P & P £	p
45	1·5	1	9	7·0 × 6·0 × 6·0	Please note, these units do not include rectifiers	1·34	30
5	4·0	3	11	10·2 × 7·0 × 8·3		2·03	42
86	6·0	5	12	10·2 × 8·9 × 8·3		3·07	52
146	8·0	6	4	8·9 × 10·2 × 10·2		3·49	52
50	12·5	11	14	13·3 × 10·8 × 12·1		5·20	67

All ratings are continuous. Standard construction: open with solder tags and wax impregnation. Enclosed styles to order.

FULL SPEC. TRANSISTORS

BC107/108/109 9·0p each	2N 3055 68p each	AD 161/162 60p pair
25+ 7p	+ mica and bushes	+ mica and bushes
100+ 6·5p	25+ 55p	25+ 55p
500+ 6p	100+ 45p	100+ 50p
Minimum order 10 pieces this range.	500+ 40p	500+ 45p
		1000+ 40p

AVOMETERS · MAINS KEYNECTOR
ELECTROSIL RESISTORS

***CARRIAGE VIA BRS**

BARRIE electronics
11 MOSCOW ROAD, QUEENSWAY
LONDON W2 4AH Tel: 01-229 6681/2
NEAREST TUBE STATIONS: BAYSWATER, QUEENSWAY

B.H. COMPONENT FACTORS LIMITED

SPECIAL RESISTOR KITS (¼W 5% or ½W 5% CARBON FILM)
10E12 Kit: 10 of each E12 value, 10 ohms—1M, a total of 610, **£2·80 net**
25E12 Kit: 25 of each E12 value, 10 ohms—1M, a total of 1,525, **£6·50 net**

POLYESTER CAPACITORS MULLARD C280 250V
μF: 0·01, 0·015, 0·022, 0·033, 0·047, 3p each; 0·068, 0·1, 0·15, 4p each; 0·22, 5p; 0·33, 7p; 0·47, 8p; 0·68, 10p; 1·0, 13p; 1·5, 20p; 2·2, 23p.

MULLARD POLYESTER CAPACITORS C296 SERIES
160V: (μF) 0·01, 0·015, 0·022, 2p; 0·047, 0·068, 3p; 0·15, 0·22, 4p; 0·33, 5p; 0·47, 6p; 0·68, 1·0, 10p.
400V: (μF) 0·001, 0·0015, 0·0022, 0·0033, 0·01, 2p; 0·015, 0·033, 3p; 0·068, 4p.

MINIATURE ELECTROLYTIC MULLARD C426 SERIES (5p each)
(μF/V) 1/63, 4/40, 8/40, 10/40, 10/64, 16/40, 20/64, 25/25, 32/10, 40/16, 64/10, 80/16, 80/25, 100/6·4, 125/16, 200/6·4, 200/10, 320/6·4, 125/10.
MULLARD C437: (μF/V) 64/64, **9p**; 160/25, **9p**; 160/40, **11p**; 640/6·4, **9p**; 1600/6·4, **14p.**

ELECTROLYTIC CAPACITORS. Tubular and large can
(μF/V) 2·5/50, **3p**; 4/10, 10/25, 16/15, 20/25, 25/15, 25/25, 40/6, 64/10, 200/6, 250/10, **4p**; 10/6, 10/50, 25/50, 32/50, 50/10, 64/25, 100/25, **5p**; 50/50, 64/40, 250/15, 1,000/3, **6p**; 100/50, 250/25, 400/10, 500/10, 500/12, 640/10, 1,000/6, **8p**; 500/25, **10p**; 500/50, **12p**; 1,000/12, **10p**; 1,000/25, 2,000/12, 2,500/12, **15p**; 1,000/50, **35p**; 2,000/25, **25p**; 2,500/25, **30p**; 2500/50, **55p**; 3,000/50, **65p**; 5,000/50, **85p**; 1,000/100, **60p**; 8/350, **12p**; 16/350, **17p**; 32/350, **22p.**

MINIATURE CERAMIC PLATE CAPACITORS
50V: (pF) 22, 27, 33, 39, 47, 56, 68, 82, 100, 120, 150, 180, 220, 270, 330, 390, 470, 560, 680, 820, 1K, 1K5, 2K2, 3K3, 4K7, 6K8. (μF) 0·01, 0·015, 0·022, 0·033, **2p.** 0·047, 30V, **3p.** 0·1, 1,100V, **5p.**
CARBON FILM RESISTORS ¼W 5%. 10 ohms—2·2M, ½W 5%, 22 ohms—1M, **1p** each or 100 for **55p**; 1,000 for **£4.**
METAL FILM RESISTORS 1W 5% 22 ohms—10M, **1½p** each or 100 for **£1.**

VEROBOARD	0·1	0·15
2½ × 5in	25p	25p
2½ × 3⅜in	23p	17p
3⅜ × 5in	29p	30p
3⅜ × 3⅜in	25p	25p
2½ × 1in 2 for	12p	12p
2½ × 5in (plain)	—	12p
2½ × 3⅜in (plain)	—	11p
5 × 3⅜in (plain)	—	20p
Insertion tool	54p	54p
Track cutter	40p	40p
Pins, pkt. 25	8p	8p

2 pin DIN Plug, **12p**; Skt., **10p.** 3 pin DIN Plug, **13p**; Skt., **10p.** 5 pin DIN Plug, 180°, **15p**; Skt., **12p.** Transistor Equiv. Book, **40p.** Carbon pots 5K–2M log, & lin, single **15p**, single with switch **24p**, dual **42p.**

IN4001	6p
IN4002	7p
IN4003	8p
IN4004	9p
IN914	6p
μL914	30p
OC71	12p
OC75	15p
OC83	18p

QUANTITY DISCOUNT
SPECIAL BULK BUY PRICES ARE AVAILABLE BY QUOTATION FOR LARGE PROJECTS

VAT: Please add VAT at the standard rate after 1st April

Screened wire, yd.	5p
Twin screened wire, yd.	9p
Stereo s.c. wire, yd.	9p
Quad screened wire, yd.	19p
3 core circ. mains cable White, 3 yds.	24p
Neon bulb 90V wire ended	5 for 20p
Preset skeleton pots 1K–1M	5p

C.W.O. only. P. & P. 10p on orders below £5.
Discount: £10—10%, £20—15%.
Export Order enquiries welcome

Dept. P.E. 61, CHEDDINGTON ROAD, PITSTONE
Near LEIGHTON BUZZARD, BEDS. LU7 9AQ
Tel.: Cheddington 668446 STD. (0296)
Inquiries—S.A.E. Catalogue FREE Callers please phone first.

AUTOMATIC EMERGENCY SUPPLY
250v 50 Hz—150 watt Inverter. Full kit of parts excluding meter. Circuit as appeared in December P.W. Complete kit—**£16·95** + 80p. P. & P.

OTHER INVERTERS AVAILABLE IN KIT FORM
150 Watt—**£13·50** + 60p P. & P. 75 Watt—**£7·80** × 60p P. & P.
300 Watt—**£17·90** + 85p P. & P. 40 Watt—**£5·20** + 40p P. & P.
25 Watt—**£2·60** + 20p P. & P.

All above operate from 12v. battery and give 250v.-50Hz. Output. 24 volt types are also available, alternative outputs or taps can be supplied. Transformers and/or Transistors can be supplied separately.

SPECIAL OFFER
12v. Fluorescent lights, suitable for tents, caravans, houses or secondary lighting for factories, hotels, etc. 12 inch—8 watt—**£3·40** post paid. 21 inch—13 watt—**£4·20** post paid. Large discounts available for quantities.

TEXAN AMPLIFIER
Fibre glass P.C. board—**£2·00** + 10p P. & P.
Transformer—**£4·00** + 30p P. & P.
Other components including Teak Cabinet—**£24·00** + Postage.

ASTRO ELECTRONICS
6 BARNES ROAD, CHESTERFIELD, DERBYSHIRE

A.M.C. ELECTRONICS LTD.

SCORPIO ELECTRONIC IGNITION UNIT

COMPLETE KIT WITH ALL PARTS AND COMPREHENSIVE CONSTRUCTION AND FAULT FINDING DATA

COMPLETE KIT	£11·00 + V.A.T.	post paid.
DATA	10p + V.A.T.	S.A.E. (Foolscap please).
TRANSFORMER	£2·30 + V.A.T.	post paid.
P.C.B. GLASS FIBRE	65p + V.A.T.	post paid.

LATEST NEWS — P.E. TRIFFID. P.C.B. 65p post free.
Please add 15p to orders under £1·50. Send S.A.E. for other itemised price

AMCEL, MAIL ORDER 160 DRAKE STREET, ROCHDALE LANCASHIRE OL16 1PY

SINE to SQUARE CONVERTOR
5Hz to 250kHz
9V operation. Sine input 1–15V—output 0–7V. Completely assembled with amplitude control and mark space preset, **£2·25** ea. P. & P. 15p.

MODERN TELEPHONES type 706. Two tone grey, **£3·75** ea. The same but black, **£2·75** ea. P. & P. 25p ea.
AS NEW type 706 **BLUE, £5** ea. P. & P. 25p.
Also **TOPAZ YELLOW £4·50** ea. P. & P. 25p.
STANDARD GPO DIAL TELEPHONE (black) with internal bell, **87p** ea. P. & P. 50p. Two for **£1·50.** P. & P. 75p. All telephones complete with bell and dial.

MULLARD ELECTROLYTICS
2200MFD 100V
10A (50°C)
70p each
BRAND NEW BOXED
10 off — 60p each
100 off — 45p each
47000 MFD 25V 28A
60p each
P. & P. 10p
LARGER REDUCTION FOR QUANTITY

POTENTIOMETERS
COLVERN 3 watt. Brand new, 5; 10; 25; 500 ohms; 1; 2·5; 5; 10; 25; 50K all at **13p** ea.
MORGANITE Special Brand new, 2·5; 10; 100; 250; 500K; 2·5 meg. 1in sealed, **17p** ea.
BERCO 2½ Watt. Brand new, 5; 10; 50; 250; 500 ohms; 1; 2·5; 5; 10; 25; 50K at **15p** ea.
STANDARD 2 meg. log pots. Current type **15p** ea.
INSTRUMENT 3in Colvern 5 ohm **35p** ea.; 50K and 100K **50p** ea.
BOURNS TRIMPOT POTENTIOMETERS. 10;, 20; 50; 100; 200; 500 ohms; 1; 2; 2·5; 5; 10; 25K at **35p** ea. ALL BRAND NEW.
RELIANCE P.C.B. mounting: 270; 470; 500 ohms; 10K at **35p** ea. ALL BRAND NEW.

20Hz to 200kHz WB SINE *AND* SQUARE GENERATOR
Four ranges. Independent amplitude controls, thermistor stabilised. Ready to use. 9V supply required. **£6·85** each. P. & P. 25p. (Not cased, not calibrated.)

WOBBULATOR
Sweeps 8 to 45MHz ready to use. 6·3V a.c. required. **£9** each. P. & P. 25p. (Not cased, not calibrated.)

HARTLEY TYPE 13A
ONLY £18·00
DOUBLE BEAM OSCILLOSCOPE
TB2Hz–750kHz. Band width 5·5MHz. Sensitivity 33Mv/cm. Calibration markers 100kHz and 1MHz. A completely reliable general purpose oscilloscope. Supplied with CIRCUIT DIAGRAM and Mains lead. Carr. £1·50.
As above. Complete with all accessories. **£25·00.** Carr. £1·50.
Many other oscilloscopes available.

GRATICULES. 12cm × 14cm in High Quality plastic. **30p** ea. P. & P. 5p.

MOTOR—miniature synchronous, size 1¾in × 2in × ¾in. 240V operation, 1 rpm. **25p** ea. P. & P. 5p.

SAVE THOSE EXPENSIVE IC's with an AP Test Clip. **£1** ea. P. & P. 10p.

P.C.B. pack S & D. Quantity 2 sq ft—no tiny pieces. **50p** plus P. & P. 20p.
FIBRE GLASS as above **£1** plus P. & P. 20p.

DELIVERED TO YOUR DOOR
1 cwt of Electronic Scrap chassis, boards, etc. No Rubbish. FOR ONLY **£3·50.**

LOOSE LEAF BINDERS. Blue plastic cover. 4 ring. Standard size. 4 for **£1.** P. & P. 35p. 25 for **£5.** Carr. £1.

Panel switches DPDT ex eq. **10p** ea.; DPST Brand new, **17p** ea.; DPST twice, brand new **25p** ea.
HEAVY DUTY 6 amp 2 pole c/o—**20p** ea.

FIRST TIME EVER at £42·50
Solartron CD711S2 Double Beam Oscilloscope d.c.—9MHz; 3mV/cm; trigger delay; crystal calibrator; 4in flat faced tube. In good working condition. Carriage £1·50.

ELECTRONIC TIMER UNITS—wall or bench mounting—2 Hybrid timer boards may be removed leaving excellent 12V battery charger; d.c. Power supply, etc. Price only **£2·50** incl. carriage.

CAPACITOR PACK—50 Brand new components only **50p.** P. & P. 17p.
POTS—10 different values. Brand new—**50p.** P. & P. 17p.
COMPONENT PACK consisting of 2·2 pole 2 amp push on/off switches; 4 pots, various, brand new; 250 resistors ¼ and ½ watt, many high stabs, etc. Fine value at **50p** per pack. P. & P. 17p.

TRIMMER PACK. 2 Twin 50/200pF ceramic 2 Twin 10/60pF ceramic; 2 min strip with 4 preset 5/20pF on each; 3 air spaced preset 30/100pF on ceramic base. ALL BRAND NEW, **25p** the lot. P. & P. 10p.

5 CRYSTALS 70 to 90kHz. Our choice, **50p.** P. & P. 15p.
Matched pairs, **50p** per pair. P. & P. 15p.

5 GOOD QUALITY MOVING COIL METERS, **£3.** P. & P. 37p.

MANUALS AVAILABLE

Cossor	Solartron	Advance	Telequipment
339	D300	DA	S31
1035	CT436	D2	S32A
1049	CD523S2	J	D43
E.M.I.	AD557	Furzehill	Hartley 13A
WM2	CD711S2	0160	CT38
WM8		1684	

This is only a small example of the manuals we have in stock, S.A.E. with your enquiries—we may be able to help.

CHILTMEAD LTD
7/9 ARTHUR ROAD, READING, BERKS. (rear Tech. College) Tel.: Reading 582605/65916

SUPERSOUND 13 HI-FI MONO AMPLIFIER

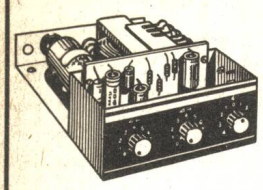

A superb solid state audio amplifier. Brand new components throughout. 5 silicon transistors plus 2 power output transistors in push-pull. Full wave rectification. Output approx. 13W r.m.s. into 8 ohm. Frequency response 12Hz—30KHz ±3db. Fully integrated pre-amplifier stage with separate Volume, Bass boost and Treble cut controls. Suitable for 8–15 ohm speakers. Input for ceramic or crystal cartridge. Sensitivity approx. 40mV for full output. Supplied ready built and tested, with knobs, escutcheon panel, input and output plugs. Overall size 3in high × 6in wide × 7¼in deep. A.C. 200/250V.

PRICE £10·50 P. & P. 25p.

DE LUXE STEREO AMPLIFIER

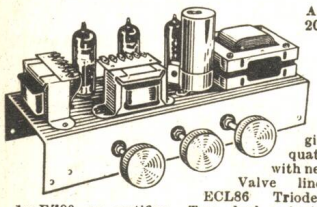

A.c. mains 200–240 volts. Using heavy duty fully isolated mains transformer with full wave rectification giving adequate smoothing with negligible hum. Valve line up:—2 × ECL86 Triode Pentodes. 1 × EZ80 as rectifier. Two dual potentiometers are provided for bass and treble control, giving bass and treble boost and cut. A dual volume control is used. Balance of the left and right hand channels can be adjusted by means of a separate "balance" control fitted at the rear of the chassis. Input sensitivity is approximately 300m/v for full peak output of 4 watts per channel (8 watts mono), into 3 ohm speakers. Full negative feedback in a carefully calculated circuit, allows high volume levels to be used with negligible distortion. Supplied complete with knobs, chassis size 11in. w × 4in. x. Overall height including valves 5in. Ready built and tested to a high standard. **Price £8·92.** P. & P. 45p.

NEW! POWER SUPPLY UNIT

200/240V A.C. input. Four switched fully smoothed D.C. outputs giving 6V and 7½V and 9V and 12V at 1 amp continuous (1½ amp intermittent).
Fitted insulated output terminals and pilot lamp indicator. Hammer finish metal case, overall size 6″ × 3½″ × 2½″. Suitable for Transistor Radios, Tape Recorders, Amplifiers, etc., etc. Ready built and tested.

PRICE £4·50 P. & P. 35p.

BLACK ANODISED 16g. ALUMINIUM HEAT SINKS. For TO3, complete with mica's and bushes. Size 2½in × 3in approx. **25p** pair. P. & P. 5p.

HIGH GRADE COPPER LAMINATE BOARDS. 8″ × 6″, 5 for **50p**. P. & P. 13p.

BRAND NEW MULTI-RATIO MAINS TRANSFORMERS. Giving 13 alternatives. Primary: 0-210-240V. Secondary combinations: 0-5-10-15-20-25-30-35-40-60V half wave at 1 amp or 10-0-10, 20-0-20, 30-0-30V, at 2 amps full wave. Size 3inL × 3½inW × 3inD. Price **£1·85**. P. & P. 30p.
MAINS TRANSFORMER. For transistor power supplies. Pri. 200/240V. Sec. 9–0–9 at 500mA. **85p**. P. & P. 13p.
Pri. 200/240V. Sec. 12–0–12 at 1 amp. **95p**. P. & P. 13p.
Pri. 200/240V. Sec. 10–0–10 at 2 amp. **£1·45**. P. & P. 30p.

GENERAL PURPOSE HIGH STABILITY TRANSISTOR PRE-AMPLIFIER. For P.U. Tape, Mike, Guitar, etc., and suitable for use with valve or transistor equipment. 9–18V. Battery or from H.T. line 200/300V. Frequency response 15Hz–25KHz. Gain 26dB. Solid encapsulation size 1¾ × 1¼ × ¾in. Brand new — complete with instructions. Price **88p**. P. & P. 13p.

HANDBOOK OF TRANSISTOR EQUIVALENTS and SUBSTITUTES

A must for servicemen and home constructors. Including many 1000's of British, U.S.A., European and Japanese transistors. ONLY **40p.** Post 5p.

V.A.T.
Prices in this advertisement (incl. P. & P.) will be subject to V.A.T. as from 1st April, 1973.

4-SPEED RECORD PLAYER BARGAINS
Mains models. All brand new in maker's packing.
LATEST B.S.R. C109/C129 4-SPEED AUTOCHANGER. With latest mono compatible cartridge **£6·97**. Carr. 50p. With stereo cartridge **£7·97**. Carr. 50p.
Garrard SP25 Mk. III with heavy precision machined die cast turntable. **£10·95**. Carr. 50p.

SPECIAL BARGAIN OFFER!
PRECISION ENGINEERED PLINTHS

Beautifully constructed in heavy gauge "Colorcoat" plastic coated steel. Resonance free. Designed to take Garrard 1025, 2000, 2025TC, 2500, 3000, 3500, 5100, SP25 II and III, SL65B, AT60, etc., or B.S.R. C109, C129, A21, etc. Black leatherette finish. Size 12½in × 14½in × 3½in high (approx. 7½in high, including rigid smoked acrylic cover). **NOW ONLY £4·50**
P. & P. 35p.

LATEST ACOS GP91/1SC Mono Compatible Cartridge with t/o stylus for LP/EP/78. Universal mounting bracket. **£1·50**. P. & P. 8p.
SONOTONE 9TAHC COMPATIBLE STEREO CARTRIDGE T/O stylus. Diamond Stereo LP and Sapphire 78. ONLY **£2·50**. P. & P. 10p. Also available fitted with twin Diamond T/O stylus for Stereo LP. **£3**. P. & P. 10p.
LATEST RONETTE T/O Stereo Compatible Cartridge for EP/LP/Stereo/78. **£1·63**. P. & P. 10p.
LATEST RONETTE T/O Mono Compatible Cartridge for EP/LP/78 mono or stereo records on mono equipment. **£1·50**. P. & P. 10p.

QUALITY RECORD PLAYER AMPLIFIER MK II
A top-quality record player amplifier employing heavy duty double wound mains transformer, ECC83, EL84, and rectifier. Separate Bass, Treble and Volume controls. Complete with output transformer matched for 3 ohm speaker. Size 7in. w. × 3 d. × 6 h. Ready built and tested. PRICE **£3·95**. P. & P. 40p. ALSO AVAILABLE mounted on board with output transformer and speaker ready to fit cabinet below. PRICE **£5·25**. P. & P. 50p.
DE LUXE QUALITY PORTABLE R/P CABINET MK II
Uncut motor board size 14½ × 12in., clearance 2in. below, 5½in. above. Will take above amplifier and any B.S.R. or GARRARD changer or Single Player (except AT60 and SP25). Size 18 × 15 × 8in. PRICE **£4·75**. P. & P. 50p.

SPECIAL OFFER!!
HI-FI LOUDSPEAKER SYSTEM

Beautifully made teak finish enclosure with most attractive Tygan-Vynair front. Size 16½in high × 10½in wide × 5½″ deep. Fitted with E.M.I. Ceramic Magnet 13in × 8in bass unit, two H.F. tweeter units and crossover. Max. power handling 10W. Available 3, 8 or 15 ohm impedance.

Our Price £8·40 Carr. 65p.
CABINET AVAILABLE SEPARATELY **£4·50**. Carr. 60p.
Also available in 8 ohm with EMI 13in × 8in. bass speaker with parasitic tweeter. **£6·50**. Carr. 65p.

LOUDSPEAKER BARGAINS
5in 3 ohm **£1·05**. P. & P. 15p. 7 × 4in 3 ohm **£1·15**. P. & P. 20p. 10 × 6in 3 or 15 ohm **£1·90**. P. & P. 30p. E.M.I. 8 × 5in 3 ohm with high flux magnet **£1·62**. P. & P. 20p. E.M.I. 13½ × 8in with high flux ceramic magnet with parasitic tweeter 3, 8, or 15 ohm **£3·20**. P. & P. 30p. E.M.I. 13 × 8in, 3 or 8 or 15 ohm with two inbuilt tweeters and crossover network **£4·20**. P. & P. 30p.
BRAND NEW. 12in 15w H/D Speakers, 3 or 15 ohm. Current production by well-known British maker. Now with Hiflux ceramic ferrobar magnet assembly **£6·75**. Guitar models: 25w **£6·75**. 35w **£8·50**. P. & P. 38p each.

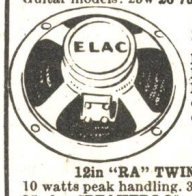

SPECIAL OFFER!

LIMITED NUMBER OF BRAND NEW ELAC 10″ TWIN CONE LOUDSPEAKERS. With large ceramic magnet and plasticised cone surround. 8 ohm impedance.

£2·75. P. & P. 25p.

12in "RA" TWIN CONE LOUDSPEAKER
10 watts peak handling. 3, 8 or 15 ohm, **£2·20**. P. & P. 30p.
35 ohm SPEAKERS 3″. ONLY **63p**. P. & P. 13p.
"POLY PLANAR" WAFER-TYPE, WIDE RANGE ELECTRO-DYNAMIC SPEAKER
Size 11¾in × 14 11/16in × 1 7/16in deep. Weight 19oz. Power handling 20W r.m.s. (40W peak). Impedance 8 ohm only. Response 40Hz–20kHz. Can be mounted on ceilings, walls, doors, under tables, etc., and used with or without baffle. Send S.A.E. for full details. Only **£5·95** each. P. & P. 25p.
VYNAIR & REXINE SPEAKERS & CABINET FABRICS app. 54 in. wide. Usually £1·75 yd., our price **75p** yd. length. P. & P. 15p per yd. (min. 1 yd.). S.A.E. for samples.

HI-FI STEREO HEADPHONES

Adjustable headband with comfortable flexifoam earmuffs. Wired and fitted with standard stereo ¼in jack plug. Frequency response 30–15,000Hz. Matching impedance 8–16 ohms. Easily converted for mono. PRICE **£2·95**. P. & P. 15p.

HIGH IMPEDANCE CRYSTAL STICK MIKES. OUR PRICE **£1·05**. P. & P. 8p.

CENTRE ZERO MINIATURE MOVING COIL METER. 100μA for balance or tuning. Approx. size 1in × 1in × ¾in. Limited number **75p**. P. & P 10p.

HARVERSONIC SUPER SOUND 10 + 10 STEREO AMPLIFIER KIT

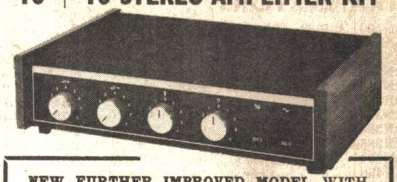

NEW FURTHER IMPROVED MODEL WITH HIGHER OUTPUT AND INCORPORATING HIGH QUALITY READY DRILLED FIBRE GLASS PRINTED CIRCUIT BOARD WITH COMPONENT IDENTIFICATION CLEARLY MARKED FOR EVEN EASIER CONSTRUCTION

A really first-class Hi-Fi Stereo Amplifier Kit. Uses 14 transistors including Silicon Transistors in the first five stages on each channel resulting in even lower noise level with improved sensitivity. Integrated pre-amp with Bass, Treble and two Volume Controls. Suitable for use with Ceramic or Crystal cartridges. (Very simple to modify to suit magnetic cartridge—instructions included). Output stage for any speakers from 5 to 15 ohms. Compact design, all parts supplied including drilled metal work, high quality ready drilled fibre glass printed circuit board, smart brushed anodised aluminium front panel with matching knobs, wire, solder, nuts, bolts—no extras to buy. Simple step by step instructions enable any constructor to build an amplifier to be proud of. Brief specification: Power output 14W r.m.s. per channel into 5 ohms. Frequency response ±3dB 12–30,000Hz. Sensitivity better than 80mV into 1MΩ. Full power bandwidth ±3dB 12–15,000Hz. Bass boost approx. to ±12dB. Treble cut approx. to −16dB. Negative feedback 18dB over main amp. Power requirements 35V at 1·0 amp. Overall size—12″ wide × 8″ deep × 2½″ high.
Fully detailed 7-page construction manual and parts list free with kit or send 18p plus large S.A.E.
PRICES AMPLIFIER KIT, **£10·50** P. & P. 15p.
(Magnetic input components 30p extra)
POWER PACK KIT, **£3** P. & P. 30p.
CABINET, **£3** P. & P 30p.
(Post Free if all units purchased at same time). Full after sales service. Also available ready built and tested, **£20·50**. Post Free.
Note: The above amplifier is suitable for feeding two mono sources into inputs (e.g. mike, radio, twin record decks, etc.) and will then provide mixing and fading facilities for medium powered Hi-Fi Discotheque use, etc.

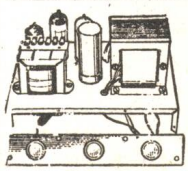

3-VALVE AUDIO AMPLIFIER HA34 MK II
Designed for Hi-Fi reproduction of records. A.C. Mains operation. Ready built on plated heavy gauge metal chassis, size 7¼in w. × 4in. d. × 4¾in. h. Incorporates ECC83, EL84, EZ80 valves. Heavy duty, double wound mains transformer and output transformer matched for 3 ohm speaker. Separate volume control and now with improved wide range tone controls giving bass and treble lift and cut. Negative feedback line. Output 4½ watts. Front panel can be detached and leads extended for remote mounting of controls. Complete with knobs, valves, etc., wired and tested for only **£4·95**. P. & P. 35p.
HSL "FOUR" AMPLIFIER KIT. Similar in appearance to HA34 above but employs entirely different and advanced circuitry. Complete set of parts, etc. **£4·10**. P. & P. 40p.

HARVERSON'S SUPER MONO AMPLIFIER

A super quality gram amplifier using a double wound fully isolated mains transformer, rectifier and ECL82 triode pentode valve as audio amplifier and power output stage. Impedance 3 ohms. Output approx. 3·5 watts. Volume and tone controls. Chassis size only 7in. wide × 3in. deep × 6in. high overall. AC mains 200/240V. Supplied absolutely Brand New, completely wired and tested with good quality output transformer.
OUR ROCK BOTTOM BARGAIN PRICE **£2·95** P. & P. 35p

10/14 WATT HI-FI AMPLIFIER KIT

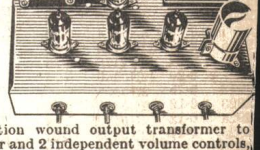

A stylishly finished monaural amplifier with an output of 14 watts from 2 EL84s in push-pull. Super reproduction of both music and speech, with negligible hum. Separate inputs for mike and gram allow records and announcements to follow each other. Fully shrouded section wound output transformer to match 3–15Ω speaker and 2 independent volume controls, and separate bass and treble controls are provided giving good lift and cut. Valve line-up 2 EL84s, ECC83, EF86 and EZ80 rectifier. Simple instruction booklet **13p** (Free with parts). **All parts sold separately.** ONLY **£7·97**. P. & P. 55p. Also available ready built and tested **£10·97**. P. & P. 60p.

Open 9-5.30 Monday to Saturday
Early closing Wed. 1 p.m.
A few minutes from South Wimbledon Tube Station

HARVERSON SURPLUS CO. LTD.
Dept. PE, 170 High St., Merton, London, S.W.19 Tel. 01-540 3985
SEND STAMPED ADDRESSED ENVELOPE WITH ALL ENQUIRIES

(Please write clearly)
PLEASE NOTE: P. & P. CHARGES QUOTED APPLY TO U.K. ONLY. P. & P. ON OVERSEAS ORDERS CHARGED EXTRA.

BRAND NEW GUARANTEED

SEMICONDUCTORS & COMPONENTS

WE SUPPLY NEARLY ALL THE COMPONENTS FOR PROJECTS IN THIS MAGAZINE

RETURN OF POST SERVICE

TRANSISTORS

2N109	0·49	2N3055	0·60
2N174	1·40	2N3390	0·20
2N176	0·75	2N3391	0·20
2N274	0·75	2N3391A	0·22
2N335	0·75	2N3392	0·13
2N351	0·95	2N3393	0·12
2N376	1·00	2N3394	0·12
2N384	0·93	2N3402	0·17
2N388A	0·40	2N3403	0·19
2N404	0·23	2N3404	0·24
2N456	0·75	2N3405	0·27
2N456A	0·75	2N3414	0·10
2N457A	0·80	2N3415	0·10
2N491	3·25	2N3416	0·15
2N584	0·26	2N3417	0·21
2N591	0·34	2N3570	1·25
2N696	0·16	2N3571	1·12
2N697	0·15	2N3572	0·97
2N698	0·25	2N3702	0·10
2N699	0·29	2N3703	0·10
2N706	0·10	2N3704	0·10
2N706A	0·12	2N3705	0·10
2N708	0·15	2N3706	0·09
2N709	0·40	2N3707	0·10
2N711	0·50	2N3708	0·07
2N718	0·21	2N3709	0·09
2N718A	0·30	2N3710	0·09
2N720	0·50	2N3711	0·09
2N721	0·55	2N3712	0·95
2N914	0·22	2N3713	1·08
2N916	0·20	2N3714	1·15
2N919	0·50	2N3715	1·23
2N929	0·20	2N3716	1·30
2N930	0·20	2N3773	2·40
		2N3781	3·67
		2N3782	3·37
		2N3789	1·76
		2N3790	2·20
		2N3791	2·06
		2N3792	2·20
2N1090	0·30	2N3794	0·12
2N1091	0·32	2N3819	0·35
2N1131	0·25	2N3820	0·48
2N1132	0·25	2N3823	0·62
2N1184	1·57	2N3824	0·75
2N1302	0·16	2N3826	0·23
2N1303	0·16	2N3854	0·16
2N1304	0·20	2N3854A	0·16
2N1305	0·25	2N3855	0·16
2N1306	0·22	2N3855A	0·16
2N1307	0·22	2N3856	0·16
2N1308	0·25	2N3856A	0·16
2N1309	0·25	2N3858	0·16
2N1483	0·90	2N3858A	0·16
2N1507	0·24	2N3859	0·16
2N1613	0·19	2N3859A	0·16
2N1631	0·38	2N3860	0·16
2N1637	0·36	2N3866	0·85
2N1638	0·32	2N3877	0·25
2N1671	1·25	2N3877A	0·26
2N1701	1·46	2N3878	1·00
2N1702	2·61	2N3879	1·46
2N1711	0·23	2N3900	0·20
2N1893	0·37	2N3900A	0·21
2N2102	0·30	2N3901	0·32
2N2147	0·70	2N3903	0·22
2N2148	0·60	2N3904	0·22
2N2192	0·40	2N3905	0·21
2N2192A	0·40	2N3906	0·22
2N2193	0·40	2N4036	0·40
2N2193A	0·42	2N4037	0·35
2N2194	0·27	2N4058	0·12
2N2194A	0·30	2N4059	0·09
2N2195	0·37	2N4060	0·11
2N2195A	0·18	2N4061	0·11
2N2218A	0·18	2N4062	0·11
2N2219	0·20	2N4302	0·25
2N2219A	0·20	2N4303	0·32
2N2220	0·20	2N4913	0·80
2N2221	0·20	2N4914	0·87
2N2221A	0·22	2N4915	0·95
2N2222	0·20	2N4916	0·20
2N2222A	0·32	2N4917	0·17
2N2368	0·11	2N4918	0·50
2N2369	0·05	2N4919	0·53
2N2369A	0·15	2N4920	0·60
2N2646	0·50	2N4921	0·50
2N2647	1·20	2N4922	0·55
2N2711	0·12	2N4923	0·60
2N2712	0·12	2N4926	0·90
2N2713	0·17	2N4927	1·00
2N2714	0·17	2N4928	1·80
2N2904	0·18	2N4929	2·23
2N2904A	0·25	2N4930	2·25
2N2905	0·26	2N4931	2·70
2N2905A	0·28	2N5172	0·12
2N2906	0·18	2N5174	0·22
2N2906A	0·23	2N5175	0·26
2N2907	0·23	2N5176	0·32
2N2907A	0·26	2N5245	0·43
2N2913	0·75	2N5190	0·92
2N2923	0·12	2N5191	0·96
2N2924	0·12	2N5192	1·24
2N2925	0·12	2N5193	1·01
2N2926			
Green	0·10	2N5194	1·10
Yellow	0·10	2N5195	1·46
Orange	0·10	2N5245	0·43
3053	0·31	2N5457	0·35

Only a few examples of our stocks can be shown here

2N5458	0·33	AF200	0·35
2N5459	0·40	AF239	0·41
3N128	0·63	AF240	0·72
3N138	1·65	AF279	0·54
3N139	1·42	AF280	0·54
3N140	0·92	AFY42	0·75
3N141	0·81	AF211	0·55
3N142	0·58	AL102	0·75
3N143	0·75	AL103	0·70
3N152	0·92	A8Y26	0·30
3N153	0·81	A8Y27	0·36
3N154	0·84	A8Y28	0·28
3N159	1·17	A8Y29	0·30
3N200	2·49	A8Y50	0·20
		A8Y55	0·35
LM741CN (d.i.l)	0·70	A8Z21	0·55
		AU103	1·25
L741C (TO5)	0·40	BC107	0·14
		BC108	0·13
40050	0·55	BC109	0·14
40251	0·81	BC113	0·16
40309	0·30	BC114	0·12
40310	0·50	BC115	0·15
40313	0·92	BC116	0·15
40316	0·50	BC116A	0·18
40318	0·92	BC117	0·21
40322	0·92	BC118	0·11
40360	0·40	BC119	0·27
40361	0·48	BC121	0·23
40362	0·50	BC123	0·29
40363	0·88	BC125	0·15
40389	0·46	BC126	0·20
40394	0·56	BC132	0·30
40406	0·40	BC134	0·11
40407	0·40	BC135	0·11
40408	0·50	BC136	0·15
40409	0·55	BC137	0·15
40410	0·53	BC138	0·24
40411	2·25	BC140	0·34
40414	3·55	BC141	0·39
40438	1·44	BC142	0·24
40467A	0·69	BC143	0·21
40468A	0·44	BC144	0·24
40600	0·69	BC145	0·21
40601	0·67	BC147	0·11
40602	0·46	BC148	0·11
40603	0·58	BC149	0·13
40604	0·56	BC153	0·18
40636	1·10	BC154	0·18
40673	0·70	BC157	0·14
AC107	0·35	BC158	0·13
AC113	0·16	BC159	0·14
AC115	0·16	BC160	0·37
AC117	0·20	BC167B	0·13
AC121	0·13	BC168B	0·11
AC126	0·25	BC168C	0·11
AC127	0·25	BC169B	0·13
AC128	0·25	BC169C	0·13
AC141K	0·30	BC170	0·11
AC142K	0·25	BC171	0·13
AC151V	0·14	BC172	0·11
AC152V	0·17	BC182	0·10
AC153	0·22	BC182L	0·10
AC153K	0·25	BC183	0·09
AC154	0·20	BC183L	0·09
AC176	0·25	BC184	0·11
AC176K	0·20	BC184L	0·11
AC187K	0·20	BC186	0·25
AC188K	0·26	BC187	0·25
ACY17	0·30	BC204	0·11
ACY18	0·25	BC205	0·10
ACY19	0·25	BC206	0·11
ACY20	0·20	BC207	0·10
ACY21	0·20	BC208	0·09
ACY22	0·13	BC211	0·30
ACY28	0·25	BC212K	0·10
ACY30	0·42	BC212L	0·12
ACY39	0·55	BC214L	0·14
ACY40	0·20	BC236	0·16
ACY41	0·20	BC237	0·08
ACY44	0·31	BC238	0·09
AD136V	0·96	BC239	0·09
AD140	0·50	BC251	0·22
AD141	0·55	BC252	0·18
AD142	0·50	BC253	0·23
AD143	0·45	BC257	0·09
AC149V	0·66	BC258	0·09
AD149V	1·26	BC259	0·13
AD150	0·63	BC261	0·20
ADZ11	1·50	BC262	0·18
ADZ12	1·75	BC263	0·23
AF106	0·27	BC300	0·42
AF109R	0·40	BC301	0·34
AF114	0·25	BC302	0·27
AF115	0·25	BC303	0·54
AF116	0·25	BC304	0·43
AF117	0·20	BC307	0·10
AF118	0·50	BC307A	0·10
AF121	0·22	BC307VI	0·10
AF124	0·24	BC308	0·09
AF125	0·20	BC308A	0·09
AF126	0·20	BC308B	0·09
AF127	0·20	BC309	0·10
AF139	0·38	BC309A	0·10
AF170	0·25	BC309B	0·10
AF172	0·25	BC313	0·30
AF178	0·55	BC327	0·24
AF179	0·65	BC328	0·22
AF180	0·50	BC337	0·19
AF186	0·40	BC338	0·19
		BCY30	0·35

BCY31	0·40	BFX30	0·25
BCY32	0·60	BFX37	0·33
BCY33	0·25	BFX44	0·33
BCY34	0·35	BFX63	2·48
BCY38	0·40	BFX68	0·30
BCY39	0·05	BFX84	0·24
BCY40	0·50	BFX85	0·30
BCY42	0·15	BFX86	0·25
BCY43	0·15	BFX87	0·27
BCY58	0·21	BFX88	0·25
BCY59	0·21	BFX89	0·45
BCY66	0·66	BFY10	0·35
BCY67	0·94	BFY11	0·45
BCY70	0·17	BFY17	0·90
BCY71	0·20	BFY18	0·35
BCY72	0·13	BFY19	0·35
BCY87	3·47	BFY20	0·50
BCY88	2·40	BFY29	0·40
BCY89	0·80	BFY37	0·20
BCZ10	0·35	BFY41	0·43
BCZ11	0·50	BFY43	0·65
BD115	0·75	BFY50	0·19
BD116	0·75	BFY51	0·18
BD121	0·75	BFY52	0·16
BD123	0·82	BFY53	0·15
BD124	0·60	BFY56	0·34
BD130	0·57	BFY64	0·41
BD131	0·40	BFY75	0·40
BD132	0·50	BFY76	0·22
BD135	0·43	BFY77	0·24
BD136	0·49	BFY78	0·36
BD137	0·55	BFY90	0·55
BD138	0·63	BRY39	0·29
BD139	0·71	BSX19	0·13
BD140	0·23	BSX20	0·12
BDY10	1·25	BSX21	0·20
BDY11	1·50	BSX26	0·34
BDY17	1·50	BSX27	0·34
BDY18	1·75	BSX28	0·25
BDY19	1·97	BSX29	0·47
BDY20	0·80	BSX30	0·68
BDY38	0·55	BSX59	0·78
BDY60	0·65	BSX60	0·54
BDY61	0·57	BSX61	0·42
BDY62	0·52	BSX76	0·15
BF115	0·23	BSX77	0·20
BF117	0·43	BSX78	0·25
BF119	0·58	BSW70	0·28
BF121	0·25	BSY24	0·20
BF123	0·27	BSY25	0·15
BF125	0·25	BSY26	0·20
BF127	0·27	BSY27	0·15
BF152	0·20	BSY28	0·15
BF153	0·29	BSY38	0·15
BF154	0·16	BSY39	0·15
BF158	0·23	BSY51	0·25
BF159	0·27	BSY52	0·25
BF160	0·23	BSY53	0·25
BF161	0·41	BSY54	0·30
BF163	0·20	BSY56	0·79
BF166	0·31	BSY65	0·15
BF167	0·21	BSY78	0·40
BF173	0·22	BSY79	0·40
BF177	0·29	BSY790	0·45
BF178	0·35	BSY95A	0·09
BF179	0·43	BU104	1·42
BF180	0·35	BU105	2·25
BF181	0·34	C111	0·53
BF182	0·40	C407	0·18
BF183	0·40	C424	0·15
BF184	0·17	C425	0·36
BF185	0·25	C426	0·25
BF194	0·14	C428	0·25
BF195	0·16	C444	0·26
BF196	0·15	D40N3	0·62
BF197	0·15	GET111	0·45
BF198	0·18	GET113	0·25
BF199	0·18	GET114	0·20
BF200	0·40	GET115	0·50
BF224J	0·14	GET119	0·35
BF225J	0·19	GET120	0·40
BF237	0·22	GET535	0·20
BF238	0·22	GET536	0·20
BF244	0·16	GET538	0·20
BF245	0·33	GET873	0·15
BF246	0·43	GET880	0·30
BF247	0·49	GET883	0·20
BF254	0·16	GET887	0·20
BF255	0·17	GET890	0·22
BF257	0·47	GET895	0·25
BF258	0·53	MA8001	0·16
BF259	0·55	MA8002	0·47
BF261	0·23	MA8003	0·47
BF264	1·45		
BF270	0·21		
BF271	0·21		
BF272	0·49		
BF273	0·15		
BF274	0·17		
BF457	0·53		
BF458	0·65		
BF459	0·65		
BF821	1·75		
BF821A	2·30		
BF828	0·74		
BF861	0·27		
BF898	0·30		
BFW10	0·61		
BFW11	0·61		
BFX13	0·23		
BFX29	0·30		

& Packing 13p per order. Europe 25p. Commonwealth (Air) 65p (MIN.) Matching charge (audio sistors only) 15p extra per pair. Prices subject to availability of stock.

TTL. LOGIC I.C. NEW PRICES

	1–24 £p	25+ £p		1–24 £p	25+ £p		1–24 £p	25+ £p
SN7400	0·20	0·18	SN7427	0·48	0·42	SN7472	0·36	0·25
SN7401	0·20	0·18	SN7430	0·20	0·18	SN7473	0·40	0·34
SN7402	0·20	0·18	SN7432	0·42	0·40	SN7474	0·40	0·34
SN7403	0·20	0·18	SN7437	0·52	0·45	SN7475	0·55	0·47
SN7404	0·22	0·18	SN7438	0·52	0·45	SN7476	0·44	0·39
SN7405	0·22	0·18	SN7440	0·20	0·18	SN7480	0·75	0·70
SN7406	0·56	0·48	SN7441AN	0·75	0·72	SN7481	1·25	1·07
SN7407	0·56	0·48	SN7442	0·79	0·63	SN7482	0·87	0·61
SN7408	0·20	0·18	SN7445	1·85	1·70	SN7483	1·00	0·82
SN7409	0·20	0·18	SN7446	2·00	1·60	SN7484	0·95	0·85
SN7410	0·20	0·18	SN7447	1·30	1·20	SN7485	2·50	2·30
SN7411	0·22	0·20	SN7448	1·04	0·92	SN7486	0·45	0·40
SN7412	0·42	0·36	SN7450	0·20	0·18	SN7490	0·75	0·70
SN7413	0·30	0·27	SN7451	0·20	0·18	SN7491	1·00	0·85
SN7416	0·30	0·40	SN7453	0·20	0·18	SN7492	0·75	0·70
SN7417	0·30	0·40	SN7454	0·20	0·18	SN7493	0·75	0·70
SN7420	0·20	0·18	SN7460	0·20	0·18	SN7494	0·85	0·80
SN7423	0·52	0·45	SN7470	0·30	0·26	SN7495	0·80	0·74
SN7425	0·48	0·42				SN7496	1·00	0·90

Small value

SUB-MIN. ELECTROLYTICS

only 6p each

SILICON RECTIFIERS

PIV	50	100	200	400	600	800	1000	1200
1A	8p	9p	10p	11p	12p	15p	20p	—
3A	15p	17p	20p	22½p	25p	27p	30p	35p
6A	—	—	25p	30p	32½p	35p	—	—
10A	30p	35p	40p	47p	56p	66p	75p	—
15A	36p	45p	48p	55p	65p	75p	87p	—
35A	70p	80p	90p	£1·00	£1·40	£1·70	£2·75	—

1 amp and 3 amp are plastic encapsulation.

DIODES & RECTIFIERS

IN34A	10p	AA119	7p	BAX16	12½p	FST3/4	22½p
IN914	7p	AA129	15p	BAY18	17½p	OA5	17p
IN916	7p	AAZ13	12p	BAY31	7p	OA10	20p
IN4007	20p	AAZ15	12p	BAY38	25p	OA9	10p
IS44	7p	AAZ17	10p	BY100	15p	OA47	8p
IS113	15p	BA100	15p	BY103	22p	OA70	7p
IS120	12p	BA102	25p	BY122	47½p	OA73	10p
IS121	14p	BA110	25p	BY124	15p	OA79	7p
IS130	8p	BA114	15p	BY126	15p	OA81	8p
IS131	10p	BA115	7p	BY127	17p	OA82	10p
IS132	12p	BA141	17p	BY164	57p	OA90	7p
IS920	7p	BA142	17p	BYX10	22p	OA91	7p
IS922	8p	BA144	12p	BYZ10	35p	OA95	7p
IS923	12p	BA145	17p	BYZ11	32p	OA2000	7p
IS940	5p	BA154	12p	BYZ12	30p	OA202	10p
		BAX13	5p	BYZ13	25p	TIV307	50p

VEROBOARD

	0.15 Matrix	0.1 Matrix
2½ × 3¾in	18p	25p
2½ × 5in	27p	27p
3¾ × 3¾in	27p	27p
3¾ × 5in	32p	31p
5 × 17in (Plain)	82p	—

Vero Pins (Bag of 36) 22p
Vero Cutter 45p
Pin insertion Tools 0·1 and 0·15 matrix) at 58p.

OPTOELECTRONICS

MINITRON 3015F 7-SEGMENT INDICATOR (16 PIN DIL) £2·00 May be driven by SN7447

TIL 209 LIGHT EMITTING DIODE. Made by TEXAS INST. (Red). 35p

B9900 PHOTORESISTOR 38p

SCORPIO ignition kit £10 + 50p P. & P.

POTENTIOMETERS

Carbon:
Log. or Lin., less switch, 16p.
Log. or Lin., with switch, 27p.
Wire-wound Pots (3W), 38p.
Twin Ganged Stereo Pots, Log. or Lin., 43p

PRESETS (CARBON)

0·1 Watt	6p	VERTICAL
0·2 Watt	6p	OR
0·3 Watt	7½p	HORIZONTAL

SLIDE POTENTIOMETERS

58mm, TRACK
SINGLE GANGED. LOG or LIN 1k to 1M. 40p each.
TWIN GANGED. LOG or LIN 1k to 500k. 60p each

WIRE-WOUND RESISTORS

2·5 watt 5% (up to 270 ohms only), 7p.
5 watt 5% (up to 8·2kΩ only), 9p.
10 watt 5% (up to 26kΩ only), 10p.

TAD 100 + CFT-470C: normal price £2·80 our price £2 only !

SPECIAL OFFER!!

ONE MONTH ONLY!

All items listed 15%off (15p in £) for retail orders accompanied by this coupon.

Tel. 01-452 0161/2/3
Telex 21492

A. MARSHALL & SON
28 CRICKLEWOOD BROADWAY, LONDON, N.W.2

VISITORS WELCOME
Hrs. 9–5.30 Mon.-Fri
9–5. Sat.

Would you spend an hour a day to earn more money in Electronics-Television-Radio?

If you're willing to give up one hour or more a day we can help you get into the lucrative growth industries of electronics, television, radio.

And if you're already *in*, we can help you get on!

With our know-how and wide experience in teaching, plus your determination to study, we can turn your interest into the technical knowledge you need for success. Once you've got the qualifications you need, you'll be in a good position to take full advantage of the opportunities which exist today in all fields of electronics—in television (colour and black/white) and in radio. (We teach you the theory and practice of valve and transistor portable circuits while you build your own 5 valve receiver, transistor portable and high grade test instruments.)

With ICS you study at home—at your own pace, when *you* choose, in the time you've got available. Your ICS tutors will give you all the help and encouragement you need to pass any exams you want to take.

Don't waste another day. Take your first step *now* towards a better paid, more assured future. Send for your FREE Careers Guide today.

ICS your key to the door of opportunity

Tick or state subject of interest and post to:
International Correspondence Schools
Dept. 230E Intertext House, Stewarts Road
London SW8 4UJ

Subject of interest.....

- ☐ Society of Engineers Graduateship (Electrical Engineering)
- ☐ C & G Telecommunications Technicians Certificates
- ☐ C & G Electrical Installation Work
- ☐ C & G Certificate in Technical Communication Techniques
- ☐ MPT General Certificate in Radio Telegraphy
- ☐ Audio, Radio & TV Engineering & Servicing
- ☐ Electronic Engineering, Maintenance, Engineering systems, Instrumention & Control systems
- ☐ Computer Engineering and Technology
- ☐ Electrical Engineering, Installations, Contracting, Appliances
- ☐ Self-build radio courses

Name.....

Address.....

.....

Occupation..... Age.....

Accredited by the Council for the Accreditation of Correspondence Colleges

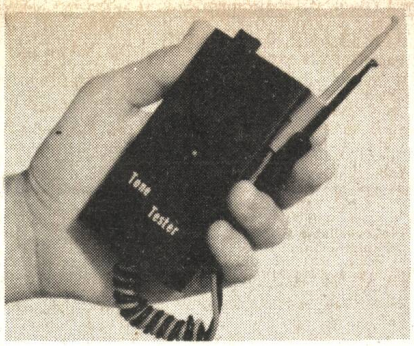

TONE TESTER

The Tone Tester is a solid-state dual impedance continuity tester with tone injection.

Applications: **Wiring. Cable installation. Production line testing. Damage free testing of solid-state assemblies.**

Power supply: integral 1·5v battery.
Continuity test: impedance–low 0—10 ohms high 0–50k ohms.
Tone injection: 1·4 Vp—p up to 300 ohms D.C. loop. *Tone injection on HTD only.*

HTD dual impedance with tone injection £5·80. **HTL** low impedance only £4·84. **HTH** high impedance only £4·96.

Highams Electronic Communications Ltd
Dept E 58–60 Redchurch St London E2

U.H.F. TV AERIALS

SUITABLE FOR COLOUR & MONOCHROME RECEPTION

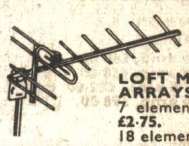

All U.H.F. aerials now fitted with tilting bracket and 4 element reflector.

LOFT MOUNTING ARRAYS
7 element £2·25. 11 element £2·75. 14 element £3·25. 18 element £3·75.

WALL MOUNTING c/w **WALL ARM AND BRACKET.** 7 element £3·25. 11 element £3·75. 14 element £4·25. 18 element £4·75.

CHIMNEY MOUNTING ARRAYS c/w **MAST AND LASHING KIT.** 7 element £4. 11 element £4·50. 14 element £4·75. 18 element £5·25.

MAST MOUNTING arrays only 7 element £2·25. 11 element £2·75. 14 element £3·25. 18 element £3·75. Complete assembly instructions with every aerial. LOW LOSS coaxial cable 9p yd.

KING TELEBOOSTERS from £3·75. LABGEAR all band V.H.F.—U.H.F.—F.M. radio mains operated pre-amps £7·50. State clearly channel number required on all orders. P. & P. on all aerials 50p accs. 15p. C.W.O. min. C.O.D. charge 25p.

BBC-ITV-FM AERIALS

BBC (band I) Wall S/D £2. **LOFT** inverted 'T' £1·25. **EXTERNAL** 'H' array only £3. **ITV (band 3)** 5 element loft array £2·50. 7 element £3. **COMBINED BBC-ITV** loft 1+5 £2·75. 1+7 £3·50. **WALL AND CHIMNEY UNITS ALSO AVAILABLE.** Pre-amps from £3·75.

COMBINED U.H.F.-V.H.F. aerials 1+5+9 £4. 1+5+14 £4·50. 1+7+14 £5. **F.M. RADIO** loft S/D £1. 3 element £3·25. 4 element £3·50. Standard coaxial plugs 9p. Coaxial cable 5p yd. Outlet box 30p. P. & P. all aerials 50p, accs. 30p. C.W.O. min. C.O.D. charge 25p. Send 5p for fully illustrated lists.

CALLERS WELCOMED
OPEN ALL DAY SATURDAY

K.V.A. ELECTRONICS
40-41 Monarch Parade, London Rd.
Mitcham, Surrey
Telephone 01-648 4884

ELECTRONIC BARGAINS

COMPAKS

Manufacturers' fall-outs which include functional and part-functional units. Ideal for learning and experimenting.

PAK 1	13 mixed 7400 series	66p
PAK 2	10 unijunction TIS43	55p
PAK 3	6 S.C.R.'s	55p
PAK 4	50 silicon and germanium NPN and PNP transistors	55p

Valve Equivalent Book 40p
Transistor Equivalent Book 40p
List over 3,000 equivalents

ACOUSTIC WADDING

Bonded Acrylic Fibre 1in thick. Per square yard **50p**

VYNIAR SPEAKER CLOTH
Black—Black and Silver—Black and Gold

Sizes:	
18in × 25in	60p
36in × 25in	£1·10
36in × 50in	£2·20

Send S.A.E. for samples

SOLDERING IRONS

	Retail Price	Our Price
Antex CCN240	£1·98	£1·58
Antex CN240	£1·87	£1·49
Antex X25	£1·92	£1·54

FERRANTI RADIO CHIP

ZN414 £1·23

AMPLIFIER MODULE

5 watt, 9 volt supply, 4, 8 or 16 Ω speaker, £3·30

Fully Guaranteed. Mail order only. P. & P. 13p. Cheque or P/O to:

T. F. J. ELECTRONICS
25 EASTBURY COURT
LEMSFORD ROAD
ST. ALBANS, HERTS.

TRANSISTOR AUDIO AND RADIO CIRCUITS

by MULLARD

£1·80. Postage 12p

TRANSISTORIZED RADIO CONTRO FOR MODELS by D. W. Aldridge. £2·50 Postage 12p.

HI FI YEAR BOOK 1973. £1·50. Postag 20p.

BEGINNER'S GUIDE TO TELEVISIO by Gordon J. King. £1·60. Postage 10p.

RADIO TECHNICIAN'S BENC MANUAL by H. W. Hellyer. £3. Postag 15p.

INTEGRATED CIRCUIT POCKET BOO by R. G. Hibberd. £2·50. Postage 12p.

FIELD EFFECT TRANSISTORS MULLARD. £1·80. Postage 12p.

HAM RADIO: A BEGINNER'S GUIDE R. H. Warring. £1·60. Postage 12p.

110 THYRISTOR PROJECTS USIN SCRs AND TRIACS by R. M. Marston. £1· Postage 8p.

50 PHOTOELECTRIC CIRCUITS AN SYSTEMS by P. S. Smith. £1·30. Postage

FOUNDATIONS OF WIRELESS AN ELECTRONICS by M. G. Scroggie. £1· Postage 25p.

RADIO VALVE & TRANSISTOR DA by A. M. Ball. **75p.** Postage 12p.

THE MODERN BOOK C

BRITAIN'S LARGEST STOCKIST
of British and American Technical Book

19-21 PRAED STREET
LONDON W2 1NP
Phone 01-723 4185
Closed Saturday 1 p.m.

VARIABLE VOLTAGE TRANSFORMERS

INPUT 230/240V a.c. 50/60 OUTPUT VARIABLE 0–260V
All Types from ¼ to 50 amp from stock.

SHROUDED TYPE

1 amp, £7·00	20 amp, £49·00
2·5 amp, £8·05	25 amp, £58·00
5 amp, £11·75	37·5 amp, £82·00
10 amp, £22·50	50 amp, £98·00
15 amp, £25·00	

2·5 amp OPEN TYPE

(Panel Mounting) ¼ amp, £4·75. 1 amp, £7·00. 2½ amp, £8·05. All carriage paid.

DOUBLE ENDED MOTOR UNIT

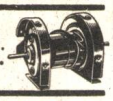

Powerful, continuously rated, 2-speed. Either 6 or 12 volt D.C. operation. PRICE £2 incl. P. & P.

12 VOLT D.C. MOTOR

Powerful 1 amp. REVERSIBLE motor. Speed 3,750 r.p.m. complete with external gear train (removable) giving approx. final speed of either 125 r.p.m. or 240 r.p.m. Size: 4½in × 2½in dia. Either type price 95p inc. P.&P.

REVERSIBLE SPLIT PHASE MOTOR

250 r.p.m., 100-115/210-240V A.C., 2in. × 1in. Ideal for rim-drive models, display, etc. Extremely powerful for size (including small capacitor). 75p incl. P. & P.

PARVALUX TYPE SDI9 230/250 VOLT A.C. REVERSIBLE GEARED MOTORS

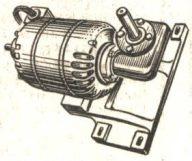

30 r.p.m. 40 lb. ins. Position of drive spindle adjustable to 3 different angles. Mounted on substantial cast aluminium base. Ex-equipment. Tested and in first-class running order. A really powerful motor offered at a fraction of maker's price. £6·80. Incl. P. & P.

PARVALUX Type: SDI.S/86896/OJ

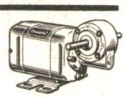

230/250V A.C. 50 r.p.m. 7 lb/in. Continuously rated. Less base. £6·30. Post Paid.

TYPE: SDI.S/89400/OM
230/250V A.C. 50 r.p.m. 22 lb/in. Continuously rated. Incl. base. £7·30. Incl. P. & P.

The above motors are new and unused.

PARVALUX TYPE SD2. 200/250 VOLT A.C./D.C. HIGH SPEED MOTOR

Speed 9,000 r.p.m. approx. or 3,200 r.p.m. if used with built-in governor, or variable speed over a wide range if used in conjunction with our Dimmer Switch, illustrated below. PRICE £2. Incl. P. & P.

600 WATT DIMMER SWITCH. Easily fitted. Fully guaranteed by makers. Will control up to 600W of all lights except fluorescent at mains voltage. Complete with simple instructions. £3 incl. P. & P.

VENNER ELECTRIC TIME SWITCH 200/250V Ex. GPO.

Tested. Manually set 2 on, 2 off every 24h. Override switch: 15A, £3·45, 20A, £3·95. Incl. P. & P. Also available with solar dial ON dusk, OFF dawn. Price as above.

24-HOUR TIMER

Can be adjusted to give a switching delay of between 2 hrs. to 24 hrs. Driven by 200/250V A.C. synchronous motor. 15 amp c/o contacts. Mfg. Crater Controls Ltd. Supplied with scale calibrated 0-10 (2 hrs. per division). Brand New. £2. Incl. P. & P.

HONEYWELL PROGRAMME TIMERS

240V. A.C. 5 r.p.m. motor. Each cam operating a c/o micro switch. Cams are individually variable, allowing inumerable combinations. Ideally suited for machinery control, automation, etc. Also in the field of entertainment, for chaser lights, animated displays, etc.
5 cam model £6. Incl. P. & P.
10 cam model £5. Incl. P. & P.
20 cam model with 15 r.p.m. motor £2. Incl. P. & P.

SIMPLE 12 CAM PROGRAMMER 240V A.C. 5 RPM MOTOR with 4 adjustable cams and 8 that may be profiled to individual requirements, £3·75. Incl. P. & P.

36V 30 AMP. A.C. or D.C. VARIABLE L.T. SUPPLY UNIT

INPUT 220/240V a.c.
OUTPUT CONTINUOUSLY VARIABLE 0–36V

Fully isolated. Fitted in robust metal case with Voltmeter. Ammeter Panel Indicator and handles. Input and output fully fused. Ideally suited for Lab. or Industrial use. £70. Incl. P. & P.

MOTOROLA MAC 11/6 PLASTIC TRIAC 400 PIV. 10 AMP

Now available **EX STOCK.** Supplied with full data and applications sheet. Price £1·12. Incl. P. & P. Suitable DIAC (RCA 40583) 30p each.

STROBE! STROBE! STROBE!

Build a Strobe Unit, using the latest type Xenon white light flash tube. Solid state timing and triggering circuit. 230/250V a.c. operation.

EXPERIMENTERS' ECONOMY KIT
Speed adjustable 1 to 30 flash per sec. All electronic components including Veroboard S.C.R. Unijunction Xenon Tube and instructions £6·55. Incl. P. & P.

NEW INDUSTRIAL KIT
Ideally suitable for schools, laboratories, etc. Roller tin printed circuit. New trigger coil, plastic thyristor. Speed adjustable 1-80 f.p.s. approx. ½ output of Hy-Lyght. Price £11. Incl. P. & P.

HY-LYGHT STROBE MK III
Designed and produced for use in large rooms, halls and the photographic field and utilises a silica tube, printed circuit, also a special trigger coil. Speed adjustable 0-20 f.p.s. Light output approx. greater than many (so called 4 Joule) strobes. £12·50. Incl. P. & P.

THE 'SUPER' HY-LYGHT KIT

Approx. four times the light output of our well proven Hy-Lyght strobe. Incorporating:
- Heavy duty power supply.
- Variable speed from 1-13 flash per sec.
- Reactor control circuit producing an intense white light.

Never before a Strobe Kit with so HIGH an output at so LOW a price. ONLY £20·75. Incl. P. & P.

ATTRACTIVE, ROBUST, FULLY VENTILATED METAL CASE. Super Hy-Lyght Kit including reflector. £7·45. Incl. P. & P. For Hy-Lyght Kit including reflector. £4·45.

7-inch POLISHED REFLECTOR
Ideally suited for above Strobe kits. Price 66p. Incl. P. & P.

FROM APRIL 1st V.A.T.
(at the standard rate)
MUST BE ADDED TO ALL PRICES

RAINBOW STROBE FOUR LIGHT CONTROL MODULE

Will operate four of our Hy-Lyght or Super Hy-Lyght Strobes in either 1, 2, 3, 4 sequence; 2 + 2; or all together. Thoroughly tested and reliable. Complete with full connection instructions. Price: £18·75. Incl. P. & P. Send S.A.E. for details.

COLOUR WHEEL PROJECTOR

Complete with oil-filled colour wheel. 100 watt lamp. 200/240V AC. Features extremely efficient optical system. £18·50 + 35p. P. & P.
6 INCH COLOUR WHEEL As used for Disco lighting effects, etc. Price £5·75 inc. p. & p.

BIG BLACK LIGHT

400Watt. Mercury vapour ultra violet lamp. Outer bulb designed to absorb visible light and transmit u.v. rays. Extremely compact and powerful source of u.v. Innumerable industrial applications also ideal for stage, display, discos, etc. P.F. ballast is essential with these bulbs. Price of matched ballast and bulb £16·50. Incl. P. & P. Spare bulb £7·30. Incl. P. & P.

BLACK LIGHT FLUORESCENT U.V. TUBES
4ft. 40 watt. Price £5·80 incl. P. & P. (For use in standard bi-pin fluorescent fittings). MINI 9 in. 6 watt black light U.V. tube. £1·45. Incl. P. & P. Complete ballast unit and holders for 9 in. tube. £1·85.

Superior Quality Precision Made NEW POWER RHEOSTATS

100 WATT. 1 ohm, 10A; 5 ohm, 4·7A; 10 ohm, 3A; 25 ohm, 2A; 50 ohm, 1·4A; 100 ohm, 1A; 250 ohm, 0·7A; 500 ohm, 0·45A; 1 kΩ, 280 mA; 1·5 kΩ, 230mA; 2·5 kΩ, 2A; 3·5kΩ, 5 kΩ, 140mA. Diameter 3½in Shaft length ⅞in, dia. ⅛in. All at £1·73. Incl. P. & P.
50 WATT. 1/5/10/25/50/100/250/500/1/1·5/2·5/5kΩ. **All at £1·23.** Incl. P. & P.
25 WATT. 10/25/50/100/250/300/500/1/1·5/2·5/3·5/5kΩ. **All at 98p.** Incl. P. & P.
Black Silver Skirted knob calibrated in Nos. 1-9. 1¼in. dia brass bush. Ideal for above Rheostats, 18p ea.

RELAYS SIEMENS, PLESSEY, Etc. MINIATURE RELAYS

Col.(1) Coil ohms	1	2	3	4
	52	4-6	6M	63p*
Col. (2)	52	4-6	4 c/o	78p*
Working	150	6-12	4 c/o	78p*
d.c. volts	185	8-12	6M	63p*
	230	6-12	2 c/o	63p*
Col. 3	410	10-18	4 c/o	73p*
Contracts	600	12-24	4 c/o	78p*
	600	9-18	2 c/o	63p*
Col. (4)	700	16-24	4M 2B	63p*
Price	700	16-24	4 c/o	78p*
HD =	700	15-35	2 c/o HD	73p*
Heavy duty	700	16-24	6M	65p*
	700	6-12	1 c/o HD	50p*
*Incl. Base	700	20-30	6 c/o	75p*
	1,250	24-36	4 c/o	63p*
All prices	2,500	36-45	6M	63p*
incl. P. & P.	2,400	30-48	4 c/o	50p
	9,000	40-70	2 c/o	50p*
	15k	85-110	6M	50p*

12 VOLT D.C. RELAY 140 ohm coil
Type 1: Three sets c/o contacts rated at 5 amps. 78p incl. P. & P. (Similar to illustration below.)
Type 2: One set of c/o contacts. 60p incl. P. & P.
Type 3: 4-8 volt, 3 c/o HD, 67 ohm coil. 78p.

SPECIAL OFFER
700 ohm 4 c/o. Ex. new equipment. £50 per 100 incl. bases (minimum 100).

'DIAMOND H' 230 VOLT A.C. RELAYS (Unused)

Three sets c/o contacts rated at 5 amps. PRICE: 60p. Incl. P. & P. (100 lots £40 including P. & P.)

MINIATURE LATCHING RELAY
Manufactured by Clare-Elliott Ltd. Type F. 2 c/o permanent latching in either direction. Coil 1150 ohm, 15-30 Volt D.C. Size ¾" high, ¾" wide, ¾" thick. Complete with 3" leads. New 73p, incl. P. & P.

UNISELECTOR SWITCHES

NEW **4 Bank 25 Way** 24V d.c. operation. £5·88, P. & P. 25p. **6 Bank 25 Way** 24V d.c. £6·75. Post Paid. **8 Bank 25 Way,** 24V d.c. operation. £7·88. Incl. P. & P.

"HONEYWELL" PUSH BUTTON, PANEL MOUNTING MICRO SWITCH ASSEMBLY

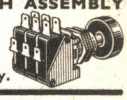

Each bank comprises a c/o rated at 10 amps 240V. A.C. Black knob 1in. Fixing hole ⅜ in. ONE bank 30p; TWO bank 40p; THREE bank 55p; incl. P. & P. Quot. for quantity.

'HONEYWELL' LEVER OPERATED MICRO SWITCH

15 amps 250 volt A.C. c/ contacts. Types N39, N95, N100, N101 NEW in maker's carton. PRICE: 10 for £1·90 incl. P. & P.

Very special offer **MICRO SWITCH**

5 amp c/o contacts. Fitted with removable metal panel assembly. Ex. P.O. 20 for £1 inc. post. (Min. order 20.)

METER BARGAIN
BALANCE/LEVEL METERS

100-0-100 Micro Amp. Size 1½in + 1½in + ⅞in. Price only 75p including P. & P.

AMMETERS NEW! 2½in. Flush round. Available in D.C. Amps 1, 5, 15, 20 or A.C. Amps 1, 5, 10, 15, 20, both types £1·75 incl. P. & P. 0-300V. A.C. £1·90 incl. P. & P.

INSULATION TESTERS *NEW!*

Test to I.E.E. Spec. Rugged metal construction, suitable for bench or field work, constant speed clutch. Size L.8in, W.4in, H.6in, weight 6lb. 1,000V, 1,000 megohms, £34·00 Incl. P. & C.
500V, 500 megohms, £28 incl. P. & C.

All Mail Orders—Callers—Ample Parking
Dept. PE4, 57 BRIDGMAN ROAD
CHISWICK, LONDON W4 5BB
Phone 01-995 1560
Showroom open Mon.-Fri.

SERVICE TRADING CO.

Personal callers only. Open Sat.
9 LITTLE NEWPORT STREET
LONDON WC2H 7JJ
Phone 01-437 0576

Practical Electronics Classified Advertisements

RATES: 9p per word (minimum 12 words). Box No. 20p extra. Semi-Display £7 per single column inch. Advertisements must be prepaid and addressed to Classified Advertisement Manager, "Practical Electronics" IPC MAGAZINES LTD., Fleetway House, Farringdon Street, London EC4H 4AD

BOOKS AND PUBLICATIONS

● **KILRIMONT BOOKS** ●
110 I.C. Projects (1971), **£1·20** + 5p post; 110 Semiconductor projects (1969), **£1·20** + 5p post; Understanding Electronic Components (1972), **£3·50**; Transistor Circuit Design Tables (1971), **£2·80**; Digital Logic (1971), **£1·50**; Audio Technicians Bench Manual (1972), **£3·00**; T.V. Technicians Bench Manual (1971), **£2·50**; Introduction to Semiconductor Devices (1972), **£1·90** + 5p post.
Many others. Please send for lists. Post free unless indicated.
KILRIMONT BOOKS (D), Kilrimont House, London Road, Braintree, Essex

THOSE 1,000 BANBURY UFO's! Details of our Prediction (and list) S.A.E. Numerous Charts, Map, Detectors. R. & E. PUBLICATIONS, Highlands, Needham Market, Suffolk.

COURSES

London Borough of Enfield
Trent Park College of Education
Cockfosters, Barnet, Herts.
TECHNOLOGY TEACHING
3-YEAR COURSE FOR MEN AND WOMEN

VACANCIES exist on the Course starting in September, 1973 for Mature Students (over 24 years) wishing to become teachers of Technology, for whom there is an increasing demand in Schools. Learning through problem solving situations forms an essential part of the Certificate Main subject "TECHNOLOGICAL STUDIES", involving techniques and methods of craft, Science and Mathematics, and offering a wide range of practical experience.

Applications will be considered from students with various qualifications and types of experience, together with an interest in the development of practical solutions to a wide range of problems.

Grants are available.

Prospectus, information and application forms from:
The Academic Registrar, Trent Park College of Education, Cockfosters, Barnet, Herts.
D. B. Denny, Chief Education Officer.

EDUCATIONAL

ENGINEERS. Get a technical certificate. Postal courses in Engineering, Electronics, Radio, TV, Computers, Draughtsmanship, Buildings, etc., FREE book from: BIET (Dept. ZC BPE 25), Aldermaston Court, Reading, RG7 4PF. Accredited by CACC.

A SUCCESSFUL CAREER IN RADIO

Get the success you deserve—take an ICS home study course. Pass C&G, M.P.T. exams FIRST TIME! Free books. Low cost. Personal tuition. Send TODAY for FREE Guide on Radio, TV, Electronics, Electrical Engineering.

Name _____

Address _____

ICS Dept. 730HI
Stewarts Road,
London SW8 4UJ

SITUATIONS VACANT

MEN! £50 p.w. can be yours

Jobs galore! 144,000 new computer personnel needed by 1977. With our revolutionary, direct-from-America, course, you train as a Computer Operator in only 4 weeks! Pay prospects? £2500+p.a. After training, our exclusive appointments bureau—one of the world's leaders of its kind—introduces you FREE to world-wide opportunities. Write or 'phone TODAY, without obligation.

London Computer Operators
Training Centre
M84, Oxford House
9-15 Oxford Street, W.1
Telephone 01-734 2874

127 The Piazza, Dept. M84
Piccadilly Plaza, Manchester 1
Telephone 061-236 2935

SERVICE SHEETS

SERVICE SHEETS for Televisions, Radios, Transistors, Tape Recorders, Record Players, etc., from **5p** with free Fault-Finding Guide. S.A.E. orders/inquiries. Catalogue **15p.** HAMILTON RADIO, 47 Bohemia Road, St. Leonards, Sussex. Telephone Hastings 29066.

SERVICE SHEETS, Radio, TV, etc. 8,000 models. Catalogue **15p.** S.A.E. enquiries. TELRAY, 11 Maudland Bank, Preston.

WANTED

TOP PRICES PAID
for new valves and components
Popular T.V. and Radio types
KENSINGTON SUPPLIES
(B) 367 Kensington Street
Bradford 8, Yorks.

WANTED URGENTLY. Back issues of P.E-June, July and August 1968. KIRK, Washfold Farm, Leyburn, Yorks. Leyburn 2193.

FOR SALE

MORSE MADE EASY!!
FACT NOT FICTION. If you start **RIGHT** you will be reading amateur and commercial Morse within a month (normal progress to be expected).
Using scientifically prepared 3-speed records you automatically learn to recognise the code **RHYTHM** without translating. You can't help it, it's as easy as learning a tune. 18 W.P.M. in 4 weeks guaranteed.
Beginner's Section only **£3·30**, complete course **£4·50** (Overseas £1 extra) details only, 4p stamp. **01-660 2896**
G3HSC (Box 19), 45 GREEN LANE, PURLEY, SURREY

SEEN MY CAT? 5,000 items. Mechanical and Electrical Gear, and materials. S.A.E. K. R. WHISTON, Dept. PE, New Mills, Stockport.

P.E. No. 1 to CURRENT ISSUE. Missing April 66, August 70, September 71, December 65. X Model 8 Avo. Ring Whitley Bay 27325.

ALL ISSUES P.E. with binders and indexes. 8 Volumes. Offers. Box No. 47.

TV LINE OUT-PUT TRANSFORMERS
Tidman Mail Order Ltd., 236 Sandycombe Road, Richmond, Surrey TW9 2EQ
01-948 3702

FIBRE OPTICS
Flexible Light Pipe for conveying light to inaccessible positions. Fibroflex Type I. Glass 1·14mm effective dia. PVC sheathed. 44p per metre. (VAT inc.), P. & P. 10p. Any quantity.

Polariser Sheet up to 1 sq. ft. max. size. 16½p per sq. in. (VAT inc.), P. & P. up to 6 in. square 10p; over 6 in. square 30p
★ Cut down glare
★ See those pixie tubes
★ Cross them for light control
★ Make your own strain gauge for plastics and glass

Circuit Board Etching Kits. Full instructions. **£1·37½** (VAT inc.), P. & P. 14p

Photographic CDS Light Cells—used (with part of original circuit free), **33p** (VAT inc.), Post free.

All items are strictly C.W.O.

From: ARVIN SERVICE COMPANY
12 CAMBRIDGE ROAD
ST. ALBANS

SLO-SYN STEPPING MOTORS. Type SS50-1001, 14V d.c. Torque 50 oz in. **£23.** A few magnetic chucks for same, **£6·50** (all new). MICHAELS, 36 Orchard Way, Stanbridge, Nr. Leighton Buzzard, Beds.

COLLARO STUDIO DECK, £9. Motek deck in recorder, **£11.** 5·10 amplifier and f.m. £1 (o.n.o.). 01-634 4290.

LADDERS

LADDERS, 24½ft **£9·80,** carr. 80p. Leafl (Dept. PEE), HOME SALES LADDE CENTRE, Baldwin Road, Stourport, Worc Tel. 029-93 2574.

AERIALS

DIRECT FROM MANUFACTURER—a co prehensive catalogue of UHF and VHF/F aerials, fixing brackets, chimney lashin clamps, masts, amplifiers, cable, etc., for t D.I.Y. enthusiast. Complete with use installation hints. Send 3p stamp to CLA DEW ENTERPRISES (PE), 261 Hard Street, London, S.E.24.

RECEIVERS AND COMPONENTS

DRY REED INSERTS

Overall length 1.85" (Body length 1.1") Diameter 0.14" to switch up to 500 mA at u to 250v D.C. Gold clad contacts. 62½p pe doz.; £3·75 per 100; £27·50 per 1,000; £250 pe 10,000. All carriage paid.
G.W.M. RADIO LTD.
40/42 Portland Road, Worthing, Sussex 0903 348

BRAND NEW COMPONENTS BY RETU Electrolytics, 16V, 25V, 50V, 1, 2·2, 4·7, mfds., **3½p**; 22, 47, **4p** (50V, **5p**); 100, **5p** (5 **6p**). Subminiature bead-type tantal 0·1/35V, 0·22/35V, 0·47/35V, 1/35V, 2·2/3 4·7/35V, 10/16V, **8p.** Mylar Film 100V, · ·002, ·005, ·01, ·02, **2p**; ·04 ,·05, **2½p**; ·068 **3p.** Polystyrene 63V, E12 series 10 pf.–10 pf., **2p.** Miniature Highstab Resistors series 5% Third Watt Carbon Film 1Ω–1 (10% over 1M) and 1W Metal Film 27Ω–10 8 for **5p.** Insured postage 8p. THE SUPPLY CO., 127 Chesterfield Road, Shef S8 0RN.

RESISTORS

CARBON FILM

$\frac{1}{20}$-$\frac{1}{8}$-$\frac{1}{4}$-$\frac{1}{2}$-1-2 WATT MOST VALUES

STD 5%, 60p/100, £5/1,000

STD 2%, 65p/100, £5-50/1,000

HI-STAB 2%, 70p/100, £6/1,000

VALUES YOUR CHOICE IN FIVES

POSTAGE FREE—C.W.O.

WRAP RESISTORS

9 ELLEN CLOSE, NORTH PETHERTON, SOMERSET

TELEPHONE: NORTH PETHERTON 662501

Trampus electronix

All Brand New. No Rejects or Remarks. Money Back Assurance.

DIGITAL INDICATORS: 5V 0-9DP, with socket and red filter, **£1·39**. Nixie type, **97p**. ½" LED 7SEG + DP Dil type, **£2·50**.

LIGHT EMIT DIODES Red: Visible red/panel clip/data **38p**. 209 type, **33p**. Infra red type, **£1**.

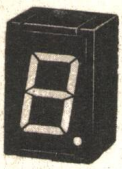

IC GAS DETECTOR. Smoke, Butane Vapour, etc., **£1·87**.

ULTRASONIC transducer/remote control. **£2**.

IC digital clock

28 pin DIL 12/24 hr. 4/6 digit, **£11·50**, data **9p**. Kit **£21**. Indicators **£1·29** ea. PCB **£1·69**, Case **35p**. **PW ELECTRONIC CAR IGNITION KIT, £6·67.**

STEREO.

QUAD AUDIO from stereo, matrix IC, **£3·67**. MAGNETIC CARTRIDGE, diamond 20–20kHz, **£4·19**. DUAL IC PREAMP **£1·67**. FM Hi-Fi TUNER **£8**. MC1310P MPX FM decoder, **£2·69**; KIT **£3·45**.

INTEGRATED CIRCUITS: with data, 709 TO5, **21p**; DIL, **28p**; 710 and 748, **33p**; 723, **55p**.

741 OP AMP DIL, **28p**. Photodetector/amp, **33p**. Voltage regulator 1½A, 5 to 20V 3 lead, **£1·49**.

RECEIVER ZN414 Ferranti 3 lead, **£1·19**. AF amps: 2W, **£1·19**; 3·5W, **£1·33**; SL403, **£1·45**.

555 Timer/mono/as table osc. clock, **95p**.

74N TTL

BRANDED TEXAS/ITT etc. FULL RANGE

Gates, 7400/1/2/3/4/5/10/20/30/40/50, etc., **15p**; 7413, **29p**; 7470/72, **29p**; 7473/74/76, **37p**; 7447, **£1·27**; 7490, **59p**; 7492, **67p**; 74121, **40p**; 74141, **99p**; **DIL SOCKETS,** high or low profile, 14 or 16 pin, **13p**. **DIL PLUG** or IC case, 16 pin, 10mm high, **35p**.

SEMICONDUCTORS

BC107, 8p. BC108, 8p. BC109, 8p. 2N3055, 40p. AC125/6/7/8, AC127/8, AC187/8, AF117, **15p**; AD161/2, **35p ea.**; BC147/8/9, **9p**; BC167/8/9, **17p**; BC177/8/9, **15p**; BC182/3/4, **9p**; BC212/3/4, **9p**; BCY70, **16p**; BD131/2, **63p**; BFY50/51/52, **17p**; OC28/35, **49p**; OC71, **27p**; TIS43 UJT, **29p**; 2N706, **12p**; 2N2369, **21p**; 2N2646, **49p**; 2N3053, **17p**; 2N3055, **40p**; 2N3614, **55p**; 2N3702/3/4/5/6/7, **10p**; 2N3708/9/10/11, **9p**.

FETS: 2N3819, **28p**; 2N3823, **29p**; 2N3866 UHF, **59p**.

ME 0411/2, **18p**; ME 4001, **12p**; ME 4102, **11p**.

DIODES:

IN914, **3p**; OA91, **5p**. **ZENERS:** BZY88 400mW, **10p**.

IN4001, 4p; IN4004, **8p**; 50V 1A Bridge, **23p**. TRANSFORMERS: ¼A mini 12/24V, **£1**; 6/12V, **£1**.

SCR 400V: 1A, **23p**; 3A, **49p**; 4A, **55p**; 6A Triac, **69p**.

CAPACITORS: 25/30V Electrolytic.

10/50/100µF, **5p**; 200/500µF, **8p**; 1,000µF, **15p**.

DISC: 22pf to 0·047µF, **4p**; up to 0·1µF, **6p**.

PRESETS: 0·25W, **5p**. RESISTORS ½W 5%, **1½p**.

CARBON POTS, 12p ea. Switch +, **12p**. Dual, **50p**.

All DIN plugs, **13p**; sockets, **9p**. Vero stocked.

Copper Board 12" × 6"; S.R.B.P., **40p**. FeC. ¼lb, **20p**.

Antex irons at R.R.P. Desolder Braid, **16p**.

WEATHER STATION barometer, temp., humid., **£3**.

FREE CATALOGUE S.A.E. Discount 20+ 10%.

C.W.O. **P. & P. UK & Europe 7p. Overseas 35p.**

P.O. BOX 29, BRACKNELL, BERKS.

—N-Channel FETs 3819E—£1

ull specification devices complete with circuit etails for building voltmeter, timer, ohm-eter, etc.

nd 10p for full list of field effect transistors and her top quality transistors available at bar-in prices.

REDHAWK SALES LTD.

Station Road, Gerrards Cross, Bucks.

MAIL ORDER ONLY

PRECISION

POLYCARBONATE CAPACITORS

Close tolerance. High stability. All 63V d.c.

0·47µF:	±5%	30p;	±2%	40p;	±1% 50p
1·0µF:	±5%	40p;	±2%	50p;	±1% 60p
2·2µF:	±5%	50p;	±2%	60p;	±1% 75p
4·7µF:	±5%	70p;	±2%	90p;	±1% £1·15
6·8µF:	±5%	95p;	±2%	£1·15;	±1% £1·50
10µF:	±5%	£1·10;	±2%	£1·40;	±1% £1·80
15µF:	±5%	£1·60;	±2%	£2·10;	±1% £2·70

TANTALUM BEAD CAPACITORS. Values available 0·1, 0·22, 0·47, 1·0, 2·2, 4·7, 6·8µF at 35V, 10µF 25V, 15µF 20V, 22µF 15V, 33µF 10V, 47µF 6V, 100µF 3V—all at **9p** each; 6 for **50p**; 14 for **£1**. Special pack 6 off each value (78 capacitors) **£5**.

NEW!—TRANSISTORS. BC107, BC108, BC109. All at **9p** each; 6 for **50p**; 14 for **£1**. All brand new and marked. Full spec. devices. May be mixed to qualify for quantity prices. **AF178 —40p** each; 3 for **£1**.

POPULAR DIODES. IN914, 7p each; 8 for **50p**; 18 for **£1. IN916, 9p** each; 6 for **50p**; 14 for **£1. 1S44, 5p** each; 11 for **50p**; 24 for **£1**. All brand new and marked.

NEW LOW PRICE—400 mW Zeners. Values available 4·7, 5·6, 6·8, 7·5, 8·2, 9·1, 10, 11, 12, 13·5, 15V. Tol. ±5% at 5mA. All new and marked. Price **10p** each; 6 for **50p**; 14 for **£1**. Special offer 6 off each voltage (66 zeners) **£4·50.**

RESISTORS. Carbon film 5%, ¼W at 40°C, ⅓W at 70°C. Range from 2·2Ω to 2·2MΩ in E12 series, i.e. 10, 12, 15, 18, 22, 27, 33, 39, 47, 56, 68, 82 and their decades. High stability, low noise. All at 1p each; **8p** for 10 of any one value; **70p** for 100 of any one value. Special pack—10 off each value 2·2Ω to 2·2MΩ (730 resistors) **£5**.

440V A.C. CAPACITORS. 0·1µF, size 1¼in × ¼in, **25p**; 0·25µF, size 1¾in × ¾in, **30p**; 0·47 and 0·5µF, size 1¾in × ¾in, **35p**; 1·0µF, size 2in × ¾in, **45p**; 2·0µF, size 2in × 1in **75p**.

SILICON PLASTIC RECTIFIERS 1·5A— Brand new wire-ended DO27. **100PIV** at **8p** each or 4 for **30p**; **400PIV** at **9p** each or 4 for **34p**; **800PIV** at **14p** each or 4 for **50p**.

5p post and packing on all orders below £5.

MARCO TRADING

(Formerly V. ATTWOOD)

Dept. E2, The Maltings, Station Road Wem, Shropshire

COMPUTER PANELS. 9in × 7½in long lead Trans. and Comps., E6, 8 Trans., **25p** (10p); E45, 16 Trans., **40p** (10p); E47, 10 Trans., **30p** (10p).

AMERICAN PANELS. 4 for **60p** (12p) with data.

M.C. METERS. 2–3in, three assorted, **£1·05** (25p).

WIRE ENDED NEONS. 10 for **45p** (8p); 20 for **75p** (8p). Bank of five with 5 C407 Driver Trans., **45p**. Bank of 30 with 5 C407 Driver Trans., **£2** (15p).

22 WAY STEPPING SWITCH with Reset, Mains Operation, **80p** (15p).

NEW 46 WAY AS ABOVE, £1·25 (25p).

CROUZET GEARED MOTOR. Mains, 15 r.p.m., a.c.i.w., **75p** (15p).

5 FIGURE RESETTABLE COUNTER. 18/22V, will work on 12V, **£2** (15p).

SILICON DIODES 650V 1½A. 10 on Tagboard, **30p** (5p).

I.C. 7400 SERIES ON PANEL(S). 10 for **75p** (10p).

COPPER CLAD PAX. PANELS. 5½in × 5½in' 6 for **30p** (10p).

POLYSTYRENE CAPACITORS. 125V, 100pF to 0·012, **20p dozen**; 0·015 to 0·068, **30p dozen** (if ordered alone **10p**).

MIXED POLYSTYRENE/S. MICA CAPS. 100 for **45p.**

7lb ASSORTED COMPONENTS, £1·50.

2lb ASSORTED COMPUTER PANELS, £1·50.

S.A.E. 9in × 4in FOR LISTS.

J.W.B. RADIO

75 HAYFIELD ROAD, SALFORD 6, LANCS

Postage in brackets *Mail order only*

FROM 1st APRIL ADD 10% FOR V.A.T.

100 WATT AMPLIFIER

Fully protected, transformerless, 9 transistor circuit. Input 500 mV. Output into 8 ohms. 0·1% distortion.

Printed circuit board and full instructions. **£1·45p** + 10p P. & P. S.a.e. for list of component bargains.

EDMUNDS COMPONENTS, 134 NORTH END ROAD, LONDON, W14. (Mail order only)

VISIT AUTO TRACTION. Thousands of bargains in surplus radio equipment. Meters, motors, relays, TR/TX, telephone equipment, aircraft equipment. S.A.E. enquiries. 27a Arragon Road, Twickenham, Middx. 01-892 9489.

Bridge of 4 ZS74 diodes, 800 p.i.v., 750MA on panel. New, **50p**, p.p.

Transformer, 9–0–9V 100mA. New **65p**, p.p.

Transformer, 24–0–24V 500mA. New, **£1·15**, p.p.

Transformer, 20V 1A. New, **£1**, p.p.

P/C Board S/S 5½in × 5½in. 10 for **50p** + 15p P. & P.

Transformers, 7·5 + 7·5V app. ½A, **60p**, p.p. 18–0–18V 200mA + 24V 40mA **70p**, p.p.

F.M. Tuner, with RF stage with AGC. 3 plug in transistors neg. earth. Size 2½in × 2in × 1½in. With circuit, **£1·25**, p.p.

Crouzet Geared Motors, 240 volt 10, 15, 30 or 60 rpm, new, **£1·40**, p.p.

Transformers, 52–0–52V 1A + 22–0–22V 0·2A, **£2**, p.p. 34–0–34V 2A + 22–0–22V–2A, **£2**, p.p.

Veeder root 7 digit counter. 115V 2·5VA. **75p**, p.p.

UHF Tuners, transistorised, £1·50, p.p.

Veroboard 0·1 4in × 2½in. 10 for **£1** + 15p p.p.

3BP1 Scope Tube with base and screen (ex equipt.), **£2·50**, p.p.

Mullard I.F. Module, A.M./F.M. to suit our tuner, transistorised, **£1·25**, p.p.

All goods subject to 10% V.A.T. from April 1st.

R.T. SERVICES (Mail order only)

77 Hayfield Road, Salford 6

ADD V.A.T. AT THE STANDARD RATE AFTER APRIL 1st

MICROCIRCUITS: 709 **28p**; 710 **36p**; 723 **57p**; 741 **28p**; 748 **37p**; PA230 **70p**; SL702C **50p**; FET Op Amp **£1·62.**

TRANSISTORS: 2N696 **14p**; 2N697 **14p**; 2N706A **11p**; 2N1613 **16p**; 2N1711 **16p**; 2N2218 **19p**; 2N2219 **19p**; 2N2219A **19p**; 2N2904 **17p**; 2N2926 RED **6p**; ORANGE **7p**; YELLOW **8p**; GREEN **9p**; 2N3053 **15p**; 2N3054 **40p**; 2N3055 **35p**; 2N3702 **10p**; 2N3703 **10p**; 2N3704 **10p**; 2N3705 **9p**; 2N3706 **9p**; 2N3709 **8p**; 2N3710 **9p**; 2N3711 **9p**; 2N4058 **12p**; 2N4059 **9p**; 2N4061 **11p**; 2N4062 **11p**; 2N5172 **10p**; 2N5550 **39p**; AC107 **28p**; AC126 **12p**; AC127 **12p**; AC128 **12p**; AC176 **15p**; ACY17 **23p**; ACY21 **17p**; AF114 **14p**; AF115 **14p**; AF116 **14p**; AF117 **14p**; AF124 **22p**; BC107A **5p**; BC107B **7p**; BC108A **5p**; BC108B **7p**; BC108C **7p**; BC109B **6p**; BC109C **7p**; BC125 **14p**; BC147A **9p**; BC167A **10p**; BC168B **9p**; BC169B **10p**; BC177 **13p**; BC178 **12p**; BC179 **16p**; BCY70 **15p**; BCY71 **22p**; BD142 **35p**; BF115 **20p**; BF194 **13p**; BFX29 **24p**; BFX84 **20p**; BFX86 **15p**; BFX87 **24p**; BFX88 **18p**; BFY50 **15p**; BFY51 **15p**; BFY52 **15p**; BLY47A **40p**; BSX20 **12p**; OC44 **12p**; OC45 **12p**; OC71 **12p**; OC72 **12p**; OC81 **18p**; OC83 **24p.**

ME SERIES AVAILABLE.

RECTIFIERS: 1A: 50V **3½p**; 100V **4p**; 200V **4½p**; 400V **5p**; 800V **6p**; 1,000V **7p**; 3A: 400V **12p.**

ZENERS BZY88 SERIES: 2·7V to 33V **8p** each.

DIODES: IN916 **4p**; OA90 **6p**; OA200 **7p**; OA202 **8p.** SCR IR122D (400V 5A) **£1·14.** BTX30–600 **75p.**

LED Panel Lamp with Bush and Data **40p.**

Soldercon DIY IC Pin Sockets **1p** per Pin.

IC Sockets HI or LO: 14 pin **12p**; 16 pin **15p.**

Carbon Film ¼W 5% Resistors E12 Values 22 to 2·2M **1p** each or **7p** per 10 of one value.

DALO ETCH RESIST FILLED FIBRE TIP PEN **80p.**

MINIATURE METAL GLAZE RESISTORS ⅛W 5% **4½p** each.

ITT POCKET MULTIMETER 27 ranges **£17.**

JEF ELECTRONICS (P.E.4)

York House, 12 York Drive, Grappenhall, Warrington, WA4 2EJ. Mail Order Only. C.W.O. P. & P. 10p per order minimum. Price List Free.

BEDFORD ELECTRONICS

2 Grove Place · Bedford

Bedford 51961

YOUR LOCAL COMPONENTS SUPPLIER

FREE CATALOGUE ON REQUEST

RADIO & TELEVISION AERIAL BOOSTERS £2·95, five television valves **45p. 50p** bargain transistor packs, bargain **£1** resistor and capacitor packs. UHF-VHF televisions **£7·50.** Carr. £1·50. S.A.E. for 3 leaflets. VELCO ELECTRONICS, Bridge St., Ramsbottom, Bury, Lancs.

SPECIAL OFFER. 100 mixed resistors. Preferred Values ¼W and ½W **£1·25,** including postage. 2·2mF 260V WKG **10p** each, including P P. ALEXANDERS, 16 Inverness Street, London, N.W.1. Tel. 465 5322.

CASED AMPLIFIERS

2 × ECC83, EL84, EZ80. 20μV I/P sensitivity 2W O/P into 7in × 4in 3Ω speaker. All contained in polished cabinet with non-standard single motor deck. Tested with circuit, **£3** (£1).

COMPUTER PANELS

Lots of transistors inc. power types, diodes, R's, C's, pot cores, etc. Some boards broken, but good value at 3lb for **£1** (25p), 7lb for **£2** (40p).

60p COMPONENT PACKS

Resistors: 350 carbon, **60p** (15p); 200 5% hi-stab, **60p** (12p); 100 1 and 2%, **60p** (8p). **Capacitors:** 150 mica, poly, ceramic, **60p** (8p); 75 electrolytic, **60p** (15p); 150 paper, foil, polyester, **60p** (15p). Any 5 packs, **£2·50** (25p).

FERRIC CHLORIDE

Anhydrous technical quality in sealed 1lb packs, **40p** (15p); 10lb, **£3·50** (50p).

Components: BC107–8–9, 8p ea., 14 for **£1**; 709C, **25p**; 741C, **25p**; 723C, **40p**; 2N3055, **35p**; 1N4003, **7p**; 1N4006, **11p**; Crofon 1610 Light Guide, 64 filament, **£1** per metre, 5+ **80p**; 10+ **70p**. Surplus capacitors MFD/V: 0·47/350, **6p**; 2/150, **2p**; 8/350, **8p**; 8/450, **10p**; 25/25, **5p**; 500/50, **12p**; 550/6, **3p**; 1000 + 500/18, **12p**—lots of others. Lots of odd units, scopes, meggers, avo's, sig. gens, etc., at shop for callers. S.A.E. list. Post in brackets, small parts 3p.

GREENWELD (PE7)

24 Goodhart Way, West Wickham, Kent. Tel. 01-777 2001. Shop at **21 Deptford Broadway, S.E.8.** Tel. 01-692 2009.

COMPONENTS—Integrated Circuits, Digital Displays, Diodes, Resistors, Capacitors, Switches. List 3p. CAVERN ELECTRONICS, 29 Clarefield Road, Leicester, LE3 6FB.

MINIATURE CARBON FILM RESISTORS. 5%, ⅛W, ¼W, ½W, E12 Series. 22ohm to 1MΩ. 10 for **7p.** 50 for **30p.** Mixed values and wattages to your choice. ELECTRONIC COMPONENTS, Lake Bargain Centre, 113 Park Road, Didcot. (Mail order only.)

MISCELLANEOUS

ENAMELLED COPPER WIRE

S.W.G.	1lb Reel	¼lb Reel
10–14	£1·15	65p
15–19	£1·15	65p
20–24	£1·18	68p
25–29	£1·25	75p
30–34	£1·30	80p
35–40	£1·40	85p

The above prices cover P. & P. in U.K. Supplied by

INDUSTRIAL SUPPLIES

102 Parrswood Rd., Withington, Manchester 20
Telephone No. 061-224 3553

AT LAST YOU CAN TRANSMIT AND FORGET ABOUT LICENCE EXAMINATIONS

because this Ministry approved transmitter/receiver kit does not use R.F.
Your transmissions will be virtually SECRET since they won't be heard by conventional means. Actually it's TWO KITS IN ONE because you get the printed-circuit boards and components for both the transmitter AND receiver. You're going to find this project REALLY FUN-TO-BUILD with the EASY-TO-FOLLOW instructions. An extremely flexible design with quite an AMAZING RANGE—has obvious applications for SCHOOL PROJECTS, LANGUAGE LABORATORIES, SCOUT CAMPS, etc.

GET YOURS! SEND **£5·50** NOW (S.A.E. for details)
TO: 'BOFFIN PROJECTS'
DEPT. KE2010
4 CUNLIFFE ROAD
STONELEIGH, EWELL, SURREY

METER REPAIRS. Ammeters, voltmeters, multi-range meters, etc. Send to METER REPAIRS, 39 Chesholm Road, London, N16 0DS.

RUN YOUR TAPE RECORDER OFF A.C. MAINS

Mains unit supplied complete and ready to plug into your cassette recorder. (State voltage, model and plug required.) **£2·50** P. & P. 15p
Also available for single outputs 6V, 9V, 12V, 18V, **£2.** P. & P. 15p.

R.C.S PRODUCTS (RADIO) LTD.
(Dept. P.E.), 31 Oliver Road, London, E.17

ASTOUNDING new **MARK 7 AC POWER UNIT** with **TWO OUTPUTS** and **LOW BATTERY DRAIN** gives the **MOST BRILLIANT** and **BEST EVER INTERNATIONAL PERFORMANCE** of all time from 12 volt **CAR BATTERY.** Fantastic for a **VAST RANGE** of **HUNDREDS** of makes and types of 200-240 volt **AC** and **UNIVERSAL AC/DC ELECTRICAL APPLIANCES** and **EQUIPMENT** within its scope. Wonderful for **FLUORESCENT TUBES** up to the **GIANT** 8ft. 125 watt size. **RECHARGES YOUR BATTERY** from any other battery by using any motorist's **AC MAINS** battery charger. Should be £14 + £1 delivery. **OUR PRICE (UNUSED** but case marked) **ONLY £6·90** + **£1** delivery. 8 day's appro. against cash. C.O.D. with pleasure. (Send SAE for details)

Dept PE, BROADWAY DISTRIBUTORS, The Generator Centre, House of Time, 273 Broadway, Rossall, Fleetwood, Lancs.

DIMMIT

range of light dimmers

- ★ professional modules for industrial use on heaters, lamps, motors, etc.
- ★ commercial modules for studio, stage, disco and clubs, etc.
- ★ attractive standard wall mounting models for home and office, etc.

Rotary and slider control versions. Ratings available: 400W, 1,000W, 2,000W.

Send 10p for complete catalogue and price list. Discount for quantities.

YOUNG ELECTRONICS
54 Lawford Road, London NW5 2LN
01-267 0201

Build the Mullard C.C.T.V. Camera
Kits are now available with comprehensive construction manual (also available separately at 65p.)
SEND 5"X7" S.A.E. FOR DETAILS TO:
CROFTON ELECTRONICS
15/17 Cambridge Road, Kingston-on-Thames, Surrey KT1 3NG

CONSTRUCTION AIDS. Screws, nuts, spacers, etc., in small quantities. Aluminium panels punched to spec. or plain sheet supplied. Fascia panels etched aluminium to individual requirements. Printed circuit boards—masters, negatives and boards, one-off or small numbers Send 6p for list. RAMAR CONSTRUCTOR SERVICES, 29 Shelbourne Road, Stratford-on-Avon, Warwks.

MUSIC

If your interest is in **SYNTHESISERS** and other **ELECTRONIC MUSIC** projects, you need our 1973 catalogue of circuit assemblies and units. Detailed and informative, complete with project layouts. Send **20p** P.O. to:
TAYLOR ELECTRONIC MUSIC DEVICES
P.O. Box 42, Chester CH1 2PW

CLEARING LABORATORY, scopes, V.T.V.M's, V.O.M's, H.S. recorders, transcription turntables, electronic testmeters, calibration units, P.S.U.'s, pulse generators, D.C. null-potentiometers, bridges, spectrum analysers, voltage regulators, sig-gens, M C relays, components, etc. Lower Beeding 236.

PSYCHEDELIC MINI-STROBE

A very POWERFUL, POCKET-SIZED STROBE-LIGHT that is SELF-CONTAINED and you can take anywhere. Go to parties and really BRAIN-FREEZE them with DAZZLING PSYCHEDELIC EFFECTS and STOP-MOTION FLASHES. Boffin's new MINI-STROBE kit constitutes a fully solid-state electronic device which is COMPLETE with FUTURISTIC case/reflector unit, printed-circuit board, electronics, and source-lamp—the only extra is a battery which you can buy locally. The whole thing can be easily built in a few hours.
A veritable FLICKERING FASCINATOR! Adjustable flash-rate.
GET ONE (or two) NOW and BEGIN STEALING THE THUNDER at DISCOS and PARTIES with your own POCKET-LIGHTNING!
SEND **£1·95** for *YOUR* MINI-STROBE, to:

Boffin Projects
4 Cunliffe Rd., Stoneleigh, Ewell, Surrey

P.E. SYNTHESISER KNOB KIT

Complete kit, colour coded as per the front cover of February 1973 issue (43 knobs including 7 with calibrated skirts). Made in good quality plastic with substantial brass inserts and grub screws. **£3·56** Post Free

DE LUXE KIT

As above but all knobs having calibrated skirts for easy recording of settings and reprogramming. **£5·36** Post Free

RE-AN PRODUCTS LTD.
BURNHAM RD., DARTFORD, KENT
Tel.: DARTFORD 20785

NYLON/A.B.S. EQUIPMENT BOXES, 4·2in × 2·1in × 1·65in inside, take up to 14 blade terminals, **50p.** Terminals **1p** each. Useful 4-way terminal blocks, spring connectors, **15p.** P. & P. 8p per order. MODEC, Curbridge Road, Witney, Oxon.

HARDWARE—Screws, nuts, washers and other useful items in small quantities. Sheet aluminium to individual requirements punched/drilled. Send 6p for list. RAMAR CONSTRUCTOR SERVICES, 29 Shelbourne Road, Stratford-on-Avon, Warwickshire.

ANALOGUE COMPUTER

Reduced to £150

Shorts General Purpose Analogue Computer, complete with stabilised power supplies and double beam oscilloscope for display of results. 18 Function Units (integrators/summers), etc. Details and parts list on request. Demonstration by appointment. Instruction Manual and some spares available. Offers considered.
J. Gray, Oakhill, Bath BA3 5HU
Phone: Oakhill 255

Versatile
10 in ONE

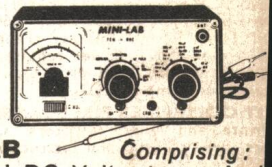

MINI-LAB *Comprising:*
• AC and DC Voltmeter • Aud
Generator • Ohm Meter • Resistan
Substitution • Capacitance Subs
tution • DC Ammeter • Battery Supp
• RF Signal Generator • RF Fie
Strength Indicator.
This new, unique instrument combines all you need for testing. Money back if not satisfied. **£11·2** plus 25p p.&

Cash with order or send S.A.E. for illustra data sheet to:
J. H. ASSOCIATES LTD. (Dept. F
Cricketfield Lane, Bishop's Stortford, H

ELECTRONICS FANATICS

whether beginner or advanced—we offer a range of over 35 SUPER projects.

Have you ever wanted to build A MACHINE THAT LEARNS? Or perhaps make a TEACHING DEVICE? Maybe you fancy the idea of an ELECTRONIC FANTASY MACHINE? How about a "Thing" capable of REPRODUCING ITSELF? Whatever your electronic turn-of-mind, there's just GOT TO BE LOADS TO INTEREST YOU in the science-fiction-world of BOFFIN.

GET YOUR CATALOGUE — SEND JUST 15p NOW!

TO: BOFFIN PROJECTS
4 CUNLIFFE ROAD
STONELEIGH, EWELL
SURREY

Designs by GERRY BROWN and JOHN SALMON and presented on TV.

FIBRE OPTIC SUPPLIERS
P.O. BOX 702, LONDON W10 6SL

FLEXIBLE LIGHT CONDUIT used to convey light to inaccessible positions for inspection, panel indicators, photo-electric and other applications.

FIBROFLEX Type I glass fibre flexible light conduit, 1·14mm active dia., bundle sheathed in P.V.C. Prices per metre (U.K. post free): 1–4, **70p**; 5–9, **55p**; 10+, **40p**; 25m, **£6** per reel. Epoxy resin plus ferrules inc. with orders over 10m.

CROFON Type 1610 plastic flexible light conduit, 64 filaments. Active dia. 1·80mm. Prices per metre: 1–4, **£1·20**; 5–9, **£1**; 10+ **80p**. 25m, **£16** per reel.

PLASTIC MONOFILAMENT Type FP20, 0·5mm dia. unsheathed. 100m, **£3·50**; 200m, **£6.**

Send S.A.E. for full range of products, price list and literature. Overseas orders add 50p please.

GLASS FIBRE P.C. BOARD—large supplies available. $\frac{1}{16}$in single sided one ounce copper, 2p per 3 sq in (under 1ft); **75p** per sq ft (over 1ft). $\frac{1}{16}$in double sided one ounce copper, **1p** per sq in (under 1ft); **£1** per sq ft (over 1ft). Please add 10p per sq ft postage and packing. We can cut to your size at 1p per cut. SOLID STATE LIGHTING, The Firs, Smallworth Lane, Garboldisham, Diss, Norfolk.

STEREO IC DECODER

HIGH PERFORMANCE PHASE LOCKED LOOP (as in 'W.W.' July '72) **MOTOROLA MC1310P**

EX STOCK DELIVERY

Specn. Separation: 40dB 50Hz—15kHz. Distortion: 0·3%. I/P level: 560mV rms. O/P level: 485mV rms per channel. Input impedance: 50k. Power requirements: 8–12V @ 16mA. Will drive up to 75mA stereo 'on' lamp or LED.

KIT COMPRISES FIBREGLASS PCB (printed and tinned), Resistors, I.C., Capacitors, Preset Potm. and Instructions. Only £3·50 post free.

LIGHT EMITTING DIODE (Red) suitable as stereo 'on' indicator. For above with panel mounting clip and instructions. Only **35p** + **p.p.**

MC1310P only £2·77 + **p.p. 6p**

16 PIN DIL SOCKETS. 16p each.

SPECIAL OFFER
4002 100V 1A RECT. DIODES. Full Specification Devices. **ONLY 6p** each.

Fi-Comp Electronics
BURTON ROAD
EGGINTON, DERBY DE6 6GY

LOUDSPEAKER BARGAINS

Fane Pop 100 Watt 18" 8 15 ohm	**£19·50**
Fane Pop 60 Watt 15" 8/15 ohm	**£11·15**
Fane Pop 50 Watt 12" 8/15 ohm	**£9·25**
Fane Pop 25/2 12" 25 watts 8/15 ohm	**£5·40**
Fane Pop 15 12" 10 watts 8/15 ohm	**£4·00**
Baker Group 25 12" 3, 8 or 15 ohm	**£6·60**
Baker Group 35 12" 3, 8 or 15 ohm	**£8·00**
Celestion PS8 for Unilex	**£2·35**
EMI 13 x 8, 3, 8 or 15 ohms	**£2·25**
EMI 13 x 8 3, 8 or 15 ohms	**£2·60**
EMI 13 x 8 twin tweeter 3, 8 or 15 ohms	**£3·60**
EMI 13 x 8 type 350 15 watt 8 ohm	**£8·00**
Richard Allen 8" 3, 8 or 15 ohm	**£2·35**
Richard Allen 12" dual cone 3 or 15 ohm	**£2·50**
Fane 8" dual cone 808T 8 or 15 ohm	**£2·85**
Fane 8" d/cone roll surround 807T 8 or 15 ohm	**£3·50**
Elac 59RM109 9" x 5" 15 ohm	**£2·70**
Elac 59RM114 9" x 5" 8 ohm	**£2·70**
Elac 6½" d/cone 8 ohm	**£2·25**
Elac 6½" d/cone, roll surround 8 ohm	**£3·50**
Elac 4" tweeter 8 ohm	**£1·50**
Crossover for above (p. & p. free)	**£1·50**
Goodmans 8 P, 8 or 15 ohm	**£4·75**
Goodmans 10 P, 8 or 15 ohm	**£5·25**
Goodmans 12 P, 8 or 15 ohm	**£10·50**
Goodmans 15 P, 8 or 15 ohm	**£17·00**
Goodmans 18 P, 8 or 15 ohms	**£27·50**
2", 2½" or 3" 80 ohm	**·65**
Phillips 5" 8 ohm	**£1·95**
7" x 4" or 8" x 5" 3 or 8 ohm	**£1·50**
10" x 6" 3, 8 or 15 ohm	**£2·00**

FREE with orders over £6—"Hi-Fi Loudspeaker Enclosures" book.

All units guaranteed new and perfect.

Prompt despatch p. & p. 25p per speaker.

WILMSLOW AUDIO, Dept. PE
10 Swan St., Wilmslow, Cheshire, SK9 1HF

SINCLAIR EQUIPMENT—

IC12 **£2·00**
Z50 **£4·25**
PZ5 **£3·97**
Z30 **£3·50**
Project 60 tuner **£16·80**
AFU **£4·50**
Stereo 60 **£7·80**
PZ6 **£6·40**

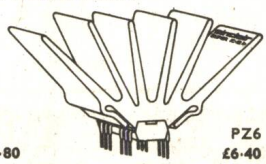

KITS OF PARTS FOR THE IC12
Includes all parts for the printed circuit and volume bass and treble controls needed to complete the mono version **£1·30.** Stereo version with balance control **£3·00.**

POWER UNITS FOR THE IC12
A set of components to construct a 30V, 0·5 Amp power supply **£2·27.** Also suitable Sinclair PZ5 fully constructed **£3·97.**

PROJECT 60 KIT **£2·50**
Our extremely popular kit contains the extra capacitors. DIN plugs and sockets, cables and fuse holder needed to complete Project 60.

S-DECS AND T-DECS

S-DECS **£1·44**
T-DECS **£2·88**
μ-DEC A **£3·00**
16 dil IC carriers **£1·25**

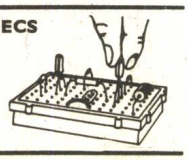

SINCLAIR EXECUTIVE CALCULATOR

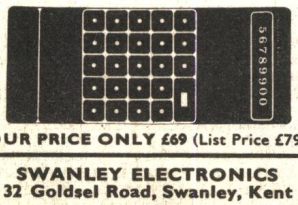

OUR PRICE ONLY £69 (List Price £79)

SWANLEY ELECTRONICS
32 Goldsel Road, Swanley, Kent

Mail order only. Postage 10p per item. Lists 10p. After April 1st please add 10% extra for V.A.T.

BELLING LEE INSULATED TERMINALS. Red or Black, 5 amp max. **10p** pair, p.p. 3½p

BERCOSTAT WIREWOUND RHEOSTAT. 50 volt, 800 Ω, 25 watts, 2in dia. **25p,** p.p. 7½p.

FINNED ALUMINIUM HEATSINK. 9in × 1¾in. Ready drilled. **20p,** p.p. 6½p.

SUB-MIN. CROC. CLIPS. Red or Black, insulated **4p.** Min. quantity, 6, p.p. 3½p.

GARRARD MAG. TAPE DECKS: 1¾i.p.s., 50V, solenoid operated brakes, etc. Mains voltage motors **£7·50** each, p.p. £1·23.

4½in PLANNAIR FANS. Complete, capacitor, ex equip. 2,800 r.p.m. **£3·50,** p.p. 40p.

ELECTRIC MOTORS, HOOVER OR CROMPTON PARKINSON. 250V. Single phase a.c.
¼ h.p., 1,440 r.p.m., **£3·75,** p.p. £1.
⅓ h.p., 1,425 r.p.m. or 2,800 r.p.m., **£6·75,** p.p. £1·25.
½ h.p., 1,440 r.p.m., **£2·25,** p.p. 75p.

AUDIO CONNECTORS

3 pin Din Plug	**13p** each.
5 pin Din Plug A type, B type	**13p** ,,
2 pin Din Speaker Plug/Socket	**10p** ,,
3 pin Din Line Socket	**13p** ,,
3·5mm Jack Plug Screened	**10p** ,,
Standard Jack Plug	**10p** ,,
Screened Standard Jack Plugs	**15p** ,,
Stereo Jack Plug	**18p** ,,
Screened Stereo Jack Plug	**18p** ,,

Phono Plugs: Red or Black **3p** each.
P.p. on above items 3½p.

MAINS NEONS
Red or Green. Size: ¾in × 1¾in. **15p,** p.p. 3½p.

LEVER ACTION P.O.1000 TYPE SWITCHES
Lock 4-pole changeover, **15p,** p.p. 3½p. Ex equip.
Lock 2-pole changeover, **10p,** p.p. 3½. Ex equip.

AUDIO LEADS
Screened Phono Leads 46in long, **15p.**
3·5mm JACK/3·5mm JACK 7ft 6in long, **40p.**
5-Pin Din A Type, 5-PIN A TYPE. Approx. 5ft long, **70p.**
P.p. on above items 5½p.

MULLARD & MALLORY SCREW TERMINAL CAPACITORS 4,500μF 64V, 7,100μF 40V, **50p** each. 20,000 30V, 25,000 25V, 35,000 15V, **30p** each, p.p. 10p.

MULLARD FULLWAVE RECTIFIERS
6-48V, 15 amp, **75p,** p.p. 8½p.

BELLING LEE 1·5 amp in-line rubber covered interference suppressor, **25p,** p.p. 8p.

RUBBER 3 PIN 5 AMP NON-REVERSIBLE CABLE CONNECTORS, 20p, p.p. 5½p.

SOLENOIDS 12 VOLT PULL ACTION
2in × 1in × ¾in, **40p,** p.p. 8p.

SIEMENS MINIATURE RELAY. Double pole changeover dust cover/base 48V, 2500, **50p,** p.p. 5p new.

OMRON MK2 MIDGET POWER RELAY. 12V d.c. Double pole changeover. New, **70p,** p.p. 5p.

STC MINIATURE RELAY 280 Ω, perspex cover, 6-15V new, **35p,** p.p. 5p.

GARDNER'S POTTED TRANSFORMER, 0-250V. Input: 18V 500m/n, 50V 150m/a, 6V 250m/a output. Size: 3in × 2½in × 2½in, **£1,** p.p. 20p. Ex equip. tested.

TELESCOPIC AERIALS
Chromed 7in closed, 28in extended, 6 section ball jointed base, **23p,** p.p. 8p new.

MULLARD 4 DM 160 INDICATORS in plastic holder/cover, ex equip., size approx. 1¾in × 1¼in × ¾in, **36p,** p.p. 8p.

PRINTED CIRCUIT BOARD/19 ACY 19's 10 OA200 Diodes: 1 reed relay: 1 AZ 229 zenner ass. capacitor/resistors. Power supply 22V, 250 m/A d.c. Output 240V a.c. **£1,** p.p. 20p. Ex equip.

WIRING CABLE
Size: 1·020. Various colours. 350yd, **60p,** p.p. 20p.

TOGGLE SWITCHES. Double throw. Ex equip, new condition, **75p** doz., p.p. 13p.

TOGGLE SWITCHES. Single pole, double throw. Ex equip., new condition, **50p** doz., p.p. 13p.

PAINTON PLUG SOCKETS. Type 159 series. Working voltage 350V a.c./d.c. current, max. 3 amp a.c./d.c. 7 pin plug and socket, **50p,** p.p. 6p. 15 pin plug and socket, **£1,** p.p. 6p. 31 WAY PLUG AND SOCKET, **£1·50,** p.p. 6p.

CASH WITH ORDER PLEASE

FIELD ELECTRIC LIMITED
3 Shenley Road
Borehamwood, Herts.
Adjacent Elstree Mainline Station
Tel.: 01-953 6009

BUILD A PROFESSIONAL SYNTHESISER

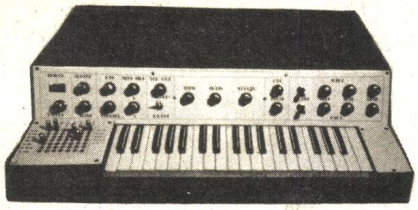

using **Dewtron** (Regd. Trademark)

PROFESSIONAL MODULES
CASH SAVINGS
by buying modules and parts in bulk!
All modules are available separately:

You too can build a professional synthesiser like the one illustrated using the professionally-proven range of Dewtron modules. **NEW MODUMATRIX** modular matrix system replaces clumsy patching. 3 and 4 octave keyboards and contacts.

VCO-2 STABLE, PRECISION V/C OSCILLATOR gives SINE, TRIANGULAR AND SQUAREWAVE outputs, 1 volt/octave voltage control. **£22** each or **£25** each 2 or more matched. **SHE-1 SAMPLE, HOLD AND ENVELOPE MODULE** gives variable attack, sustain, touch-sensitive playing when used with VCO-2 signals. **£15.**

Modules (except VCO-1) guaranteed two years.

Ring Modulator RM2, **£8.** Voltage-controlled Oscillator VC01, **£10·50,** giving sawtooth and square-wave outputs. Envelope shapers, ES1, self-triggered or ES2 keyboard-triggered, either type **£13.** White noise type WN1, **£7.** Voltage-controlled amplifier VCA1, **£10.** Voltage-controlled selective amplifier (filter for waa-waa, etc.) SA1, **£12.** Voltage-controlled Phase PH1, **£17.** Automatic Announcement Fader module for fading of music by microphone announcement, AF1, **£9.** etc., etc. ALL MODULES ARE BUILT, TESTED AND SEALED FOR LONG LIFE. Simply connect coloured wire connections as per easy instructions, build cabinet and wire in controls and patchboard connections! Joystick controls **£4·50.** REVERB Module and spring unit **£15.**

*With over 7 years' unblemished reputation in these pages, **Dewtron** continues to lead in new technical developments in electronic sound effects! Ask any of our customers. See our products in the music stores, too. Suppliers of special equipment to a leading group. Our modules are used in professional equipment by other manufacturers and in our own built synthesisers, e.g. "Gipsy" G.I. Send 15p for full catalogue of our famous musical effects.*

D.E.W. LTD. **254 Ringwood Road, FERNDOWN, Dorset BH22 9AR**

NEW COMPONENTS

Post and packaging free for orders over £1·50, include 10p P&P for each single pack under £1·50.
200 Mixed Resistors all types, **50p.** 100 Mixed Modern and Miniature Resistors, **50p.** 10mF 64V Electrolytic Caps, 5 for **25p;** 12 for **50p.** 640mF 16V Electrolytic Caps, 3 for **30p;** 7 for **60p.** 10mF 63V WIMA non-electrolytic, **15p** each. 3200mF 10V, **15p;** 3 for **38p;** 5 for **60p.**

SEMICONDUCTORS

Any 6 of the following, **50p,** or **10p** each. OC71, BFY50, 2N3702, CV8615, BSY95A, NTG885, 2N930, OA81, 2 x 1N914. (OR P60 **50p**).

CONSTRUCTORS' ITEMS

Subminiature Omron 12V d.c. relays mounted on CCT board, 3 for **60p,** P&P 9p; mounted on CCT board with components, 2 for **60p,** P&P 7p. GPO Relays, various 200Ω–7000Ω, **30p each.** Uniselectors, 10 pole, 25 way, £1 each, P&P 25p. Heavy Duty Foot Pedals, **50p,** P&P 20p. 6V 5 digit High Speed Counters, **£1·50,** 15p P&P.

DICTATING MACHINES

£2·50 each—ideal for spares, motor, power pack, record/replay, electronics with mike **£3·25.**

TRANSFORMERS

Mains—13V 2·5A and 15V 0·75A **£1·45,** 20p P&P. Mains—13V 1A 12V 0·5A, **£1·25,** 20p P&P. Mains—13V 5A and 24V 2A, **£2,** 25p. P&P. Mains—24V 100 mA and 6V 100mA, **75p,** 10p P&P.
Power Pack—suitable to run Transistor Radio or Cassettes Recorder, 5·5V, 100mA, smoothed d.c. output £1·20, 20p P&P.

EX COMPUTER CIRCUIT BOARDS

10 Boards, **50p,** 8p P&P; 25 Boards, **£1,** 18p P&P.
2 Boards with 2 power transistors, 1E 4 x OC28 type, **50p,** 7p P&P.

LAWBAK ELECTRONICS

(HI-FI AND COMPONENTS SPECIALISTS)
18 HIGH RD., SWAYTHLING, SOUTHAMPTON
Telephone: Southampton 58479
No Half Day Closing
Discount and Credit Terms Available

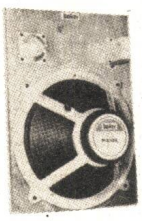

BAKER 12in. MAJOR £9

30-14,500 cps. Double cone woofer and tweeter combination. Baker ceramic magnet assembly, flux density 145,000 gauss. BASS RESONANCE 40 c.p.s. 20 watt RMS.

MAJOR MODULE KIT **£11·50**

30-17,000 cps. with tweeter, crossover and baffle.

BAKER LOUDSPEAKERS FULL RANGE

Regent 12 in.	£8	Superb 12 in.	£15	Group 25 12 in.	£8
Major 12 in.	£9	Auditorium 12 in.	£14	Group 35 12 in.	£9
Deluxe 12 in.	£10	Auditorium 15 in.	£20	Group 5015in.	£20

BAKER LOUDSPEAKER CO., BENSHAM MANOR PASSAGE
THORNTON HEATH, SURREY Tel. 01-684 1665

MINIATURE PUSH-BUTTON SWITCHES

4 pole changeover, 250V. Switching 0·1A and carrying 5A. 12·7mm pitch. Total depth 64mm. Available in banks of 1, 3 or 5. Actions available: independent, normal interlock, or momentary. Price per switch unit **40p.**
Mains switch 250V 5 amp can be fitted separately or on same frame as above: 1 pole changeover, **50p;** 2 pole changeover, **90p.**
Illumination for above (12V lamp holder, button) **50p.** The Main Switch above with 12mm threaded bush and nut for panel mounting: 1 pole changeover, **90p;** 2 pole changeover, **£1·05.**

NEON in amber lens and holder with resistance for 250V operation, **15p.**

MINIATURE SLIDER SWITCH 2 pole changeover. Outside sizes 25mm × 8mm switching 0·3A and carrying 1A, **12p.**

MINI MOTOR BOOSTER (P.E. July 1972). Complete kit of parts excepting motor **£2·25,** or built and tested, **£3.** Using 2N3054 and OC202.

All components supplied separately.

2N3054	50p	BC107	09p	BC169	15
2N3055	70p	BC108	10p	OA200	06
OC202	95p	BC109	10p	IN4001	07

P. & P. up to £3—10p. Over £3—free—Postal only.

BORDER ELECTRONICS (Supplies and Manufacture)
8 Broompark, KELSO, Roxburghshire TD5 7SN
Tel.: Kelso 2864

FREE!

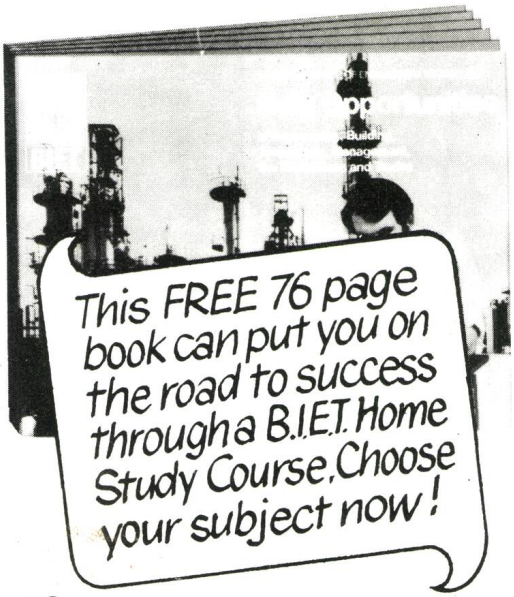

over 150 ways to engineer a better future

HIGHER PAY · A BETTER JOB · SECURITY

find out how in just 2 minutes

at's how long it will take you to fill in the coupon. Mail to B.I.E.T. and we'll send you full details and a free ok. B.I.E.T. has successfully trained *thousands* of men at me - equipped them for higher pay and better, more inter- ing jobs. We can do as much for YOU. A low-cost B.I.E.T. me study course gets results fast - makes learning easier l something to look forward to. There are no books to buy l you can pay-as-you-learn.

y not do the thing that really interests you? Without losing a 's pay, *you* could quietly turn yourself into something of an ert. Complete the coupon (or write if you prefer not to cut the e). No obligation and nobody will call on you . . . but it could be best thing you ever did.

hers have done it, so can you

sterday I received a letter from the Institution informing that my lication for Associate Membership had been approved. I can honestly that this has been the best value for money I have ever obtained – a echoed by two colleagues who recently commenced the course".— lent D.I.B., Yorks.

mpleting your course, meant going from a job I detested to a job I love, with unlimited prospects".—Student J.A.O. Dublin.

training with B.I.E.T. quickly changed my earning capacity and, he next few years, my earnings increased fourfold".—Student P., Bucks.

ND OUT FOR YOURSELF

se letters – and there are many more on file at Aldermaston Court eak of the rewards that come to the man who has given himself specialised know-how employers seek. There's no surer way of ing ahead or of opening up new opportunities for yourself. It cost you a stamp to find out how we can help *you*. **Write to E.T. Dept.BPE03 Aldermaston Court, Reading RG7 4PF.**

CUT OUT THIS COUPON

Tick or state subject of interest. Post to address below.

MECHANICAL
- A.M.S.E. (Mech.) ☐
- Boiler Inspect. & Operation ☐
- C & G Eng. Crafts ☐
- C & G Fabricat. ☐
- Diesel Eng. ☐
- Eng. Inspection ☐
- Eng. Metallurgy ☐
- Inst. Eng. & Tech. ☐
- Inst. Motor Ind. ☐
- Mainten. Eng. ☐
- Mechanical Eng. ☐
- Sheet Metal Work ☐
- Welding ☐

ELECTRICAL & ELECTRONIC
- A.M.S.E. (Elec.) ☐
- C & G Elec. Eng. ☐
- C & G Elec. Inst. ☐
- C & G Elec. Tech. ☐
- Computer Elect. ☐
- Elec. Maths ☐
- Elec. Science ☐
- Electronic Eng. ☐
- Electrical Eng. ☐
- Install. & Wiring ☐
- Meters & Measuring Instruments ☐

MANAGEMENT & PRODUCTION
- Auto. Control ☐
- Computer Prog. ☐
- Electronic Data Processing ☐
- Estimating ☐
- Foremanship ☐
- Inst. Cost & Man Accountants ☐
- Inst. Marketing ☐
- Management ☐
- Metrication ☐
- Motor Trade Man. ☐
- Network Plan. ☐
- Numerical Cont. ☐
- Operational Research ☐
- Personnel Man. ☐
- Planning Eng. ☐
- Production Eng. ☐

Man. Prod.—cont.
- Quality Control ☐
- Salesmanship ☐
- Storekeeping ☐
- Work Study ☐
- Works Management ☐

DRAUGHTSMANSHIP
- A.M.I.E.D. ☐
- Design of Elec. Machines ☐
- Die & Press Tool Design ☐
- Electrical Draughtsmanship ☐
- Gen. Draughtsmanship ☐
- Jig & Tool Des. ☐
- Tech. Drawing ☐

RADIO & TELE-COMMUNICATIONS
- Colour TV ☐
- C & G Radio/TV/ Electronics ☐
- C & G Telecomm. Tech. ☐
- Prac. Rad. Elec. (with kit) ☐
- Radio Amateurs Exam. ☐
- Radio Servicing & Repairs ☐
- Radio & TV Eng. ☐
- Trans. Course ☐
- TV Main. & Serv. ☐

AUTO & AERO
- Aero Eng. ☐
- A.M.I.M.I. A.E.C. Cert. ☐
- Auto Engineer. ☐
- Auto Repair ☐
- C & G Auto. Eng. ☐
- Garage Management ☐
- MAA/IMI Dipl. ☐
- Motor Vehicle Mechanics ☐

CONSTRUCTIONAL
- A.M.S.E. (Civil) ☐
- Architecture ☐

Constructional-cont.
- Building ☐
- Building Drawing ☐
- Build. Foreman ☐
- Carpentry & Join. ☐
- Civil & Municipal Engineering ☐
- Constructional Engineering ☐
- Construction ☐
- Surveyors ☐
- Institute Clerk of Works ☐
- Council Eng. ☐
- Geology ☐
- Health Eng. ☐
- Heat & Vent. ☐
- Hydraulics ☐
- Inst. of Builders ☐
- Inst. Works & Highway Sup. ☐
- Painting & Dec. ☐
- Public Hygiene ☐
- Road Engineer. ☐
- Structural Eng. ☐
- Surveying ☐

GENERAL
- Agricultural Eng. ☐
- Council of Eng. Inst. ☐
- Farm Science ☐
- General Educat. ☐
- Gen. Plastics ☐
- Pract. Maths ☐
- Pract. Slide Rule ☐
- Pure & Applied Maths ☐
- Refrigeration ☐
- Rubber Tech. ☐
- Sales Engineers ☐
- Tech. Report Writing ☐
- Timber Trade ☐
- University Ent. ☐

Coaching for many major exams. including ONC, C & G, etc.

G.C.E.
58 'O' & 'A' LEVELS SUBJECTS
Over 10,000 group passes

POST TODAY FOR A BETTER TOMORROW

To B.I.E.T., Dept. BPE03 Aldermaston Court, Reading RG7 4PF ON **BPE03**

NAME.....
Block Capitals Please
ADDRESS.....

OTHER SUBJECTS..... AGE.....

Accredited by C.A.C.C.

BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY

hed approximately on the 15th of each month by IPC Magazines Ltd., Fleetway House, Farringdon Street, London, E.C.4. Printed in England by Chapel River Press, er, Hants. Sole Agents for Australia and New Zealand—Gordon & Gotch (A/sia) Ltd.: South Africa—Central News Agency Ltd.: Rhodesia and Zambia—Kingstons Ltd.: frica—Stationery and Office Supplies Ltd. Subscription Rate (including postage): For one year to any part of the world £2·65 (£2.13.0).

cal Electronics is sold subject to the following conditions, namely, that it shall not, without the written consent of the Publishers first given, be lent, resold, hired out o wise disposed of by way of Trade at more than the recommended selling price shown on the cover, and that it shall not be lent, resold or hired out or otherwise disposed of in ated condition or in any unauthorised cover by way of Trade, or affixed to or as part of any publication or advertising, literary or pictorial matter whatsoever.

Henry's

YOUR COMPLETE AUDIO-ELECTRONIC STORES

More of everything at the right price. All your electronic requirements within 200 yards – call and see for yourself.

BUILD THE TEXAN

★ FREE TEAK CASE with complete kits!

FEATURES: New slim design with 6 ICs, IC sockets, 10 silicon transistors, 4 rectifiers, 2 zeners. Special Gardners low field slim line transformer. Fibre glass PC panel. Complete chassis work.

HIGH QUALITY & STABILITY ARE PREDOMINATE FEATURES —DEVELOPED BY TEXAS ENGINEERS FOR PERFORMANCE, RELIABILITY AND EASE OF CONSTRUCTION.

FACILITIES: On/off switch indicator, headphone socket, separate treble, bass, volume and balance controls, scratch and rumble filters, mono/stereo switch, Input selec[illegible] P.U., Radio Tuner, Aux. Can be altered for Mic, Tape [illegible] etc. (Parts list Ref. 20 on request). Constructional D[illegible] No. 21. 30p.

SPECIAL KIT PRICE **£28·50** P. & P. COMPLETE WITH FREE TEAK CABINET

20 + 20 WATT INTEGRATED I.C. STEREO AMPLIFIER

(As featured in "Practical Wireless" May to August 1972)

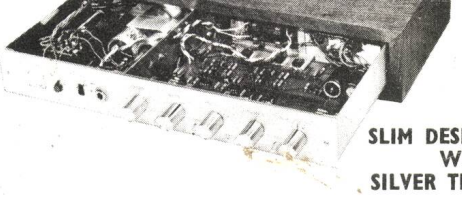

SLIM DESIGN WITH SILVER TRIM

Overall chassis size 14½ in. x 6 in. x 2 in. high

Designer approved kits distributed by Henry's!

LOW COST HI-FI SPEAKERS

E.M.I. Size 13½in x 8½in and Ceramic Magnet

TYPE 150 6 watt, 3, 8 or 15 ohms **£2·20.** Post 22p.

TYPE 150TC Twin cone version **£2·75.** Post 22p.

TYPE 450 10 watt with twin tweeters and crossover, 3, 8 or 15 ohms. **£3·85.** Post 25p.

TYPE 350 20 watt with tweeter and crossover, 8 and 15 ohms. **£7·70.** Post 28p.

POLISHED CABINETS 150, 150TC, 450 **£4·60.** Post 30p.
ASSEMBLED IN POLISHED CABINETS (8 OHM)
SERIES 6 (Assembled 150TC) per pair **£16·50.** Post 70p.
SERIES 8 (Assembled 450) per pair **£18·95.** Post 70p.

TEST EQUIPMENT Just a selection

SE250B Pocket Pencil Signal Injector, **£1·90**
SE500 Pocket Pencil Signal Tracer, **£1·50**
THL33D Robust 2 K/Volt, **£4·55**; with case **£4·95**
TE15 Grid Dip Meter 440 KHz—280 MHz, **£13·45**
500 30 K/Volt Multimeter, **£9·25**; with leather case, **£10·50**
200H 20 K/Volt Multimeter, **£4·20**; with case **£4·95**
AF105 50K/V Multimeter, **£8·50**; with case, **£9·50**
U4341 AC/DC Multimeter with transistor tester with steel case, **£10·50**
TE20D RF Generator 120KHz—500MHz, **£15·95.** Carr. 35p
TE22D Audio Generator 20Hz—200KHz, **£17·50.** Carr. 35p
CI-5 3in Pulse Scope 10Hz—10MHz, **£39·00.** Carr. 50p
TE65 Valve Voltmeter 28 ranges, **£17·50.** Carr. 40p

ALL NOMBREX MODELS IN STOCK

ML3 MW/LW TUNER TO BUILD

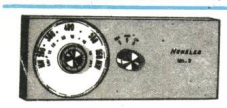

Uses Mullard Module. Slow motion tuning. Built-in battery. Ferrite aerial. Overall size 7in x 2¾in x 3¼in. TOTAL COST TO BUILD **£4·85.** Post 15p. All parts sold separately—Leaflet No. 6.

BUILD THIS VHF FM TUNER

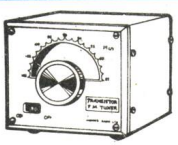

5 TRANSISTORS 300kc/s BANDWIDTH PRINTED CIRCUIT, HIGH FIDELITY REPRODUCTION. MONO AND STEREO. A popular VHF FM Tuner for quality and reception of mono and stereo. There is no doubt about it—VHF FM gives the REAL sound. All parts sold separately.
Free Leaflet No. 3 & 7. **TOTAL £6·97,** p.p. 20p.
Decoder Kit **£5·97.** Tuning meter unit **£1·75.**
Mains unit (optional) Model PS900 **£2·47.** Post 20p.
Mains unit for Tuner and Decoder PS6/12 **£3·25.** Post 20p.

"BANDSPREAD" PORTABLE TO BUILD

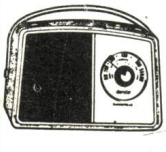

Printed circuit all transistor design using Mullard RF/IF Module. Medium and Long Wave bands plus Medium Wave Bandspread for extra selectivity. 600mW push-pull output, fibre glass PVC covered cabinet, car aerial. Attractive appearance and performance. TOTAL COST TO BUILD **£7·98,** p.p. 32p (Batt. 22p). All parts sold separately —Leaflet No. 2.

PA—DISCO—LIGHTING

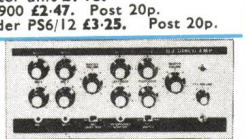

UK's Largest Range—Write phone or call in. Details and demonstrations on request.

DJ30L 3 Channel sound to light unit, 3kW. **£29·50**
DJ40L 3 Channel Mic (Built-in) to light, 3kW. **£38·75**
DJ70S 70 watt Disco amp/mixer, **£49·75**
DISCOAMP 100 watt Disco amp/mixer, **£65·85**
DJ105S 30 watt Disco amp/mixer, **£32·25**
Anti-Feedback Quality Mic., **£11·50**
DJ500 50 watt PA amplifier, **£43·95**
DJ700 70 watt **£52.75**
Group 300 150 watt rms Group Valve amplifier, **£86·00**
● **Portable discos—details on request**
● **Credit terms for callers**

FIBRE OPTICS · LIGHTING · MICS · EFFECTS · PROJECTORS · SPOTS · DIMMERS · STANDS · MIXERS · SPEAKERS
Everything for PA — Disco — Lighting.
FREE Stock List Ref. No. 18.

CATALOGUE

Fully detailed and illustrated covering every aspect of Electronics—plus data, circuits and information.
10,000 Stock lines at Special Low Prices and Fully Guaranteed.

PRICE 55p Post paid
(40p FOR CALLERS)

PLUS! FIVE 10p VOUCHERS

Send to this address—Henry's Radio Ltd. (Dept. PE), 3 Albemarle Way, London, E.C.1—for catalogue by post only. All other mail and callers to "303", see above.

SINCLAIR PROJECT 60 MODULES —SAVE POUNDS

Z30 **£3·57** Z50 **£4·37**
STEREO 60 **£7·97** PZ5 **£3·97**
PZ6 **£6·37** PZ8 **£4·77.**
Transformer for PZ8 **£2·95.**
Active Filter Unit **£4·45.**
Stereo FM Tuner **£16·95.**
IC12 **£1·80** Q16's **£15** pair.
Post, etc. 20p per item.

PACKAGE DEALS Post 25p
2 x Z30, Stereo 60, PZ5 **£15·95**
2 x Z30, Stereo 60, PZ6 **£18·00**
2 x Z50, Stereo 60, PZ8 **£20·25**
Transformer for PZ8 **£2·95**
PROJECT 605 KIT **£19·95**

ELECTRONIC KITS

Henry's introduce new huge range of audio and electronic kits now in stock, everything supplied, tremendous value. Detailed list Ref. No. 14 on request.

IC RECEIVER

ZN414 Radio integrated circuit as featured in Practical Wireless, January, 1973; Practical Electronics, February, 1973. Price **£1·20.**

BATTERY TAPE DECK

Garrard 9V tape deck with heads, etc. As previously advertised. Limited quantity **£9·50.** Post 30p.

LEARN A LANGUAGE

Recorded Cassettes with step by step phrase books. French, German, Spanish, Italian. **£1·49** per cassette. **£5·50** per set of four.

DISCO SPOTBANK

As illustrated on the front cover of Practical Wireless April, 1973. **£12·75.** P. & P. 35p.

HI-FI EQUIPMENT

Warehouse prices with BIG DISCOUNTS plus demonstrations (for callers) and GUARANTEES.

FREE 24-page detailed brochure (Ref. No. 17

★ You can see the savings

EMI HIGH QUALITY CASSETTES

The best U.K. low noise tape but at a special price. "Living Sound" cassettes meet the highest international standards (IEC94A). Fantastic price savings.

	C60	C90	C12
3 for	**£1·10**	**£1·47**	**£1·8**
6 for	**£2·00**	**£2·85**	**£3·5**
10 for	**£3·10**	**£4·65**	**£5·6**
RRP each	**71p**	**98p**	**£1·4**

Full guarantee. Post paid.

See earlier page of this magazine for transistors and semiconductor devices.

ULTRASONIC TRANSDUCERS

Operate at 40kc/s up to [illegible] yds. Ideal remote switching and signalling. Complete with circuits and circuits.
PRICE PER PAIR **£5·90.** Post

MARRIOT TAPE HEAD

4 TRACK MONO
or 2 TRACK STEREO

"17" High Impedance **£2**
"18" Med. Impedance **£2**
"36" Med.-Low Imp. **£3**
Erase Heads for above
"63" 2 track mono — High Impedance **£1**
"43" Erase Head for above

7 SEG & NIXIE TUBE

(Post 15p per 1 to 6)

XN3, XN13, GN6 0–9 [illegible] view with data, **85p.**
GNP-7, GNP-8 0–9 side view with decimal points and data **95p.**
3015F 7 seg. **£2** each, **£7** per with data.
12 and 24 hour clock circuit Ref. No. 31 **15p.**

MINIATURE AMPLIFIER

5 transistor. 300mW. Fitted volume and sensitivity control 9 volt operated. **£** each, p.p. 15p.

QUALITY SLIDER CONTROL

60mm stroke singles ganged. Complete with knobs 5kΩ, 10kΩ, 25kΩ, 100kΩ, 250kΩ, 500kΩ. 1 meg. Log or Lin. **40p** each, 10kΩ, 25kΩ, 50kΩ, 100kΩ, 250kΩ, Log or Lin. ganged. **60p** each.

VAT

Prices DO NOT include Value Added Tax. From 1st April, 1973, 10% must be added and shown separately to your total order (inclusive of post/packing). Help us to help you receive your order without delay.

Henry's RADIO LIMITED

EDGWARE ROAD, W2

404-406 Electronic Components and Equipment 01-402 8381
354-356 High Fidelity and Tape Equipment 01-402 5854/4736
309 PA-Disco-Lighting High Power Sound 01-723 6963
303 Special offers and bargains store
All mail to 303 Edgware Road, London W2 1BW

Open:- 9 am 6 days a week (309 closed Thursday) All stores open all day Saturday